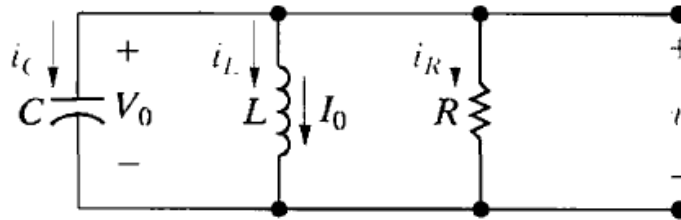



Quiz 3 (Total 120 points)

It is a closed-book, closed-note quiz. Cheating leads to 0% score. Calculator is allowed. Please show the process of thinking/calculation. Indicate your final answers clearly. Unit is needed if applicable.


1. The circuit elements in the following circuit are $R = 200 \Omega$, $C = 200 \text{ nF}$, and $L = 50 \text{ mH}$. The initial inductor current is -45 mA , and the initial capacitor voltage is 15 V .
 - a) Calculate the initial current in each branch of the circuit. (15%)
 - b) Find $v(t)$ for $t \geq 0$. (15%)
 - c) Find $i_L(t)$ for $t \geq 0$. (15%)



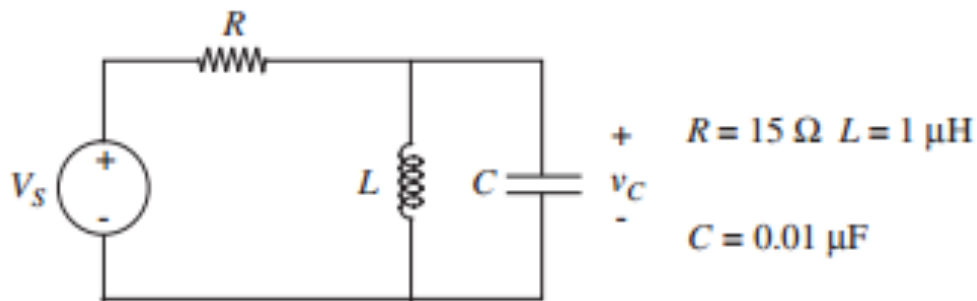2.
 - a) Is the zero input response of the circuit shown in the following figure under-damped, overdamped, or critically-damped? (10%)



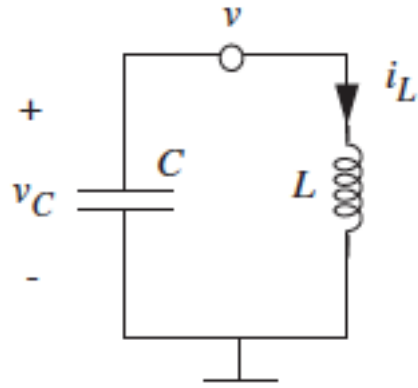- b) What is the form of the zero input response (v_C) for the same circuit in part (a)? Make a rough sketch. (20%)
3. In the following undriven LC circuit, assume $C = 1 \mu\text{F}$ and $L = 100 \mu\text{H}$, and the initial condition $i_L(t=0)=0 \text{ A}$, and $V_C(t=0)=1 \text{ V}$. Find the expression of $i_L(t)$ and $V_C(t)$ for $t > 0$. (20%)



4. For the following circuit, find and sketch the zero-input response, $v_2(t)$ for $t > 0$. Assume $v_2(t=0)=1$ V, $v_1(t=0)=0$ V. (25%)

