

1.  
(a)

$$i_R = \frac{v}{R} = \frac{15}{200} = 75 \text{ mA}$$

$$i_C = -(i_L + i_R) = -(-45 + 75) = -30 \text{ mA}$$

- (b)

$$\alpha = \frac{1}{2RC} = \frac{1}{2 \cdot 200 \cdot 200 \cdot 10^{-9}} = \frac{1}{8 \cdot 10^{-5}} = 12500$$

$$\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{50 \cdot 10^{-3} \cdot 200 \cdot 10^{-9}}} = 10^4 = 10000$$

$$s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2} = -12500 \pm 7500 = -5000, -20000$$

$$v(t) = A_1 e^{-5000t} + A_2 e^{-20000t} \text{ ----- eq. 1}$$

Initial condition:

$$v(0) = 15 = A_1 + A_2 \text{ ----- eq. 2}$$

$$\frac{dv(0)}{dt} = -\frac{v(0) + Ri_L(0)}{RC} = -\frac{15 + 200 \cdot (-45) \cdot 10^{-3}}{200 \cdot 200 \cdot 10^{-9}} = -150000$$

From eq.1:

$$\frac{dv}{dt} = -5000A_1 e^{-5000t} - 20000A_2 e^{-20000t}$$

At t = 0:

$$-150000 = -5000A_1 - 20000A_2 \text{ ----- eq. 3}$$

Solve eq.2 and eq.3:

$$\begin{cases} A_1 = 10 \\ A_2 = 5 \end{cases}$$

$$\Rightarrow v(t) = 10e^{-5000t} + 5e^{-20000t} \text{ (V), } t > 0$$

- (c)

$$i_L = \frac{1}{L} \int_{-\infty}^t v dt = \frac{1}{50 \cdot 10^{-3}} (10e^{-5000t} + 5e^{-20000t})$$

$$= -0.04e^{-5000t} - 0.005e^{-20000t} \text{ (A) } t > 0$$

2.

$$\text{a) } \frac{d^2 v_C}{dt^2} + \frac{1}{RC} \frac{dv_C}{dt} + \frac{1}{LC} = 0$$

$$2 \cdot \alpha = \frac{1}{RC}$$

$$\omega_o^2 = \frac{1}{LC}$$

$\alpha < \omega_o \rightarrow$  UNDERDAMPED


$$\text{b) } v_C = K e^{-\alpha t} \cdot \cos(\omega_d \cdot t + \phi)$$

$$\omega_d = \sqrt{\omega_o^2 - \alpha^2}$$

$$\phi = \tan^{-1}\left(\frac{\alpha}{\omega_d}\right)$$

$$\omega_o = 10 \times 10^6$$

$$\alpha = 3.33 \times 10^6$$


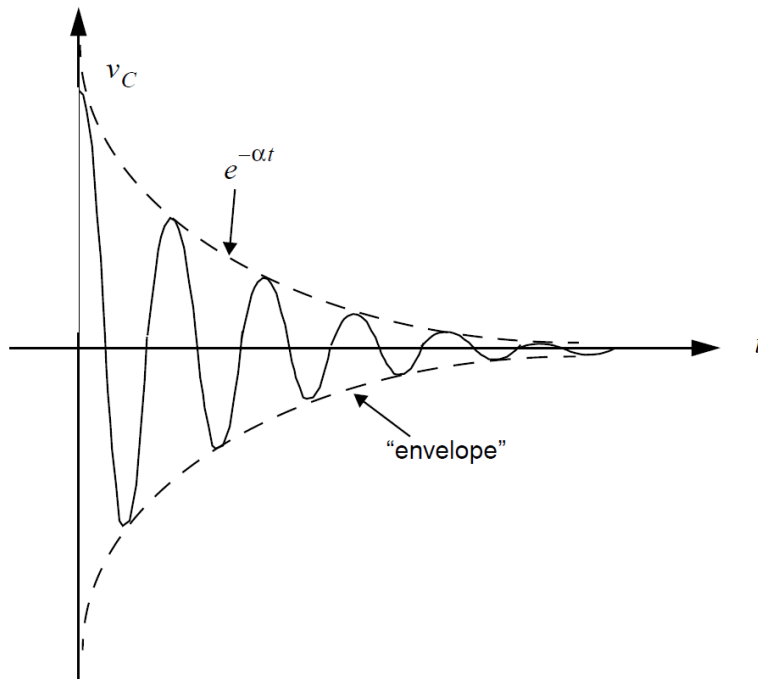


3.

$$\omega_o = \frac{1}{\sqrt{LC}} = 10^5 \text{ rad/s}$$

$$v_C(t) = v_C(0) \cos(\omega_o t) = 1.0 \cos(10^5 t)$$
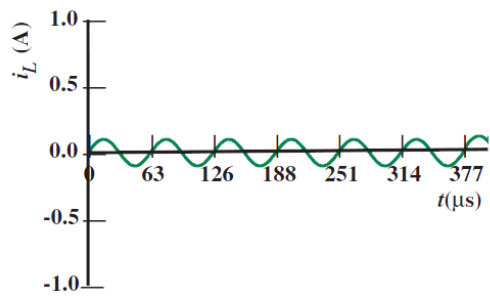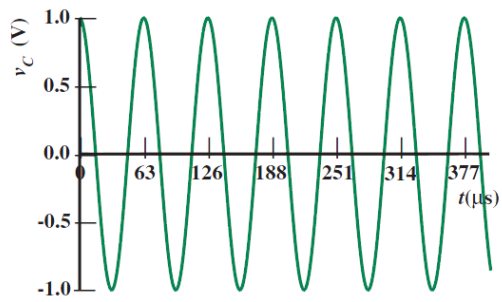
$$i_L(t) = \sqrt{\frac{C}{L}} v_C(0) \sin(\omega_o t) = 0.1 \times \sin(10^5 t).$$



4.

$$\frac{v_1}{8k} + \frac{v_1 - v_2}{6k} + \left(\frac{1}{24}\mu F\right) \frac{dv_1}{dt} = 0$$

$$v_1 - \left(\frac{1}{18}\mu F\right) \frac{dv_2}{dt}(6000) - v_2 = 0 \rightarrow v_1 = v_2 + \frac{1}{3000} \frac{dv_2}{dt}$$

Rearrange equation as follow:

$$v_2 = A e^{-1000t} + B e^{-9000t}$$

Initial conditions allow us to find constants  $A$  and  $B$ :

$$A + B = 0 \rightarrow \text{from } v_2(0) = 0$$

$$A + B - \frac{1}{3}A - 3B = 1 \rightarrow \text{from } v_1(0) = 1\text{Volt}$$

$$A = \frac{3}{8}$$

$$B = -\frac{3}{8}$$

$$v_2 = \frac{3}{8}(e^{-1000t} - e^{-9000t})$$