
EE2210 Lecture 8B: Damped Second-Order Systems

Chapter 12 of textbook



Ping-Hsuan Hsieh (謝秉璇)

Delta Building R908

EXT 42590

phsieh@ee.nthu.edu.tw


Review

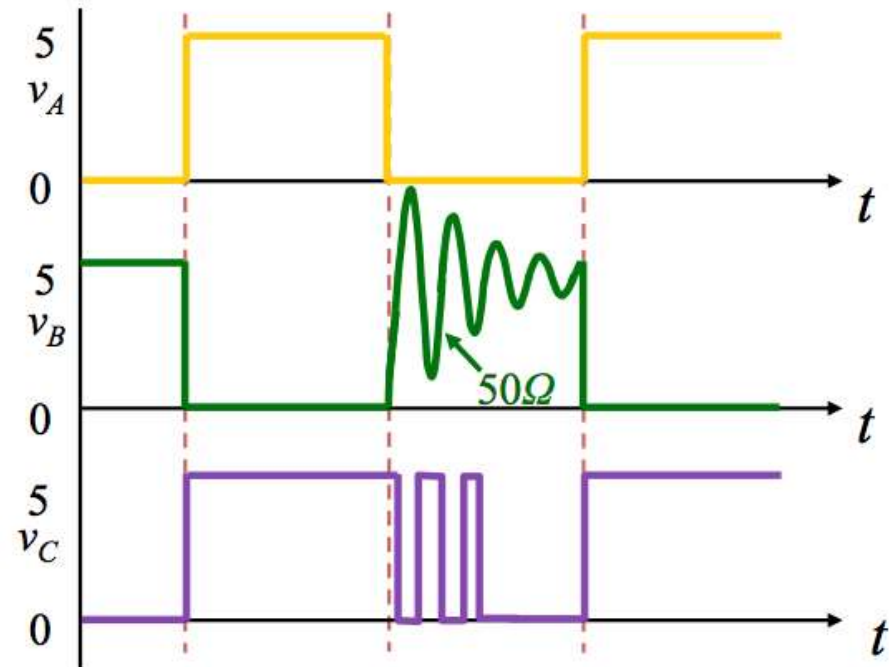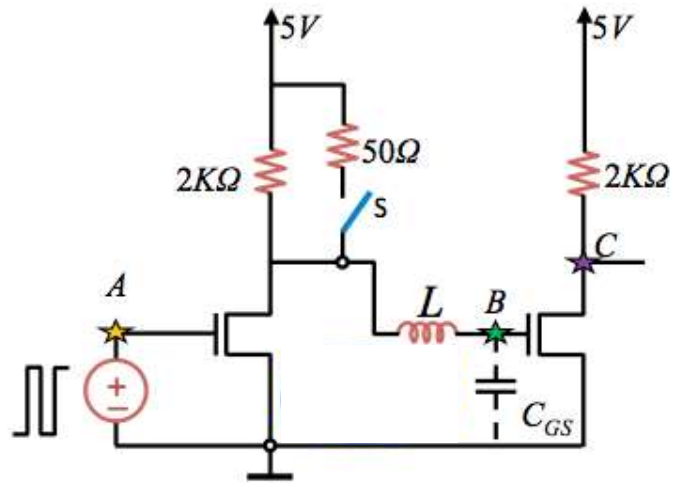

LC Circuit in Last Lecture...

- ◆ We solved
- ◆ For input
- ◆ and initial conditions
- ◆ Total solution:

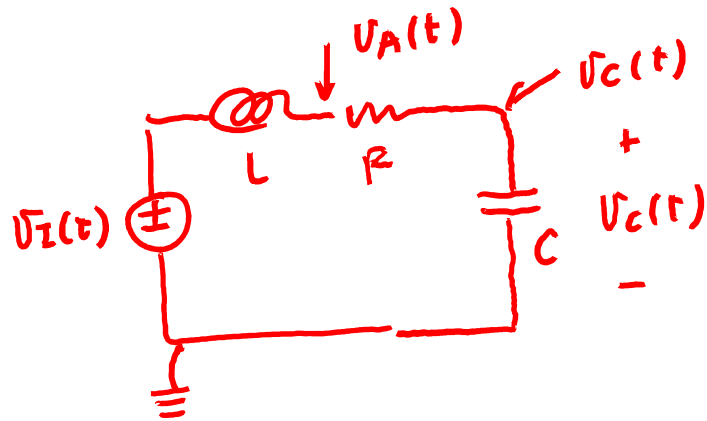Let's Analyze the RLC Network (Damped Oscillator)



two energy-storage element
 $v_C(t)$, $i_L(t)$

◆ Node method:

$$\text{KCL @ } v_C \rightarrow \downarrow \quad \frac{v_A - v_C}{R} = C \frac{dv_C}{dt}$$

$$\text{@ } v_A \rightarrow \rightarrow \quad \frac{1}{L} \int_{-\infty}^t (v_I - v_A) dt = \frac{v_A - v_C}{R}$$

we focus on $v_C(t)$, need to get rid of v_A

Setup the Differential Equation

- ◆ Need to get rid of v_A

$$\frac{v_A - v}{R} = C \frac{dv}{dt} \Rightarrow v_A = RC \frac{dv}{dt} + v$$


$$\frac{1}{L} \int_{-\infty}^t (v_I - v_A) dt = \frac{v_A - v}{R}$$

$$\frac{1}{L} \int_{-\infty}^t (v_I - v_A) dt = C \frac{dv}{dt}$$


$$\frac{1}{L} (v_I - v_A) = C \frac{d^2 v}{dt^2}$$

$$\frac{1}{L} (v_I - RC \frac{dv}{dt} - v) = C \frac{d^2 v}{dt^2}$$
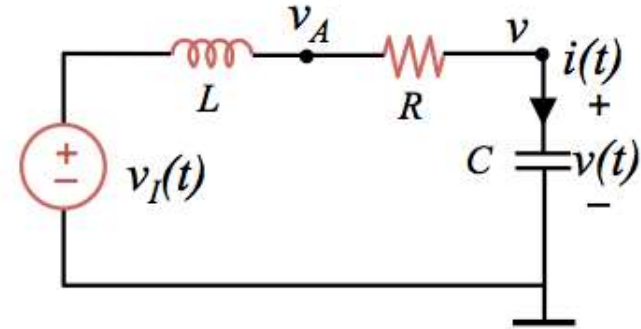
$$\frac{d^2 v}{dt^2} + \frac{R}{L} \frac{dv}{dt} + \frac{1}{LC} v = \frac{1}{LC} v_I$$



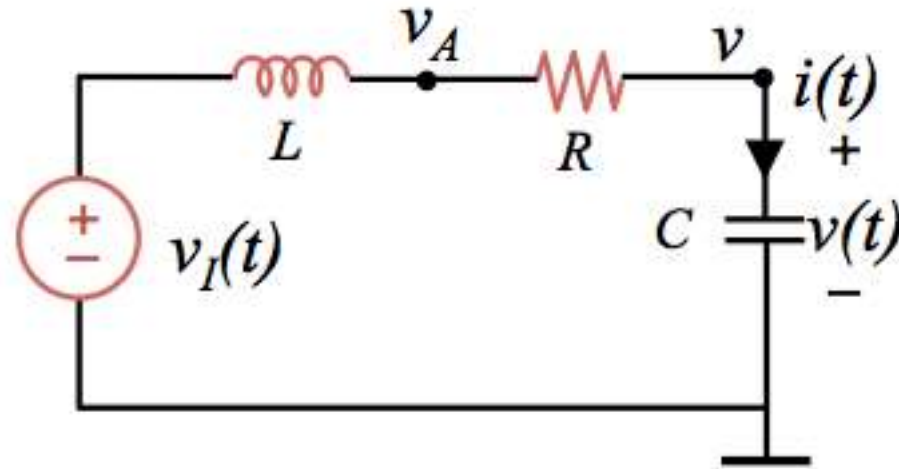Setup the Differential Equation **Differently**




Method of Particular and Homogeneous Solutions

◆ Four-step procedure

$$\frac{d^2v}{dt^2} + \frac{R}{L} \frac{dv}{dt} + \frac{1}{LC} v = \frac{1}{LC} v_I$$


1. Find the particular solution $v_P(t)$
2. Find the homogeneous solution $v_H(t)$
 - Four-step procedure
3. The total solution is the sum of the particular solution and homogeneous solution
4. Use initial condition to solve for the remaining constraints

Let's Solve

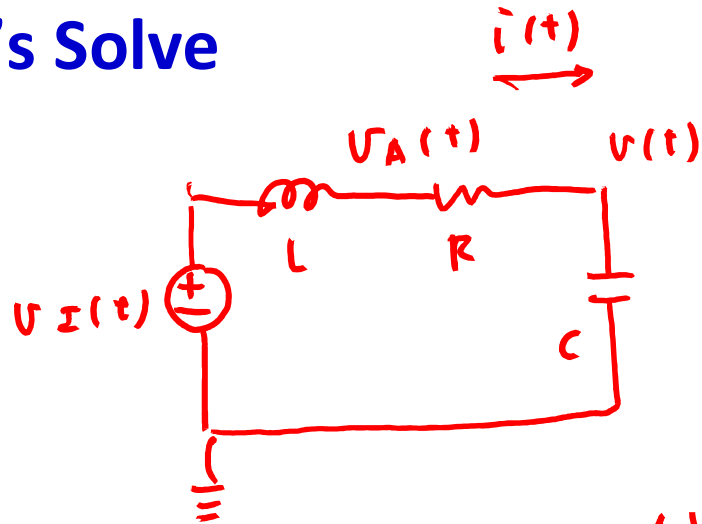

$$\frac{d^2 v}{dt^2} + \frac{R}{L} \frac{dv}{dt} + \frac{1}{LC} v = \frac{1}{LC} v_I$$

For $v_I(t) = V_I \cdot u(t)$

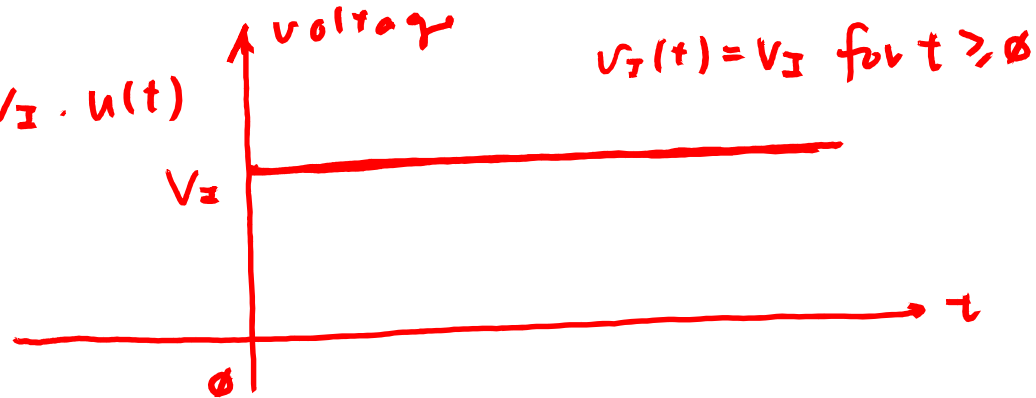

For $v(\emptyset) = \emptyset$
 $i(\emptyset) = \emptyset$) zero-state response

want to solve $v(t)$ for $t \geq 0$

1. Particular Solution

$$\frac{d^2v}{dt^2} + \frac{R}{L} \frac{dv}{dt} + \frac{1}{LC} v = \frac{1}{LC} v_I$$

$$\text{for } \frac{1}{\omega} v_p(t) = v_I$$

2. Homogeneous Solution

- ◆ Look for solution to

$$\frac{d^2 v_H(t)}{dt^2} + \frac{R}{L} \frac{dv_H(t)}{dt} + \frac{1}{LC} v_H(t) = 0$$

$$\frac{d^2 v}{dt^2} + \frac{R}{L} \frac{dv}{dt} + \frac{1}{LC} v = \frac{1}{LC} v_I$$

- ◆ Four-step method

(2A) $\uparrow \frac{1}{A}$ $v_H(t) = A \cdot e^{st}$ $A \neq 0$ (~~find~~ A, s)

(2B) $\cancel{A} \cdot \cancel{s^2} \cdot \cancel{e^{st}} + \frac{R}{L} \cancel{A} \cdot \cancel{s} \cdot \cancel{e^{st}} + \frac{1}{LC} \cancel{A} \cdot \cancel{e^{st}} = 0$

char. eq. $\cancel{s^2} \frac{R}{L} s + \frac{1}{LC} = 0$

(2C) $\uparrow \frac{R}{L}$ s_1, s_2

(2D) $v_H(t) = A_1 \cdot e^{s_1 t} + A_2 \cdot e^{s_2 t}$

2. Homogeneous Solution

$$\frac{d^2 v_H(t)}{dt^2} + \frac{R}{L} \frac{dv_H(t)}{dt} + \frac{1}{LC} v_H(t) = 0$$

$$s^2 + \frac{R}{L} s + \frac{1}{LC} = 0$$

$$\Rightarrow s^2 + 2 \cdot \frac{R}{2L} s + \frac{1}{LC} = 0$$

$$\Rightarrow s^2 + 2\alpha s + \omega_0^2 = 0$$

$$\left(\begin{array}{l} \alpha = \frac{R}{2L} \\ \omega_0^2 = \frac{1}{LC} \end{array} \right.$$

$$s_1 = -\alpha + \sqrt{\alpha^2 - \omega_0^2}$$

$$s_2 = -\alpha - \sqrt{\alpha^2 - \omega_0^2}$$

3. Total Solution

4. Find unknowns from initial conditions

Let's Stare at the Total Solution for a While Longer

$$v(t) = V_I + A_1 e^{-\alpha t} e^{\left(\sqrt{\alpha^2 - \omega_0^2}\right)t} + A_2 e^{-\alpha t} e^{\left(-\sqrt{\alpha^2 - \omega_0^2}\right)t}$$

- ◆ There are 3 possible cases:

$\alpha > \omega_0$ over-damped

$\alpha = \omega_0$ critically-damped

$\alpha < \omega_0$ underdamped

$$\begin{cases} \alpha = \frac{R}{2L} \\ \omega_0^2 = \frac{1}{LC} \end{cases}$$