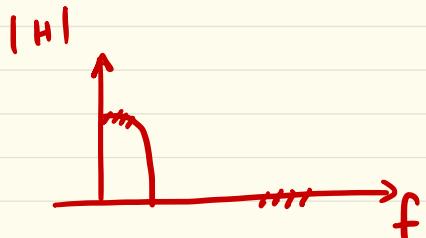



Frequency response




Low-pass
=



High-pass

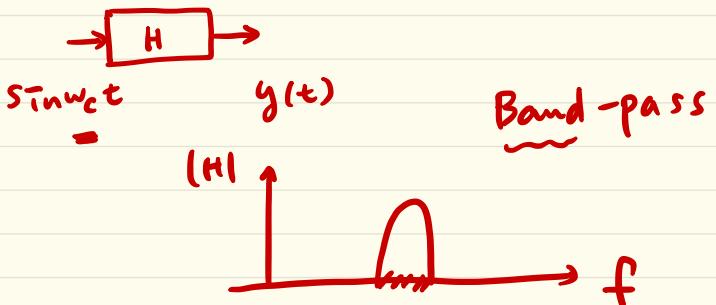


Band-pass

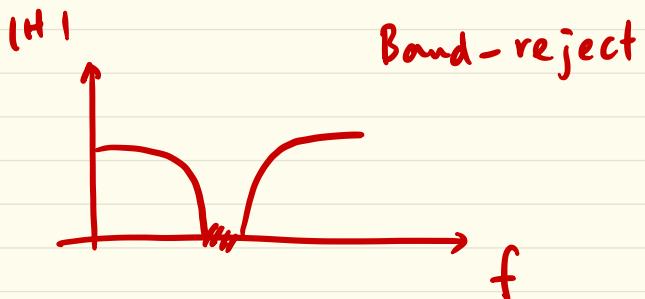

Band-reject



Square Wave

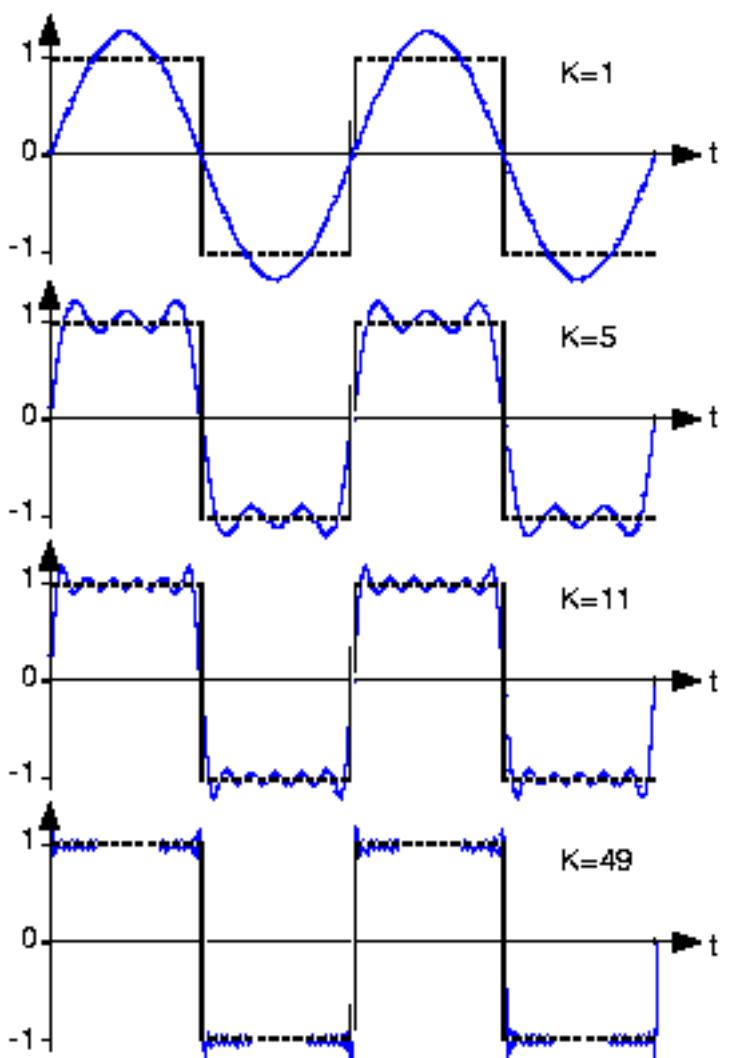


- For example, a square wave can be constructed by multiple (ideally infinite) sine waves at different frequencies.



Complex Numbers (Appendix C).

- $x = a + jb = |x| \angle x = \sqrt{a^2 + b^2} \cdot \tan^{-1} \frac{b}{a}$

$$= |x| \cos x + j |x| \sin x$$

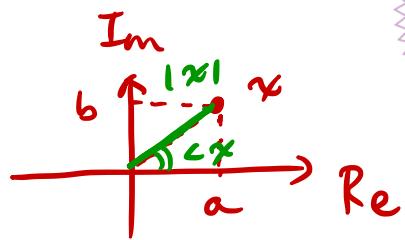

- x, y : complex numbers

$$A = x \cdot y \Rightarrow |A| = |x| \cdot |y|, \quad \angle A = \angle x + \angle y$$

$$B = \frac{x}{y} \Rightarrow |B| = \frac{|x|}{|y|}, \quad \angle B = \angle x - \angle y$$


- $x(t) = |x| \cos(\omega t + \angle x) = \operatorname{Re} [|x| \cdot e^{j(\omega t + \angle x)}] \xrightarrow{\text{Phasor}} |x| \angle x \cdot e^{st}$

complex amplitude



Sinusoidal Response of RC Network

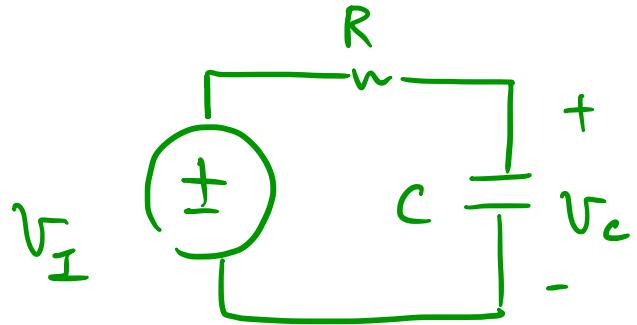- Find $v_C(t)$ for $t \geq 0$. Assume $v_I(t) = V_i \cos(\omega t)$ for $t \geq 0$ and $v_I(t) = 0$ for $t < 0$. Initial condition $v_C(0) = 0$.






Our Usual Approach

1. Write DE for circuit by applying node method.
2. Find particular solution v_P by guessing and trial & error.
3. Find homogeneous solution v_H .
4. Total solution is $v_P + v_H$, then solve for remaining constants using initial conditions .



Step 1: Set Up the Differential Equation

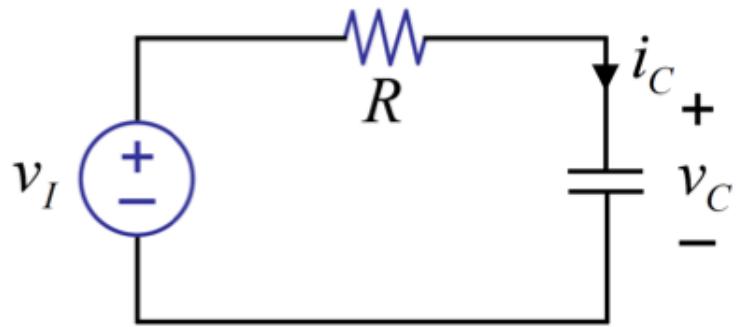

1.. KCL @ v_C .

$$\frac{v_C - v_I}{R} + C \frac{dv_C}{dt} = 0$$

$$\Rightarrow RC \frac{dv_C}{dt} + v_C = v_I = V_i \cdot \cos \omega t \quad \text{for } t \geq 0$$



Step 2: Find the Particular Solution

$$RC \frac{dv_P}{dt} + v_P = V_i \cos(\omega t)$$

Assume

1. $V_p = V_i \cdot \cos \omega t$ It is: $-RC \cdot V_i \cdot \omega \cdot \sin \omega t + V_i \cdot \omega \sin \omega t \neq V_i \cdot \cos \omega t$

2. $V_p = V_i \cdot \sin \omega t$ X

3. $V_p = V_i \cdot \cos(\omega t + \varphi)$ X



Sneaky Approach

$$RC \frac{dv_p}{dt} + v_p = V_i \cos(\omega t)$$

- Instead of input $v_I(t) = V_i \cos \omega t$
- Find particular solution for another input $v_{IS}(t) = V_i e^{st}$

$A \cos \omega t \rightarrow \boxed{\text{linear}} \rightarrow \underline{y} = \operatorname{Re}(\tilde{y})$

$$RC \cdot \frac{d\tilde{V}_p}{dt} + \tilde{V}_p = V_i \cdot e^{st} \quad (e^{st} = e^{j\omega t})$$

$\frac{A \cdot e^{j\omega t}}{\downarrow} \rightarrow \boxed{\text{linear}} \rightarrow \tilde{y} = I_m(A e^{j\omega t}) \rightarrow I_m(\tilde{y})$

Assume $\tilde{V}_p = V_p \cdot e^{st}$ $\leftarrow \lambda$

$$\Rightarrow RC \cdot V_p \cdot s \cdot e^{st} + V_p \cdot e^{st} = V_i \cdot e^{st}$$

$$\Rightarrow e^{st} (sRC V_p + V_p - V_i) = 0$$

$$\Rightarrow V_p = \frac{V_i}{1 + sRC}, \quad s \neq -\frac{1}{RC}$$



Sneaky Approach

- Assume $s = j\omega$, then particular solution for input $v_{IS}(t) = V_i \exp(st)$

$$\tilde{V}_p = V_p \cdot e^{st} = \frac{V_i}{1 + sRC} e^{st}$$

Complex complex
amplitude exponential

- Finding the particular solution to $v_{IS}(t) = V_i \exp(j\omega t)$ was easy.
- From Euler relation $v_{IS}(t) = V_i \exp(j\omega t) = V_i \cos(\omega t) + j \sin(\omega t)$
- An inverse superposition argument, assuming system is real and linear.



Sneaky Approach

$v_p(t)$ particular response to $V_i \cos \omega t$

$v_{ps}(t)$ particular response to $V_i \exp(j\omega t)$

- Let's try to find v_p from v_{ps} :

$$\begin{aligned} v_p(t) &= \operatorname{Re}(\tilde{v}_p) = \operatorname{Re}\left(\frac{V_i}{1+j\omega RC} \cdot e^{j\omega t}\right) \\ &= \operatorname{Re}\left(\frac{V_i}{\sqrt{1+(\omega RC)^2}} \cdot e^{j\arctan(-\omega RC)} \cdot e^{j\omega t}\right) \\ &= \frac{V_i}{\sqrt{1+(\omega RC)^2}} \cdot \cos\left(\omega t + \arctan(\omega RC)\right) \end{aligned}$$



Step 3: Homogeneous Solution

- Recalled from Chapter 10, the homogeneous solution for

RC circuit v_H : $v_H(t) = A \cdot e^{-t/RC}$

- The total solution:

$$v_C(t) = v_P(t) + v_H(t) = \frac{V_i}{\sqrt{1 + (\omega RC)^2}} \cdot \cos(\omega t + \tan^{-1}(\omega RC)) + A \cdot \exp\left(-\frac{t}{RC}\right)$$

Given

$$v_C(t=0) = 0 \Rightarrow A = -\frac{V_i}{\sqrt{1 + (\omega RC)^2}} \cdot \cos\left(-\tan^{-1}(\omega RC)\right)$$

Sinusoidal Steady State

Exercise 12.2



- The total solution

$$v_C(t) = \frac{V_i}{\sqrt{1+(\omega RC)^2}} \cos(\omega t + \phi) - \frac{V_i}{\sqrt{1+(\omega RC)^2}} \cos \phi \cdot e^{\frac{-t}{RC}}$$

where $\phi = \tan^{-1}(-\omega RC)$

- We are usually interested only in the particular solution for sinusoids, i.e., after the transients have died.



- When $t \rightarrow \infty$,

$$v_C(t) = \frac{V_i}{\sqrt{1+(\omega RC)^2}} \cdot \cos(\omega t + \tan^{-1}(\omega RC))$$

Steady-state response