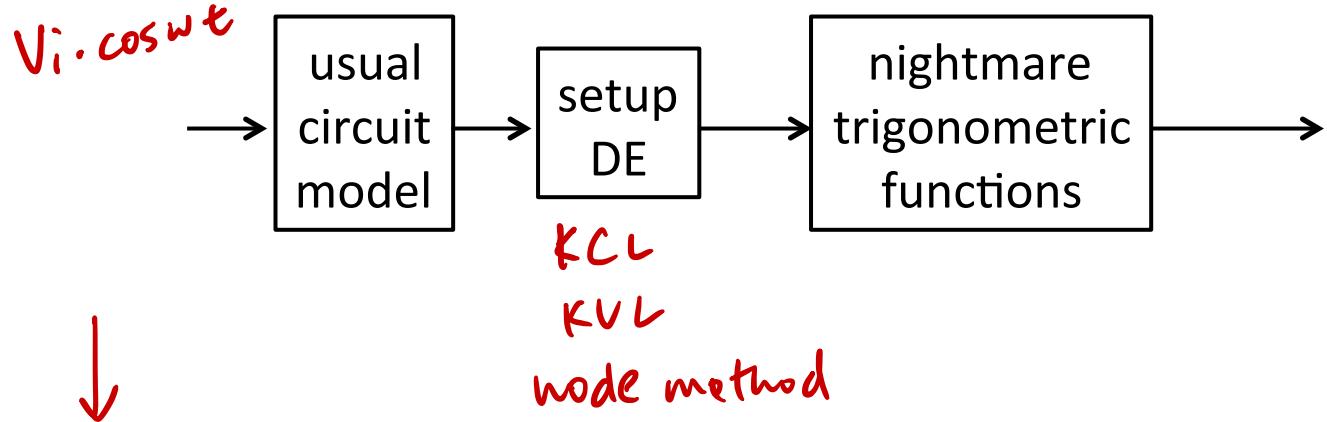





Review: Sinusoidal Steady State Analysis Approach





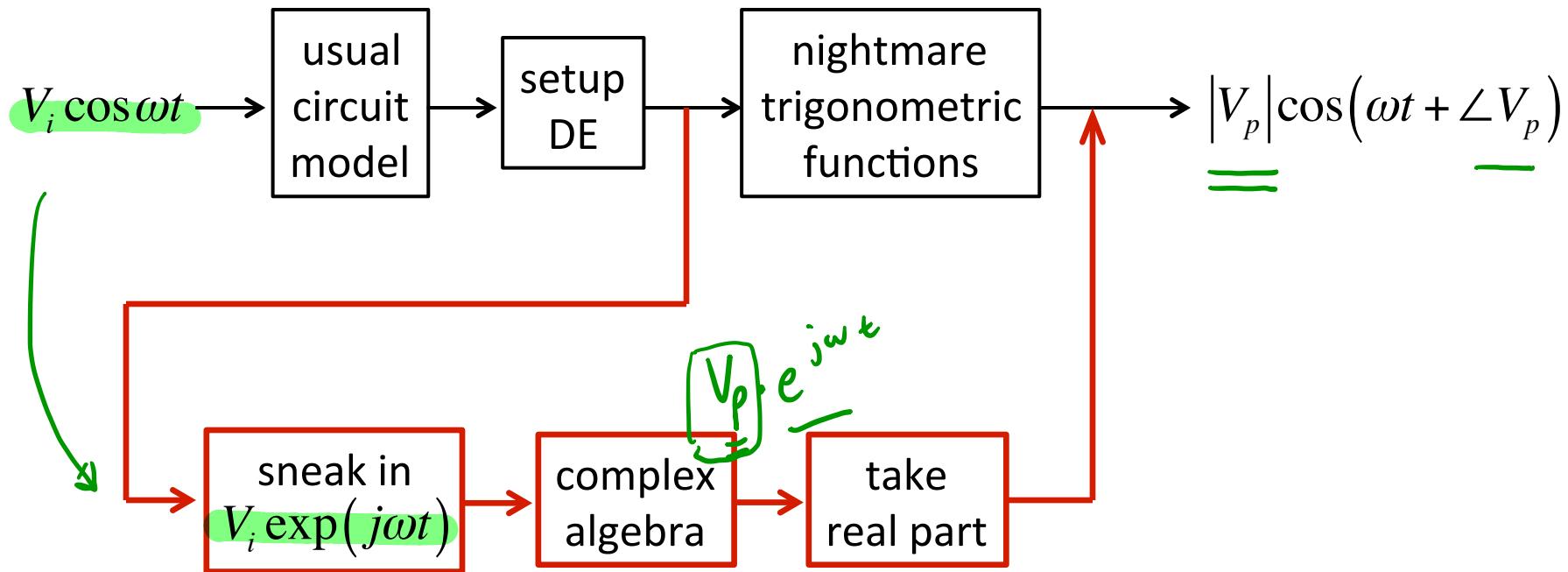Review: Sinusoidal Steady State Analysis Approach




$$V_p = \frac{V_i}{1+j\omega RC} \quad \text{complex amplitude}$$

- ❑ V_p contains all the information we need.
 - Complex amplitude gives the amplitude and phase of the output cosine.





Review

Practice

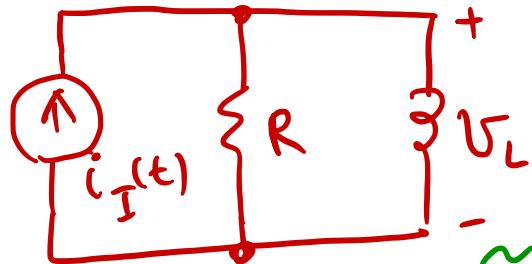

$$\tilde{i}_I = \frac{\tilde{V}_L}{R} + \frac{1}{L} \int \tilde{V}_L dt$$
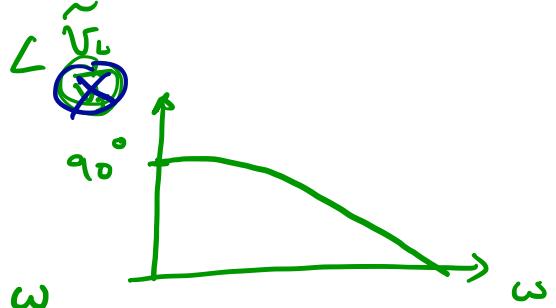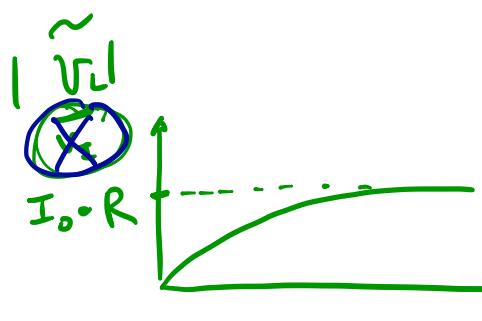
$$\Rightarrow \tilde{V}_L = \text{Re}(\tilde{V}_L) = \frac{I_0 \cdot \omega RL}{\sqrt{R^2 + \omega^2 L^2}} \cos\left(\omega t + \tan^{-1}\left(\frac{R}{\omega L}\right)\right)$$



Find SSS of $V_L(t)$.

$$i_I(t) = I_0 \cos \omega t \rightarrow \tilde{i}_I = I_0 \cdot e^{j\omega t}$$

$$i_I(t) \rightarrow \tilde{i}_I \rightarrow \tilde{V}_L \rightarrow V_L(t)$$

$$\frac{1}{dt} \rightarrow \tilde{V}_L$$



Review

Frequency response

1) magnitude plot

① sketch low freq asymptote

$\omega \rightarrow 0$

② : high freq

$\omega \rightarrow \infty$

③ Two asymptotes intersect at corner freq.

2) phase plot

① $\Phi_0 \pm \left(\frac{1}{j_0} \omega_c \right)$

② $\Phi_0 \pm (j\omega_c)$

③ At corner freq, the phase is 45° or -45°


— — —



Review

Plot $|H(j\omega)|$ and $\angle H(j\omega)$, $H(j\omega) = \frac{V_o}{V_i}$

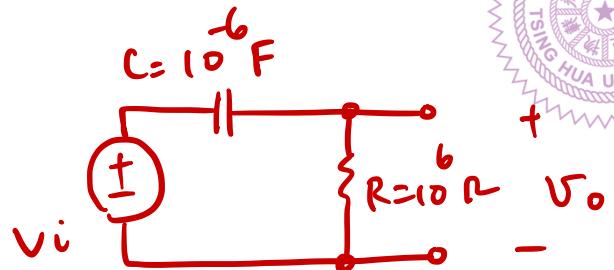Assume $V_i(t) = 5 \cos \omega t \rightarrow 5 \cdot e^{j\omega t}$



$$C \frac{d(V_i - V_o)}{dt} = \frac{V_o}{R} \Rightarrow$$

$$\frac{dV_i}{dt} = V_o + \frac{dV_o}{dt} = 5 \cdot j\omega \cdot e^{j\omega t}$$

$$\tan \frac{\omega}{\omega^2}$$


particular

$$V_o = A e^{j\omega t} \Rightarrow A = \frac{5 j\omega}{1 + j\omega}$$


$$|H| = \frac{\omega}{\sqrt{1 + \omega^2}}, \angle H = \tan^{-1}\left(\frac{1}{\omega}\right)$$

$$H = \frac{V_o}{V_i} = \frac{\frac{5 j\omega}{1 + j\omega}}{5} = \frac{j\omega}{1 + j\omega} = \frac{\omega^2}{\omega^2 + 1}$$

(dB)
 $|H|$ High-pass

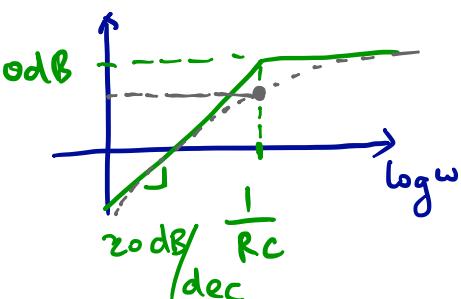

$$\omega_c = \frac{1}{RC}$$

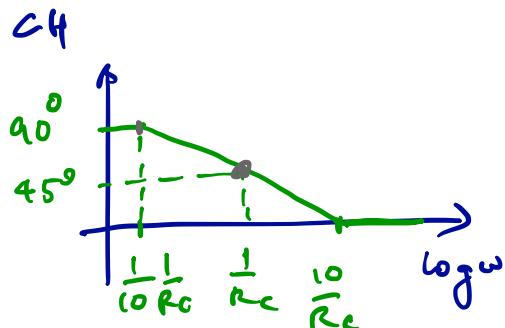



There You Have It!

1. Replace the (sinusoidal) source by their complex (or real) amplitude.

$$V_i \cos \omega t \rightarrow \underbrace{V_i e^{j\omega t}}$$


$$R \rightarrow R, C \rightarrow \frac{1}{j\omega C}, L \rightarrow j\omega L$$

2. Replace circuit elements by their **impedances**. The resulting diagram is called the impedance model of the network.

3. Determine the complex amplitude of voltages and currents in the circuit using any standard circuit analysis method.


4. Obtain the time variables from the complex amplitudes. For example, for a voltage signal with complex amplitude of V_o :

$$\Rightarrow \underbrace{V_o(t)}_{=} = \underbrace{|V_o| \cdot \cos(\omega t + \angle V_o)}$$

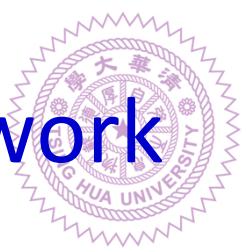

Another Example – Recall Series RLC Network

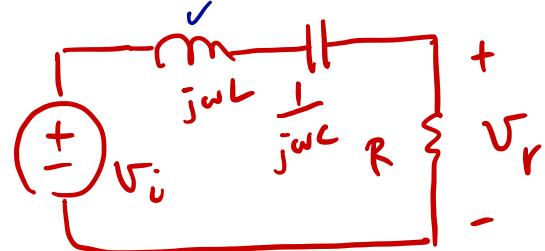- Remember, we only want the steady-state response to sinusoid.






$$V_i = V_i \cdot \cos \omega t \rightarrow V_i \cdot e^{i\omega t}$$

$$\sqrt{V_r} = |V_r| \cdot \cos(\omega t + \angle V_r)$$

= = = =
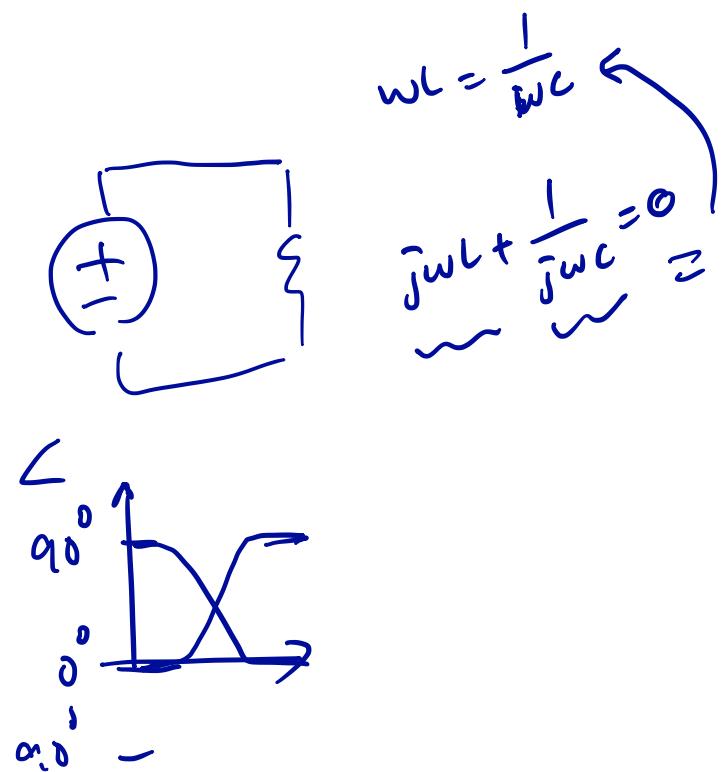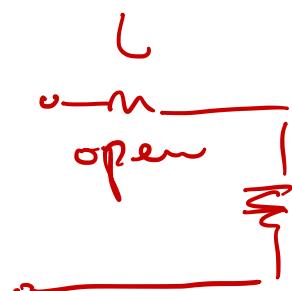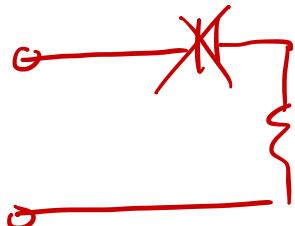
$$V_r = V_i \cdot \frac{R}{jwL + \frac{1}{jwC} + R}$$





Series RLC Network

H

- The transfer function

$$\frac{V_r}{V_i} = \frac{\frac{sR}{L}}{s^2 + \frac{sR}{L} + \frac{1}{LC}} = \frac{\frac{j\omega R}{L}}{-\omega^2 + \frac{j\omega R}{L} + \frac{1}{LC}}$$

- Review complex algebra in Appendix C of textbook!!



Graphically

- Magnitude plot $\left| \frac{V_r}{V_i} \right| = \frac{\omega RC}{\sqrt{(1 - \omega^2 LC)^2 + (\omega RC)^2}}$


• At low ω :

$$|H| \approx \omega RC$$

• At high ω :


$$|H| \approx \frac{\omega RC}{\omega^2 LC} = \frac{R}{\omega L}$$

• At $\omega = \frac{1}{\sqrt{LC}}$, $|H| \approx \frac{\omega RC}{\omega RC} = 1$

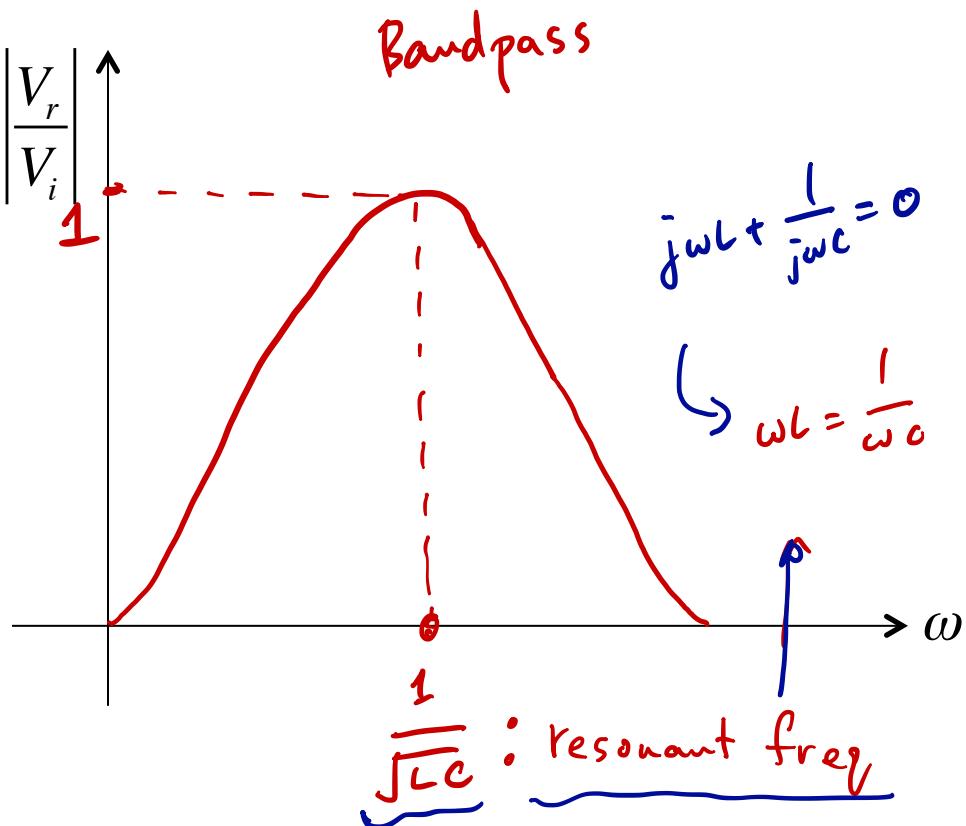

- Passes signals of frequencies in a middle band.

The Big Picture Again

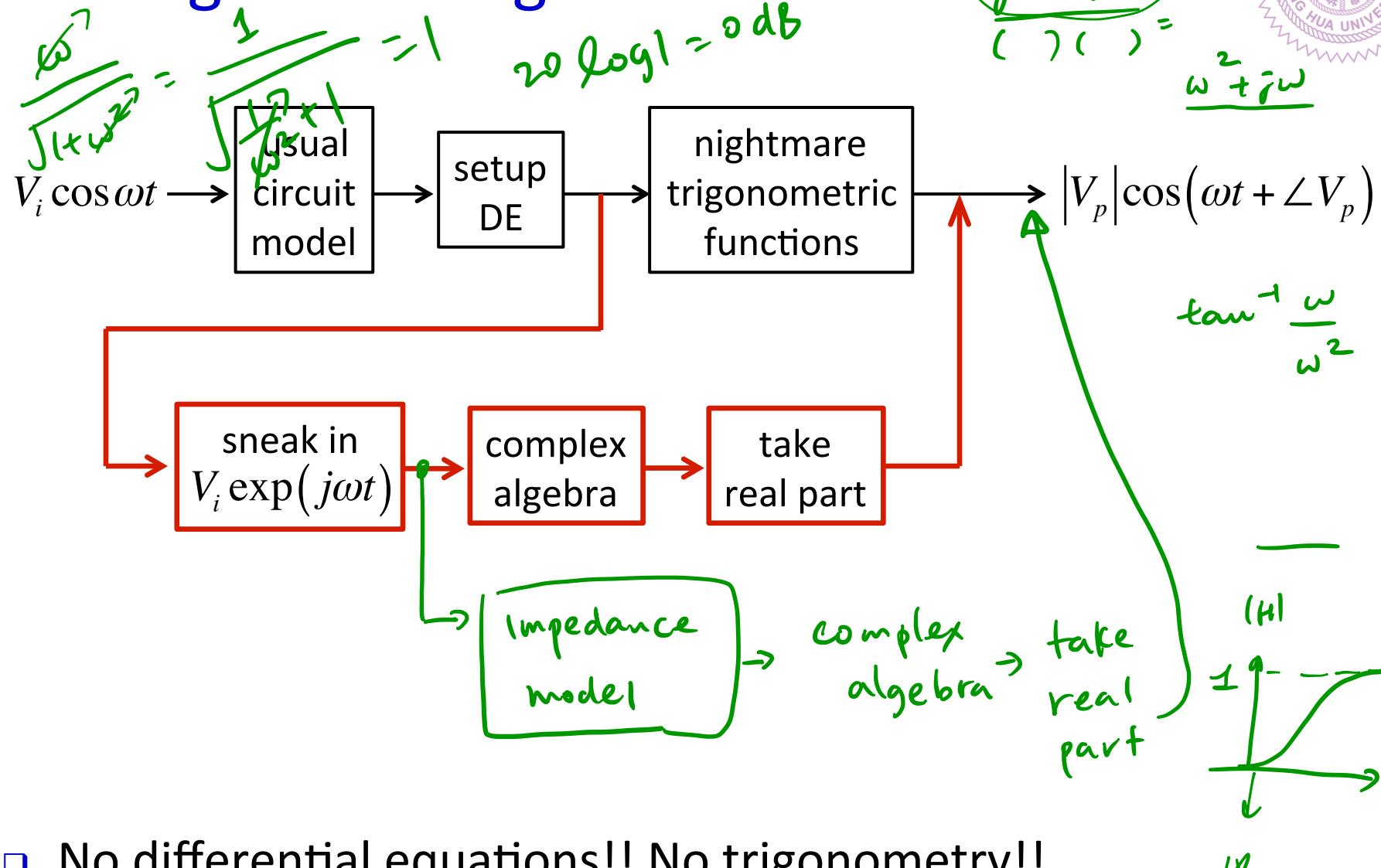

- No differential equations!! No trigonometry!!