

2/20/2019 (wed)



# Electric Circuits

## Lecture 2 Resistive Networks

EE2210, Spring 2019

Jenny Yi-Chun Liu

[jennyliu@gapp.nthu.edu.tw](mailto:jennyliu@gapp.nthu.edu.tw)



# Lecture Outline

- Review
- Chapter 2 in the textbook
  - Kirchoff's laws (KCL, KVL)
  - Voltage and current dividers
  - Series and parallel simplification
  - Dependent sources
  - Circuit analysis examples



# Review

## □ Lumped circuit element

- Element described by its v-i relation
- Power consumed by element is  $\mathbf{v \cdot i}$

## □ Lumped matter discipline (LMD)

1) ■  $\frac{\partial \phi_B}{\partial t} = 0$  outside elements

2) ■  $\frac{\partial q}{\partial t} = 0$  inside elements

3) ■ Signal speeds of interest should be way lower than speed of light.

□ Maxwell's equations simplify to algebraic KVL & KCL under LMD.

⦿ ■ Kirchhoff's Voltage Law (KVL):  $\sum_k v_k = 0$  for loop.

⦿ ■ Kirchhoff's Current Law (KCL):  $\sum_j i_j = 0$  for node.



# Example 1 –



## Terminal Variables and Power into a Resistor

- A resistor (10 Ohms) is connected to an arbitrary circuit at points x and y. Assume the current flowing into the network at node x is 2 A.

$$i_R = -2 \text{ A}$$

$$V = R \cdot i_R = 10 \cdot (-2) = -20 \text{ V}$$
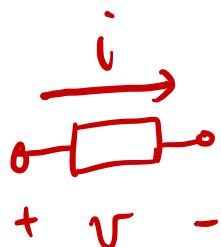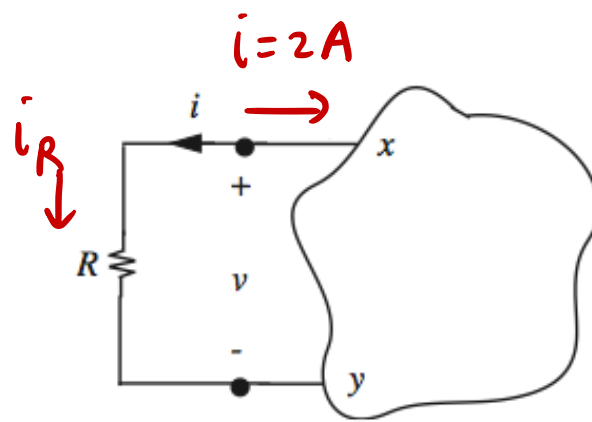
$$P = V \cdot i_R = (-20) \cdot (-2) = 40 \text{ Watt (Joule/sec)}$$



$$P = V \cdot i$$




## Example 2 – Power Supplied by a Battery

- The same example but replaced with a 3-V battery.

$$\dot{i}_1 = -2 \text{ A}$$


$$v = 3 \text{ V}$$

$$p = v \cdot i = -6 \text{ W}$$

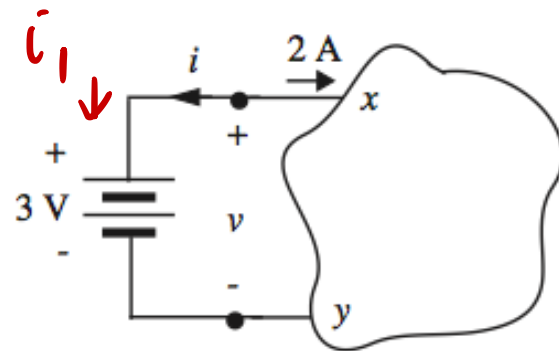

# Example 3 – AC (alternating current) Power

$\begin{cases} dc \\ ac \end{cases}$

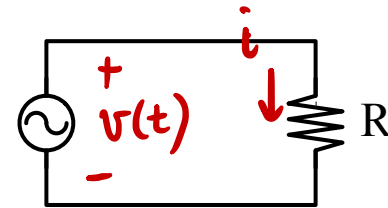


□ 110-V 60-Hz AC voltage,  $R = 50\Omega$

$$v(t) = \underbrace{\sqrt{2} \cdot 110}_{\text{amplitude (V)}} \cdot \sin(\underbrace{2\pi \cdot 60 t}_{\text{frequency (Hz)}})$$

$\sqrt{2} \cdot 110$

$$i(t) = \frac{v(t)}{50}$$
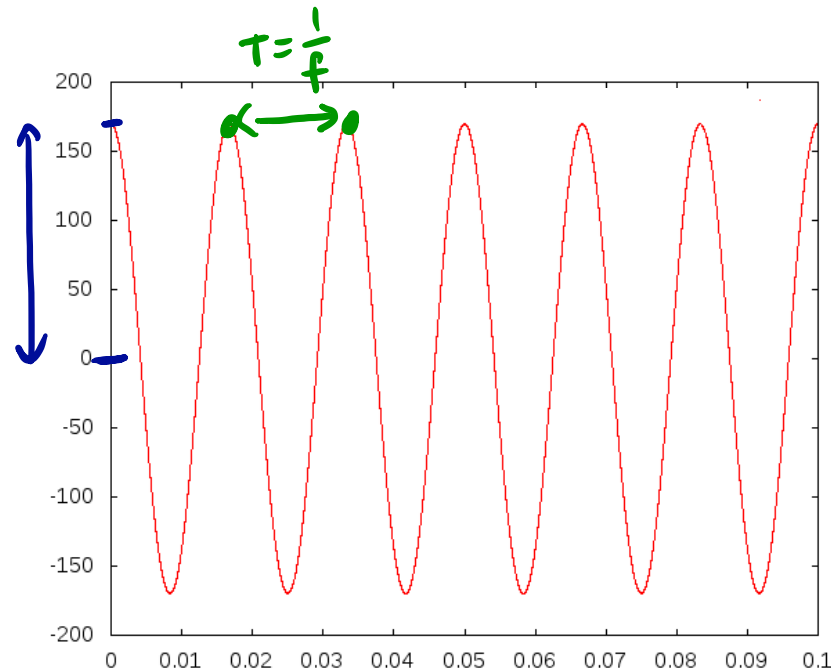
$$p(t) = \frac{110^2}{50} (1 - \cos(2\pi \cdot 120t))$$



□ What would be the power dissipated by the resistor if the voltage was a constant value of 110 V?

$$v(t) = 110 \text{ V} \quad p(t) = 110 \cdot \frac{110}{50}$$




## Chapter 2 Resistive Networks


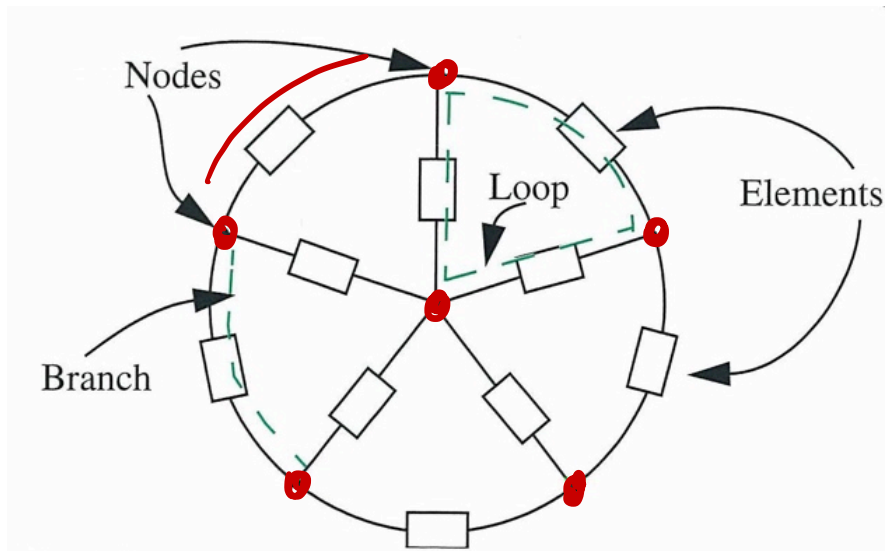
# Terminology

- Element is accessed through its terminals.
- Node: the junction point where the terminals of two or more elements are connected.
- Branch: the connection between nodes.
- Loop: a closed path through a circuit along its branches.




*6 nodes*  
*10 branches (10 elements)*




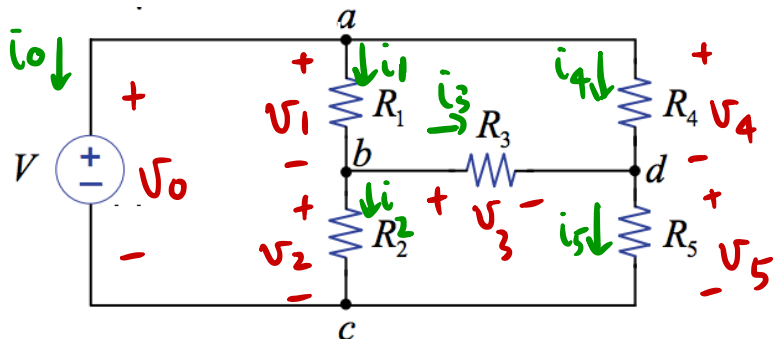
# Basic KVL/KCL Method of Circuit Analysis

- Analyzing a circuit means to find out all the element v's and i's.



6 elements, 12 unknowns  
( $v_0, v_1, \dots, v_5, i_0, i_1, \dots, i_5$ )

1. Label all elements' v's and i's.
2. Write element v-i relationship.

- For voltage source

- For current source


3. Write KCL for all nodes.
4. Write KVL for all loops.

- Basically lay out all equations...


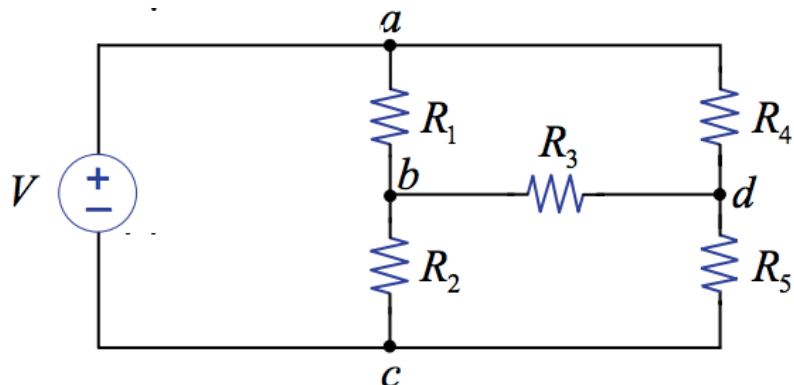
# Basic KVL/KCL Method of Circuit Analysis

- Goal: find out all element v's and i's (12 unknowns).
- Step 2: Write v-i relation for all elements.




*6 equations*

$$V_0 = V$$
$$V_1 = i_1 \cdot R_1$$
$$V_2 = i_2 \cdot R_2$$
$$V_3 = i_3 \cdot R_3$$
$$V_4 = i_4 \cdot R_4$$
$$V_5 = i_5 \cdot R_5$$


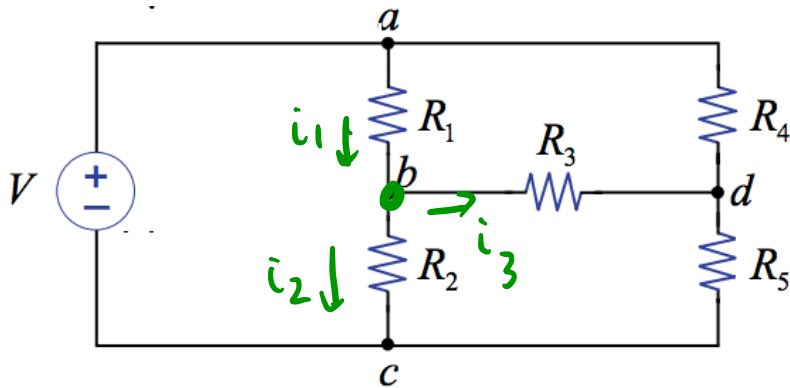
# Basic KVL/KCL Method of Circuit Analysis

- Goal: find out all element  $v$ 's and  $i$ 's (12 unknowns).
- Step 3: Apply KCL at the nodes.
  - Use convention: e.g., sum currents leaving the node.



$$\text{node a: } i_0 + i_1 + i_4 = 0$$

$$\text{node b: } i_2 + i_3 - i_1 = 0$$

$$\text{node c: } -i_0 - i_2 - i_3 = 0$$


$$\text{node d: } -i_3 - i_4 + i_5 = 0$$

4 equations, 3 independent equations


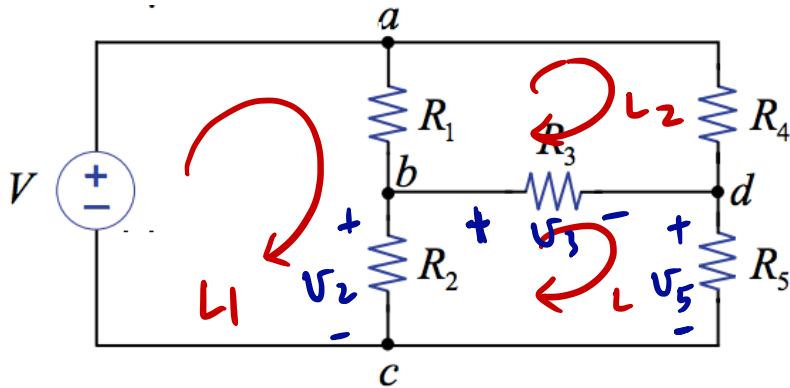
# Basic KVL/KCL Method of Circuit Analysis

- Goal: find out all element  $v$ 's and  $i$ 's (12 unknowns).
- Step 4: Apply KVL for the loops
  - Use convention: e.g., as you go around the loop, assign first encountered sign to each voltage.



$$L_1: v_1 + v_2 - v_0 = 0$$

$$L_2: v_4 - v_3 - v_1 = 0$$

$$L_3: v_5 - v_2 + v_3 = 0$$

3 independent equations



# Basic KVL/KCL Method of Circuit Analysis

□ 12 equations for 12 unknowns.

■ 1. Element  $v$ - $i$  relationships

$$v_0 = V_0 \quad v_3 = i_3 \cdot R_3$$

$$v_1 = i_1 \cdot R_1 \quad v_4 = i_4 \cdot R_4$$

$$v_2 = i_2 \cdot R_2 \quad v_5 = i_5 \cdot R_5$$


■ 2. KCL at the nodes

$$a: \quad i_0 + i_1 + i_4 = 0$$

$$b: \quad i_2 + i_3 - i_1 = 0$$

$$d: \quad i_5 - i_3 - i_4 = 0$$

$$c: \quad -i_0 - i_2 - i_5 = 0$$

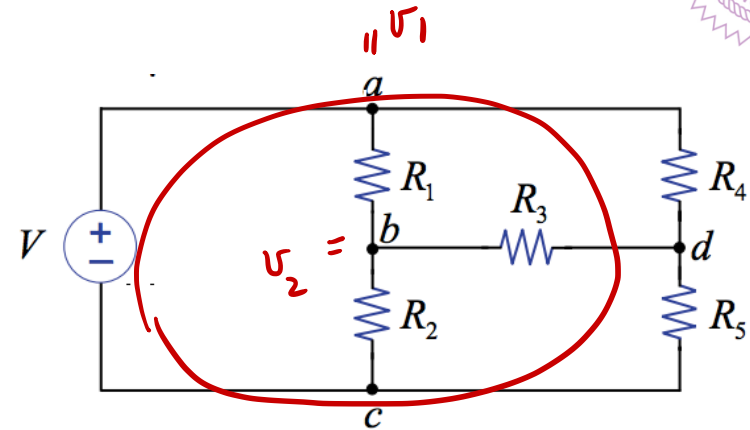

3. KVL for the loops

$$L1: \quad -v_0 + v_1 + v_2 = 0$$

$$L2: \quad v_1 + v_3 - v_4 = 0$$


$$L3: \quad v_3 + v_5 - v_2 = 0$$

$$L4: \quad -v_0 + v_4 + v_5 = 0$$

□ Circuit components are connected to each other on various nodes in the circuit.

■ Using node voltages, instead of component voltages, as the main variables can reduce the computation complexity.

# Voltage Divider

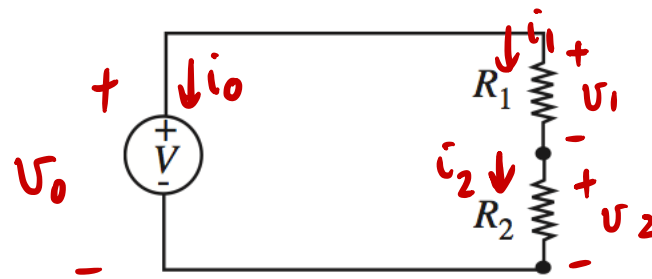

- An isolated loop with  $>2$  resistors and a voltage source in series.

## 1. Element relationship laws:

$$V_0 = V_0$$

$$V_1 = i_1 \cdot R_1$$

$$V_2 = i_2 \cdot R_2$$

## 2. KCL at nodes.

$$\text{node a: } i_1 + i_0 = 0$$

$$\text{node b: } i_1 - i_2 = 0$$

## 3. KVL for loops.

$$-V_0 + V_1 + V_2 = 0$$

$$\Rightarrow \left. \begin{array}{l} V_1 = V_0 \cdot \frac{R_1}{R_1 + R_2} \\ V_2 = V_0 \cdot \frac{R_2}{R_1 + R_2} \\ i_1 = i_2 = \frac{V_0}{R_1 + R_2} \end{array} \right\}$$



# Voltage Divider



## □ Voltage division

- The two resistors divide the voltage  $V$  in proportion to their resistance.

$$\frac{V_1}{V_2} = \frac{R_1}{R_2}$$

## □ Power into each resistor

$$P_1 = \underbrace{V_1}_{-} \cdot \underbrace{i_1}_{-} = \frac{V_0^2 \cdot R_1}{(R_1 + R_2)^2}$$

$$V_0 = V_0$$

$$P_2 = V_2 \cdot i_2 = \frac{V_0^2 \cdot R_2}{(R_1 + R_2)^2}$$

## □ Resistors in series

- Equivalent resistance

$$R_{eq} = \sum_i R_i$$

