

3/4/2019 (Mon)

•  $v(t) = \sqrt{2} \cdot 110 \cdot \sin(2\pi \cdot 60t)$

$f = 60 \text{ Hz}$   
 $f = \cancel{60} \text{ Hz}$

amplitude  
 $V_{\text{amp}}$

$$V_{\text{rms}} = \sqrt{\frac{1}{T} \int_0^T v^2(t) dt}, \quad T = \frac{1}{60} \text{ s}$$

$$V_{\text{rms}} = \frac{1}{\sqrt{2}} V_{\text{amp}}$$

$$= \sqrt{60 \int_0^{\frac{1}{60}} 2 \cdot 110^2 \cdot \sin^2(2\pi \cdot 60t) dt}$$

$$= \sqrt{60 \cdot \int_0^{\frac{1}{60}} 2 \cdot 110^2 \cdot \frac{1}{2} (1 - \cos(2 \cdot 2\pi \cdot 60t)) dt}$$

$$= \sqrt{60 \cdot 110^2 \cdot \int_0^{\frac{1}{60}} 1 - \cos(2 \cdot 2\pi \cdot 60t) dt} = \sqrt{60 \cdot 110^2 \cdot (t - \sin 4\pi \cdot 60t) \Big|_0^{\frac{1}{60}}}$$

$$= \sqrt{60 \cdot 110^2 \cdot \frac{1}{60}} = 110 \text{ V}$$

## • Review:

### - KCL, KVL

1) <sup>label</sup>  $v$ 's,  $i$ 's

2) <sup>write</sup>  $v$ - $i$  relationship of each component

3) write KVL, KCL


4) Solve KVL, KCL

### - Voltage divider: resistors in series


$$\frac{V_1}{V_2} = \frac{R_1}{R_2}$$

$$\frac{P_1}{P_2} = \frac{R_1}{R_2}$$

$$R_{eq} = \sum_i R_i$$

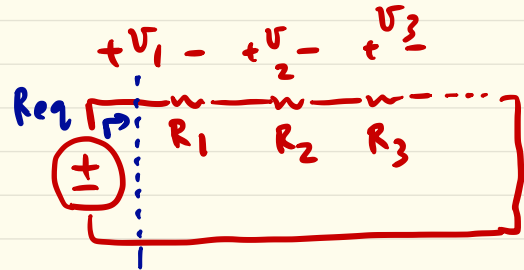

# Current Divider

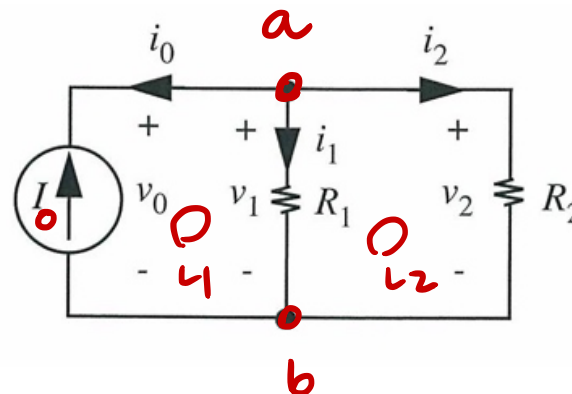

□ A node with >2 resistors and a current source in parallel.

## 1. Element relationship laws

$$i_0 = -I_0$$

$$v_1 = i_1 \cdot R_1$$

$$v_2 = i_2 \cdot R_2$$

## 2. KCL at nodes

$$\text{node a: } i_0 + i_1 + i_2 = 0$$

## 3. KVL for loops

$$L_1: -v_0 + v_1 = 0$$

$$L_2: -v_1 + v_2 = 0$$

$\Rightarrow$

$$i_1 = I_0 \frac{R_2}{R_1 + R_2}$$

$$i_2 = I_0 \frac{R_1}{R_1 + R_2}$$


$$v_0 = v_1 = v_2 = \frac{I_0}{\frac{1}{R_1} + \frac{1}{R_2}}$$

$$\text{let } \frac{1}{R_1} = G_1, \frac{1}{R_2} = G_2, v_1 = v_2 = \frac{I_0}{G_1 + G_2}$$

R: resistance (R), G: conductance ( $1/R$ )<sup>16</sup>



# Current Divider

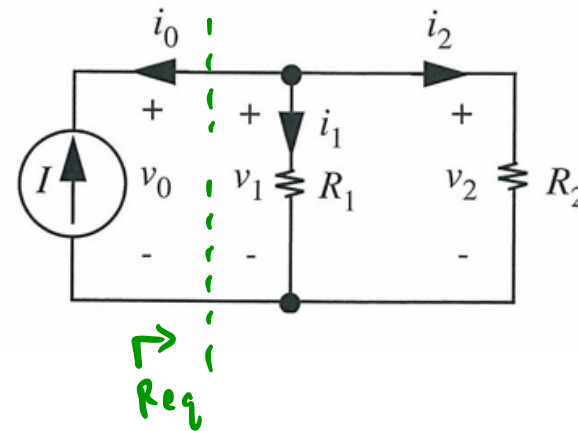


## Current division

- The two resistors divide the current  $I$  in proportion to their conductance.

$$\frac{i_1}{i_2} = \frac{G_1}{G_2} = \frac{R_2}{R_1}$$
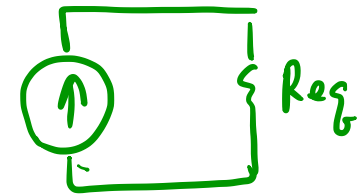
## Power into each resistor

$$P_1 = v_1 \cdot i_1 = \frac{I_0^2 \cdot G_1}{(G_1 + G_2)^2}, \quad P_2 = v_2 \cdot i_2 = \frac{I_0^2 \cdot G_2}{(G_1 + G_2)^2}$$



$$\frac{P_1}{P_2} = \frac{G_1}{G_2}$$

## Resistors in parallel

- Equivalent conductance

$$G_{eq} = G_1 + G_2, \quad R_{eq} = \frac{1}{G_{eq}} = \frac{1}{G_1 + G_2} = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2}}$$


$$G_{eq} = \sum_i G_i$$

$$R_{eq} = \frac{1}{\sum_i \frac{1}{R_i}}$$




# Element Combination Simplification

## Resistors in series

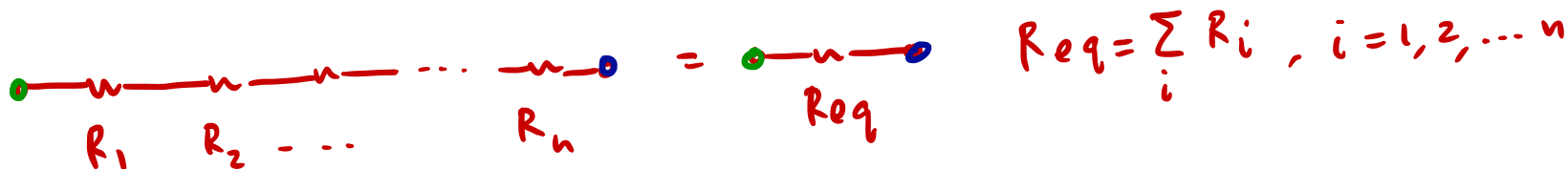

## Resistors in parallel

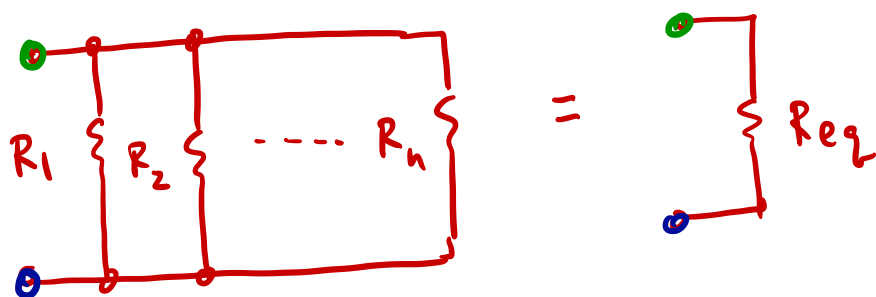



$$R_{eq} = \frac{1}{G_{eq}} = \frac{1}{\sum_i G_i}, \quad i=1, 2, \dots, n$$

$$\frac{1}{R_{eq}} = \sum_k \frac{1}{R_k}, \quad k=1, 2, \dots, n$$




# Element Combination Simplification



• Voltage sources in series

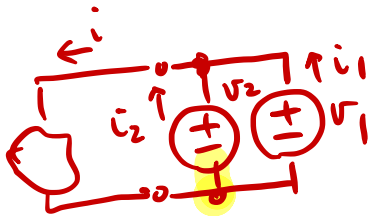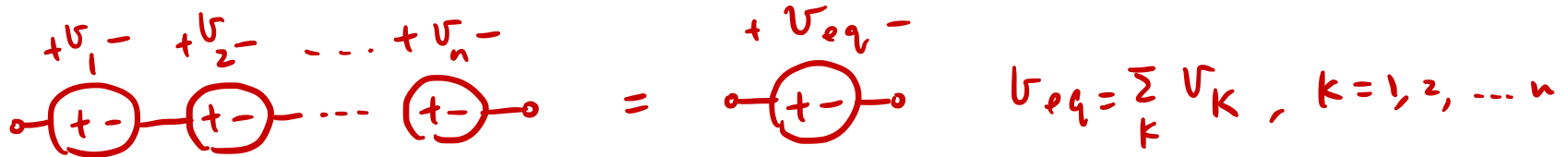

• Current sources in parallel

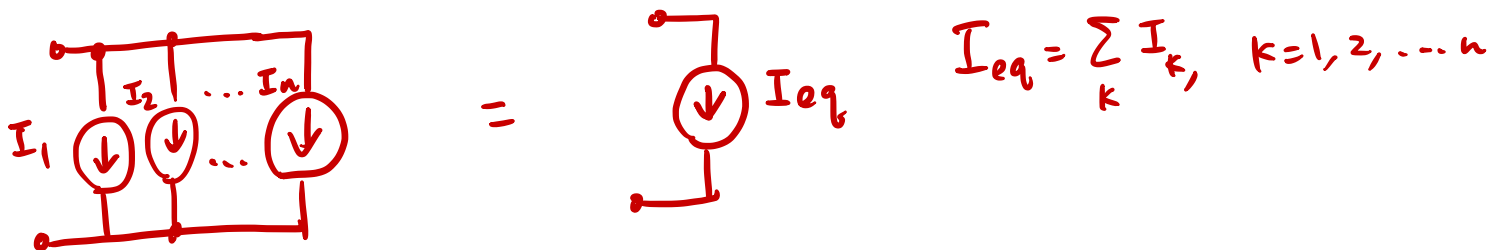
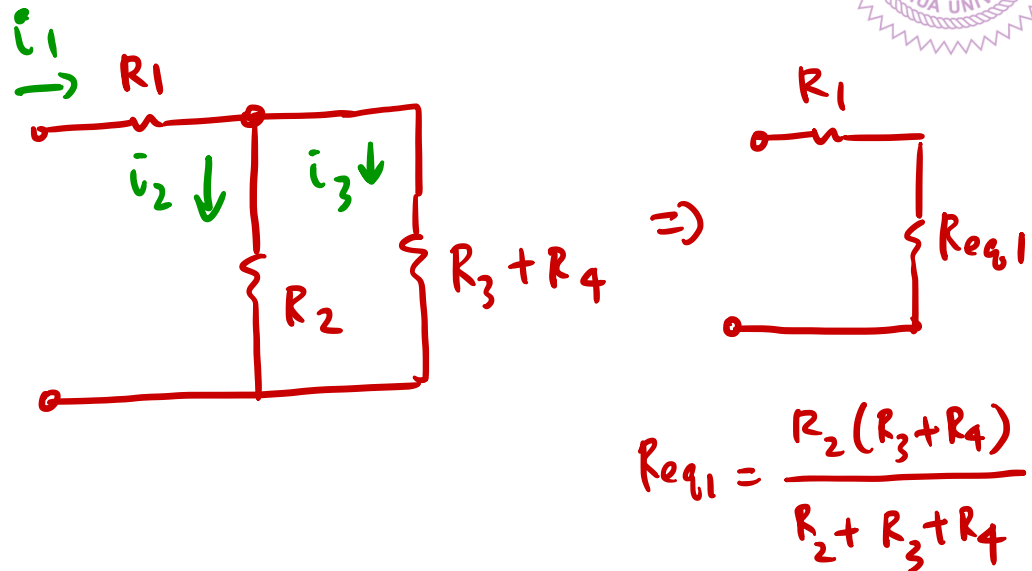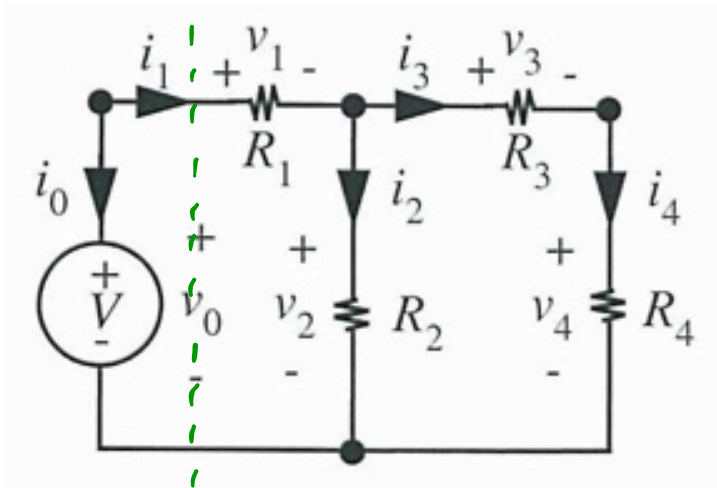
# Circuit Analysis with Element Combination Technique



$\Rightarrow$   $R_{eq} = R_1 + \frac{R_2(R_3 + R_4)}{R_2 + R_3 + R_4}$ ,  $i_1 = \frac{V_0}{R_{eq}}$

$V_1 = i_1 \cdot R_1$



$V_2 = V_0 - V_1$ ,  $i_2 = \frac{V_2}{R_2}$

$i_3 = i_4 = i_1 - i_2$ ,  $V_3 = i_3 \cdot R_3$ ,  $V_4 = i_4 \cdot R_4$
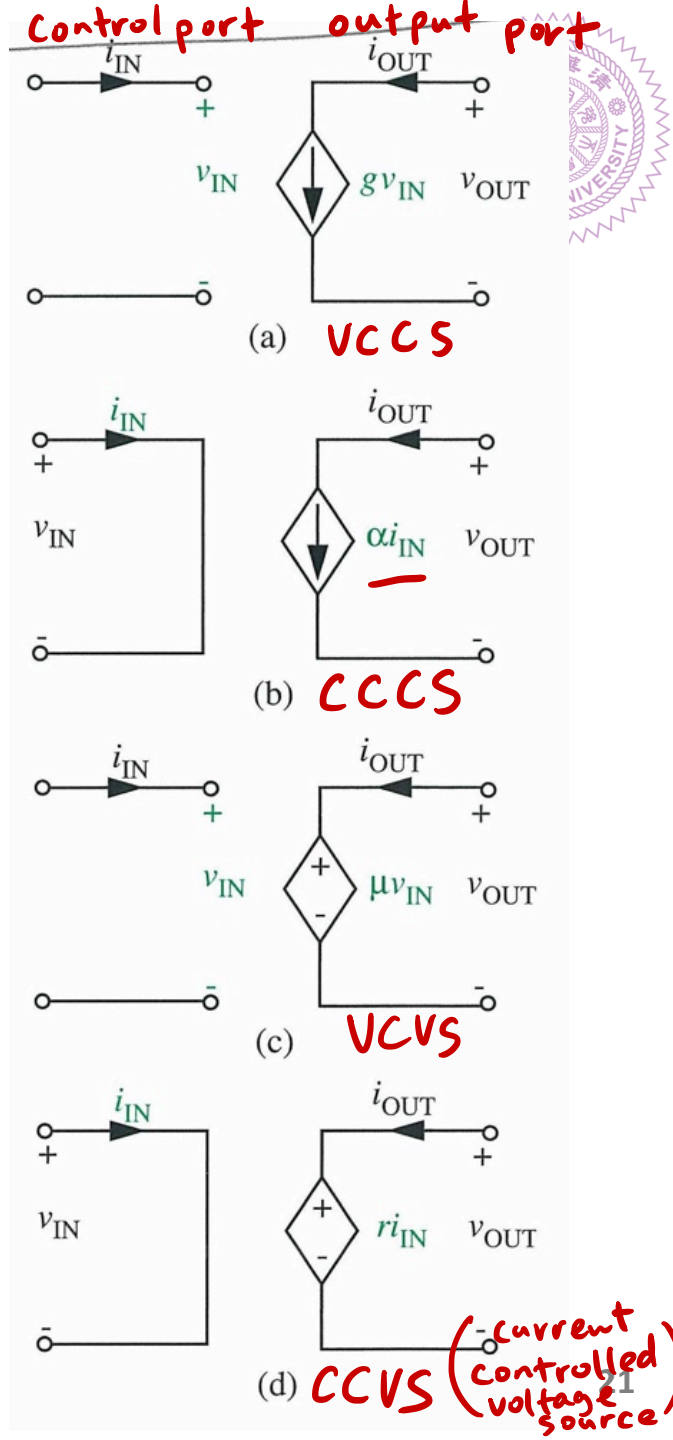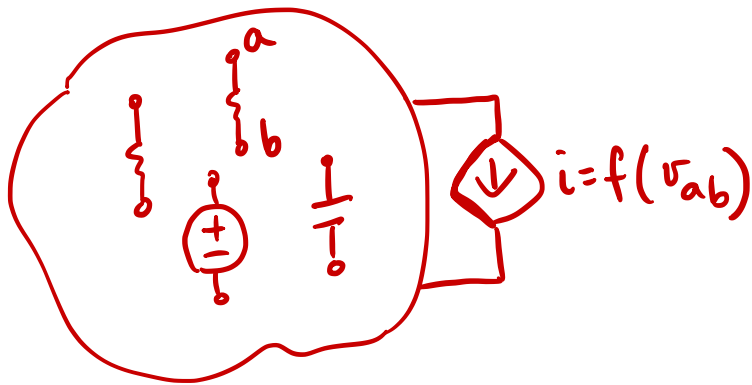
# Dependent Sources

(can be linear or nonlinear)  
2-port element

- Independent sources: the values (voltages, currents) are independent of circuit operation. (1 port element)
- Dependent sources: the values are controlled by some other parameters in the system.






## Dependent source

Example 1.

CCVS

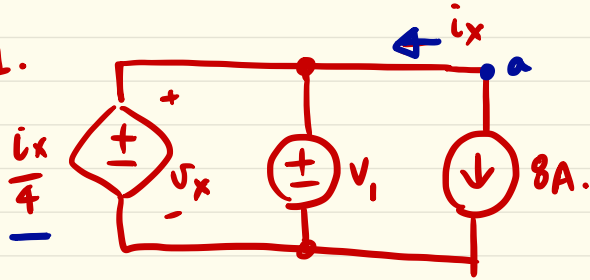

Find  $V_1$ .


$$\text{KCL: } 8 + i_x = 0$$

$$U_x = \frac{i_x}{4}$$

$$i_x = -8 \text{ A}, \quad U_x = \frac{-8}{4} = -2 \text{ V}$$

$$V_1 = -2 \text{ V}$$

Example 2. Find  $V_1$

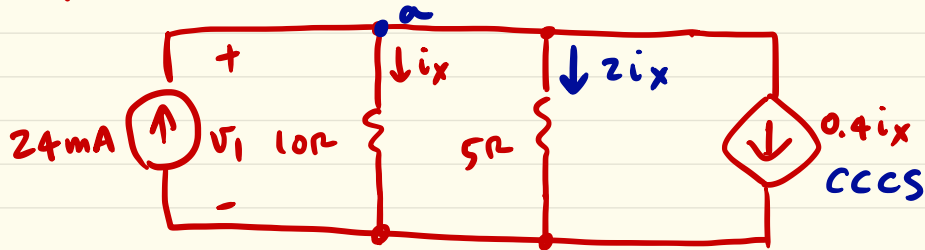

KCL


node a:  $24\text{mA} = i_x + 2i_x + 0.4i_x$

$$\Rightarrow i_x = 7.05\text{mA}$$

$$V_1 = i_x \cdot 10 = 70.5\text{mV}$$



# Circuit Analysis Example I

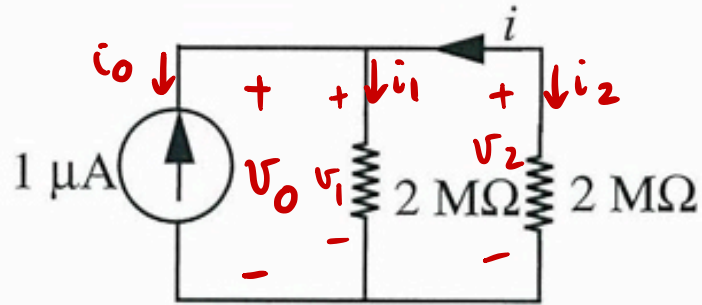

1)  $i_0 = -1 \mu A$

$$v_1 = i_1 \cdot 2M$$

$$v_2 = i_2 \cdot 2M$$

2) KCL:  $i_0 + i_1 + i_2 = 0$

3) KVL:  $v_0 = v_1$

$$v_1 = v_2$$


4) Solve equations

$$i_1 = i_2 = -\frac{1}{2} i_0 = 0.5 \mu A$$

$$v_0 = v_1 = v_2 = 0.5 \mu A \cdot 2M \Omega = 1 V$$



# Circuit Analysis Example II

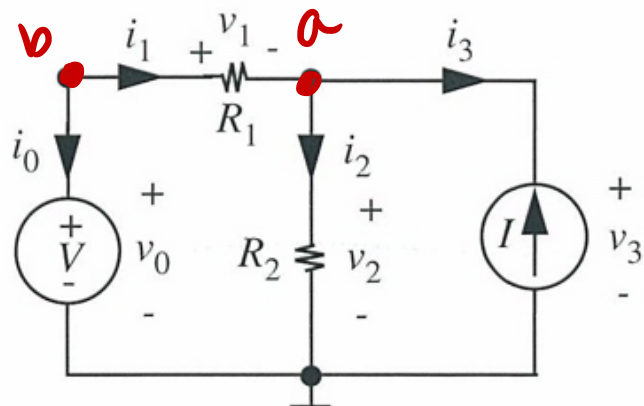

1)  $V_0 = V$

$$V_1 = i_1 R_1$$

$$V_2 = i_2 R_2$$

$$i_3 = -I$$

2) KCL :

node a :  $i_1 - i_2 - i_3 = 0$

node b :  $i_0 + i_1 = 0$

3) KVL =

L1 :  $V_0 - V_1 - V_2 = 0$

L2 :  $V_2 - V_3 = 0$

4)  $i_0 = -i_1 = \frac{R_2}{R_1 + R_2} I - \frac{1}{R_1 + R_2} V$

$$i_2 = \frac{R_1}{R_1 + R_2} I + \frac{1}{R_1 + R_2} V$$

$$i_3 = -I$$

$$V_0 = V$$

$$V_1 = -\frac{R_1 R_2}{R_1 + R_2} I + \frac{R_1}{R_1 + R_2} V$$

$$V_2 = V_3 = \frac{R_1 R_2}{R_1 + R_2} I + \frac{R_2}{R_1 + R_2} V$$