



# Electric Circuits

## Lecture 3 Network Theorems

EE2210, Spring 2019

Jenny Yi-Chun Liu

[jennyliu@gapp.nthu.edu.tw](mailto:jennyliu@gapp.nthu.edu.tw)



# Lecture Outline

## □ Review

- KCL, KVL (method 1)
- Element combination (method 2)

## □ Chapter 3 in the textbook

- Node analysis (method 3)
- Linearity
- Superposition (method 4)
- Thévenin and Norton (method 5 and 6)





## Chapter 3 Network Theorems



# Node Voltage

- Node voltage: the potential difference between the given node and a reference node, which is usually ground (zero V).
  - Current flows from the node with higher potential to the node with lower potential.
  - It is common to choose the node that has the maximum number of elements connected to it as the reference node.

# Example – Reference Node

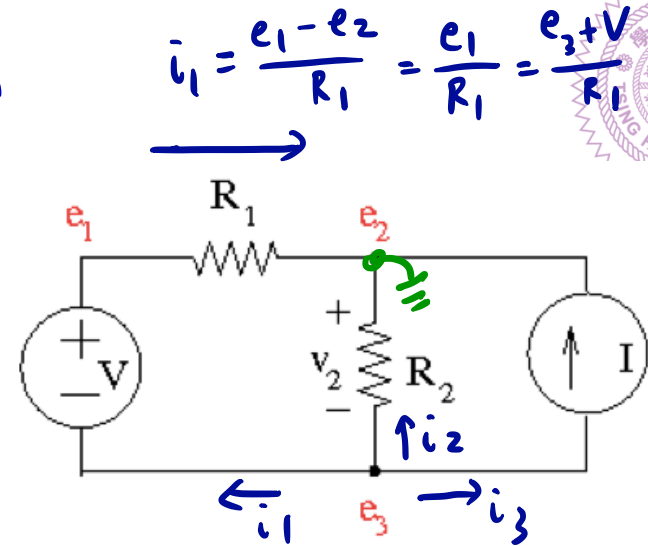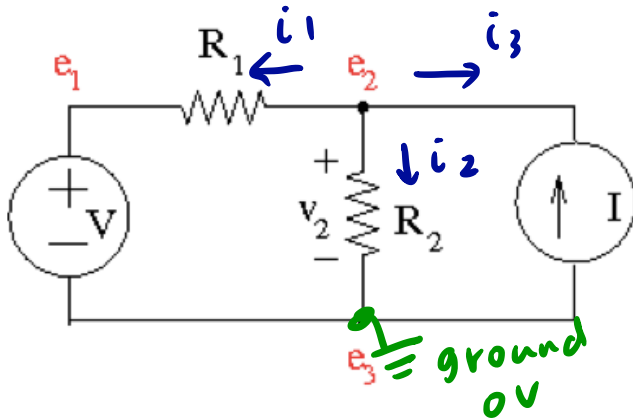

Given  $V=5V$ ,  $I=3A$ ,  $R_1=3\Omega$ ,  $R_2=5\Omega$

Case 1: Set  $e_3$  as reference node

KCL at  $e_2$ :  $i_1 + i_2 + i_3 = 0$

$$\Rightarrow \frac{e_2 - e_1}{R_1} + \frac{e_2}{R_2} - I = 0$$

$$\Rightarrow \frac{e_2 - 5}{3} + \frac{e_2}{5} - 3 = 0 \Rightarrow e_2 = 8.75V$$

Case 2: Set  $e_2$  as reference node

KCL at  $e_3$ :  $i_1 + i_2 + i_3 = 0$

$$\Rightarrow \frac{e_3 + V}{R_1} + \frac{e_3}{R_2} + I = 0$$

$$\Rightarrow \frac{e_3 + 5}{3} + \frac{e_3}{5} + 3 = 0 \Rightarrow e_3 = -8.75V$$



# Method 3: Node Analysis

- The most efficient utilization of KCL and circuit elements' laws to solve for the voltages and currents of all elements of a given circuit.




1. Select a node as a reference (ground) node.
2. Label node voltages to the remaining nodes with respect to ground.
  - These are the primary unknowns.
3. Apply KCL to all but the ground node.  
Use device laws to express the branch currents in terms of node voltages.
4. Solve the  $n - 1$  equations for node voltages.
5. Calculate all branch voltages and currents based on elements' laws.



# Example – Using Node Method

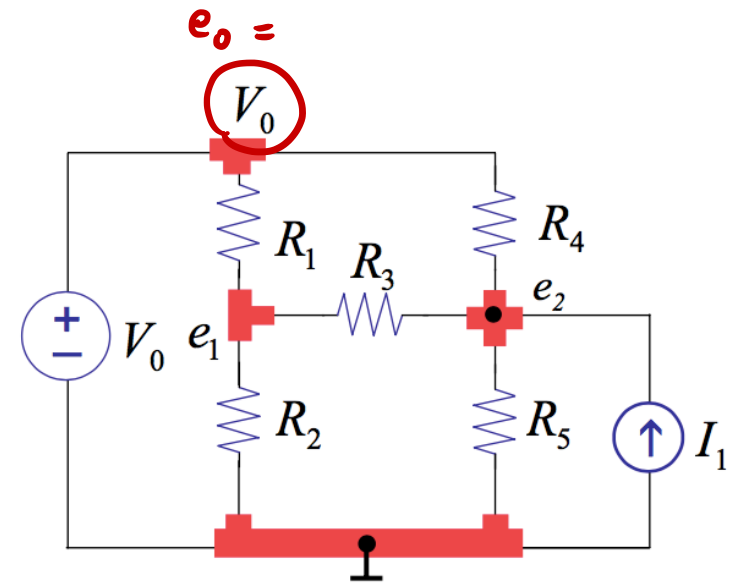1. Select a node as a reference (ground) node.
  2. Label node voltages to the remaining nodes with respect to ground.
- 4 nodes*





# Example – Using Node Method


3. Apply KCL to all but the ground node. Use device laws to express the branch currents in terms of node voltages.
  - For convenience, write  $G_i = \frac{1}{R_i}$
  - To avoid mistakes use convention: e.g., always sum currents leaving a node

$$\text{KCL @ } e_1: \frac{e_1 - v_0}{R_1} + \frac{e_1 - e_2}{R_3} + \frac{e_1}{R_2} = 0$$

$$\Rightarrow (e_1 - v_0)G_1 + (e_1 - e_2)G_3 + e_1 \cdot G_2 = 0 \quad (1)$$

$$\text{KCL @ } e_2: (e_2 - v_0) \cdot G_4 + (e_2 - e_1) \cdot G_3 + e_2 \cdot G_5 - I_1 = 0 \quad (2)$$

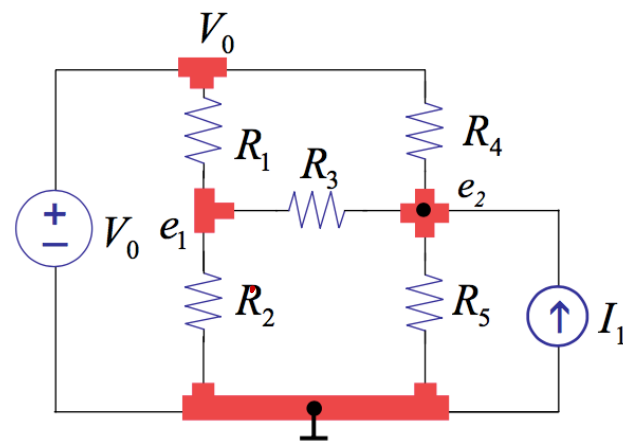From (1) and (2), express  $e_1, e_2$  as a function of  $v_0, I_1, G_1, G_2, G_3, G_4, G_5$








# Example – Using Node Method

4. Solve the  $n - 1$  equations for node voltages

$$\text{KCL at } e_1 \quad (e_1 - V_0)G_1 + (e_1 - e_2)G_3 + (e_1 - 0)G_2 = 0$$

$$\text{KCL at } e_2 \quad (e_2 - e_1)G_3 + (e_2 - V_0)G_4 + (e_2 - 0)G_5 - I_1 = 0$$
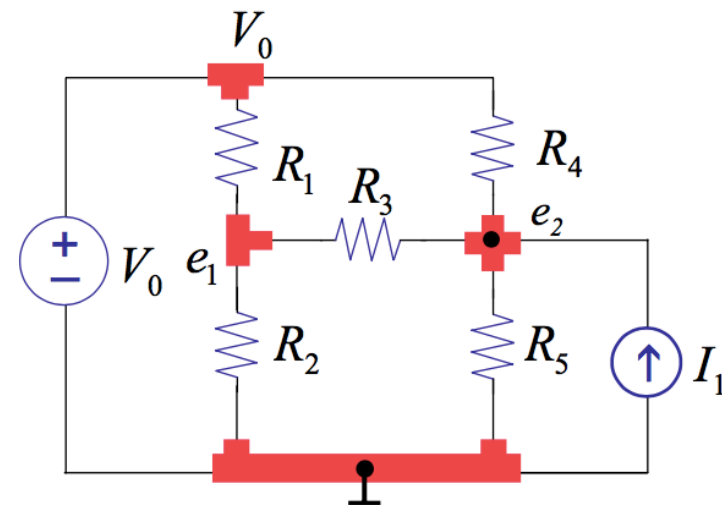
$$\begin{cases} e_1 (G_1 + G_2 + G_3) + e_2 (-G_3) = V_0 \cdot G_1 \\ e_1 (-G_3) + e_2 (G_3 + G_4 + G_5) = V_0 \cdot G_4 + I_1 \end{cases}$$



- linear equations with 2 unknowns
- Check the units



# Example – Using Node Method

5. Calculate all branch voltages and currents based on elements' laws.

$$v = i \cdot R$$

