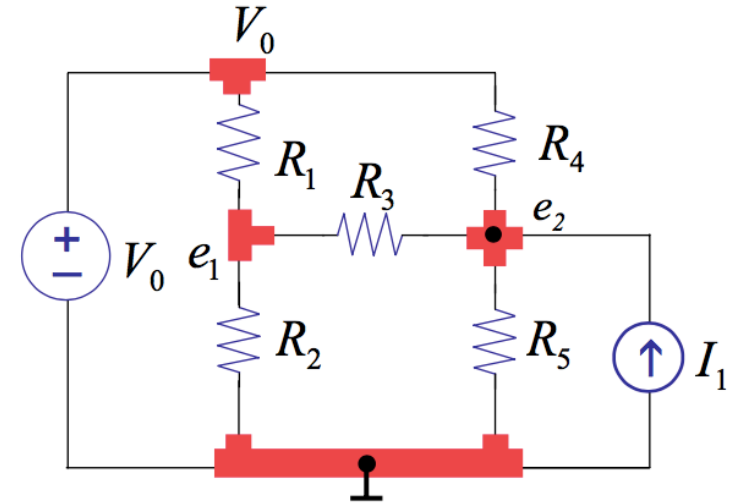




# 3/6/2019 (Wed) Revisit Step 4

$$\begin{cases} e_1(G_1 + G_2 + G_3) + e_2(-G_3) = V_0(G_1) \\ e_1(-G_3) + e_2(G_3 + G_4 + G_5) = V_0(G_4) + I_1 \end{cases}$$



• In matrix form:

$$\left[ \begin{array}{c|c} G_1 + G_2 + G_3 & -G_3 \\ \hline -G_3 & G_3 + G_4 + G_5 \end{array} \right] \begin{bmatrix} e_1 \\ e_2 \end{bmatrix} = \begin{bmatrix} G_1 V_0 \\ G_4 V_0 + I_1 \end{bmatrix} = \begin{bmatrix} G_1 & 0 \\ G_4 & 1 \end{bmatrix} \begin{bmatrix} V_0 \\ I_1 \end{bmatrix}$$

↑ conductivity matrix     
 ↑ unknown node voltages     
 ↑ sources




# Revisit Step 4

$$\left[ \begin{array}{c|c} G_1 + G_2 + G_3 & -G_3 \\ \hline -G_3 & G_3 + G_4 + G_5 \end{array} \right] \begin{bmatrix} e_1 \\ e_2 \end{bmatrix} = \begin{bmatrix} G_1 V_0 \\ G_4 V_0 + I_1 \end{bmatrix}$$

$$e_1 = \frac{(G_3 + G_4 + G_5)(G_1 V_0) + (G_3)(G_4 V_0 + I_1)}{G_1 G_3 + G_1 G_4 + G_1 G_5 + G_2 G_3 + G_2 G_4 + G_2 G_5 + G_3 G_4 + G_3 G_5}$$

$$e_2 = \frac{(G_3)(G_1 V_0) + (G_1 + G_2 + G_3)(G_4 V_0 + I_1)}{G_1 G_3 + G_1 G_4 + G_1 G_5 + G_2 G_3 + G_2 G_4 + G_2 G_5 + G_3 G_4 + G_3 G_5}$$

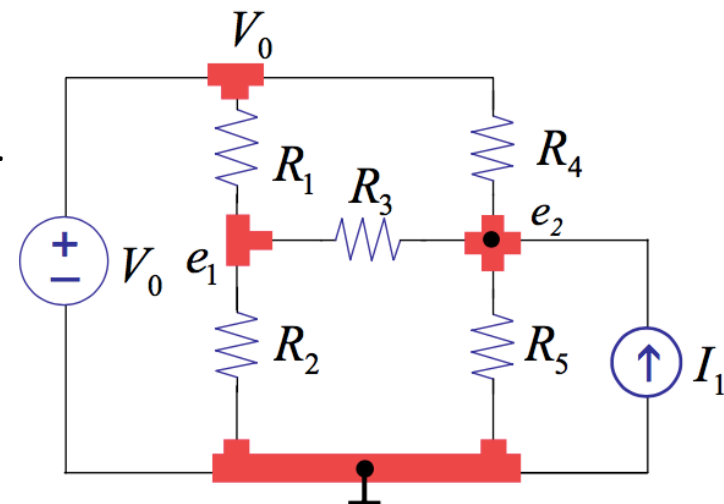
- The same denominator for  $e_1$  and  $e_2$ .
- No negative terms in denominator.
- Linear in  $V_0$  and  $I_1$ .





# More Example – Node Method

□ Determine the current  $i$ .

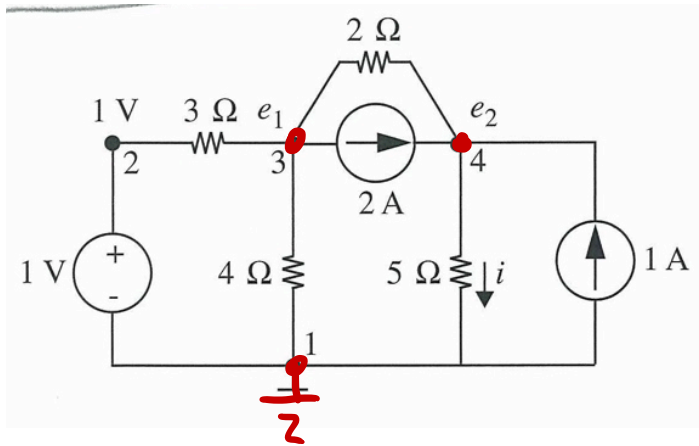

1. Choose node 1 = ground (0 V)

2. Label the nodes ( $e_1, e_2$ )

3. KCL @  $e_1$ :  $\frac{e_1 - 1}{3} + \frac{e_1}{4} + \frac{e_1 - e_2}{2} + 2 = 0$


KCL @  $e_2$ :  $-2 + \frac{e_2 - e_1}{2} + \frac{e_2}{5} - 1 = 0$

4. Solve KCL  $\Rightarrow e_1 = 0.05 \text{ V}, e_2 = 4.75 \text{ V}$


5.  $i = \frac{e_2}{5} = 0.95 \text{ A}$



# Floating Independent Sources

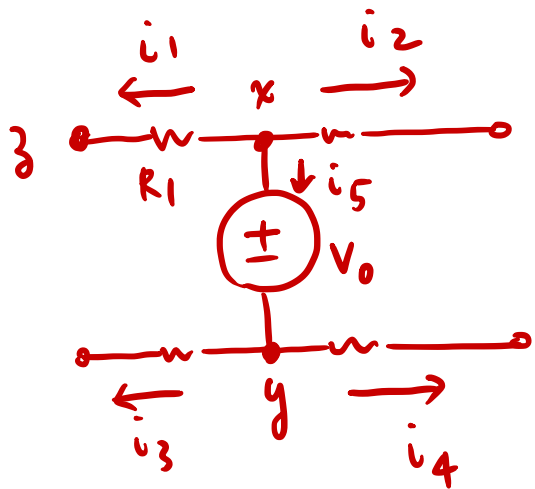
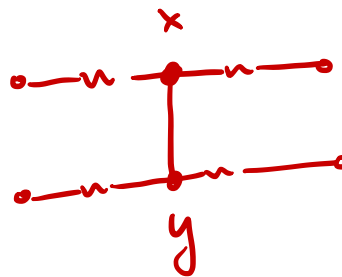
$$\begin{aligned} \text{KCL @ } x \quad i_1 + i_2 + i_5 &= 0 \\ + \quad \text{@ } y \quad i_3 + i_4 - i_5 &= 0 \\ \hline \Rightarrow i_1 + i_2 + i_3 + i_4 &= 0 \end{aligned}$$




$x, y$ : supernode



# Linearity 线性关系

□ Consider this circuit

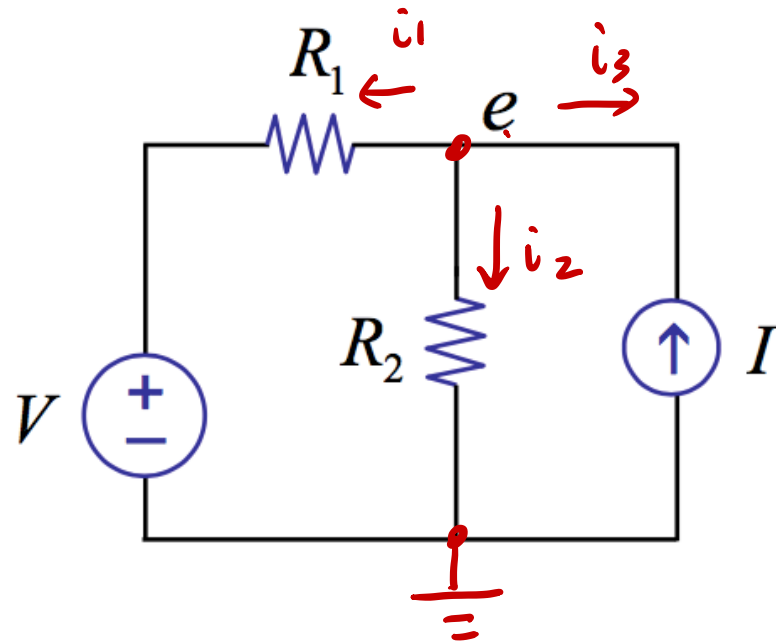

□ Write node equation.

$$\text{KCL @ } e; \quad \frac{e-V}{R_1} + \frac{e}{R_2} - I = 0$$


$e, V, I$  have linear relationship (no  $e^2, eV, I^2, \sqrt{e}, \dots$ )



# Linearity
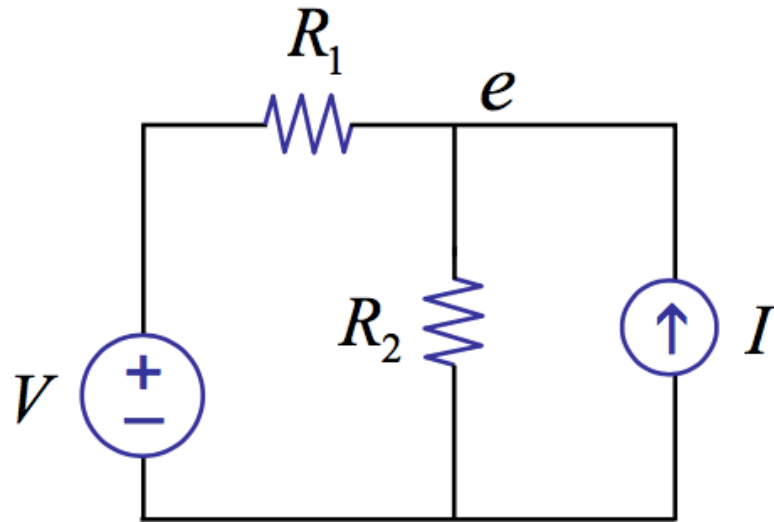
## □ Node equation

$$\frac{e-V}{R_1} + \frac{e}{R_2} - I = 0 \quad \text{linear in } e, V, I$$



$$\left(\frac{1}{R_1} + \frac{1}{R_2}\right) \cdot e = \frac{V}{R_1} + I$$

$$\Rightarrow e = \underbrace{\frac{R_2}{R_1 + R_2} V}_{e_1} + \underbrace{\frac{R_1 R_2}{R_1 + R_2} I}_{e_2}$$


$$\Rightarrow \underbrace{(G_1 + G_2)}_{\text{conductivity matrix}} \cdot \underbrace{e}_{\text{unknown}} = \underbrace{\frac{V}{R_1} + I}_{\text{source matrix}}$$

Source matrix  
(linear sum of all sources)
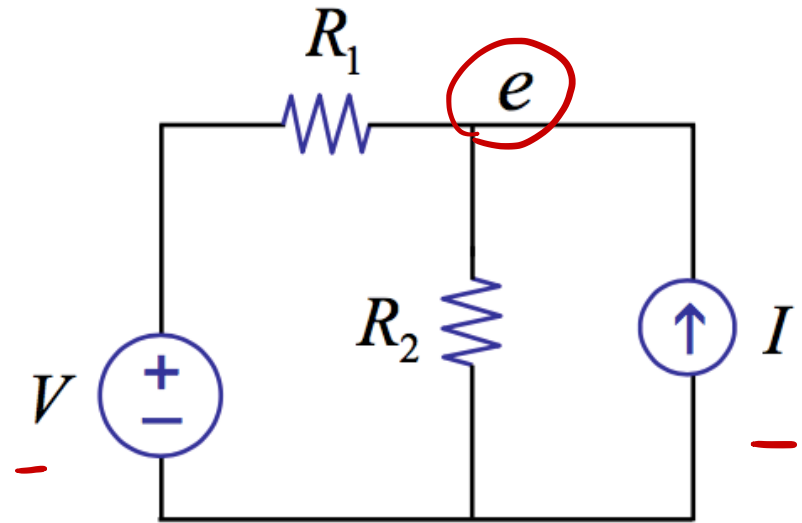
# Linearity ✗

$$\frac{e-V}{R_1} + \frac{e}{R_2} - I = 0$$

$$\left[ \frac{1}{R_1} + \frac{1}{R_2} \right] \cdot e = \frac{V}{R_1} + I$$



# Linearity

$R, L, C$ , independent source




## □ Linearity

1. ■ Homogeneity
2. ■ Superposition



# Homogeneity (scaling)


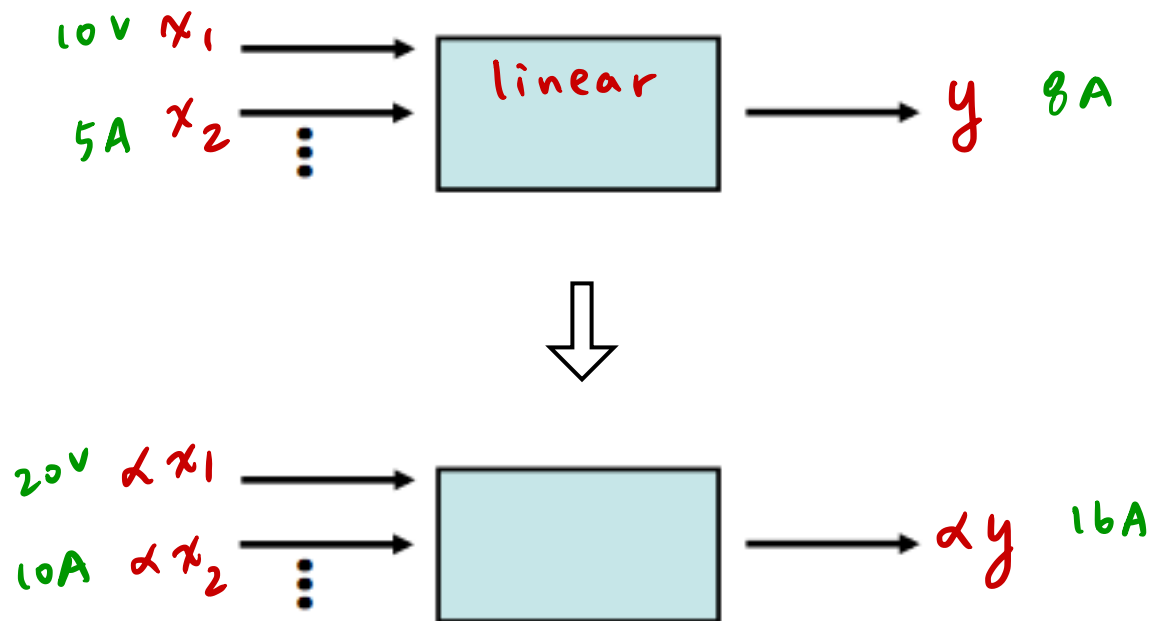


$\alpha$ : scaling factor

$$y = f(x)$$

$$\alpha y = f(\alpha x)$$

# Superposition

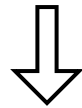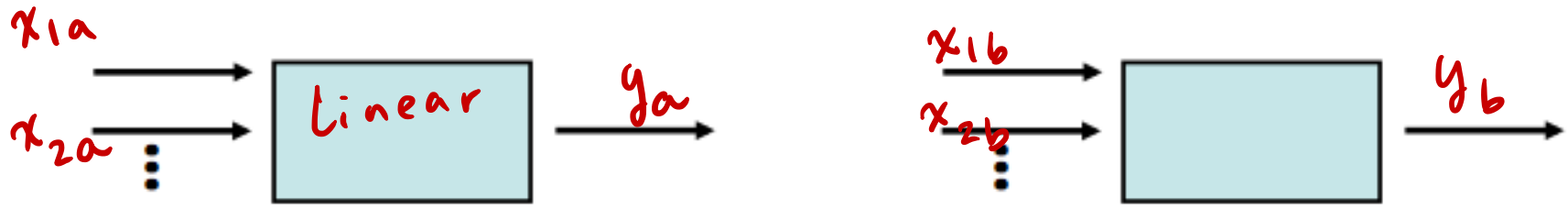

$$y_a = f(x_a)$$



$$y_b = f(x_b)$$

$$\Rightarrow y_a + y_b = f(x_a + x_b)$$

$$f(ax_1 + bx_2) = a f(x_1) + b f(x_2)$$



# Specific Superposition Example

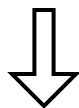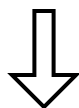

$e_1, e_2$ : partial response

$e$ : total response




# Method 4: Superposition

1. Find the partial responses of the circuit to each source acting along.
  2. Sum the individual responses.
- \* Dependent sources remain active at all time. Only the independent sources are turned ON and OFF.**



# Each Source Acting Alone Means...

- Voltage source

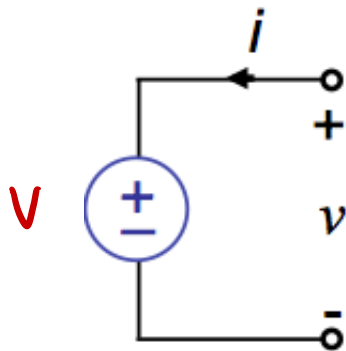


$$V = 0$$



short

- Current source

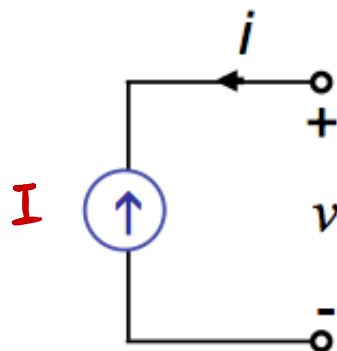

$$I = 0$$





open



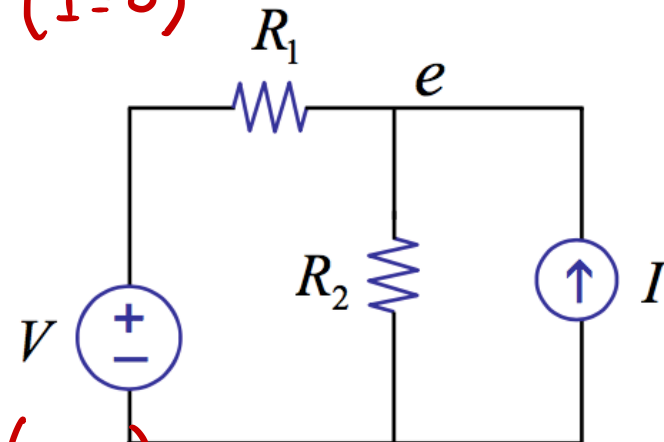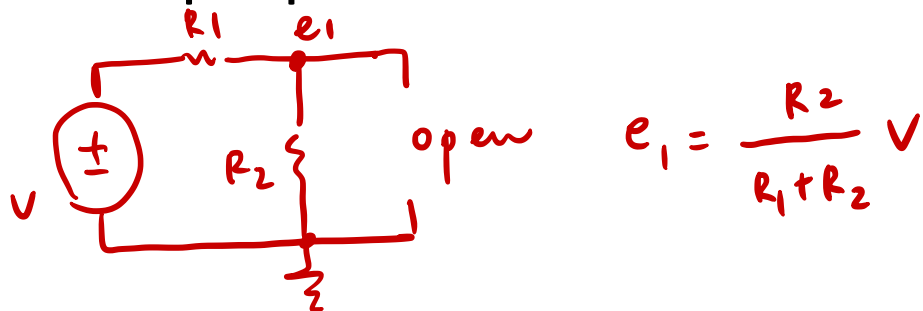
# Example – Analysis Using Superposition

- Superposition – with  $V$  acting alone ( $I=0$ )



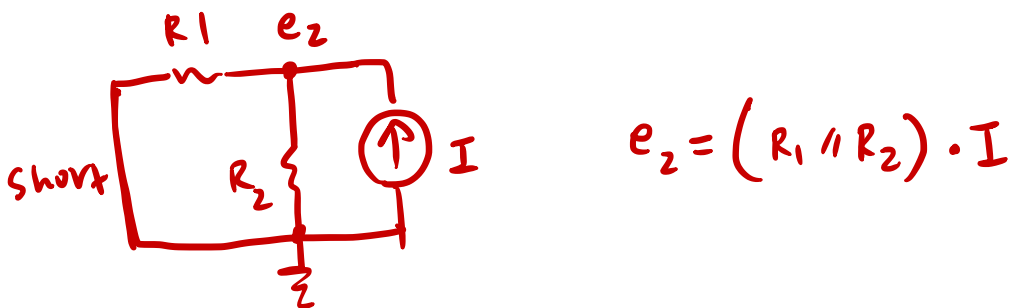- Superposition – with  $I$  acting alone ( $V=0$ )




- Sum two partial responses

$$\text{Total response } e = e_1 + e_2 = \frac{R_2}{R_1 + R_2} V + \frac{R_1 R_2}{R_1 + R_2} I$$




# Example – Resistive Adder Circuit

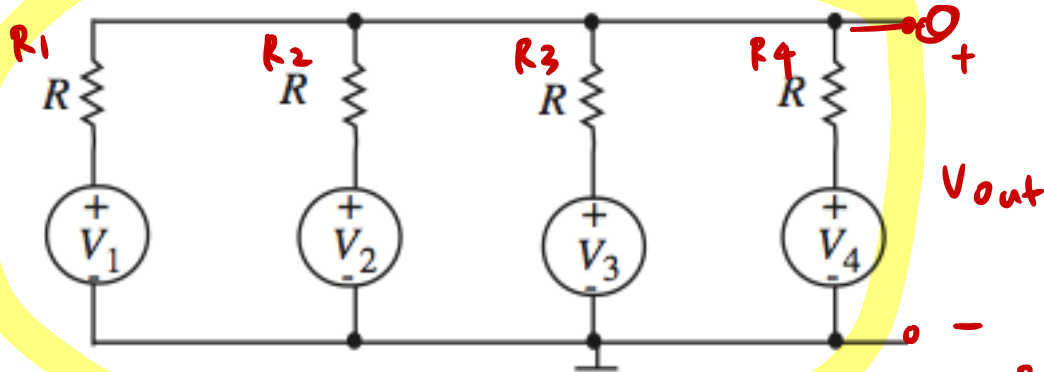

Find  $V_{out}$

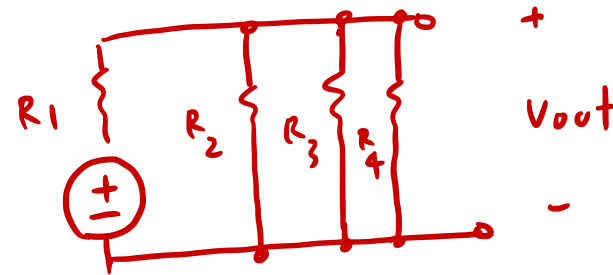
1) Partial response due to  $V_1$

$$V_{out,1} = \frac{R_2 \parallel R_3 \parallel R_4}{R_1 + (R_2 \parallel R_3 \parallel R_4)} \cdot V_1 = \frac{1}{4} V_1$$



⇒ Total response
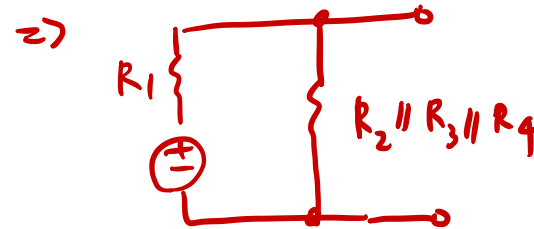
$$V_{out} = \frac{1}{4} V_1 + \frac{1}{4} V_2 + \frac{1}{4} V_3 + \frac{1}{4} V_4$$





# Yet Another Method?

□ Arbitrary network

By superposition


$$v = \sum_m \alpha_m V_m + \sum_n \beta_n I_n + Ri$$

#1                      #2                      #3

depend only on  
the network N.  
independent of  
external source

↑  
due to external source.  
(all  $V_m, I_m = 0$ )

$$v = V_{TH} + R_{TH} \cdot i$$

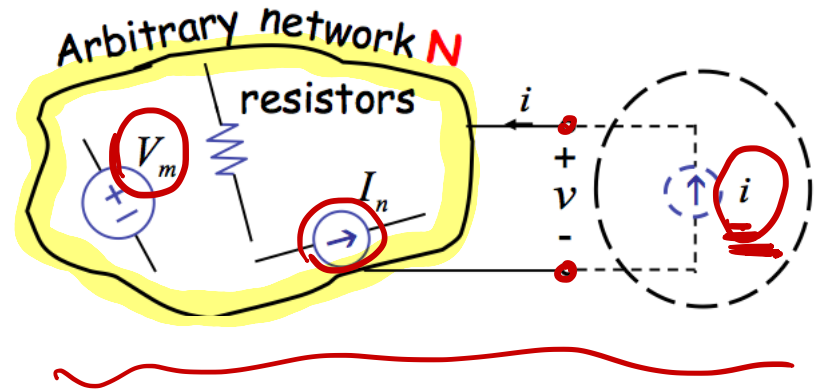

1. Independent of external excitation and behave like a voltage.
  - Let's call it ' $v_{TH}$ '
2. Independent of external excitation and behave like a resistor.
  - Let's call it ' $R_{TH}$ '