

3/11/2019 (Mon)




# Yet Another Method?

## □ Arbitrary network

By superposition

$$v = \sum_m \alpha_m V_m + \sum_n \beta_n I_n + Ri$$
$$= \underbrace{\sum_m \alpha_m V_m}_{\#1} + \underbrace{\sum_n \beta_n I_n}_{\#2} + Ri = \#3$$

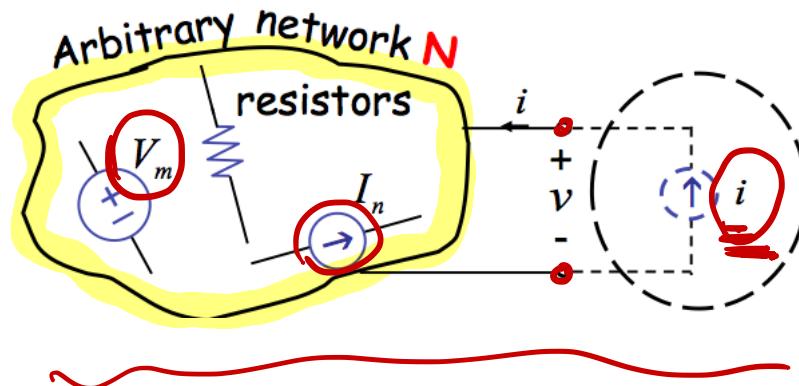depend only on  
the network N.  
independent of  
external source



due to external source .  
( all  $V_m, I_m = 0$ )

$$v = V_{TH} + R_{TH} \cdot i$$


1. Independent of external excitation and behave like a voltage.
  - Let's call it ' $v_{TH}$ '
2. Independent of external excitation and behave like a resistor.
  - Let's call it ' $R_{TH}$ '




# Arbitrary Network

$$v = \sum_m \alpha_m V_m + \sum_n \beta_n I_n + Ri$$

$$v = v_{TH} + R_{TH} \cdot i$$

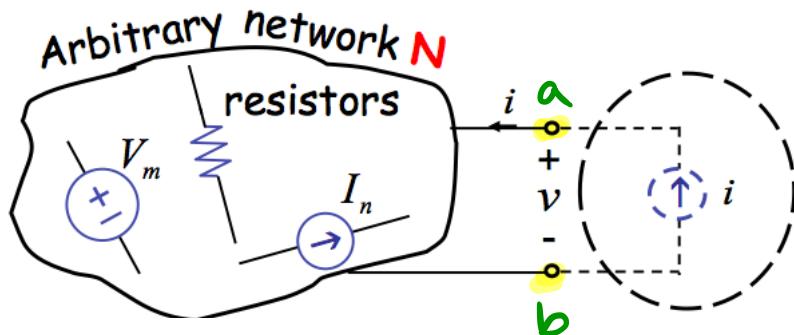

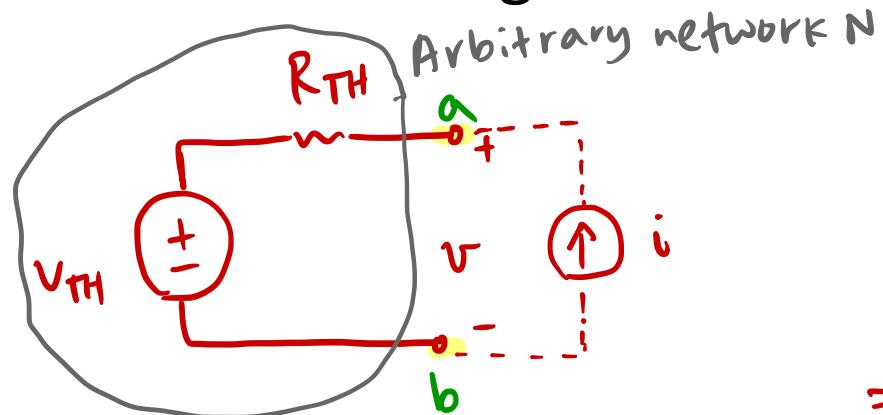- In other words, as far as the external world is concerned (for the purpose of the  $i-v$  relation), 'arbitrary network  $N$ ' is indistinguishable from:



$$v_{TH} = v_{open} \Big|_{i=0}$$

$$R_{TH} = \frac{V}{i} \Big|_{\substack{\text{internal} \\ \text{independent source} = 0}}$$



$\Rightarrow$  Thevenin Equivalent circuit



# Arbitrary Network

$$v = v_{TH} + R_{TH} i$$


~~This equation is incorrect.~~

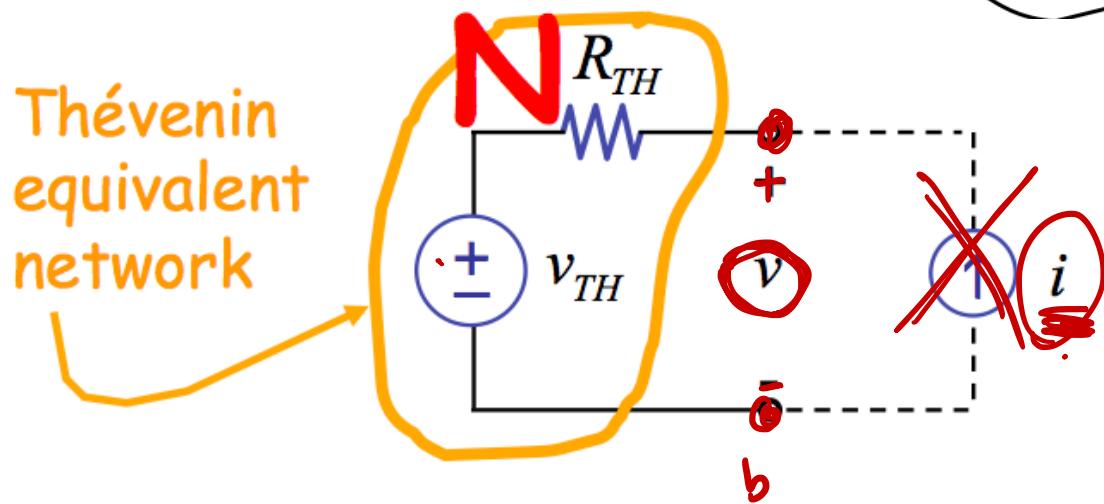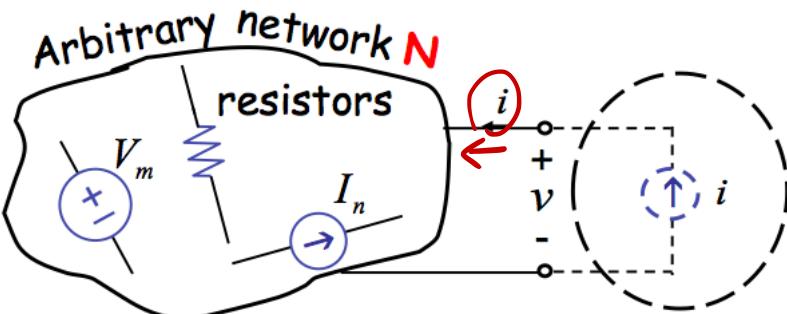

- How to derive  $v_{TH}$  and  $R_{TH}$ ?
- $v_{TH} \rightarrow$  Open circuit voltage seen at terminal pair (aka port).
- $R_{TH} \rightarrow$  Resistance of network seen from port (with  $V_m$ 's and  $I_n$ 's set to 0).



# Method 5: The Thévenin Method



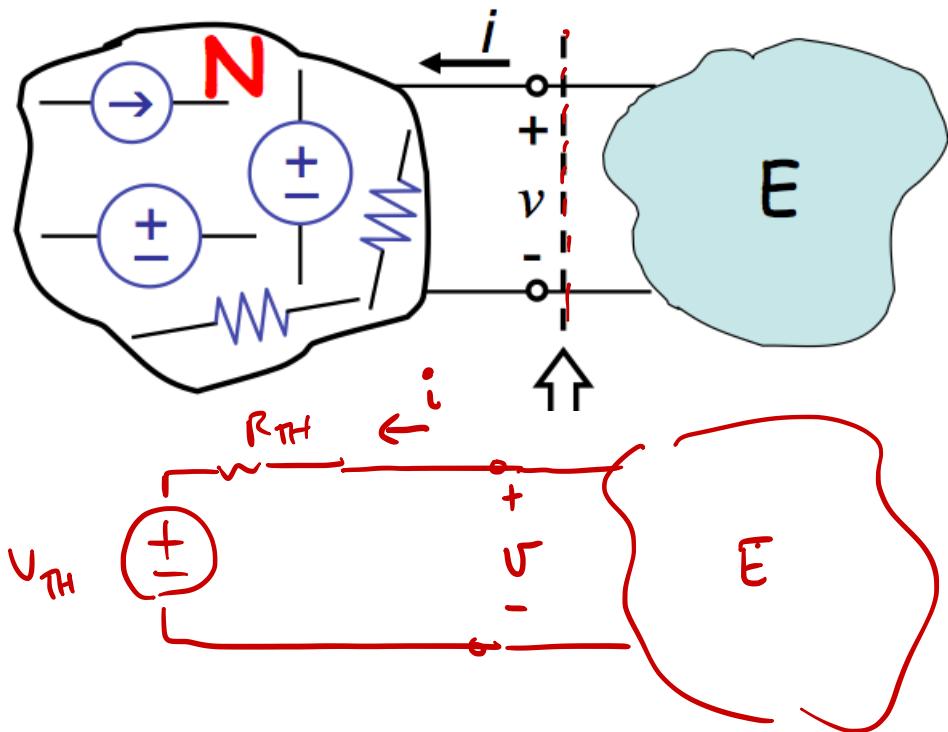


- Replace network  $N$  with its Thévenin equivalent
- Solve with external network  $E$



# Example – Using Thévenin Method

Find  $i_1$ .

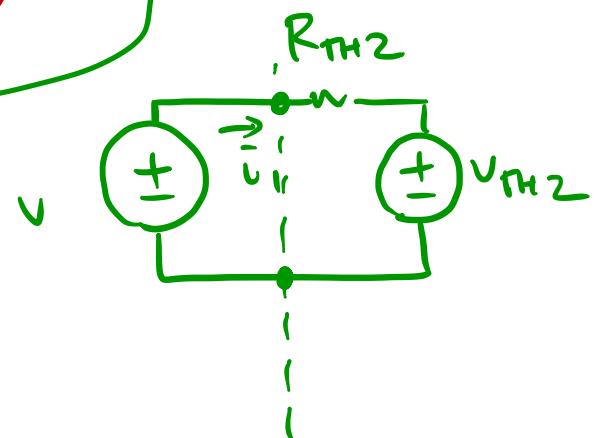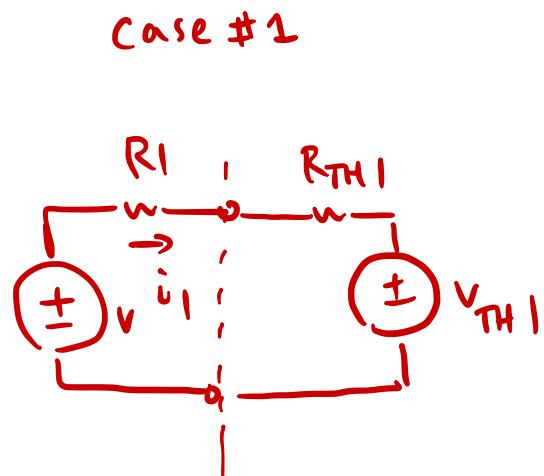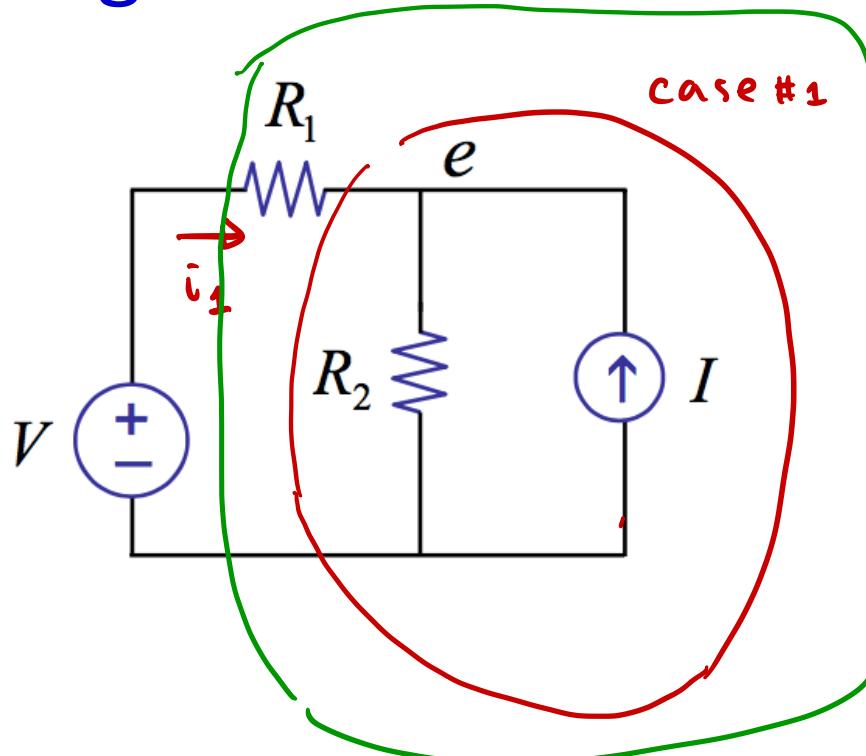




# Example – Using Thévenin Method

## □ Case 1

1)  $V_{TH}$ : open circuit  $v$  of network  $N$


$$V_{TH} = I \cdot R_2$$

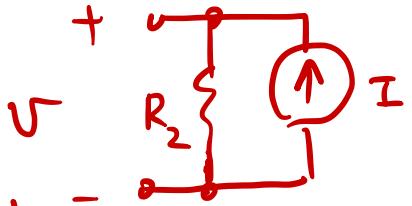


2)  $R_{TH}$ : set all independent

source = 0, measure  $\frac{v}{i}$

$$\Rightarrow R_{TH} = R_2$$

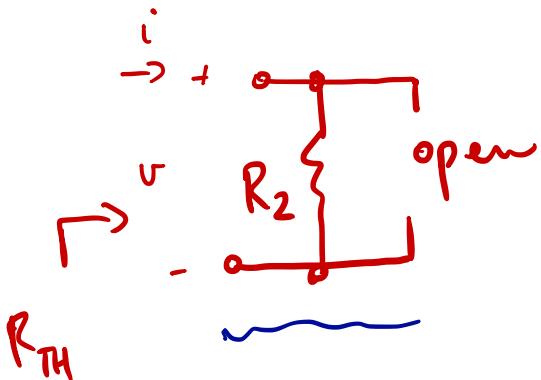



$$R_{TH} = R_2$$

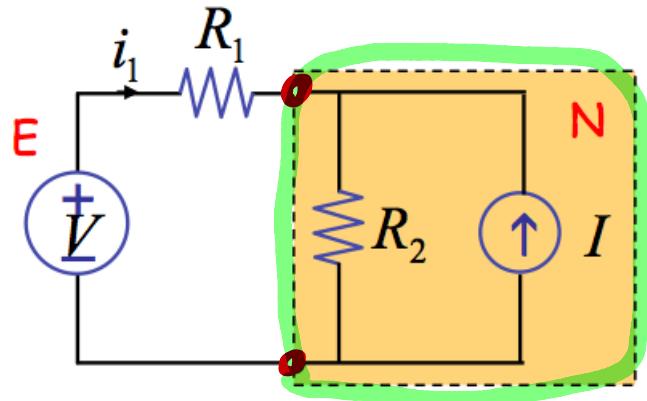



$$V_{TH} = IR_2$$

$$R_{TH} = R_2$$

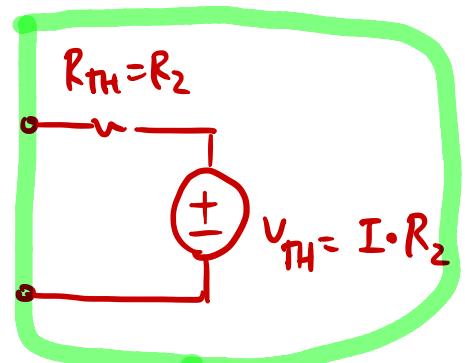

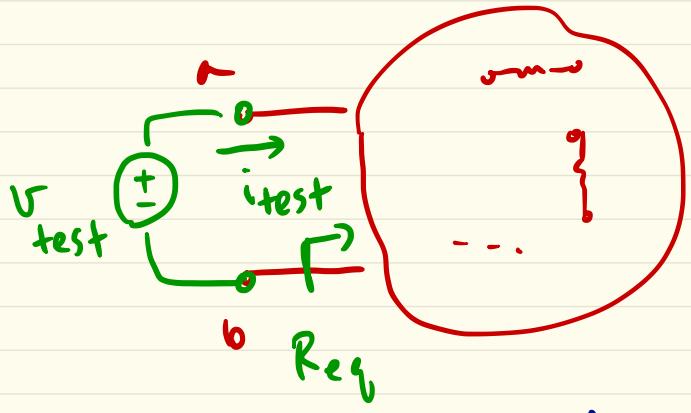

$$Req = \frac{V_{test}}{i_{test}}$$

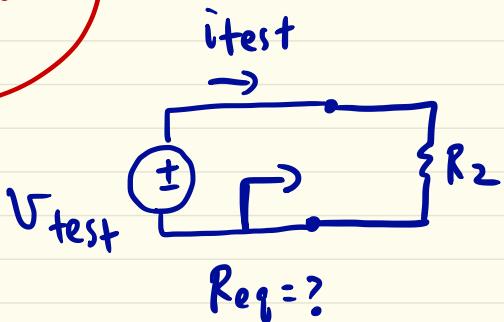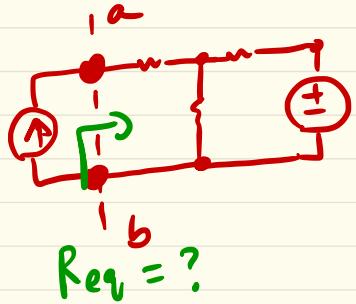


$$\frac{V_{test}}{i_{test}} = R_2$$

# Example – Using Thévenin Method


## □ Case 2

1)  $V_{TH2} =$

$$V_{open} = I \cdot R_2$$

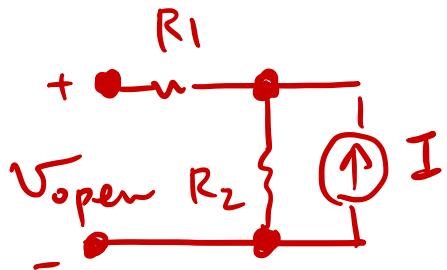


2)  $R_{TH2} = R_1 + R_2$

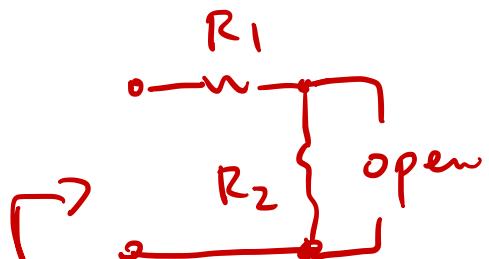

$R_{TH2}$

$$R_{TH2} = R_1 + R_2$$

$\Rightarrow$

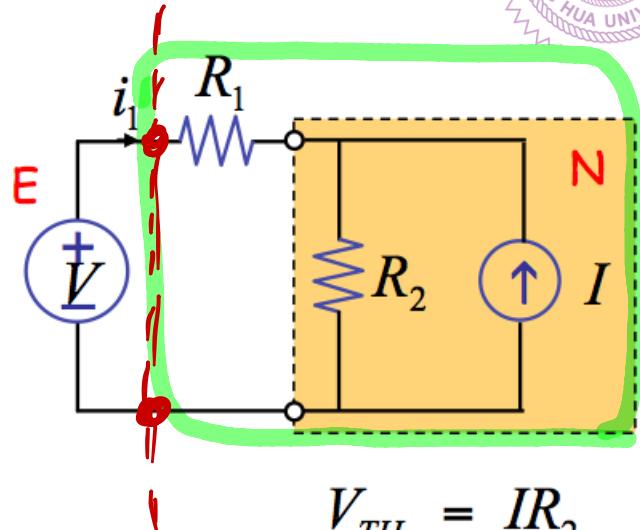

$$V_{TH} = IR_2$$


$$R_{TH} = R_2$$



# Example – Using Thévenin Method


- Solve with external network E

Case #1

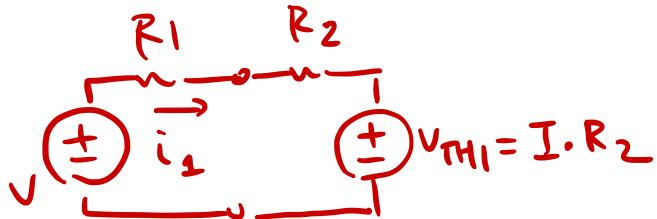

$$i_1 = \frac{V - V_{TH1}}{R_1 + R_2}$$


$$= \frac{V - I \cdot R_2}{R_1 + R_2}$$

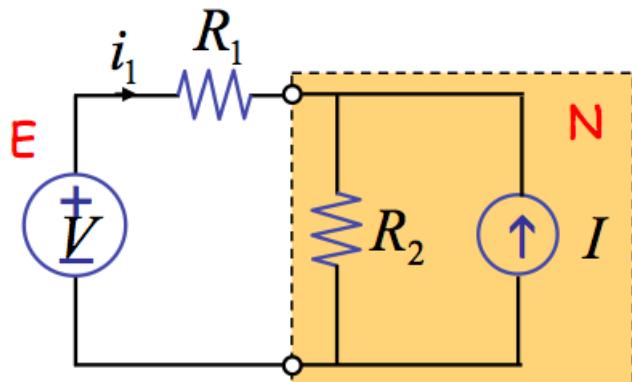

$$V_{TH} = IR_2$$

$$R_{TH} = R_2$$

Case #2

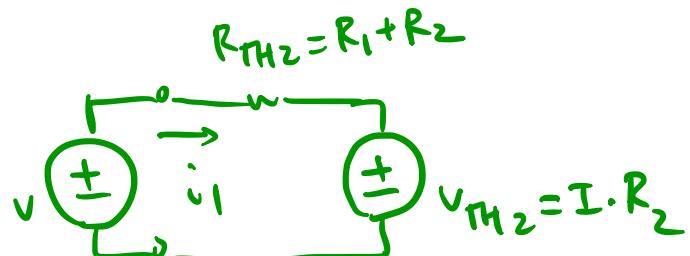

$$i_1 = \frac{V - V_{TH2}}{R_{TH2}}$$



$$= \frac{V - I \cdot R_2}{R_1 + R_2}$$



# Example – Using Thévenin Method


- Graphically...

$$V = V_{TH} + R_{TH} \cdot i$$

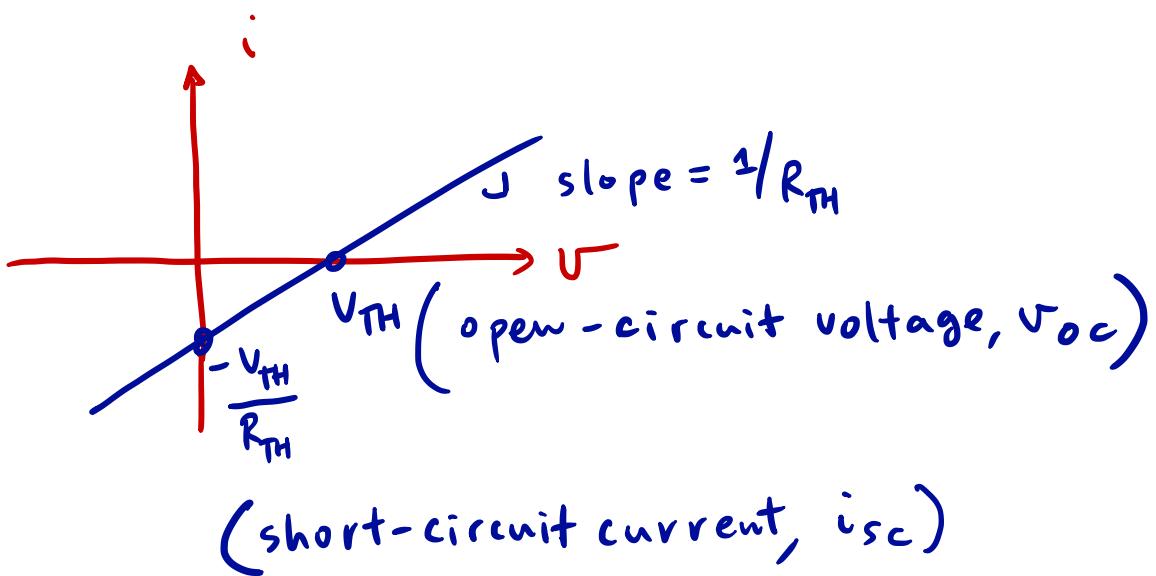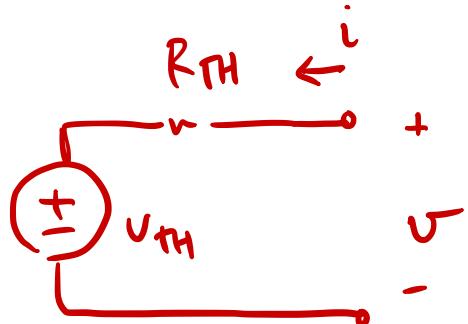




# Method 6: The Norton Method

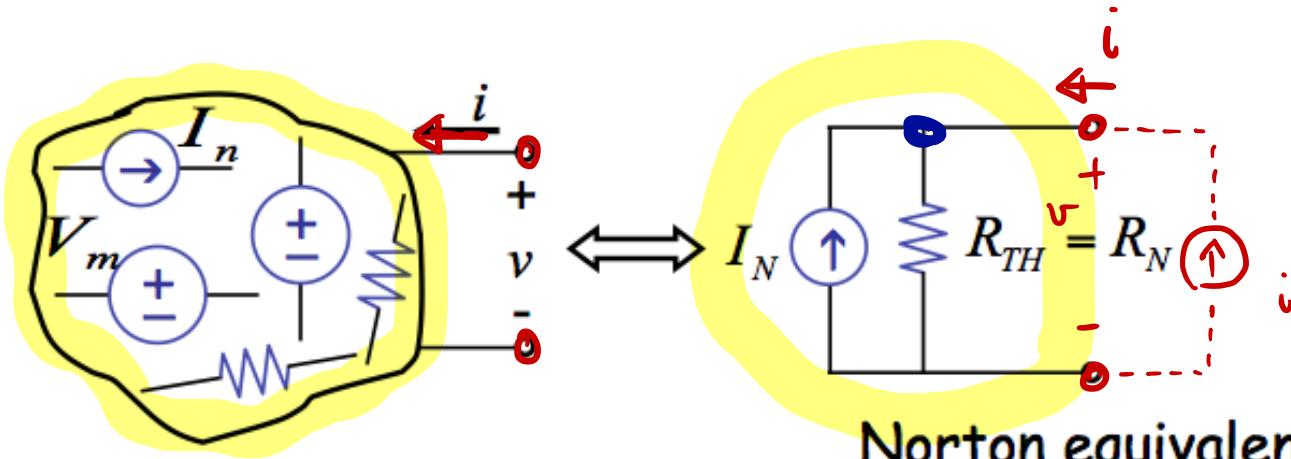


$$(\text{Thevenin: } V = V_{TH} + R_{TH} \cdot i)$$
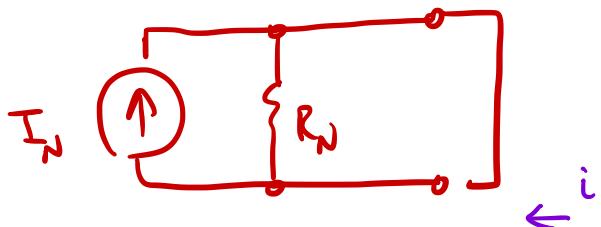
$$\text{Norton: } i = -I_N + \frac{V}{R_N}$$



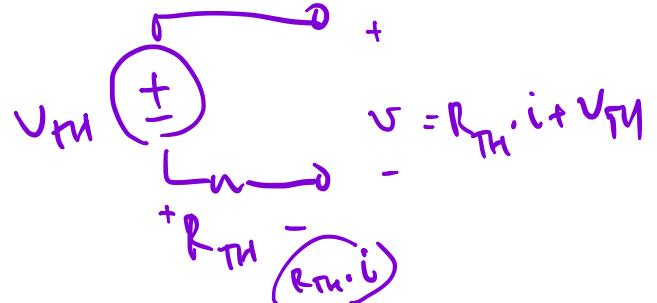
$I_N$ : short circuit current seen at port,  $-I_N = i_{sc} = i$



$$R_N = R_{TH}, \text{ set independent source } = 0$$



# Thévenin and Norton

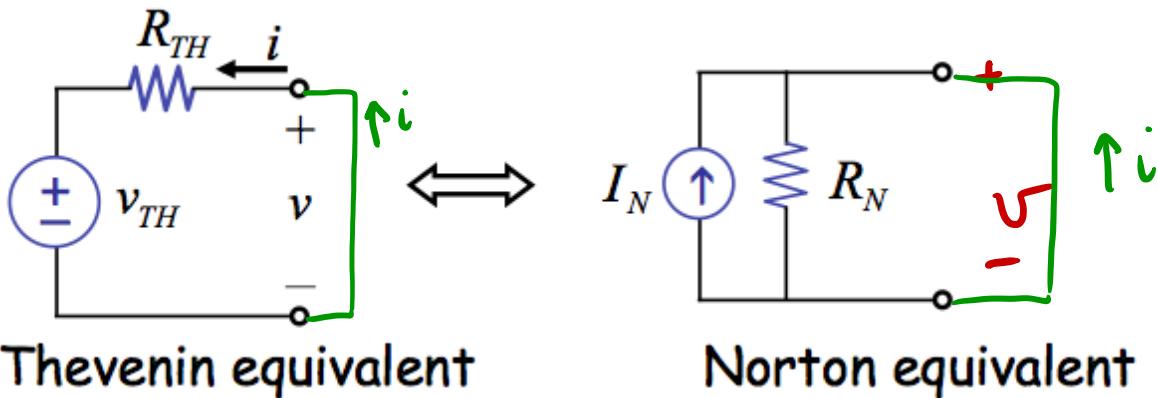

Equivalent resistance

$$R_{TH} = R_N$$

open-circuit voltage,  $V_{OC}$

$$V_{TH} = I_N \cdot R_N$$


short-circuit current,  $i_{SC}$

$$\frac{-V_{TH}}{R_{TH}} = -I_N$$


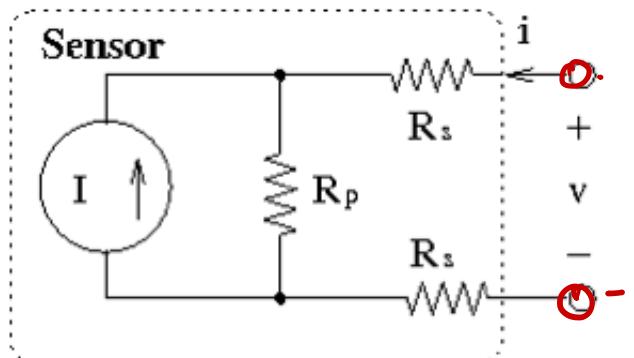
# Example – Thévenin and Norton

- A light sensor is modeled as a current source that produces a current proportional to the intensity of light.
  - Leakage through the sensor is modeled as  $R_p$ .
  - Resistance in the contacts (wires) is modeled as  $R_s$ .
- Thévenin equivalent circuit:



Thevenin equivalent circuit diagram: A voltage source  $V_{TH}$  is in series with a load resistor  $R_M$ . The output voltage  $V$  is measured across the load resistor  $R_M$ . A red equation  $V = V_{TH} + R_M \cdot i$  is written next to the diagram.

$$V = V_{TH} + R_M \cdot i$$


$$V_{TH} = I \cdot R_p$$

$$R_M = 2R_s + R_p$$



# Example – Thévenin and Norton


- Norton equivalent circuit:

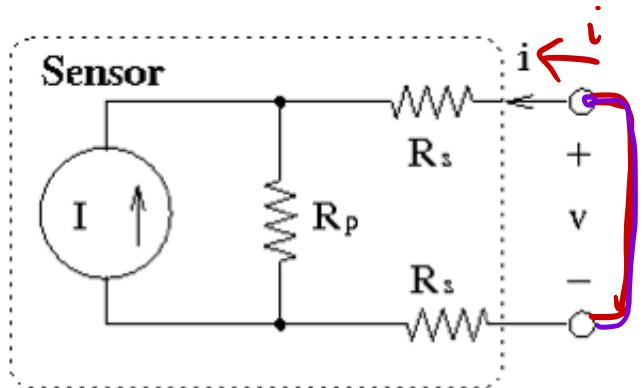

$$i = -I_N + \frac{v}{R_N}$$

$$I_N = I \cdot \frac{R_p}{R_p + 2R_s} \quad |_{v=0}$$

$$R_N = R_p + 2R_s$$

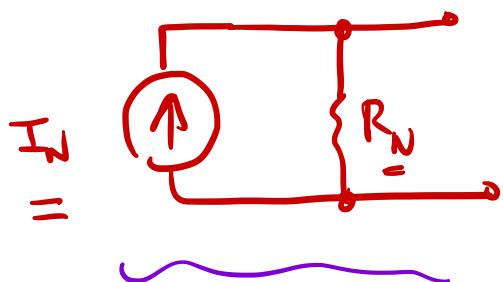



# Summary


## ❑ Basic circuit analysis methods

- KCL, KVL
- Element combination rules
- Node method
- Superposition
- Thévenin
- Norton


For all lumped elements

For linear circuits only


Example. Use superposition. Find  $V_o$

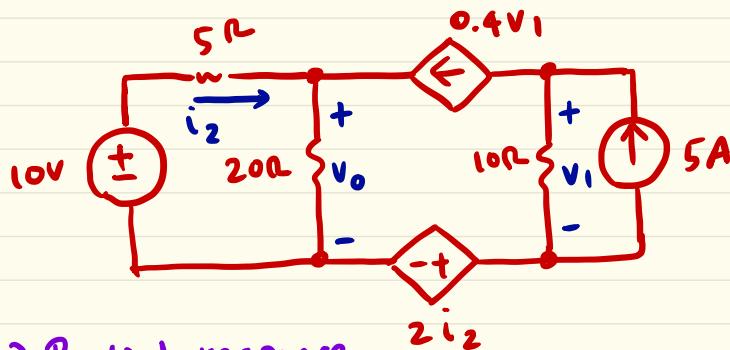

1) Find partial response due to

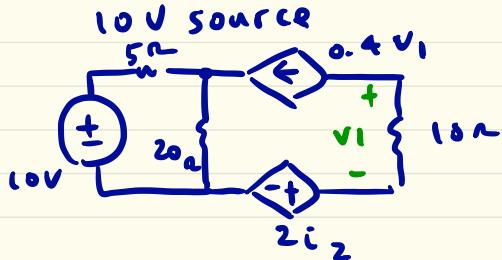

2) Partial response due to 5A source

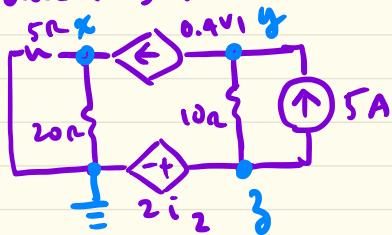

$$\text{KCL at } X: \frac{V_x}{5} + \frac{V_x}{20} - 0.4V_1 = 0$$


$$@ y: 0.4V_1 + \frac{V_y - V_3}{10} - 5 = 0$$

$$V_3 = 2i_2, V_1 = V_y - V_3$$

$$V_1 = 10V$$

$$V_x = V_{o,2} = 16V$$
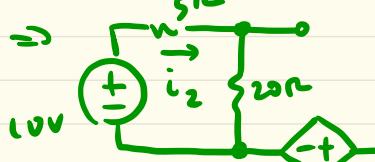
$$\frac{-V_1}{10} = 0.4V_1 \Rightarrow V_1 = 0V$$



$$i_2 = \frac{10V}{20+5} = \frac{2}{5} A$$

$$V_{o,1} = \frac{2}{5} \times 20$$

$$= 8V$$

3) Total response

$$V_o = V_{o,1} + V_{o,2} = 24V$$