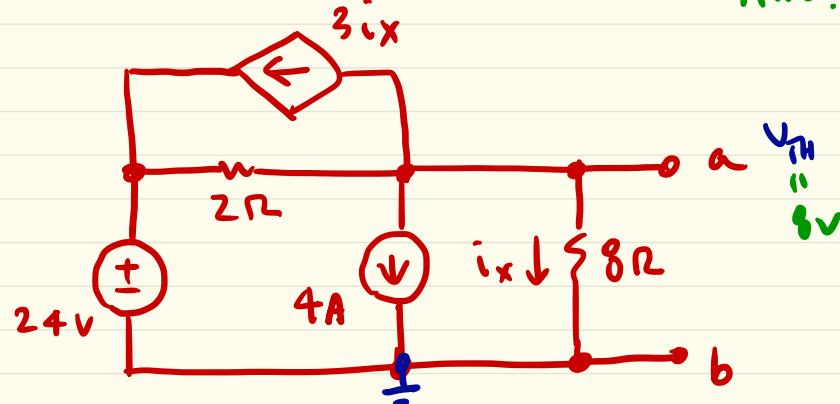


4


3/27 % Quiz 1

(wed)

Example: Thevenin Equivalent (port at node a, b)




Ans:  $R_{TH} = 1\Omega$

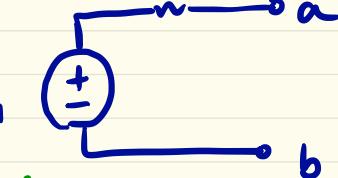

1)  $V_{TH}$ :  $\left\{ \begin{array}{l} KCL @ a: \frac{V_a - 24}{2} + 4 + 3i_x + i_x = 0 \\ \Rightarrow V_a = 8V = V_{TH} \end{array} \right.$



$$i_x = \frac{V_a}{8}$$

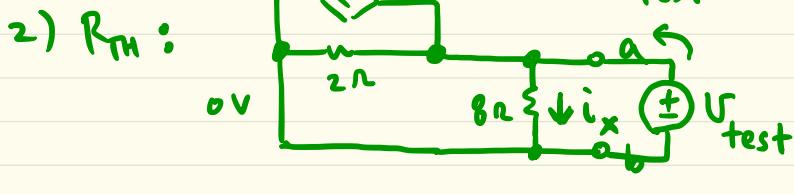


$KCL @ a:$


$$\frac{U_{test}}{2} + 3 \cdot \frac{U_{test}}{8} + \frac{U_{test}}{8} - i_{test} = 0$$
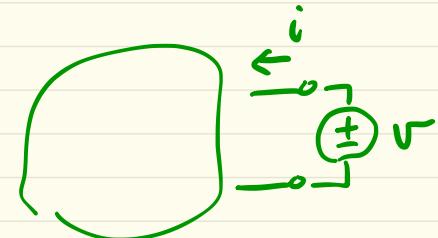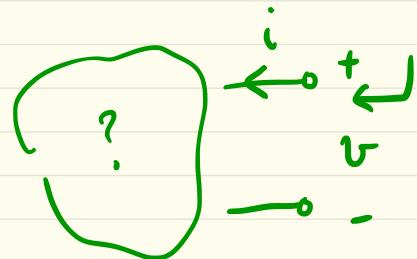
$$\Rightarrow \frac{U_{test}}{i_{test}} = 1\Omega = R_{TH}$$




$$\frac{v}{i} = R$$

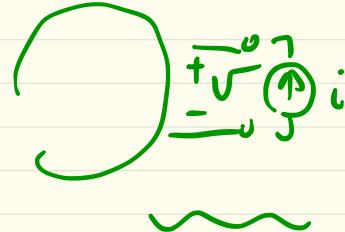

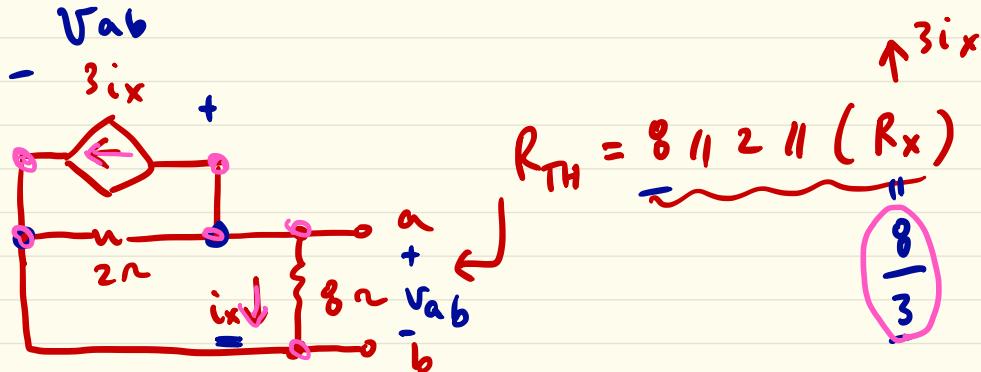
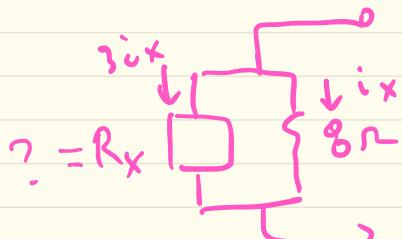
$$= \frac{1}{\frac{1}{8} + \frac{3}{8}} \parallel 2 = 2 \parallel 2 = \underline{1\Omega}$$




$$0 \cdot i_x = R_x \cdot 3ix$$

$$\Rightarrow R_x = \frac{8}{3}$$

## Lecture 2.

1)

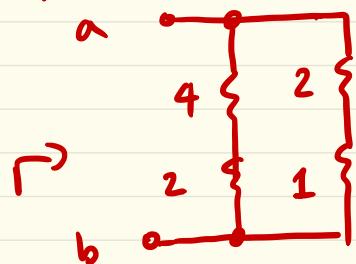


Find  $R_{in}$

$\Gamma$

$$= \left[ \begin{array}{c} \textcircled{6} \\ \textcircled{3} \end{array} \right] = \left[ \begin{array}{c} \textcircled{6} \\ \textcircled{3} \end{array} \right] R_{in} = 6//3 = 2 \Omega$$

$R_{in}$


• Practice

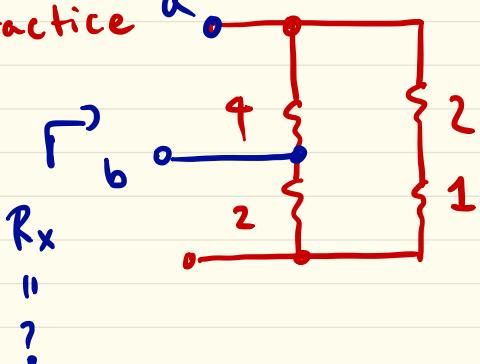

$R_x$

//

?

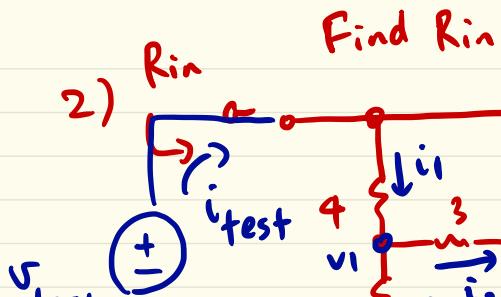

①

$$\begin{aligned} \text{KCL: } i_{\text{test}} &= i_1 + i_4 \\ i_1 &= i_2 + i_3 \\ i_3 + i_4 &= i_5 \end{aligned}$$

②

$$i_1 = \frac{v_{\text{test}} - v_1}{4}$$

$$i_2 = \frac{v_1}{2}$$

$$i_3 = \frac{v_1 - v_2}{3}$$

$$i_4 = \frac{v_{\text{test}} - v_2}{2}$$


$$i_5 = \frac{v_2}{1}$$

(i) ①  $\Rightarrow$

$$\frac{v_{\text{test}}}{i_{\text{test}}} = R_{\text{in}} = 2 \Omega$$



$$v_1 = v_2 = \frac{v_{\text{test}}}{3}, i_3 = 0 \text{ A}$$


3)

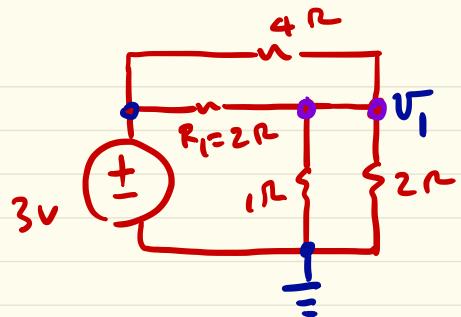Find power dissipated by  $R_1$ 


$$\frac{3 - V_1}{(4 \parallel 2)} = \frac{V_1}{(1 \parallel 2)} \Rightarrow V_1 = 1 \text{ V}$$
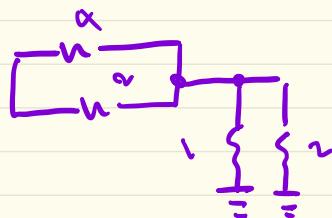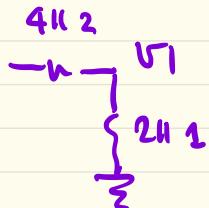
$$P = V \cdot i = (3 - 1) \cdot \frac{3 - 1}{2} = 2 \text{ W}$$





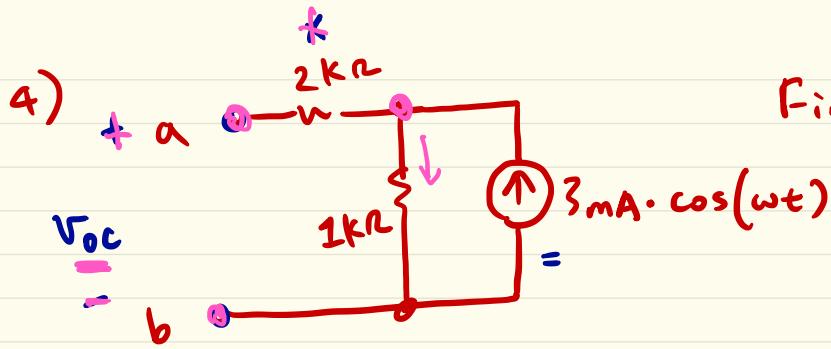


Find Thévenin equivalent.

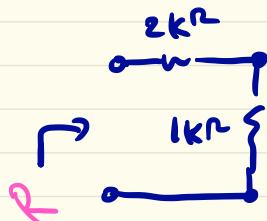

$$R_{TH} = 3 \text{ k}\Omega$$

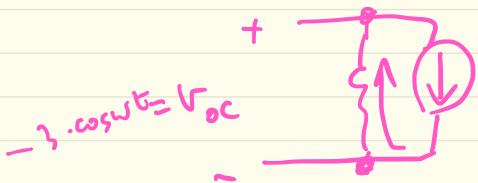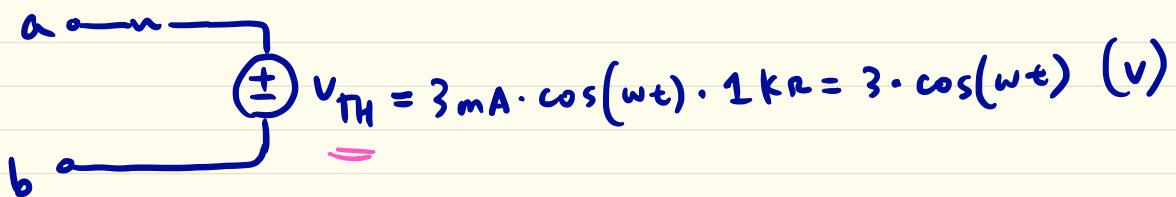


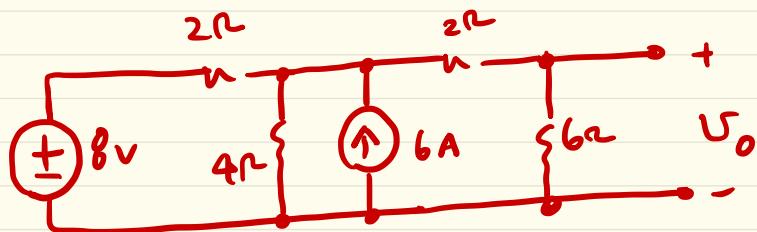5) Practice . Find  $V_o$  by ① node method, ② Superposition







$$\text{Ans. } V_o = 8.55 \text{ V}$$

6)

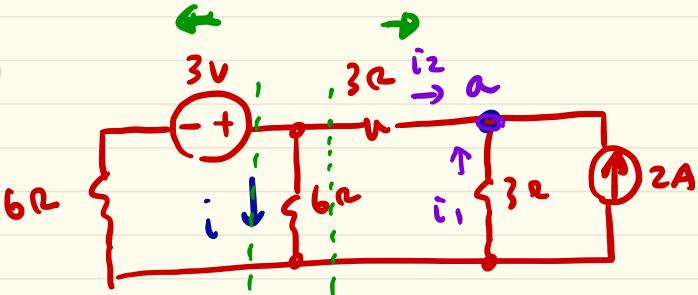

Find  $i$ . use Norton to simplify analysis.

$$i_2 + i_1 + 2 = 0$$

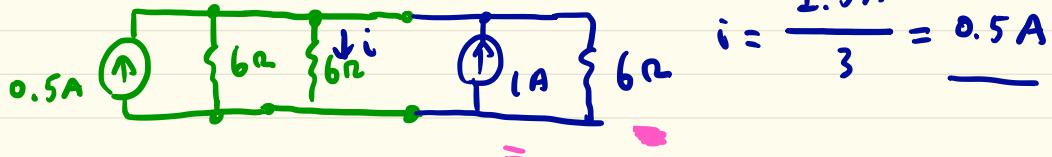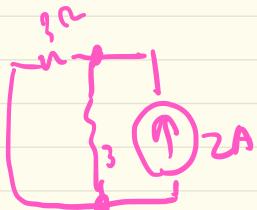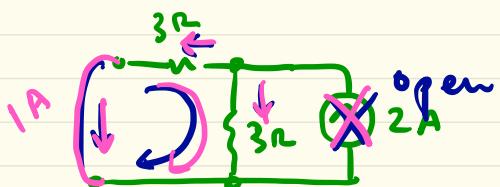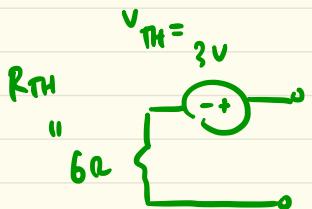

$$i = \frac{1.5A}{3} = 0.5A$$