

Under-damped

$$v(t) = V_I + K_1 e^{-\alpha t} \cos \omega_d t + K_2 e^{-\alpha t} \sin \omega_d t$$

◆ Furthermore, $v(0) = 0$ and $i(0) = 0$

$$1.) \quad v(0) = 0 \Rightarrow V_I + K_1 = 0 \Rightarrow K_1 = -V_I$$

$$2.) \quad i(0) = 0 \Rightarrow i = C \frac{dv}{dt} = C \cdot K_1 (-\alpha e^{-\alpha t} \cos \omega_d t - e^{-\alpha t} \cdot \omega_d \cdot \sin \omega_d t) + C \cdot K_2 (-\alpha e^{-\alpha t} \sin \omega_d t + e^{-\alpha t} \cdot \omega_d \cdot \cos \omega_d t)$$

$$i(0) = C K_1 (-\alpha) + C K_2 \omega_d = 0 \Rightarrow K_2 = -\frac{\alpha}{\omega_d} \cdot V_I$$

$$3.) \quad v(t) = V_I - V_I \cdot e^{-\alpha t} \cos \omega_d t - \frac{V_I \cdot \alpha}{\omega_d} \cdot e^{-\alpha t} \cdot \sin \omega_d t$$

Under-damped


$$v(t) = V_I - V_I e^{-\alpha t} \cos \omega_d t - V_I \frac{\alpha}{\omega_d} e^{-\alpha t} \sin \omega_d t$$

- ◆ Scaled sum of sines (of the same frequency) are also sines (Appendix B.7)

Use

$$A_1 \cos \omega_d t + A_2 \sin \omega_d t = \sqrt{A_1^2 + A_2^2} \cdot \cos\left(\omega_d t - \tan^{-1} \frac{A_2}{A_1}\right)$$
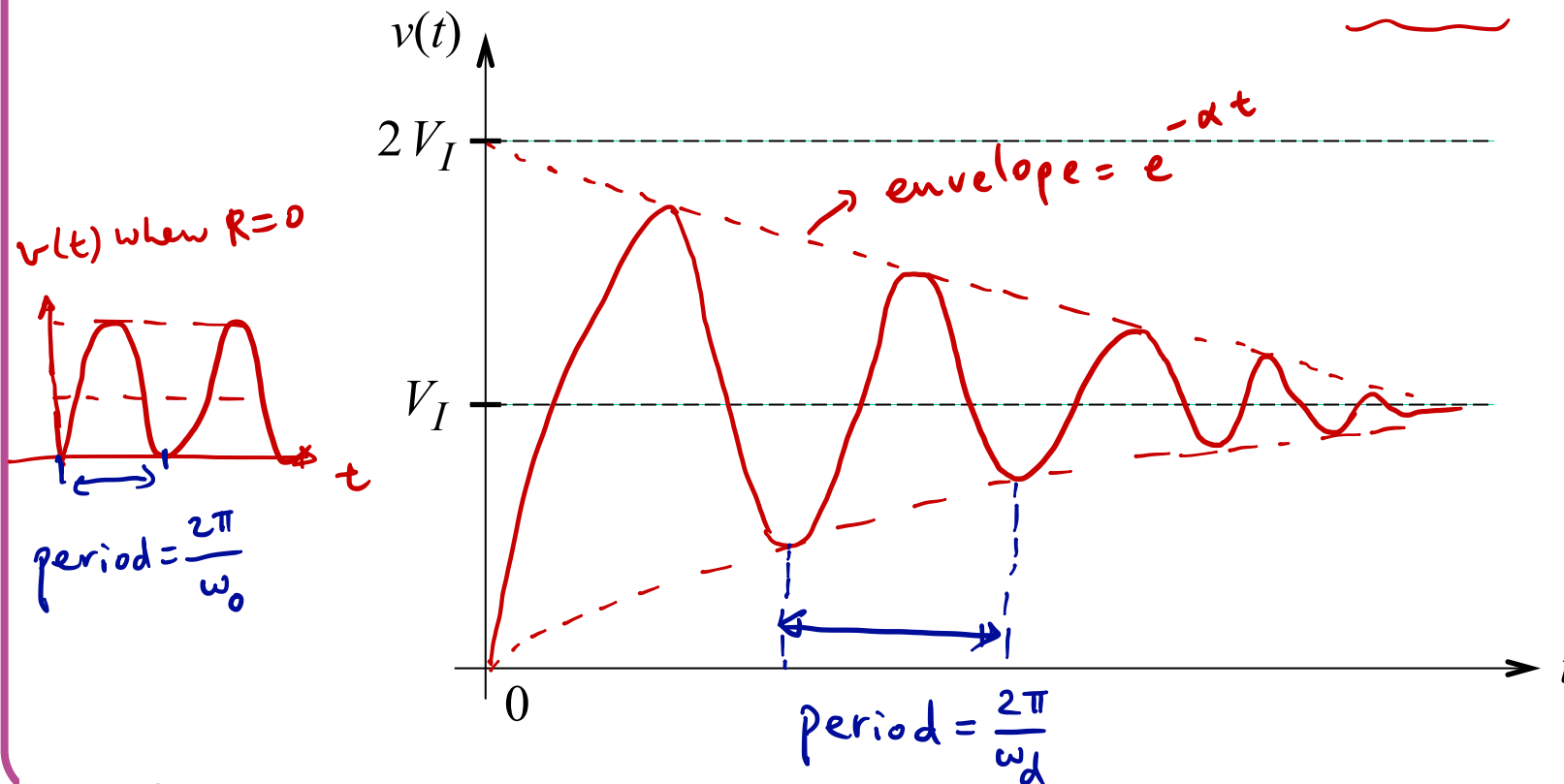
$$\Rightarrow \text{Rewrite } v(t) = V_I + e^{-\alpha t} \cdot V_I \cdot \frac{\omega_0}{\omega_d} \cdot \cos\left(\omega_d t - \tan^{-1} \frac{\alpha}{\omega_d}\right)$$



Critically-Damped

Section 12.2.3


$$s_1 = s_2 = -\alpha$$

- $\alpha > \omega_0$ over-damped
- $\alpha < \omega_0$ under-damped
- $\alpha = \omega_0$ critically-damped





◆ Total solution will be in the form of
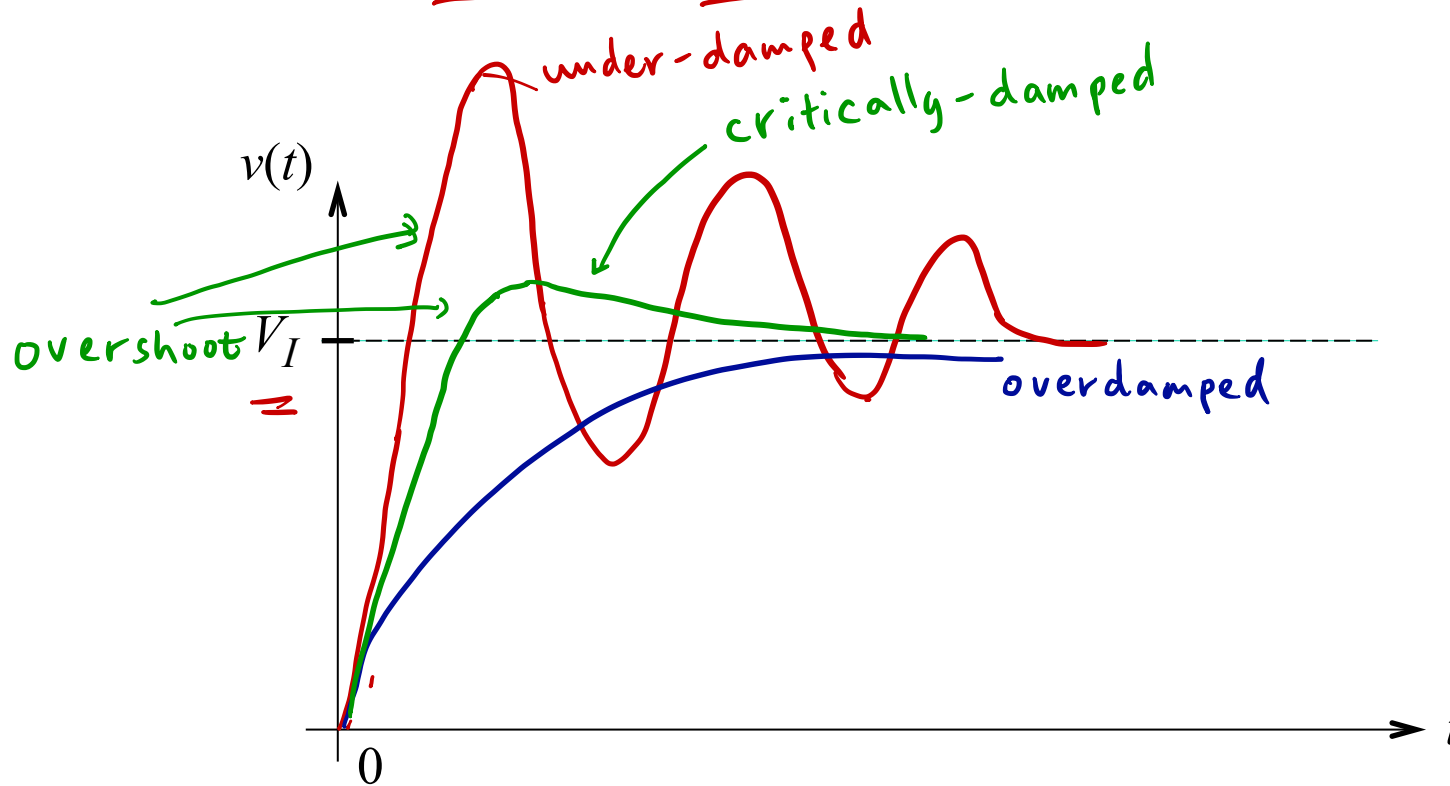
$$v(t) = V_I + A_1 e^{-\alpha t} + A_2 e^{-\alpha t}$$



Remember This?

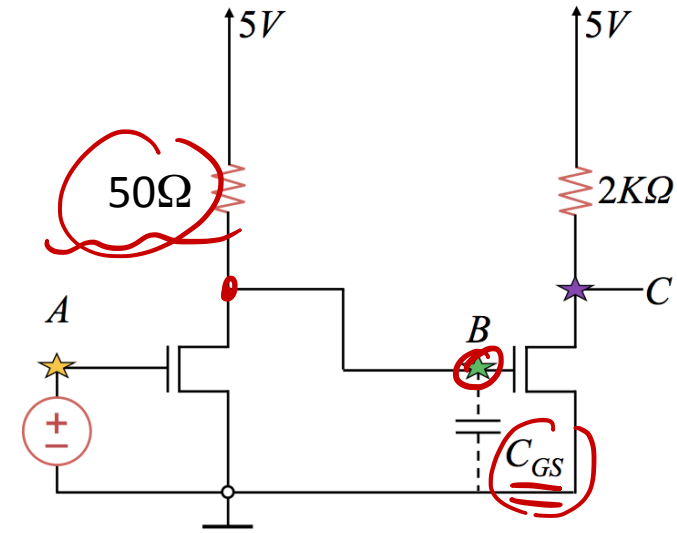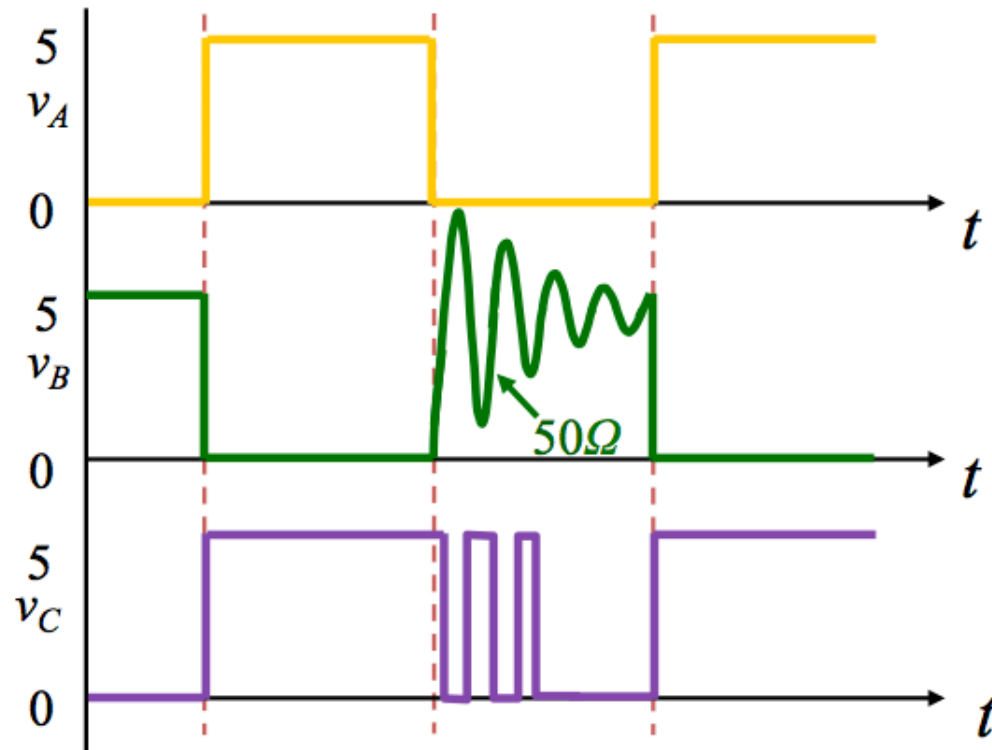- ◆ With 50Ω load resistor, hoping to speed up the pull up




$$R \uparrow \quad \frac{1}{RC}$$

Speed $\Rightarrow R \downarrow$
 \downarrow
 oscillation

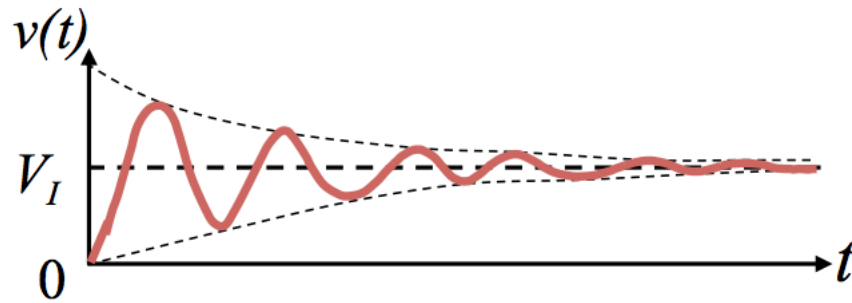Example 12.2.3

Easy Way: Characteristic Equation Tells the Whole Story



◆ For series RLC circuit:


$$\frac{d^2 v(t)}{dt^2} + \frac{R}{L} \frac{dv(t)}{dt} + \frac{1}{LC} = V_I(t)$$

$$\begin{aligned} \text{Characteristic equation} &= s^2 + \frac{R}{L}s + \frac{1}{LC} = 0 \\ &\Rightarrow \underbrace{s^2 + 2\alpha s + \omega_0^2 = 0} \\ &\quad \underbrace{\Rightarrow \alpha, \omega_0} \end{aligned}$$

Section 12.7

Intuitive Analysis (12.7)

◆ What if $v(0) > 0$ and $i(0) < 0$?

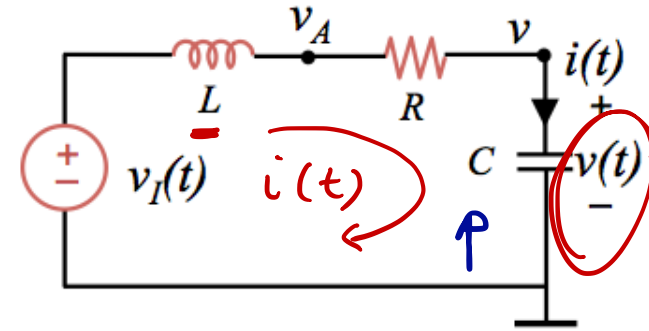

1. Given $v(0)$ and $i(0)$


2. Find $v(t \rightarrow \infty) = V_I$

3. Characteristic equation

$$s^2 + \frac{R}{L}s + \frac{1}{LC} = 0$$


$\Rightarrow \alpha, \omega_0$

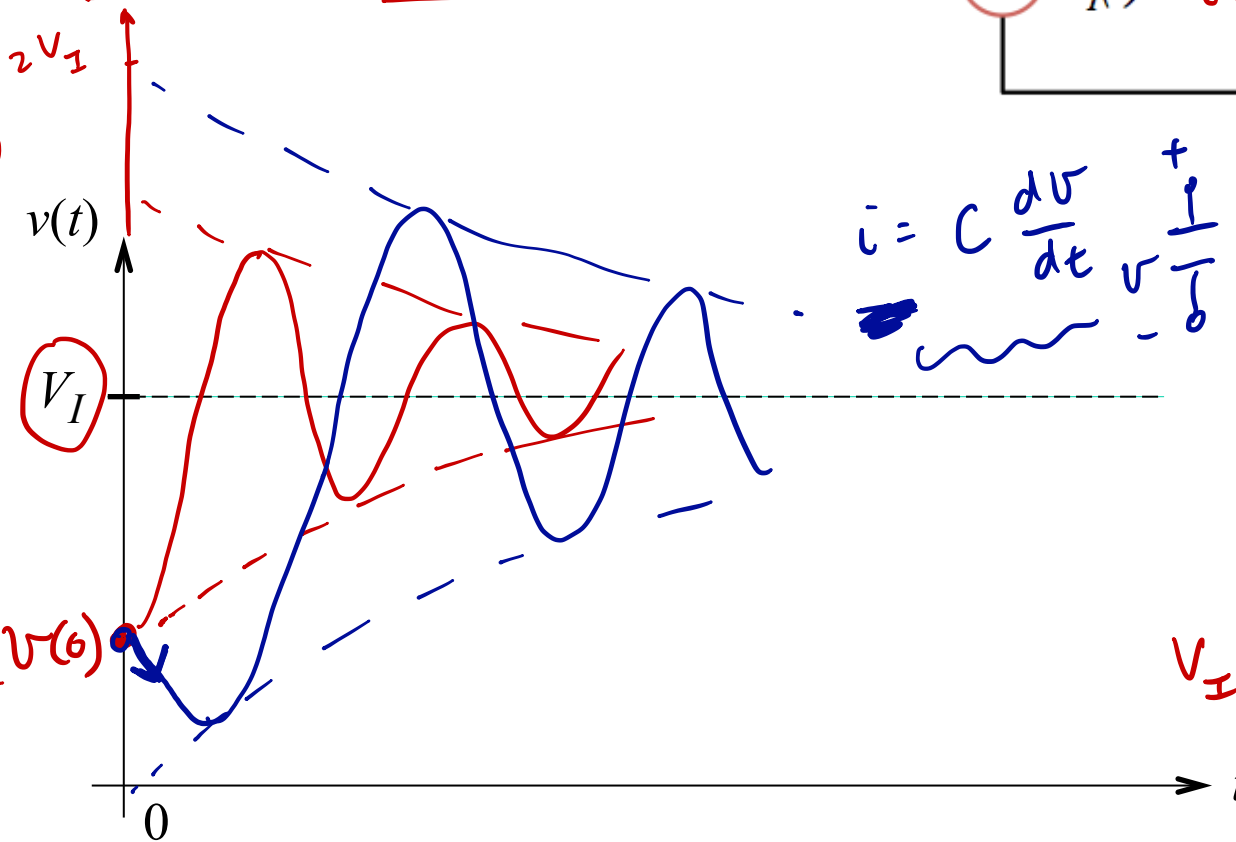\Rightarrow underdamped, overdamped, critically-damped




$$i = C \frac{dv}{dt}$$

$$i_c = 0$$

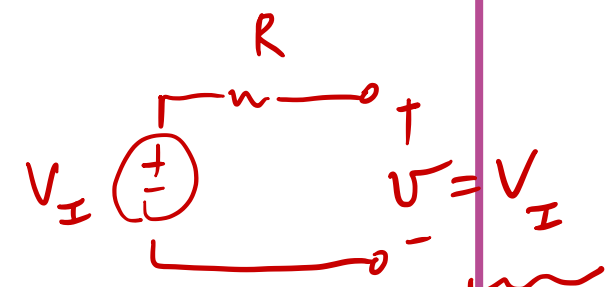

Example

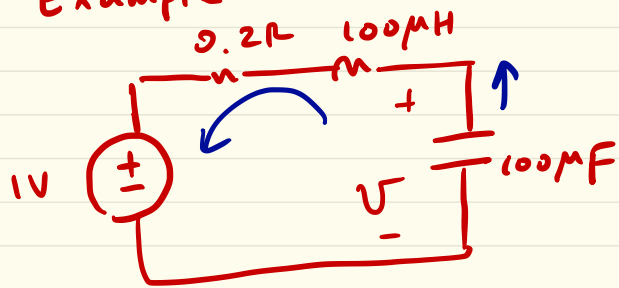

1)


Given $v_c(0) = 0.5V$

$$\underline{i_L(0) = -0.5A}$$

$$V_I = 1V$$

$$\underline{i_L(t=0^+) < 0}$$

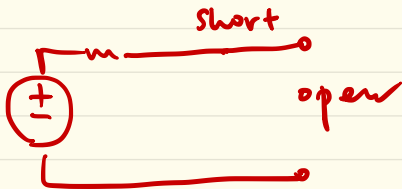2) Final value $V(t \rightarrow \infty) = V_I = 1V$




3) Characteristic equation: $s^2 + \frac{R}{L}s + \frac{1}{LC} = 0$ $s^2 + 2\alpha s + \omega_0^2 = 0$

$$\alpha = \frac{R}{2L} = 10^3 \text{ rad/s}, \quad \omega_0 = \frac{1}{\sqrt{LC}} = 10^4 \text{ rad/s} \Rightarrow \alpha < \omega_0$$

underdamped.

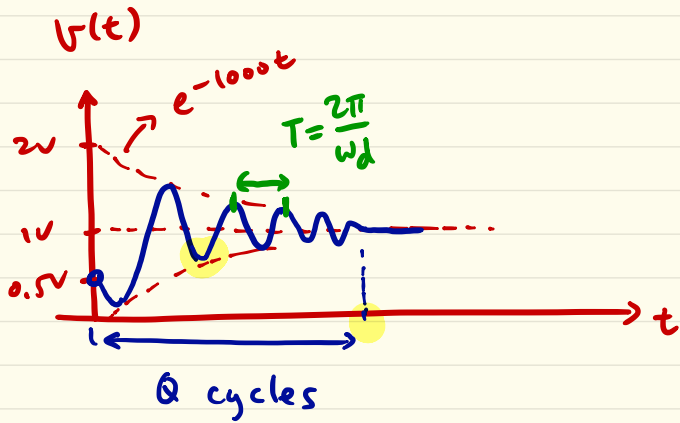
$$\omega_d = \sqrt{\omega_0^2 - \alpha^2} = 9950 \text{ rad/s}, \quad Q = \frac{\omega_0}{2\alpha} = 5$$




In the plot

- 1) initial value ✓
- 2) Final value ✓
- 3) Q cycles
- 4) T

Practice

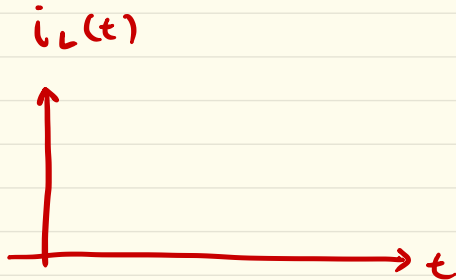


In steady state

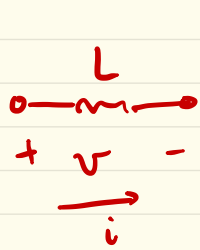

$$V = L \frac{di}{dt} = 0$$

L = short circuit

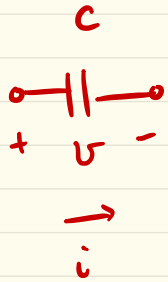

$$i = C \frac{dV}{dt} = 0$$

C = open circuit


What about Other Variables?

$$\underline{v(t)} \rightarrow \underline{i(t)} = i_L(t) = i_R(t)$$


$$i(t) = C \frac{dv}{dt}$$

$$v_L(t) = L \frac{di_L(t)}{dt}$$

$$v_R(t) = R \cdot i_R(t)$$

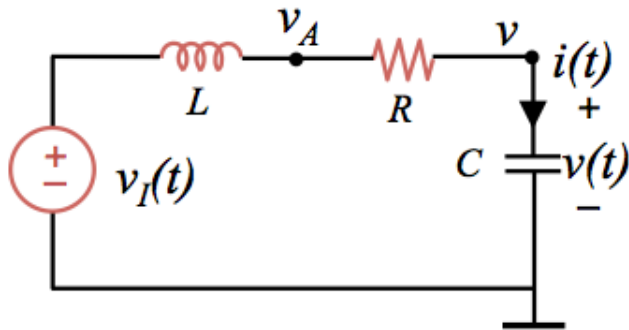

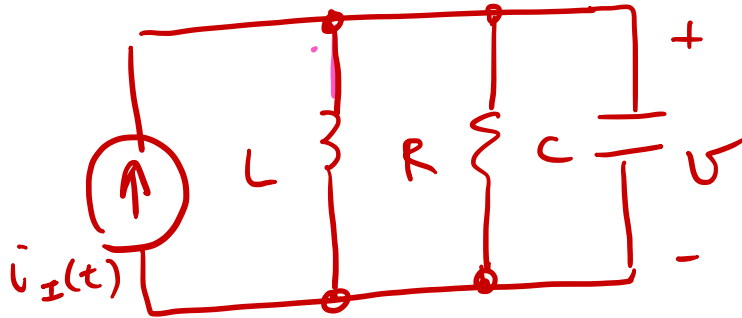Parallel RLC – Characteristic Equation Says It All



$$\text{KCL: } C \frac{dV}{dt} + \frac{V}{R} + \frac{1}{L} \int V(t) dt = i_I(t)$$

$$C \frac{d^2 V}{dt^2} + \frac{1}{R} \frac{dV}{dt} + \frac{1}{L} V = 0$$


$$\Rightarrow \text{Characteristic equation: } s^2 + \frac{1}{RC} s + \frac{1}{LC} = 0$$

$$s^2 + 2\alpha s + \omega_0^2 = 0 \Rightarrow$$

$$\alpha = \frac{1}{2RC}$$

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

Two-Capacitor Circuits

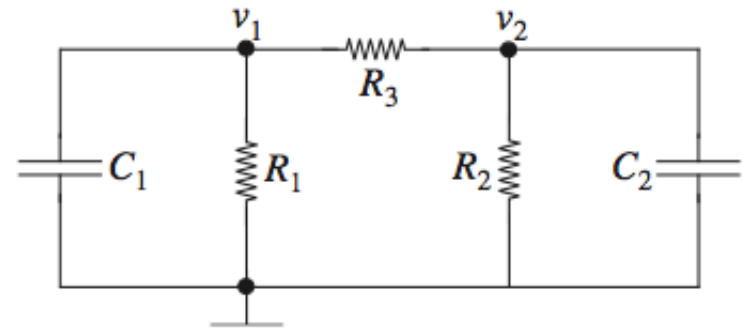


Two-Capacitor Circuits

KCL

For Node #1 $C_1 \frac{dv_1(t)}{dt} + \frac{1}{R_1} v_1(t) + \frac{1}{R_3} (v_1(t) - v_2(t)) = 0$

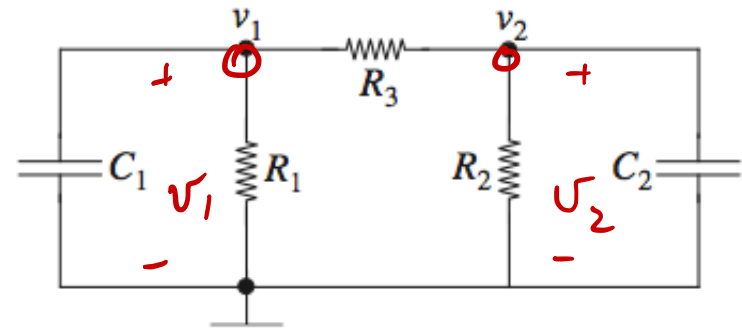For Node #2 $C_2 \frac{dv_2(t)}{dt} + \frac{1}{R_2} v_2(t) + \frac{1}{R_3} (v_2(t) - v_1(t)) = 0$



Express $v_2(t)$ in terms of $v_1(t)$ $v_2(t) = R_3 C_1 \frac{dv_1(t)}{dt} + \left(1 + \frac{R_3}{R_1}\right) v_1(t)$

Differential equation of $v_1(t)$ $\frac{d^2 v_1(t)}{dt^2} + \left(\frac{1}{R_1 C_1} + \frac{1}{R_2 C_2} + \frac{1}{R_3 C_1} + \frac{1}{R_3 C_2}\right) \frac{dv_1(t)}{dt} + \left(\frac{1}{R_1 R_2 C_1 C_2} + \frac{1}{R_1 R_3 C_1 C_2} + \frac{1}{R_2 R_3 C_1 C_2}\right) v_1(t) = 0.$

$\Rightarrow s^2 + 2\alpha s + \omega_0^2 = 0$

$\Rightarrow \alpha, \omega_0 \quad s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$

- ◆ Circuits with only resistors and capacitors have characteristic equations with only real non-positive roots.

Undriven RLC

Given $V_L(0)$ and $\frac{dV_L(0)}{dt}$.

$\Rightarrow V_L, i_L = ?$

