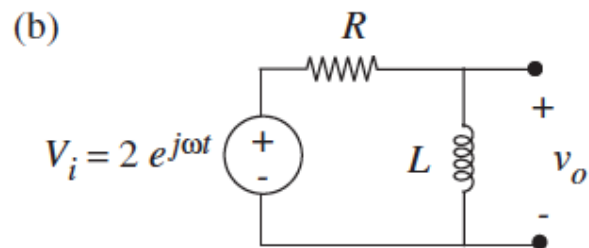



Practice problems for Lecture 11 – Lecture 13

Textbook: Foundations of Analog and Digital Electronic Circuits by Anant Agarwal and Jeffery H. Lang, 1st edition, Elsevier.


- Write expressions for $H(j\omega) = V_o/V_i$, its magnitude $|H(j\omega)|$, and its phase angle $\angle H(j\omega)$, as a function of ω in the following figure.



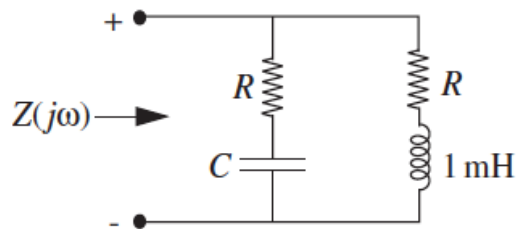
- The impedance of the network shown in the following figure is found to be $2 \text{ k}\Omega$ and is purely real for all frequencies. The value of the inductor is 1 mH as shown. What are the values of R and C ?



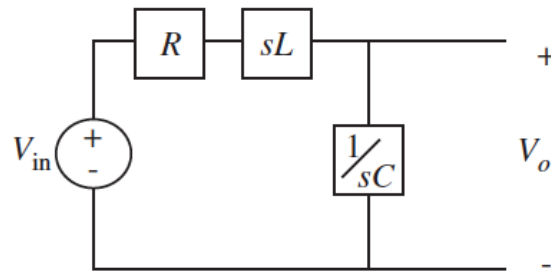
- The circuit shown in the following figure has an input voltage $v_{inl}(t) = V_1 \cos(120\pi t)$, and $L = 500 \text{ mH}$, $C = 80 \text{ }\mu\text{F}$, and $R = 50 \text{ }\Omega$. Compute the transfer function $H(s) = V_o(s)/V_{inl}(s)$.



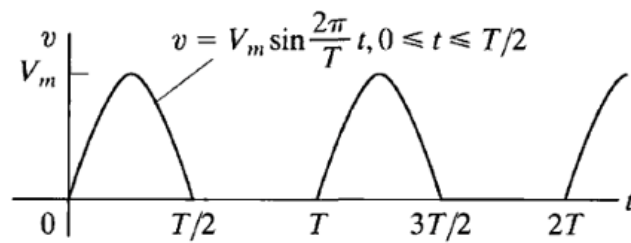
4. Find the rms value of the half-wave rectified sinusoidal voltage shown.



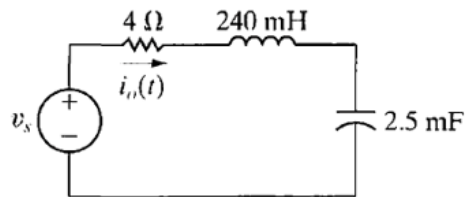5. Find the steady-state expression for $i_0(t)$ in the circuit in the following figure if $v_s = 100\sin 50t$ mV.



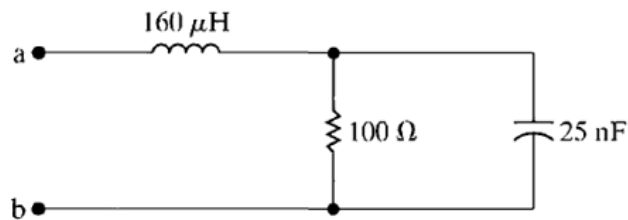- 6.
- (a) For the circuit shown in the figure below, find the frequency (in radians per second) at which the impedance Z_{ab} is purely resistive.
- (b) Find the value of Z_{ab} at the frequency of (a).



7. A resistor denoted as R_L is connected in parallel with the capacitor in the circuit in the following Figure 14.7.

- Derive the expression for the voltage transfer function $\frac{v_o}{v_i}$.
- At what frequency will the magnitude of $H(j\omega)$ be maximum?
- What is the maximum value of the magnitude of $H(j\omega)$?
- At what frequency will the magnitude of $H(j\omega)$ equal its maximum value divided by $\sqrt{2}$?

Figure P14.7

