

1.

$$\frac{V_o}{V_i} = \frac{Ls}{Ls + R} = \frac{\omega L}{\sqrt{(\omega L)^2 + R^2}} e^{j\phi}$$

$$\phi = \tan^{-1} \left( \frac{R}{\omega L} \right)$$

2.

Solution:

$$Z = \frac{(R + \frac{1}{Cs})(R + Ls)}{2R + \frac{1}{Cs} + Ls} = \frac{R(LCs^2 + (\frac{L}{R} + RC)s + 1)}{LCs^2 + 2RCs + 1}$$

In order for  $Z$  to always be purely real,

$$\left( \frac{L}{R} + RC \right) = 2RC$$

$$L = R^2C$$

Then

$$Z = R = 2000$$

independent of  $\omega$ .

$$.001 = 2000^2 C$$

$$C = 2.5 \cdot 10^{-10} \text{ Farads}$$


ANS::  $R = 2000$  and  $C = 2.5 \cdot 10^{-10}$  Farads

3.

Solution:

a)
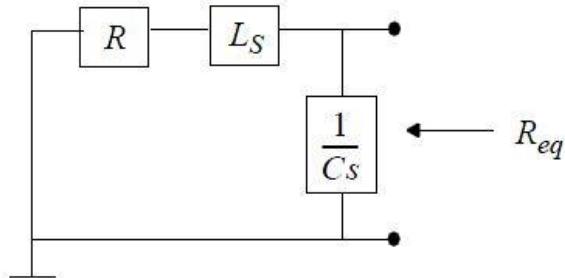
$$H(s) = \frac{1}{LCs^2 + RCs + 1} = \frac{1}{(1 - \omega^2 LC) + j\omega RC}$$



4.

$$\begin{aligned} V_{rms} &= \sqrt{\frac{1}{T} \int_0^{\frac{T}{2}} V^2 dt} = \sqrt{\frac{1}{T} \int_0^{\frac{T}{2}} \left( V_m \sin\left(\frac{2\pi}{T}t\right) \right)^2 dt} = \sqrt{\frac{V_m^2}{T} \int_0^{\frac{T}{2}} \sin^2\left(\frac{2\pi}{T}t\right) dt} \\ &= \sqrt{\frac{V_m^2}{T} \frac{T}{2\pi} \int_0^{\frac{T}{2}} \sin^2\left(\frac{2\pi}{T}t\right) d\frac{2\pi}{T}t} \\ &= \sqrt{\frac{V_m^2}{T} \frac{T}{2\pi} \int_0^{\frac{T}{2}} \frac{1 - \cos\left(2 * \frac{2\pi}{T}t\right)}{2} d\frac{2\pi}{T}t} \\ &= \sqrt{\frac{V_m^2}{2\pi} \left[ \frac{2\pi}{T} \frac{t}{2} - \frac{\sin\left(2 * \frac{2\pi}{T}t\right)}{4} \right]_0^{T/2}} = \sqrt{\frac{V_m^2}{2\pi} \left[ \frac{\pi}{2} \right]} = \frac{V_m}{2} \end{aligned}$$

Note:

$$\sin^2(x) = \frac{1 - \cos(2x)}{2}$$

5.

$$\omega = 50$$

$$Z = R + j\omega L + \frac{1}{j\omega C} = 4 + j * 50 * 0.24 - j \frac{1}{50 * 0.0025} = 5.66 \angle 45^\circ \Omega$$

$$I_0 = \frac{V}{Z} = \frac{0.1 \angle -90^\circ}{5.66 \angle 45^\circ} = 17.67 \angle -135^\circ \text{ mA}$$

$$i_0 = 17.67 \cos(50t - 135^\circ) \text{ mA}$$

6.

(a)

$$Z_{ab} = j\omega L + R \parallel \left( \frac{1}{j\omega C} \right) = j\omega L + \frac{-\frac{jR}{\omega C}}{R - \frac{j}{\omega C}} = j\omega L + \frac{-jR}{\omega CR - j} = j\omega L + \frac{-jR(\omega CR + j)}{(\omega CR)^2 + 1}$$

Pure resistive  $\rightarrow \text{Im}(Z_{ab}) = 0$

$$\therefore \omega L - \frac{\omega CR^2}{(\omega CR)^2 + 1} = 0 \rightarrow \omega^2 = \frac{\left(\frac{CR^2}{L}\right) - 1}{(CR)^2} = 900 * 10^8$$

$$\omega = 300 \text{ krad/s}$$

(b)

$$Z_{ab}(300 * 10^3) = j48 + \frac{100(-j133.33)}{100 - j133.33} = 64 \Omega$$

7.

a)  $H(jw) = \frac{v_o}{v_i} = \frac{1/sC \parallel R_L}{R + 1/sC \parallel R_L} = \frac{R_L}{sRCR_L + (R + R_L)}$

b)  $|H(jw)| = \frac{R_L}{\sqrt{wRCR_L^2 + (R + R_L)^2}}$   $|H(jw)|$  is maximum at  $w=0$

c)  $|H(jw)|_{max} = \frac{R_L}{R + R_L}$

d)  $|H(jw)| = \frac{R_L}{\sqrt{2(R + R_L)}} = \frac{1/RC}{\sqrt{w_c^2 + [(R + R_L)/RR_L C]^2}}$   $w_c = \frac{1}{RC} \left( 1 + \left( \frac{R}{R_L} \right) \right)$