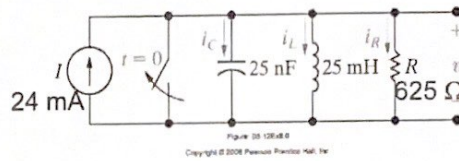



The Third Exam. of Electric Circuits

December 5, 2022


1. A circuit is shown as follows. Find $i_L(t)$ when $i_L(0^+) = i_L(0^-) = 0$ and $v_c(0^+) = v_c(0^-) = 0$.



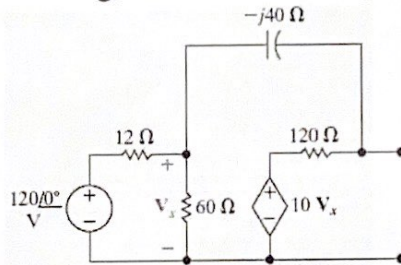2. For a circuit shown in the following, find its Thévenin equivalent circuit looked from the right-hand side port.




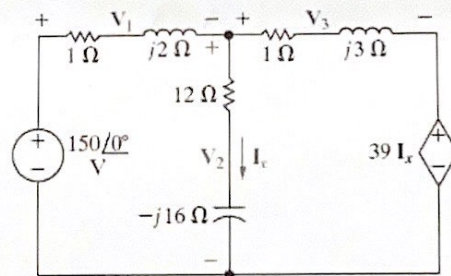3. A circuit is shown as follows. Find V_1 and V_2 .



4. For the circuit shown in the following, Load 1 absorbs an average power of 6 kW at a leading power factor of 0.6 and Load 2 absorbs 20 kVA at a lagging power factor of 0.6. Given that $f = 60$ Hz, compute the value of the capacitor that would correct the power factor to 1 if placed in parallel with the two loads.

$0.015 - j0.02$
 $0.0275 + j0.01$

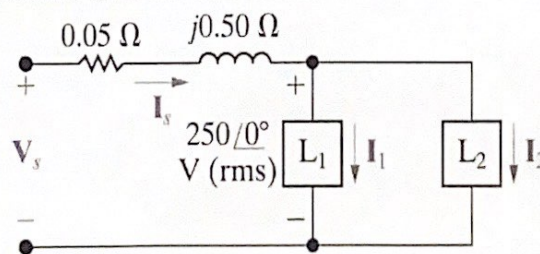

$X = \frac{250}{Q} = -j0.5$
 $Q =$

5. For a circuit shown as follows, find the maximum power transfer if $5000 \Omega \geq R_L \geq 0 \Omega$ and $0 \geq X_C \geq -3000 \Omega$.

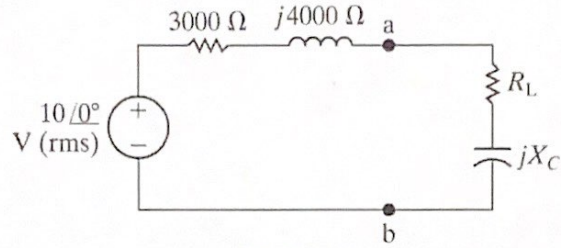


Figure 10-23E:10 9
Copyright © 2008 Pearson Prentice Hall, Inc.