

EE2210 Electric Circuits H.W.1 Ans.



1.

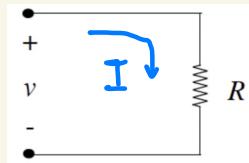


Figure 1.

$$V = 2V_0 \cos(\omega t)$$

$$I = \frac{2V_0}{R} \cos(\omega t)$$

$$P_{avg} = \frac{1}{T} \int_0^T \left[\frac{4V_0^2}{R} \cos^2(\omega t) \right] dt$$

$$= \frac{1}{T} \int_0^T \left[\frac{4V_0^2}{R} \cdot \frac{1 + \cos(2\omega t)}{2} \right] dt = \frac{2V_0^2}{R}$$

2.

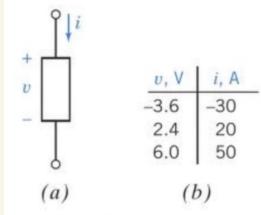


Figure 2.

2-(a)

$V(V)$	$I(A)$
--------	--------

$$\begin{array}{l|l} -3.6 & -30 \\ 2.4 & 20 \\ 6 & 50 \end{array} \quad \begin{array}{l} \text{slope} = \frac{2.4 - (-3.6)}{20 - (-30)} = 0.12 \text{ (V/A)} \\ \text{slope} = \frac{6 - 2.4}{50 - 20} = 0.12 \text{ (V/A)} \end{array}$$

\Rightarrow $I-V$ plot is a straight line

with slope = 0.12 (V/A) , so this element is linear.

2-(b)

We can get $I-V$ function from (a)

$$\Rightarrow V = 0.12 I$$

$$\text{As } I = 40 \text{ mA}$$

$$\Rightarrow V = 0.12 \times 40 \times 10^{-3} = 4.8 \text{ mV}$$

3.



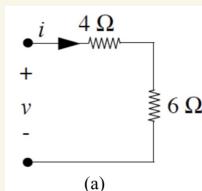



Figure 3.

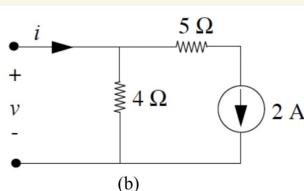
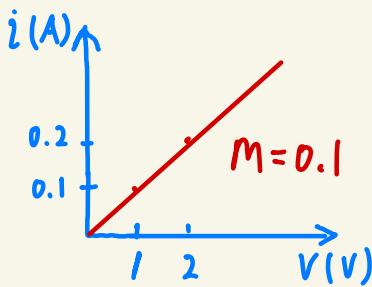
$$(a) V = i \times (4 + 6) \\ = 10 \cdot i$$


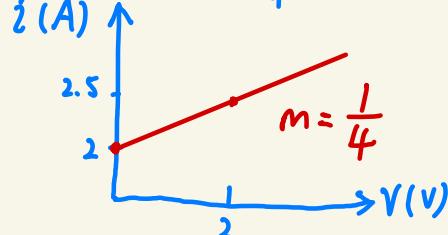
$$(b) \begin{cases} V = 0, i = 2 \\ V = 1, i = 2 + \frac{1}{4} \\ V = 2, i = 2 + \frac{2}{4} \end{cases} \Rightarrow i = \frac{1}{4}V + 2$$



4.


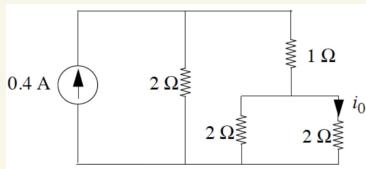


Figure 4.

4.

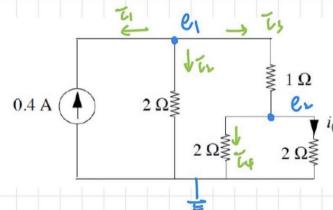

$$\bar{e}_0 = \frac{e_2}{2}$$

$$KCL @ e_1: -0.4 + \frac{e_1}{2} + \frac{e_1 - e_2}{1} = 0$$

$$KCL @ e_2: \frac{e_2 - e_1}{1} + \frac{e_2}{2} + \frac{e_2}{2} = 0$$

$$\Rightarrow e_1 = 0.4V, e_2 = 0.2V$$

$$\Rightarrow \bar{e}_0 = \frac{0.2}{2} = 0.1A \text{ } \star$$

5.


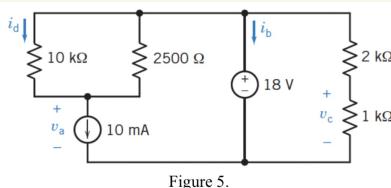


Figure 5.

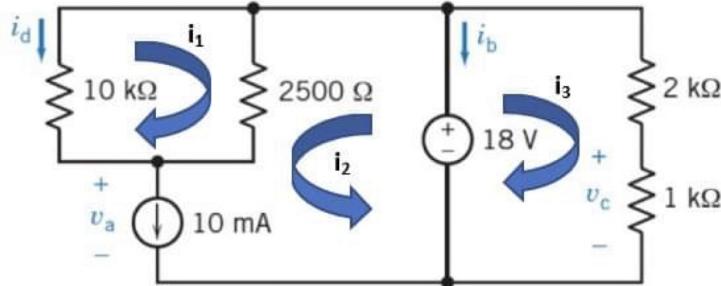

(a)

$$\text{Mesh1: } i_1 \times 10k + (i_1 + i_2) \times 2500 = 0$$

$$\text{Mesh2: } i_2 = 10\text{mA}$$

$$\text{Mesh3: } 18 - i_3 \times 2k - i_3 \times 1k = 0$$

$$i_1 = -2\text{mA}, i_2 = 10\text{mA}, i_3 = 6\text{mA}$$

$$v_c = i_3 \times 1k = 6\text{mA} \times 1k = 6\text{V}$$

$$v_a = 18 - (i_1 + i_2) \times 2500 = 18 - (-2\text{mA} + 10\text{mA}) \times 2500 = -2\text{V}$$


$$i_b = -(i_2 + i_3) = -(10\text{mA} + 6\text{mA}) = -16\text{mA}$$

$$i_d = -i_1 = 2\text{mA}$$

(b)

The power supplied by the voltage source is $18 \times (-i_b) = 18 \times 16\text{mA} = 288\text{mW}$

6

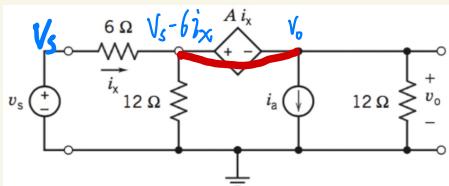

$$\begin{cases} \frac{V_o}{12} + i_a + \frac{V_s - 6i_x}{12} - i_x = 0 \\ V_s - 6i_x = V_o + A i_x \end{cases}$$

$$\Rightarrow V_o = \frac{12 - A}{A + 24} V_s - \frac{12(A+6)}{A+24} i_a$$


題目給: $V_o = 2V_s + 9$

$$\therefore \frac{12 - A}{A + 24} = 2 \Rightarrow A = -12 \quad \text{※}$$

$$\frac{-12(A+6)}{A+24} i_a = 9 \Rightarrow i_a = \frac{3}{2} A \quad \text{※}$$

7.

HW1

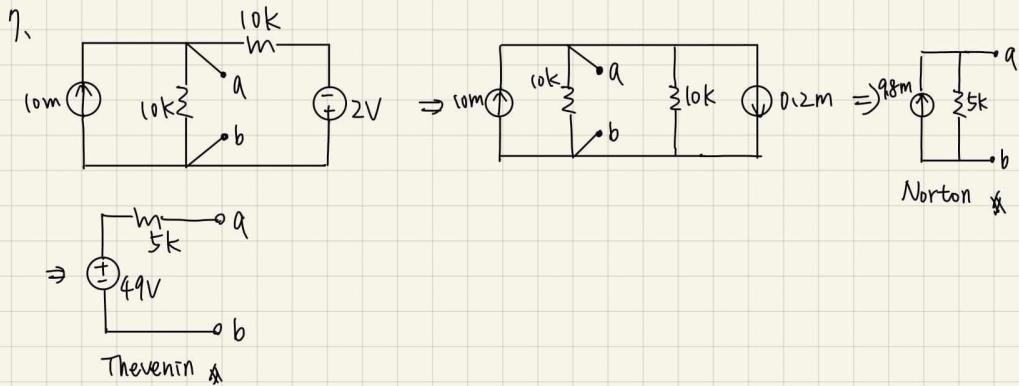

8.

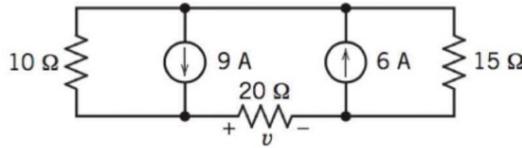
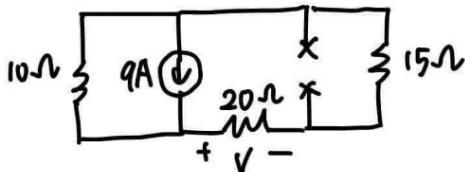
8. Use superposition to find the voltage v in Figure 8. (10%)

Figure 8.


①



$$V = 9 \times \frac{10}{(50+5)+10} = 2A$$

$$V_1 = 20 \times 2 = 40V$$

②

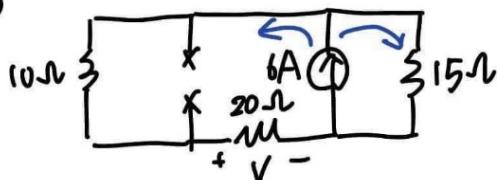

$$V = 6 \times \frac{15}{(10+20)+15} = 2A$$

$$V_2 = 20 \times 2 = 40V$$

$$\text{total } V = V_1 + V_2 = 80V$$

9.

9. Determine the voltage v_5 in Figure 9. (8%)



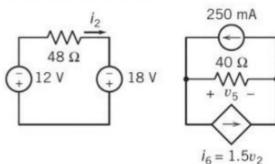


Figure 9.

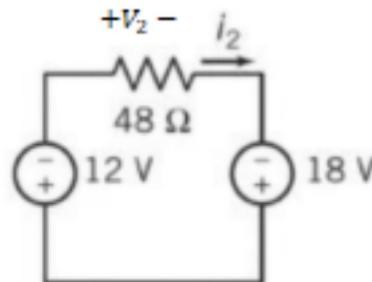
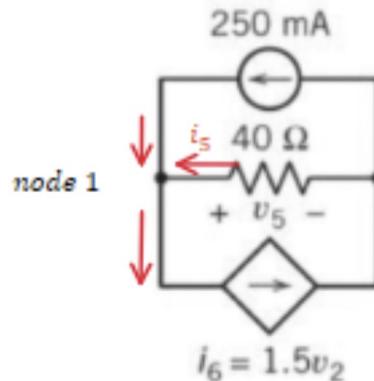
$$\begin{aligned} V_2 &= -12V - (-18V) = 6V \\ \rightarrow i_6 &= 1.5V_2 = 9A \end{aligned}$$



From node 1,

Current in = Current out

$$250\text{ mA} + i_5 = i_6 = 9\text{ A}$$

$$\rightarrow i_5 = 9\text{ A} - 250\text{ mA} = 8.75\text{ A}$$

$$\rightarrow V_5 = R * I = 40 * 8.75 = 350\text{ V}$$

$$V_5 = -350\text{ V}$$