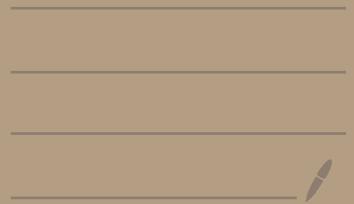



# EE2210 Electric circuits HW2 Ans.

---


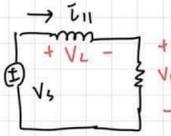
## HW 2 - 1

By superposition:  $V_S = L \cdot \frac{d\tilde{i}_{11}}{dt} + \tilde{i}_{11}R$



① particular solution:  $\tilde{i}_{11} = \frac{V_S}{R}$

② homogeneous solution:


$$L \frac{d\tilde{i}_{11}}{dt} + \tilde{i}_{11}R = 0 \rightarrow \text{Assume } \tilde{i}_{11} = A e^{st}$$

$$sLA e^{st} + RA e^{st} = 0 \rightarrow (sL + R) = 0 \rightarrow s = -\frac{R}{L}$$

$$\Rightarrow \tilde{i}_{11} = \frac{V_S}{R} + A e^{-\frac{R}{L}t}$$

initial condition:  $\tilde{i}_{11}(0) = \frac{V_S}{R} + A = 0 \rightarrow A = -\frac{V_S}{R}$
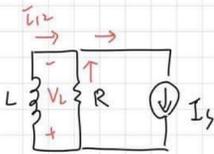
$$\Rightarrow \tilde{i}_{11}(t) = \frac{V_S}{R} - \frac{V_S}{R} e^{-\frac{R}{L}t}$$



$$I_S = \tilde{i}_R + \tilde{i}_{12} = \frac{V_L}{R} + \frac{1}{L} \int_{-\infty}^t V_L dt$$

$$I_S = \frac{V_L}{R} + \tilde{i}_{12}(0) + \frac{1}{L} \int_0^t V_L dt$$

$$\frac{d}{dt} \Rightarrow \frac{1}{R} \frac{dV_L}{dt} + \frac{1}{L} V_L = 0 \Rightarrow V_L = A e^{-\frac{R}{L}t}$$

initial condition:  $\tilde{i}_{12}(0) = 0 = I_S - \frac{A \cdot 1}{R} \rightarrow A = I_S \cdot R$


$$\Rightarrow \tilde{i}_{12}(t) = I_S - I_S e^{-\frac{R}{L}t}$$

$$\Rightarrow \tilde{i}_1(t) = \tilde{i}_{11}(t) + \tilde{i}_{12}(t)$$


$$= \frac{1}{3000} [1 - e^{-3000t}] + \frac{1}{1000} [1 - e^{-3000t}]$$

#

2.

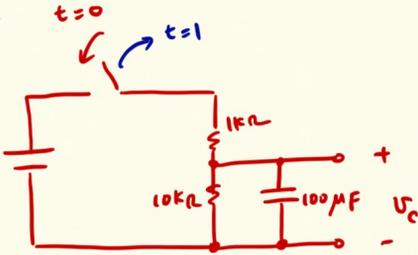


1) For  $t < 0$ ,

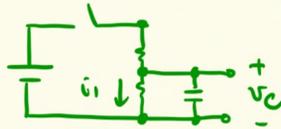

$$i_1 = 0$$

$$V_c = 0$$



2)  $0 < t < 1$ ,

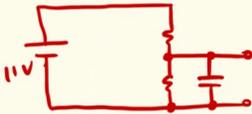

$$\frac{11 - V_c}{1k} = \frac{V_c}{10k} + 100\mu \cdot \frac{dV_c}{dt} \Rightarrow V_c = 10 - 10 \cdot e^{-t/(9.09m)} \text{ V}$$

when  $t \rightarrow \infty$ ,  $V_c \rightarrow 10V$

3)  $t > 1$ ,

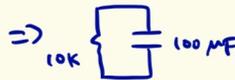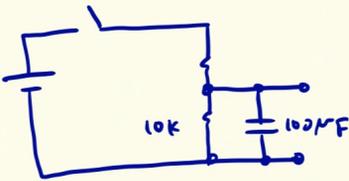


with initial condition

$$V_c(t=1)$$

$$= 10 - 10 \cdot e^{-1/(9.09m)}$$

$$\approx 10 \text{ V}$$

$$V_c = 10 \cdot e^{-t} \text{ V}$$

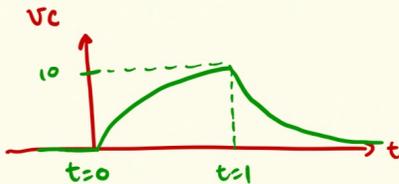

$$V_c = 0$$

$$V_c = 10 - 10 \cdot e^{-t/9.09m}$$

$$V_c = 10 \cdot e^{-t}$$

3、

$$\dot{i}(t) = C \frac{dV_C}{dt} \quad , \quad V_C = \frac{1}{C} \int_{-\infty}^t \dot{i}(\tau) d\tau$$

$$V(t) = i(t) \times 8 + \frac{1}{C} \int_{-\infty}^t i(\tau) d\tau$$

$$= 8i(t) + \frac{1}{C} \int_{-\infty}^0 i(\tau) d\tau + \frac{1}{C} \int_0^t i(\tau) d\tau$$

$$= 8 \cdot 3e^{-25t} + (-2) + \frac{1}{0.1} \int_0^t 3e^{-25\tau} d\tau$$

$$= 24e^{-25t} - 2 + 3 \times \frac{1}{0.1} \times \left(\frac{1}{-25}\right) e^{-25\tau} d\tau \Big|_0^t$$

$$= 24e^{-25t} - 2 - \frac{6}{5} (e^{-25t} - 1)$$

$$= 22.8e^{-25t} - 0.8 \text{ #}$$

$$V_C = V(t) - i(t) \times 8 = 22.8e^{-25t} - 0.8 - 8 \times 3e^{-25t}$$

$$= -1.2e^{-25t} - 0.8 \text{ #}$$

## HW2-4

For  $0 < t < 1\mu$ ,

$$\begin{aligned}i_L(t) &= \frac{1}{L} \int_0^t v_s(t) dt + I_0 \\ &= \frac{1}{5m} \int_0^t 4m dt + (-2\mu) = \underline{0.8t - 2\mu} \text{ A}\# \end{aligned}$$

For  $1\mu < t < 3\mu$ ,


$$\begin{aligned}i_L(t) &= \frac{1}{5m} \int_{1\mu}^t (-1m) dt + i(1\mu) \\ &= -0.2(t - 1\mu) + (-1.2\mu) = \underline{-0.2t - 1\mu} \text{ A}\# \end{aligned}$$

For  $t > 3\mu$ ,

$$\begin{aligned}i_L(t) &= \frac{1}{5m} \int_{3\mu}^t 0 \cdot dt + i(3\mu) \\ &= -0.2 \times 3\mu - 1\mu = \underline{-1.6\mu} \text{ A}\# \end{aligned}$$


5.

Use equivalent circuit

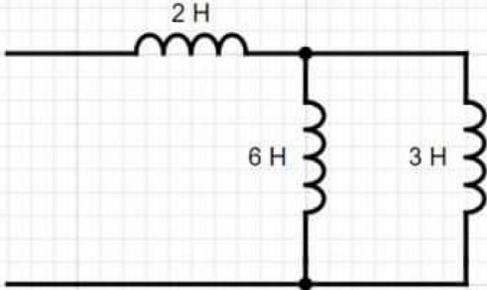

$$L_{\text{eq}} = 2 + \frac{1}{\frac{1}{6} + \frac{1}{3}} = 4 \text{ H}$$

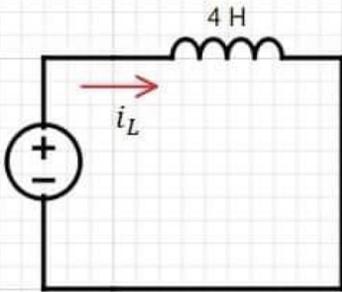Thus, ordinary circuit can be re-draw as below




Then,

$$V = L \frac{di_L}{dt} \rightarrow i = \frac{1}{L} \int_0^t V d\bar{t} = \frac{1}{4} \int_0^t 10 * \cos(10\bar{t}) d\bar{t} = 0.25 * \sin(10t) \text{ A}$$

## HW2

b.

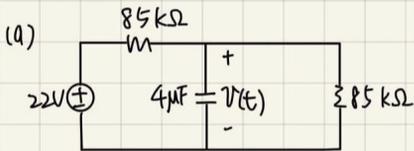


at steady state:

$$V(t) = 11\text{ V}$$

$$E = \frac{1}{2} C V^2 = \frac{1}{2} \cdot 4\text{ }\mu\text{F} \cdot 11^2 = 242\text{ }\mu\text{J}$$

(b)

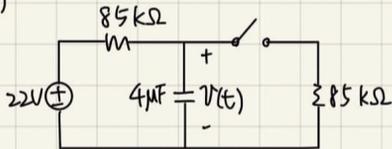


at steady state:

$$V(t) = 22\text{ V}$$


$$E = \frac{1}{2} C V^2 = \frac{1}{2} \cdot 4\text{ }\mu\text{F} \cdot 22^2 = 968\text{ }\mu\text{J}$$

7.

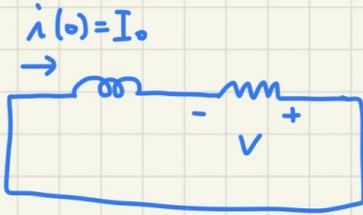

$$R = R_1 \parallel R_2 = \frac{R_1 R_2}{R_1 + R_2}$$
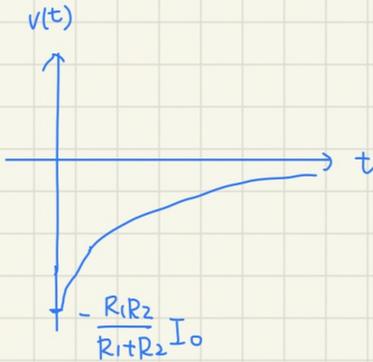
$$v(t) = -\frac{R_1 R_2}{R_1 + R_2} I_0 e^{-\frac{R_1 R_2}{R_1 + R_2} \cdot \frac{t}{L}} \quad \#$$



8.

$$V = L \frac{di}{dt}$$

$$P = I V = (\cos(100t)) \cdot L \cdot (-\sin(100t) \cdot 10)$$

$$= I \cdot L \frac{di}{dt} = \begin{cases} -500 \sin(100t) \cos(100t), & t \geq 0 \\ 0 & t < 0 \end{cases}$$

$$= \frac{d}{dt} \left( \frac{1}{2} L I^2 \right)$$

$$E = \frac{1}{2} L I^2 = \begin{cases} \frac{5}{2} (\cos(100t))^2, & t \geq 0 \\ 0 & t < 0 \end{cases}$$