

EE2210 Electric circuits HW3 Ans.



1. Determine i and v for the circuit in Figure 1. (16%)

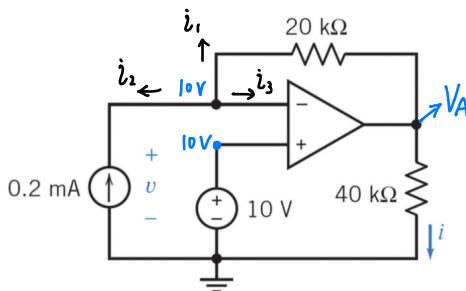


Figure 1.

The voltages at the input nodes of an ideal OP amplifier are equal!

$$\therefore V = 10 \text{ (V)} \quad \text{※}$$

Apply KCL at inverting input node of OP

$$i_1 + i_2 + i_3 = 0$$

$$\frac{10 - V_A}{20 \times 10^3} + (-0.2 \times 10^{-3}) + 0 = 0 \quad \therefore V_A = 6 \text{ (V)}$$

$$i = \frac{V_A}{40 \text{ k}} = \frac{6}{40000} = \underline{0.15 \text{ (mA)}} \quad \text{※}$$

2.

$$\textcircled{2} \quad \frac{0 - V_a}{60k} + \frac{0 - 3.75}{30k} = 0, \quad V_a = -7.5V$$


$$\frac{V_a - 0}{60k} + \frac{V_a - 0}{15k} + \frac{V_a - V_o}{12k} = 0$$

$$\xrightarrow{60k} V_a + 4V_a + 5V_a - 5V_o = 0, \quad 10V_a = 5V_o, \quad V_o = 2V_a = -15V$$

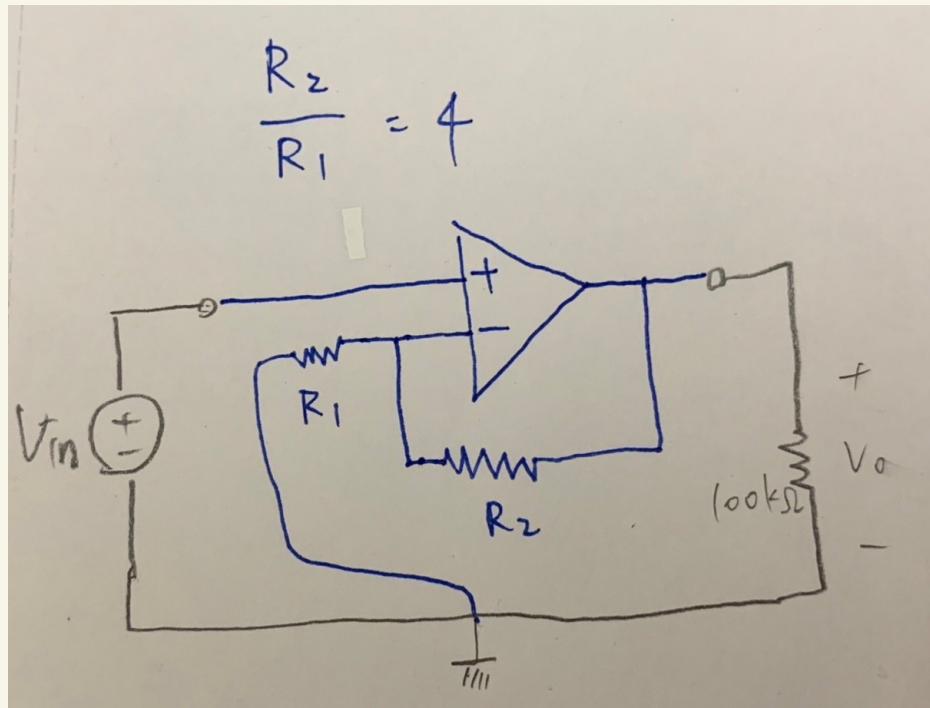3. We want positive gain.

∴ Connect V_{in^+} to the positive side of the OP
 V_{in^-} to the negative side

$$-\frac{V_{in}}{R_1} = \frac{V_{in} - V_o}{R_2} \Rightarrow \frac{V_o}{V_{in}} = 1 + \frac{R_2}{R_1} = 5 \Rightarrow \frac{R_2}{R_1} = 4 *$$



4.


$$(a) RC \frac{dV_C}{dt} + V_C = U_M = 10 \quad , \quad V_{in} = 10u(t)$$

$$\Rightarrow V_{C,p} = 10$$

$$\Rightarrow V_{C,h} = A e^{-t/\tau_{RC}}$$

$$\Rightarrow V_C(0) = 0 \Rightarrow 10 + A = 0, \quad A = -10 \Rightarrow V_C = 10 - 10e^{-t}$$
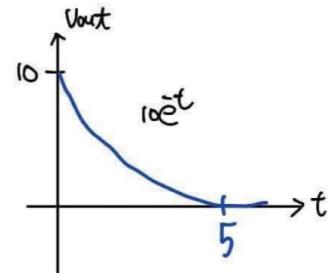
$$\therefore V_{out} = 10 - (10 - 10e^{-t}) = 10e^{-t}$$




$$(b) 2R i_L + L \cdot \frac{di_L}{dt} = U_M = 10 \quad , \quad U_M = 10u(t)$$

$$\Rightarrow i_L, p = \frac{10}{2R}, \quad i_L, h = A e^{t/2R/L}$$


$$\Rightarrow i_L(0) = 0 = \frac{10}{2R} + A, \quad A = -\frac{10}{2R}$$

$$\Rightarrow i_L = \frac{10}{2R} - \frac{10}{2R} e^{-t/2R/L}$$
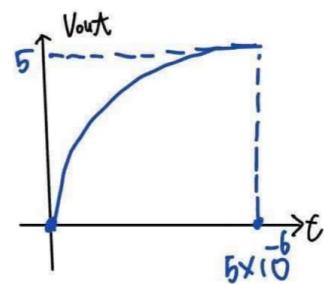
$$\Rightarrow V_{out} = i_L \cdot R = 5 - 5e^{-(5/R)t}$$



5.

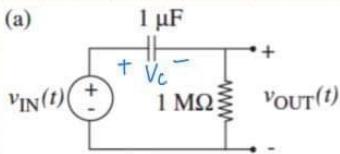

$$C \frac{dV_C}{dt} = \frac{V_{out}}{R} \Rightarrow 1\mu \frac{dV_C}{dt} = \frac{V_{out}}{1M} \Rightarrow \frac{dV_C}{dt} = V_{out}$$

$$\because V_C = V_{IN} - V_{out}$$

$$\frac{d(V_{IN} - V_{out})}{dt} = 10 - \frac{dV_{out}}{dt} = V_{out}$$

$$V_{out} = V_{outH} + V_{outP}$$


$$V_{outH} + \frac{dV_{outH}}{dt} = 0, \text{ if } V_{outH} = Ae^{st}$$

$$Ae^{st} + Ase^{st} = Ae^{st}(1+s) = 0 \quad \therefore s = -1$$

$$V_{outP} = 10$$

$$V_{out}(0) = 0 = A + 10, \quad \therefore A = -10$$
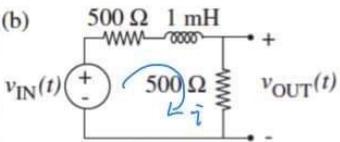
$$\Rightarrow V_{out}(t) = -10e^{-t} + 10 \quad (t \geq 0) \quad *$$



$$\bar{i} = \frac{V_{out}}{500}$$

$$V_{IN} - 500\bar{i} - L \frac{di}{dt} = V_{out}$$

$$10t - 500 \cdot \frac{V_{out}}{500} - 1m \cdot \frac{1}{500} \frac{dV_{out}}{dt} = V_{out}$$

$$10t - 2V_{out} - 2 \times 10^6 \frac{dV_{out}}{dt} = 0$$

$$\frac{dV_{out}}{dt} + 10^6 V_{out} = 5 \times 10^6 t$$

$$V_{outH}(t) = A e^{-10^6 t}, \quad V_{outf}(t) = B + Ct$$

$$\frac{dV_{outf}}{dt} + 10^6 V_{outf} = C + 10^6(B + Ct) = C + B10^6 + Ct \cdot 10^6 = 5 \times 10^6 t$$

$$\therefore C = 5$$

$$5 + B \cdot 10^6 = 0 \Rightarrow B = -5 \times 10^{-6}$$

$$V_{out}(t) = A e^{-10^6 t} - 5 \times 10^{-6} + 5t$$

$$V_{out}(0) = A - 5 \times 10^{-6} = 0, \quad A = 5 \times 10^{-6}$$

$$\therefore V_{out}(t) = 5 \times 10^{-6} e^{-10^6 t} - 5 \times 10^{-6} + 5t \quad (t \geq 0) \quad *$$

