

EE2210 Electric Circuits
Homework 3 (Lecture 6-7)
Total points: 100

Fall 2022

Please write down clearly the calculation/thinking process of each question. Unit is needed when applicable.

Due: December 5th, 10:10am

1. Determine i and v for the circuit in Figure 1. (16%)

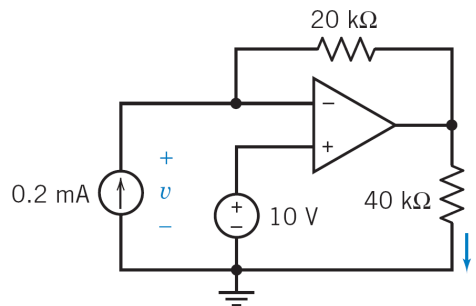


Figure 1.

2. Determine v_a and v_o for the circuit in Figure 2. (15%)

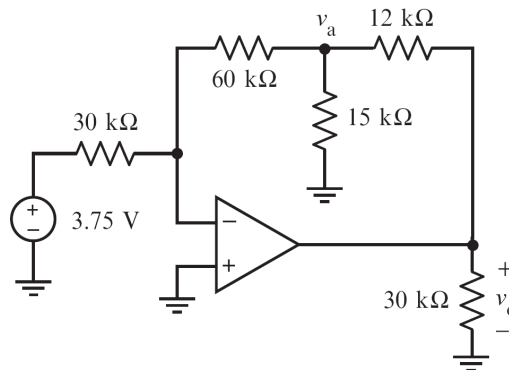


Figure 2.

3. Design the operational amplifier in Figure 3 such that $v_o = 5v_{in}$. (15%)

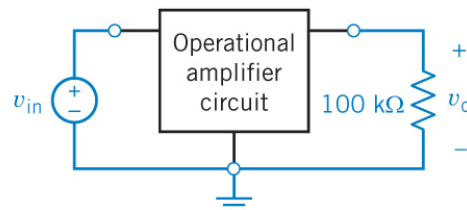


Figure 3.

4. Determine and plot $v_{out}(t)$ for the circuit in Figure 4(a) and 4(b). The input is a 10-V

step function, $v_{in}(t) = 10*u(t)$. (18%)

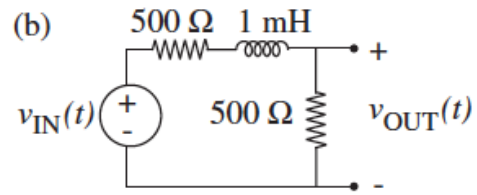
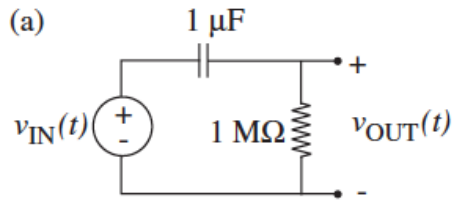


Figure 4.

- Determine and plot $v_{out}(t)$ for the circuits in Figure 4(a) and 4(b) assuming the input is a 10-V ramp function, that is $v_{in}(t) = 0$ for $t < 0$ and $v_{in}(t) = 10*t$ for $t \geq 0$. (18%)
- Determine and plot $v_{out}(t)$ for the circuits in Figure 4(a) and 4(b) assuming the input is a 10-V impulse function, that is $v_{in}(t) = 10*\delta(t)$. (18%)