
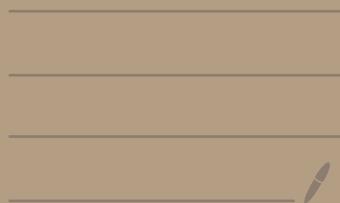


# EE2210 Electric circuits HW4 Ans.

---

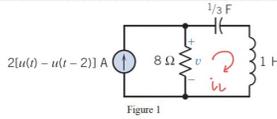

# HW4 - 1



superposition:  $I_{in} = 2u(t)$

$$\begin{cases} (I_{in} - \bar{i}_L) \cdot R = V_C + L \cdot \frac{d\bar{i}_L}{dt} \\ \bar{i}_L = \bar{i}_C = C \cdot \frac{dV_C}{dt} \end{cases}$$

$$\Rightarrow \frac{d^2 V_C}{dt^2} + \frac{R}{L} \frac{dV_C}{dt} + \frac{V_C}{LC} = \frac{I_{in} \cdot R}{LC}$$

$$V_{C,p} = I_{in} \cdot R = 16 u(t)$$

$$V_{C,h} = A_1 e^{s_1 t} + A_2 e^{s_2 t}$$

characteristic eqn:  $s^2 + 8s + 3 = 0$

$$\rightarrow s = -4 \pm \sqrt{13}$$

initial condition:



$$\begin{cases} V_C = 16 + A_1 + A_2 = 0 \\ \bar{i}_L = C(A_1 s_1 + A_2 s_2) = 0 \end{cases}$$

$$\Rightarrow A_1 = \frac{16s_2}{s_1 - s_2} = \frac{-3\sqrt{13} - 8}{13} \approx -16.875$$

$$A_2 = \frac{16s_1}{s_2 - s_1} = \frac{3\sqrt{13} - 8}{13} \approx 0.875$$

$$V_{C1} = 16 - 16.875 e^{(-4+\sqrt{13})t} + 0.8 e^{(-4-\sqrt{13})t}$$

②  $I_{in} = -2u(t-2)$

→ replace  $t \rightarrow t-2$  and multiply negative sign from above.

$$\Rightarrow V_{C2} = -16 + 16.875 e^{(-4+\sqrt{13})(t-2)} - 0.8 e^{(-4-\sqrt{13})(t-2)}$$

$V_C = V_{C1} + V_{C2}$

$$= [16 - 16.875 e^{(-4+\sqrt{13})t} + 0.8 e^{(-4-\sqrt{13})t}] u(t)$$

$$+ [-16 + 16.875 e^{(-4+\sqrt{13})(t-2)} - 0.8 e^{(-4-\sqrt{13})(t-2)}] u(t-2)$$

(V) \*

$$2. \quad (a) \quad \dot{i}_R = \frac{V_0}{R} = \frac{15}{200} = 75 \text{ mA}$$

$$\dot{i}_C = -\dot{i}_L - \dot{i}_R = 45 - 75 = -30 \text{ mA} \#$$

$$(b) \quad \dot{i}_R + \dot{i}_L + \dot{i}_C = 0$$

$$\frac{V}{R} + \frac{1}{L} \int_0^t v \, dt + \dot{i}_L(0) + C \frac{dV}{dt} = 0 \Rightarrow C \frac{d^2V}{dt^2} + \frac{1}{R} \frac{dV}{dt} + \frac{1}{L} V = 0$$

$$\Rightarrow \frac{d^2V}{dt^2} + \frac{1}{RC} \frac{dV}{dt} + \frac{1}{LC} V = 0 \Rightarrow s^2 + 25000s + 10^8 = 0 \Rightarrow s = -20000 / -5000$$

$$\therefore v(t) = A_1 e^{-20000t} + A_2 e^{-5000t}, \quad v(0) = A_1 + A_2 = 15 \quad \text{--- (1)}$$

$$-20000 A_1 - 5000 A_2 = -375000 + 225000 = -150000 \Rightarrow A_1 + 0.25 A_2 = 7.5 \quad \text{--- (2)}$$


$$\text{solve (1), (2)} \Rightarrow A_1 = 5, \quad A_2 = 10, \quad v(t) = 5e^{-20000t} + 10e^{-5000t}$$

$$(c) \quad \dot{i}_L(t) = \frac{1}{L} \int_0^t v(\tau) \, d\tau + \dot{i}_L(0) = 20 \int_0^t (5e^{-20000\tau} + 10e^{-5000\tau}) \, d\tau - 0.045$$

$$= -0.005 e^{-20000t} - 0.04 e^{-5000t} \#$$

3.

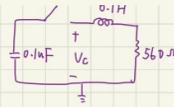(a) By KVL,  $V_C(t) + L \frac{d\lambda(t)}{dt} + \lambda(t)R = 0$



$$\lambda(t) = C \frac{dV_C(t)}{dt} \Rightarrow V_C + LC \frac{d^2 V_C}{dt^2} + RC \frac{dV_C}{dt} = 0$$

$$\Rightarrow \frac{d^2 V_C}{dt^2} + \frac{R}{L} \frac{dV_C}{dt} + \frac{1}{LC} V_C = 0 \Rightarrow \frac{d^2 V_C}{dt^2} + 5600 \frac{dV_C}{dt} + 10^8 V_C = 0$$

$$\therefore \begin{cases} \omega_0 = \frac{1}{\sqrt{LC}} = 10000 \\ \alpha = \frac{R}{2L} = 2800 \end{cases} \Rightarrow \omega_0 > \alpha \Rightarrow \begin{cases} s_{1,2} \text{ complex conjugate} \\ \text{under-damped} \end{cases}$$

$$\therefore V_C(t) = A_1 e^{-\alpha t} e^{j(\omega_0^2 - \alpha^2)t} + A_2 e^{-\alpha t} e^{-j(\omega_0^2 - \alpha^2)t}$$

$$= A_1 e^{-2800t} e^{j9600t} + A_2 e^{-2800t} e^{-j9600t}$$

$$= e^{-2800t} (K_1 \cos 9600t + K_2 \sin 9600t)$$

$$\therefore V_C(0^+) = 100V = K_1$$

$$\therefore \lambda(t) = C \frac{dV_C}{dt} = C \times [-2800 e^{-2800t} (100 \cos 9600t + K_2 \sin 9600t) + e^{-2800t} \times (-9.6 \times 10^5 \sin 9600t + 9600 K_2 \cos 9600t)]$$

$$\lambda(0) = 0 = C \times [-2800 \times 100 + 9600 K_2] \Rightarrow K_2 = 29.1\bar{6}$$


$$\therefore V_C(t) = e^{-2800t} (100 \cos 9600t + 29.1\bar{6} \sin 9600t),$$

$$\lambda(t) = C \frac{dV_C}{dt} = (10^{-9}) \times e^{-2800t} \times [(-28 \times 10^5 + 9600 \times 29.1\bar{6}) \cos 9600t + (-2800 \times 29.1\bar{6} - 9.6 \times 10^5) \sin 9600t]$$



$$= -\frac{5}{48} e^{-2800t} \sin 9600t \text{ \#}$$

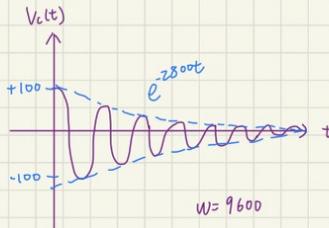(b)  $\begin{cases} \alpha = \frac{R}{2L} = 2800 \\ \omega_0 = \frac{1}{\sqrt{LC}} = 10000 \end{cases} \Rightarrow \omega_0 > \alpha \Rightarrow V_C \text{ is under damping}$

$$V_C(t) = e^{-2800t} (100 \cos 9600t + 29.1\bar{6} \sin 9600t)$$




4.

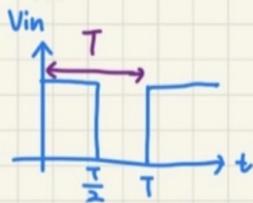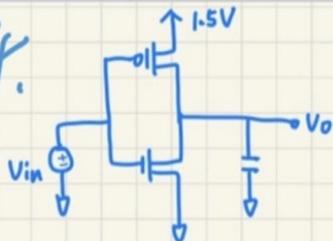

$0 < t < \frac{T}{2}$

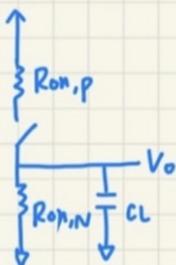$V_{in} = V_{high}$   $\left\{ \begin{array}{l} \text{Nmos on} \\ \text{Pmos off} \end{array} \right.$  discharging  $C_L$



$V_{o, initial} = V_s, V_{o, final} = 0$


$V_o(t) = 0 + (0 - V_s) e^{-t/R_{on}C_L}$

$E_1 = \int_0^{T/2} \frac{V_o^2}{R_{on}} dt = \frac{V_s^2 C_L}{2} (1 - e^{-2(T/2)/R_{on}C_L})$

$\approx \frac{V_s^2 C_L}{2} (\because T/2 \gg R_{on}C_L)$

$\frac{T}{2} < t < T$

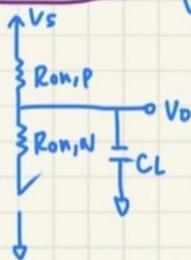$V_{in} = V_{low}$   $\left\{ \begin{array}{l} \text{Nmos off} \\ \text{Pmos on} \end{array} \right.$  charging  $C_L$



$V_{o, initial} = 0, V_{o, final} = V_s$



$V_o(t) = V_s + (0 - V_s) e^{-t/R_{on}C_L}$

$E_2 = \int_{T/2}^T \frac{(V_s - V_o)^2}{R_{on}} dt \approx \frac{V_s^2 C_L}{2} (\because T/2 \gg R_{on}C_L)$

$E_{total} = E_1 + E_2 = V_s^2 C_L, \bar{P} = \frac{E_{total}}{T} = E_{total} \cdot f = V_s^2 C_L f$

Static power = 0 W    Dynamic power =  $1.5^2 \cdot 10 \cdot 10^{-15} \cdot 10^7 = 0.225 \mu W$

5.

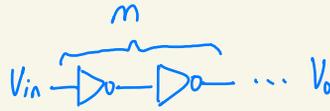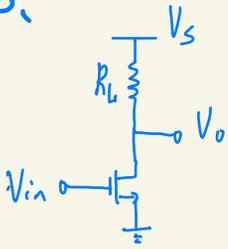

If  $V_{in}$  is high, nmos turns on, then the static power consumption is

$$V_s \cdot \left( \frac{V_s}{R_L + R_{on}} \right) = \frac{V_s^2}{R_L + R_{on}}$$

Over the inverter chain, only half of inverters will turn on because of the inverting property, the total static power cons.

is

$$\frac{m}{2} \times \frac{V_s^2}{R_L + R_{on}} \quad \text{✗}$$