

EE2210 Electric Circuits
Homework 4 (Lecture 8-10)
Total points: 105

Fall 2022

Please write down clearly the calculation/thinking process of each question. Unit is needed when applicable.

Due: December 26th, 10:10am.
 Total: 110 points

1. Find $v(t)$ for $t \geq 0$ for the circuit in Figure 1. (20%)

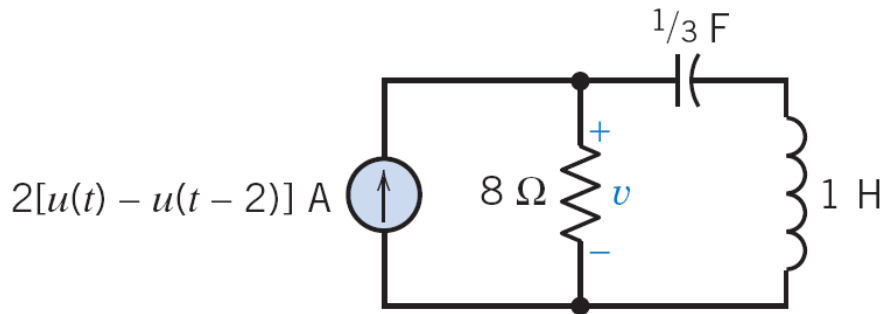


Figure 1

2. Consider the circuit in Figure 2. The elements have the values: $R = 200 \Omega$, $C = 200 \text{ nF}$, and $L = 50 \text{ mH}$. The initial inductor current $i_L(0)$ is -45 mA , and the initial capacitor voltage $v(0)$ is 15 V .
- Calculate the initial current in each branch of the circuit. (10%)
 - Derive $v(t)$ for $t \geq 0$. (10%)
 - Derive $i_L(t)$ for $t \geq 0$. (10%)

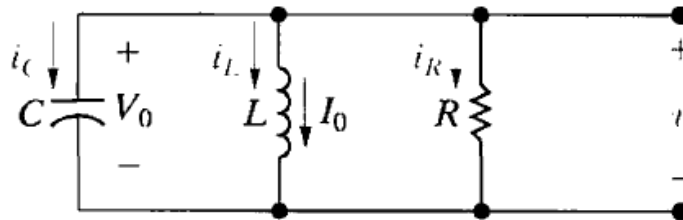


Figure 2.

3. The $0.1 \mu\text{F}$ capacitor in Figure 3 is charged to 100 V before $t = 0$. At $t = 0$, the capacitor is discharged through a series combination of a 100 mH inductor and a 560Ω resistor.
- Derive $i(t)$ for $t \geq 0$. (10%)
 - Derive and plot $v_C(t)$ for $t \geq 0$. (15%)

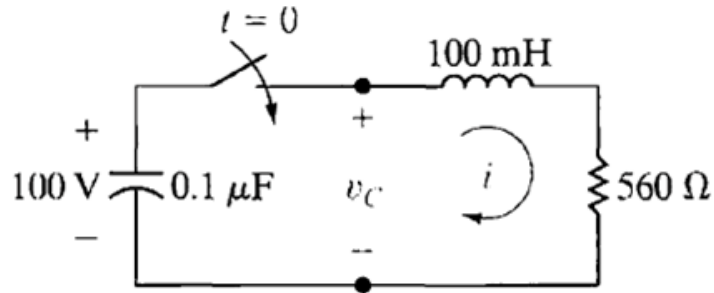


Figure 3.

4. Consider the CMOS inverter in Figure 4. Find the static power and dynamic power of this circuit. The input voltage v_{in} is a 10-MHz square wave. The on resistor of the MOS is R_{on} for both PMOS and NMOS. $R_{on} = 10 \text{ Ohms}$. The inverter state is fully settled in each half cycle (during charging and discharging the capacitor). (25%)

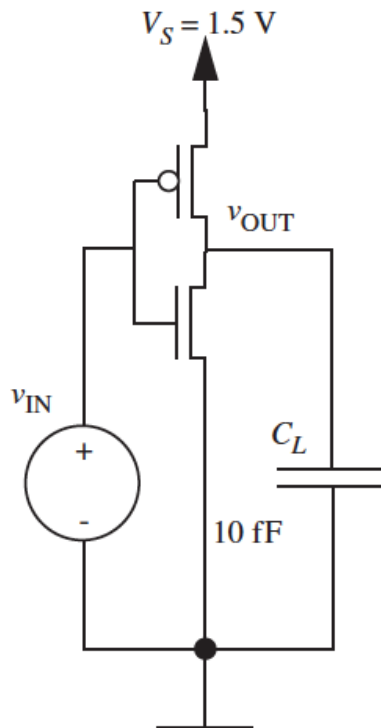


Figure 4.

5. Assume a circuit has m NMOS inverters connected in series with $m \gg 1$. Each inverter is built with an NMOS and a resistor R_L . The power supply is V_S and the on resistor of each NMOS is R_{on} . Find the static power of the inverter chain. (10%)