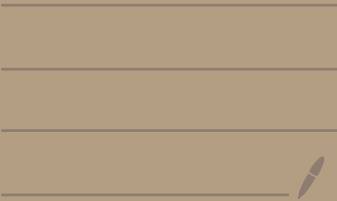





# EE2210 Electric circuits HW5 Ans.

---



$$1. (a) \frac{V_o}{V_i} = \frac{j\omega L}{R + j\omega L}, \quad |H(j\omega)| = \frac{\omega L}{\sqrt{R^2 + \omega^2 L^2}}$$

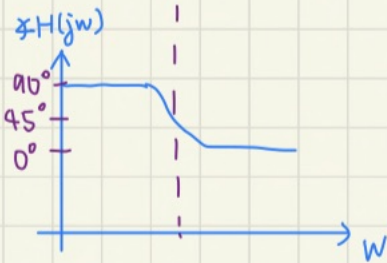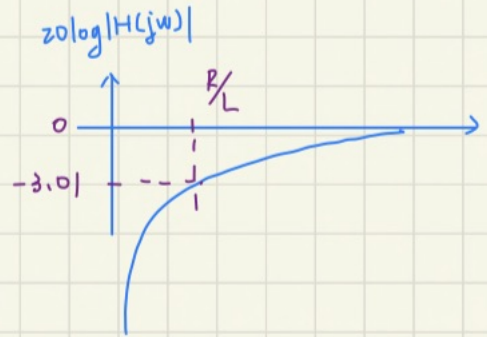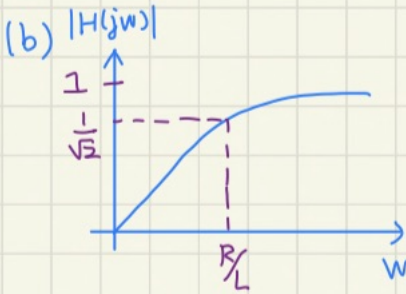
$$\angle H(j\omega) = 90^\circ - \tan^{-1}\left(\frac{\omega L}{R}\right) = \tan^{-1}\left(\frac{R}{\omega L}\right)$$



$$2. V_{in}(t) = V_i \cos(120\pi t), \quad \text{where } \omega = 120\pi$$

$$H(s) = \frac{V_o(s)}{V_{in}(s)} = \frac{1/sC}{R + sL + 1/sC} = \frac{1/j\omega \cdot 80 \cdot 10^{-6}}{50 + j\omega 0.15 + 1/j\omega \cdot 80 \cdot 10^{-6}} = -0.193 - j0.062 = 0.203 \angle 197.8^\circ$$

3.

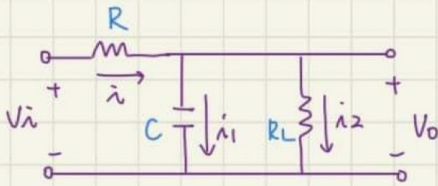

(a) Step 1: set up DE

$$i = i_1 + i_2 \Rightarrow \frac{V_i - V_o}{R} = C \frac{dV_o}{dt} + \frac{V_o}{R_L} \Rightarrow RC \cdot \frac{dV_o}{dt} + \left(1 + \frac{R}{R_L}\right) V_o = V_i$$

Step 2: Find Particular Solution

$$\because V_i = 10 \cos(100t + 45^\circ) \Rightarrow \tilde{V}_i = 10 \cdot e^{j100t} \cdot e^{j45^\circ}$$

Let  $\tilde{V}_{op} = A e^{st}$  where  $s = j \cdot 100$ ,  $\tilde{V}_{op} = A e^{j100t}$   $\uparrow$   $\wedge$  DE

$$RC \cdot A \cdot j100 \cdot e^{j100t} + A e^{j100t} + \frac{R}{R_L} A e^{j100t} = 10 e^{j100t} \cdot e^{j45^\circ}$$

$$\Rightarrow \left( RC \cdot j100 + 1 + \frac{R}{R_L} \right) \cdot A = 10 e^{j45^\circ} \quad \therefore A = \frac{10}{\left(1 + \frac{R}{R_L}\right) + j(100RC)} e^{j45^\circ}$$

$$= \frac{10}{\sqrt{\left(1 + \frac{R}{R_L}\right)^2 + (100RC)^2}} \cdot e^{j \cdot \tan^{-1}\left(-\frac{100RC}{1 + R/R_L}\right)} \cdot e^{j45^\circ} \quad \uparrow \text{  $\square$  } \tilde{V}_{op}$$

$$V_{op} = \text{Re}[\tilde{V}_{op}] = \frac{10}{\sqrt{\left(1 + \frac{R}{R_L}\right)^2 + (100RC)^2}} \cos\left[100t + 45^\circ - \tan^{-1}\left(\frac{100RC}{1 + R/R_L}\right)\right] \text{ (V)} \quad \#$$

Steady-state response

Step 3: Find Homogeneous Solution ( $V_i = 0$ )

$$\text{Let } V_{oh} = B e^{\alpha t} \quad \uparrow \text{  $\wedge$  } \text{ DE} \Rightarrow RC \cdot \alpha \cdot B e^{\alpha t} + \left(1 + \frac{R}{R_L}\right) \cdot B e^{\alpha t} = 0$$

$$\therefore \alpha = \frac{-(1 + R/R_L)}{RC} \Rightarrow V_{oh} = B \cdot e^{-\frac{(1 + R/R_L)}{RC} t}$$

Step 4: Total Solution ( $V_o(0) = V_{op}(0) + V_{oh}(0) = 0$ )

$$V_{op}(0) + B = V_1 \Rightarrow B = -V_{op}(0) + V_1 = \frac{-10}{\sqrt{\left(1 + \frac{R}{RL}\right)^2 + (100RC)^2}} \cos\left[45^\circ - \tan^{-1}\left(\frac{100RC}{1 + \frac{R}{RL}}\right)\right] + V_1$$

$$\therefore V_{oh} = \left\{ \frac{-10}{\sqrt{\left(1 + \frac{R}{RL}\right)^2 + (100RC)^2}} \cos\left[45^\circ - \tan^{-1}\left(\frac{100RC}{1 + \frac{R}{RL}}\right)\right] + V_1 \right\} e^{-\left(\frac{1 + \frac{R}{RL}}{RC}\right)t} \quad (V)$$

transient response

$$\Rightarrow V_o(t) = V_{op}(t) + V_{oh}(t)$$

$$= \frac{10}{\sqrt{\left(1 + \frac{R}{RL}\right)^2 + (100RC)^2}} \cos\left[45^\circ - \tan^{-1}\left(\frac{100RC}{1 + \frac{R}{RL}}\right)\right] \left[1 - e^{-\left(\frac{1 + \frac{R}{RL}}{RC}\right)t}\right] + V_1 e^{-\left(\frac{1 + \frac{R}{RL}}{RC}\right)t} \quad (V)$$

$$(b) \quad H(j\omega) = \frac{\left(\frac{1}{sC} \parallel RL\right)}{R + \left(\frac{1}{sC} \parallel RL\right)} \quad \text{where } \frac{1}{sC} \parallel RL = \frac{\frac{RL}{sC}}{\frac{1}{sC} + RL} = \frac{RL}{1 + sCR}$$



$$= \frac{\frac{RL}{1 + sCR}}{R + \frac{RL}{1 + sCR}} = \frac{RL}{RL + R + sCR \cdot RL} \quad \text{where } s = j\omega$$

$$= \frac{RL}{R + RL + j\omega R \cdot RL \cdot C}$$

$$(c) \quad |H(j\omega)| = \frac{RL}{\sqrt{(R + RL)^2 + (\omega RRLC)^2}}$$

$\therefore$  when  $\omega \rightarrow 0$ ,  $|H(j\omega)|$  will be maximum.

(d)  $\omega = 0$  1st  $\lambda$ ,  $|H(j\omega)| = \frac{R_L}{R + R_L}$

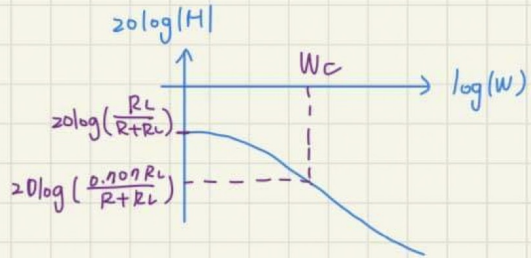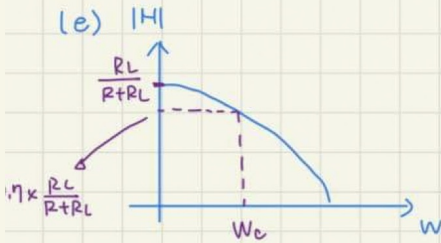

when  $\omega_c = \frac{1}{C \cdot \frac{R \cdot R_L}{R+R_L}} = \frac{R+R_L}{R \cdot R_L \cdot C}$

$|H(j\omega)| = \frac{1}{\sqrt{2}} \cdot \frac{R_L}{R+R_L}$



①:  $\log(0.1\omega_c)$

②:  $\log(\omega_c)$

③:  $\log(10\omega_c)$

4.

$$\begin{aligned}
 Z(s) &= (R+sL) \parallel (R + \frac{1}{sC}) = \frac{R^2 + \frac{R}{sC} + sLR + \frac{L}{C}}{2R + sL + \frac{1}{sC}} \\
 &= \frac{sCR^2 + R + s^2RLC + sL}{2sCR + s^2LC + 1} = \frac{(R - \omega^2RLC) + j\omega(L + CR^2)}{(1 - \omega^2LC) + j\omega(2RC)} \\
 &= \frac{[(1 - \omega^2LC) - j\omega(2RC)][(R - \omega^2RLC) + j\omega(L + CR^2)]}{(1 - \omega^2LC)^2 + \omega^2 4R^2C^2}
 \end{aligned}$$

①  $\text{Im}(z) = 0$ , for all  $\omega$

$$-2RC(R - \omega^2RLC) + (1 - \omega^2LC)(L + R^2C) = 0$$

$$-R^2C + \omega^2R^2C^2L + L - \omega^2L^2C = 0$$

$$(L - R^2C) + \omega^2LC(R^2C - L) = 0$$

$$\Rightarrow L = R^2C = 0.001 \Rightarrow C = \frac{10^{-3}}{R^2}$$

②  $\text{Re}(z) = 2000$ , for all  $\omega$

$$(1 - \omega^2LC)(R - \omega^2RLC) + \omega^2 2RC(L + R^2C)$$

$$= R - \omega^2RLC \cdot 2 + \omega^4RC^2L^2 + \omega^2 4RCL$$

$$= R + 2\omega^2RLC + \omega^4RC^2L^2$$

$$= R - 2\omega^2L\left(\frac{10^{-3}}{R}\right) + \omega^4L^2\left(\frac{10^{-6}}{R^3}\right)$$

$$(1 - \omega^2LC)^2 + \omega^2 4R^2C^2 = \omega^2 4LC + (1 + \omega^4L^2C^2 - 2\omega^2LC)$$

$$= \omega^4L^2C^2 + 2\omega^2LC + 1$$

$$2 \times 10^3 [\omega^4L^2C^2 + 2\omega^2LC + 1] = R [\omega^4L^2C^2 + 2\omega^2LC + 1]$$

$$\Rightarrow R = 2000 \Omega, C = \frac{10^{-3}}{4 \times 10^6} = 250 \text{ pF} \#$$