

Midterm: 11/7 (Mon) 10:10am-12

Lec1 - Lec 5



Electric Circuits

Quiz 1 Discussion


EE2210, Fall 2022

Jenny Yi-Chun Liu

jennyliu@gapp.nthu.edu.tw





Score Distribution

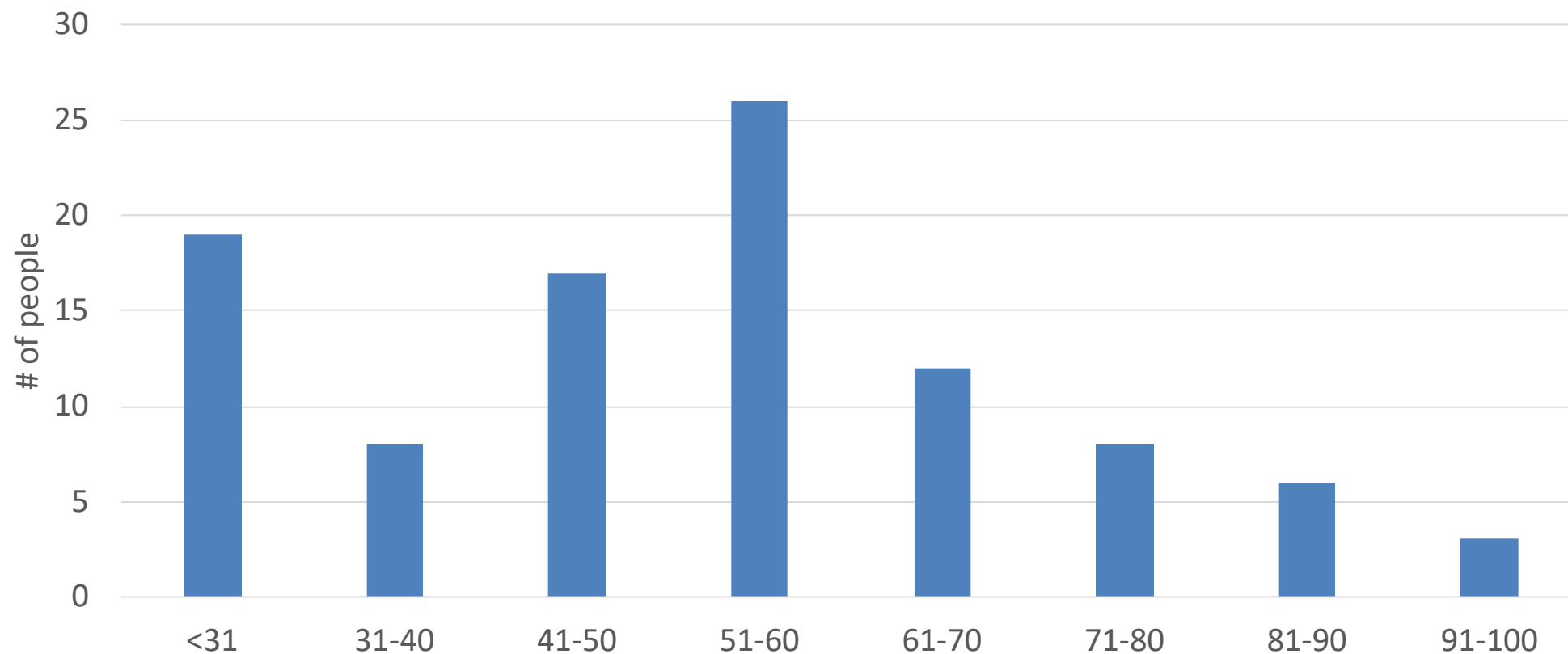

- Average: 50
- Standard deviation: 23.1



Q1

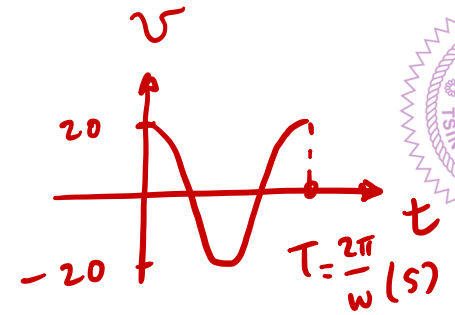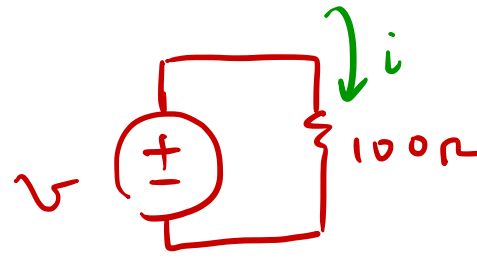

1. A sinusoidal voltage source, $v = 20 \cdot \cos(\omega t)$ (V), is connected across a 100-Ohm resistor.

$$f = \frac{\omega}{2\pi} \text{ (Hz, } 1/\text{s)}$$

1. 2. What is the current flowing through the resistor? (4%)

2. 3. What is the instantaneous power supplied by the source to the resistor? (Hint: instantaneous power is a function of time, which indicates the power at any instant of time.) (10%)

~~★~~ i - v R C L

$$1. i = \frac{v}{R} = \frac{20 \cos \omega t}{100} = \frac{1}{5} \cos \omega t \text{ A}$$

$$2. \star \underline{p(t) = v \cdot i} = 20 \cdot \cos \omega t \cdot \frac{1}{5} \cos \omega t = \underbrace{4 \cos^2 \omega t}_{> 0} = 4 \cdot \frac{1 + \cos 2\omega t}{2} = \underline{2(1 + \cos 2\omega t)} \text{ W}$$



* Energy = ?

3. 4. What is the average power supplied by this sinusoidal source? (10%)


4. 5. An ideal square wave generator is used as the voltage source instead of the sinusoidal source. If the square wave signal has a peak-to-peak value of 20 V and a zero average value, what is the average power supplied by the source? (10%)

$$3. \underline{P_{avg}} = \frac{1}{T} \int_0^T \frac{1}{2} (1 + \cos 2\omega t) dt = 2 \text{ W}$$



$$T = \frac{2\pi}{2\omega}$$


V_{square}
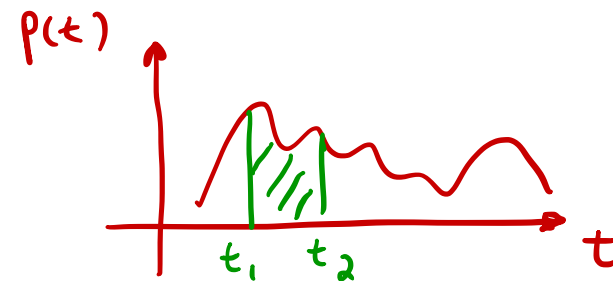
$$\underline{p(t)} = \frac{V^2}{R} = \frac{100}{100} = 1$$



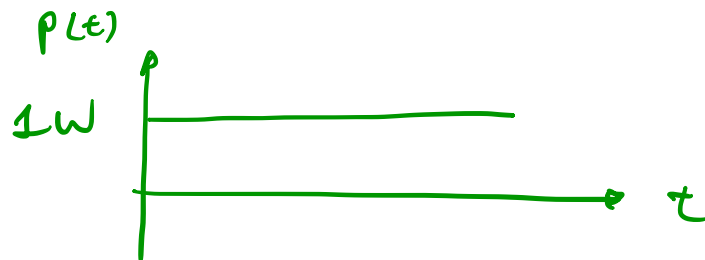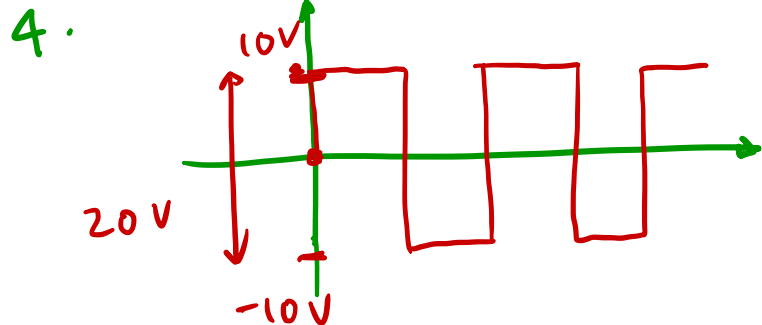
$$\frac{1}{t_2 - t_1} \int_{t_1}^{t_2} p(t) dt$$




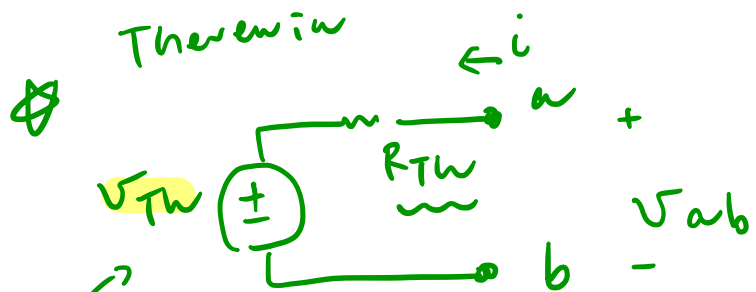

Q2

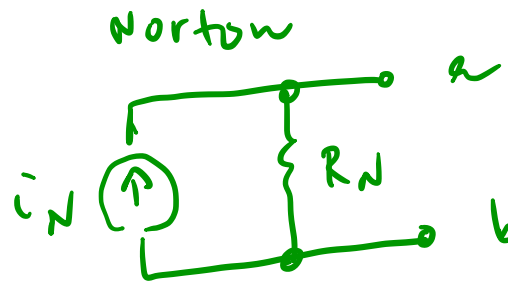

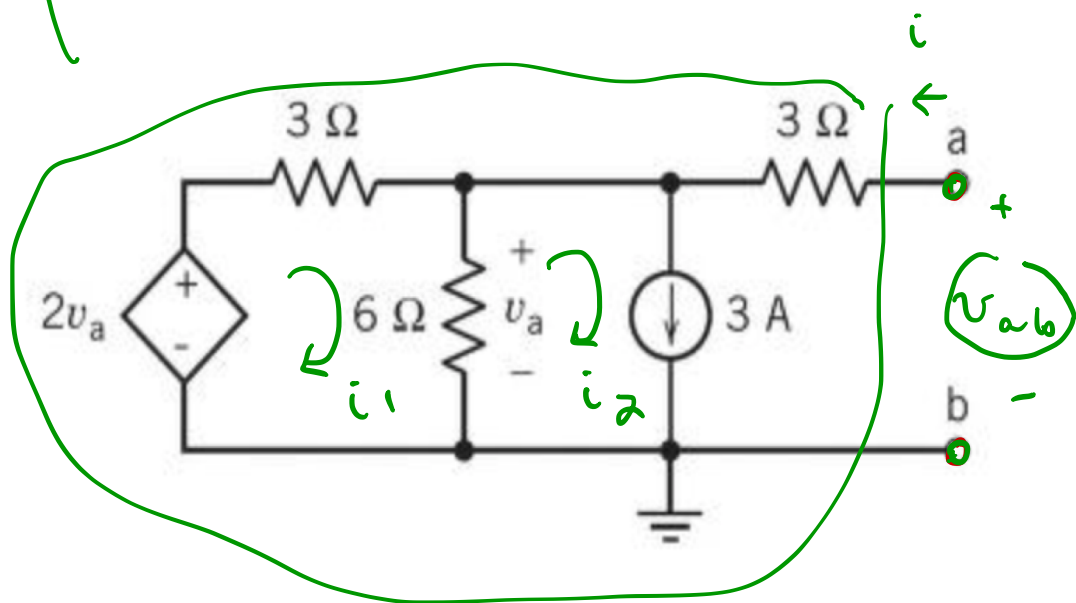- Find the Thevenin and Norton equivalent circuits of the following circuit with respect to the terminals a, b in the following figure. (16%)




Mesh analysis

$$i_2 = 3 \text{ A}$$

$$\begin{cases} \text{KVL: } 2v_a - 3i_1 - 6(i_1 - i_2) = 0 \\ v_a = 6(i_1 - i_2) \end{cases}$$

unknowns: i_1, v_a
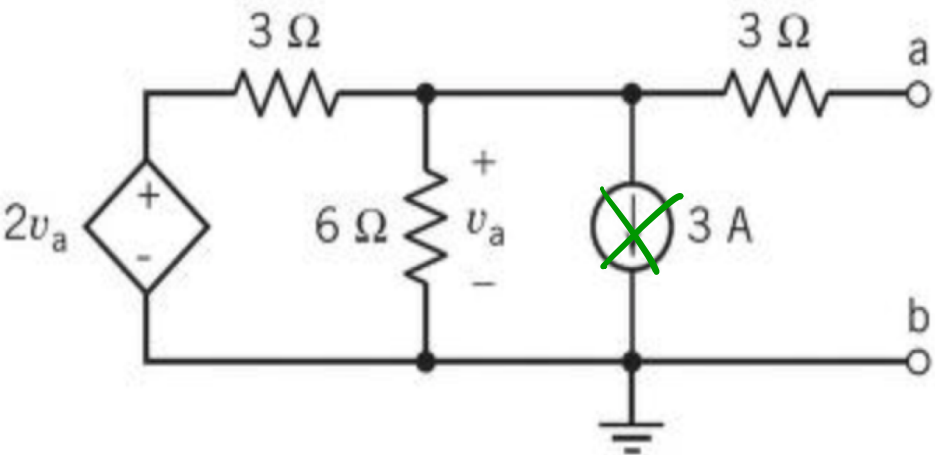
$$\Rightarrow \begin{aligned} v_a &= 18 \text{ V} = V_{Th} \\ i_1 &= 6 \text{ A} \end{aligned}$$






$$2v_a = v_a + 2v_a - 2v_{test}$$

$$v_a = 2v_{test}$$

thevenin's

Norton

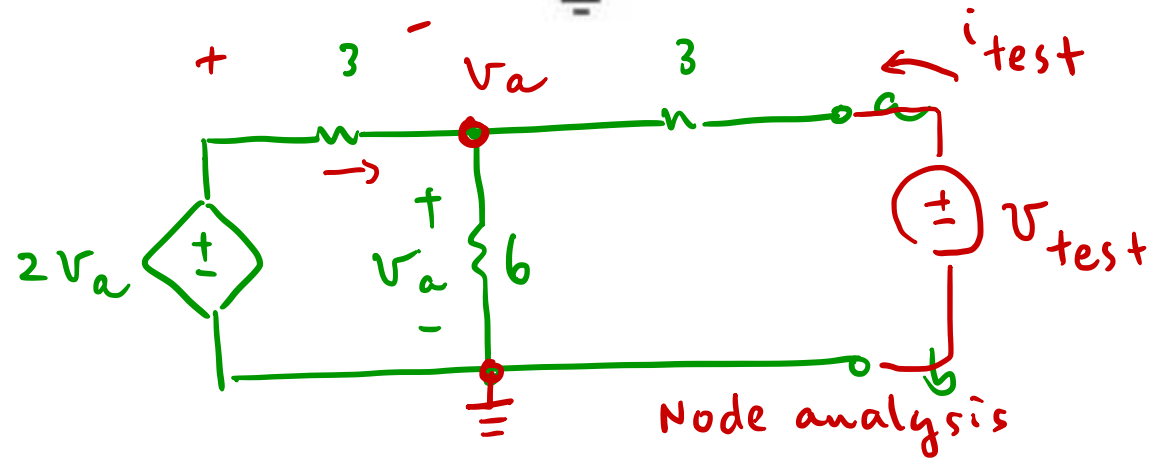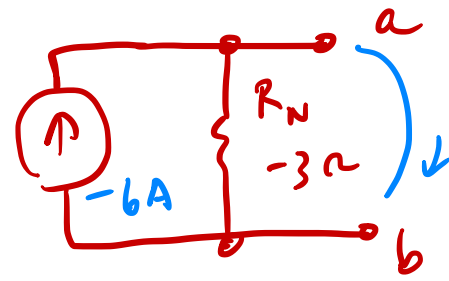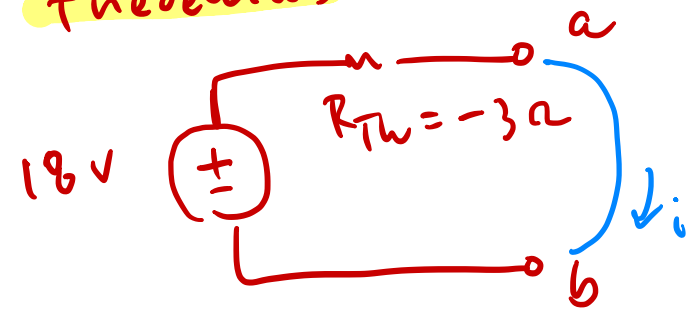

$$R_{Th} = \frac{v_{test}}{i_{test}}$$

$$= -3 \Omega$$

KCL: $\frac{v_a}{3} = \frac{v_a}{6} + \frac{v_a - v_{test}}{3}$ @ v_a

@ v_{test}

$$\frac{v_a - v_{test}}{3} = -i_{test}$$

$$\frac{2v_{test} - v_{test}}{3} = -i_{test} \Rightarrow \frac{v_{test}}{3} = -i_{test}$$



* R, C, L
series, parallel



Q3

$$R = \frac{1}{\frac{1}{10} + \frac{1}{40}} = 8 \Omega$$

- Find the node voltage potential $v(t)$ in the following figure. (12%)


Superposition

$$12 + 15 \cos(8t) \text{ V}$$

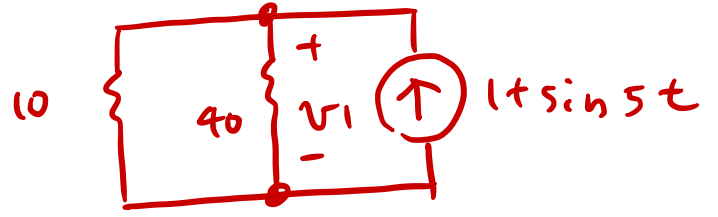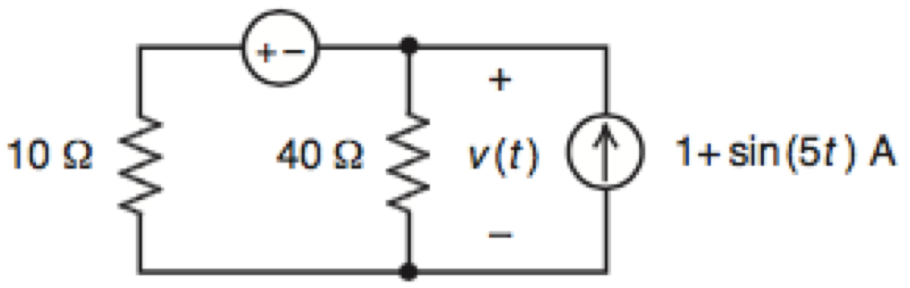


$$v_1 = (1 + \sin 5t) \cdot (10 \parallel 40) = 8 + 8 \sin 5t$$

$$12 + 15 \cos 8t$$

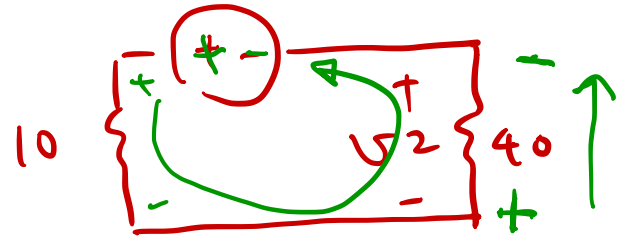
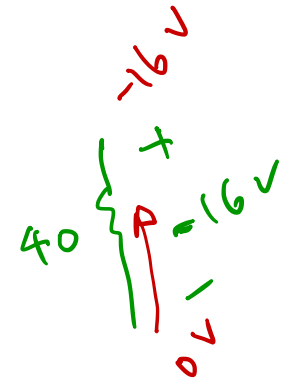
$$v_2 = - \frac{(12 + 15 \cos 8t) \cdot 40}{10 + 40} = -9.6 - 12 \cos 8t$$




$$v = v_1 + v_2 = -1.6 + 8 \sin 5t - 12 \cos 8t \text{ V}$$






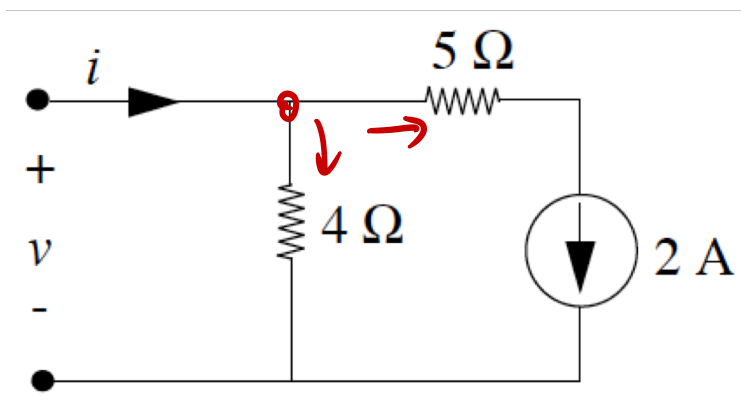Q4

- Sketch the $i - v$ characteristics for the networks in the following figures. (10%)



$$i = \frac{v}{4} + 2$$

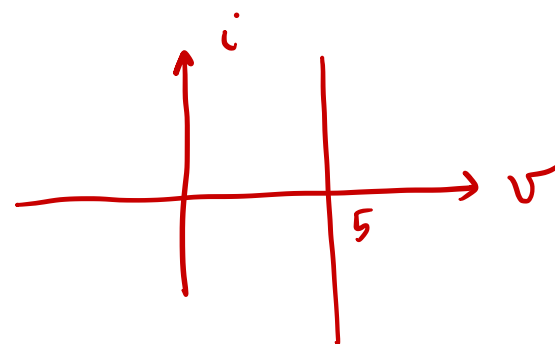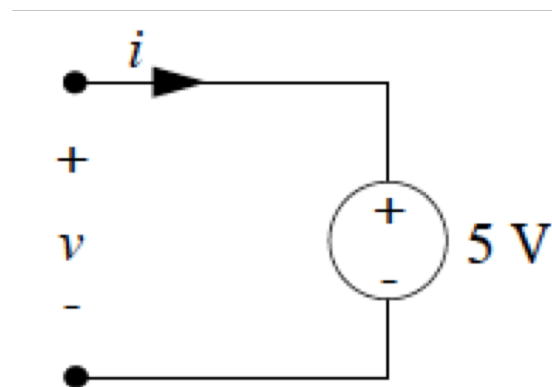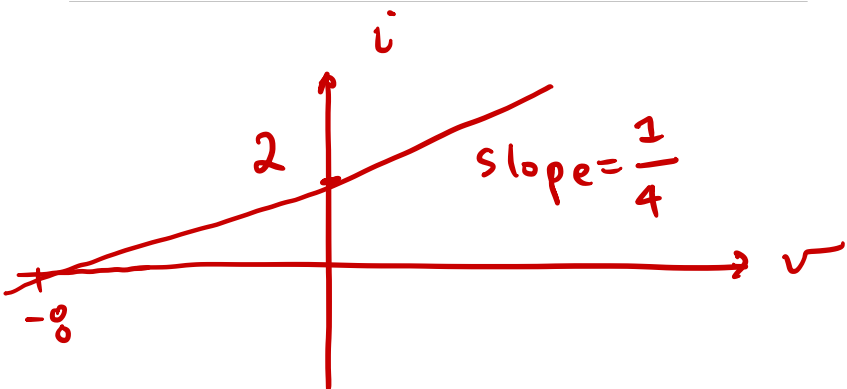


Q5




5

7

3

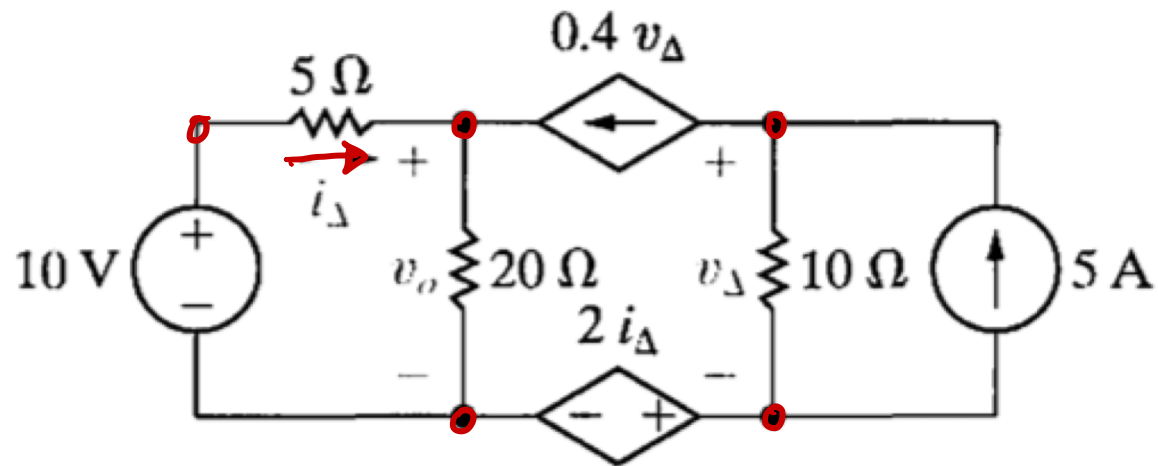- How many nodes, how many branches, and how many meshes are in the following figure? (6%)
- Find the voltage v_o in the network in the following figure using superposition. (12%)



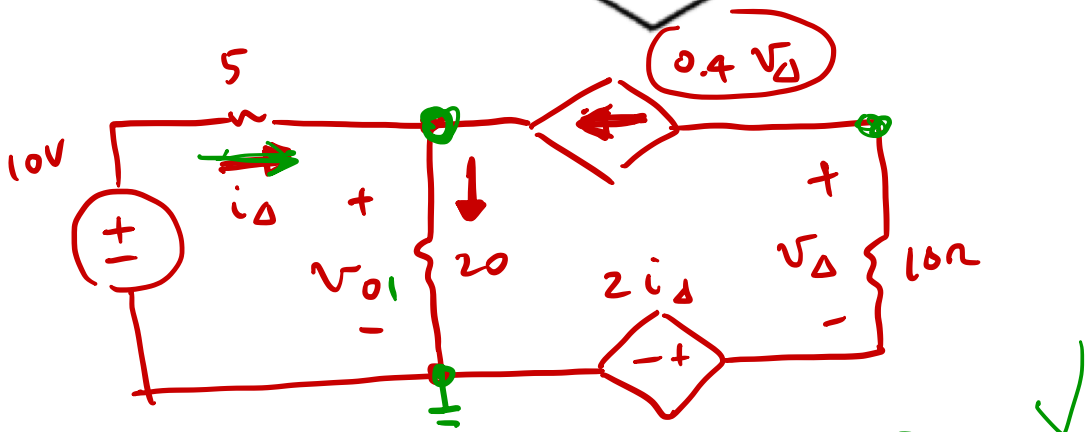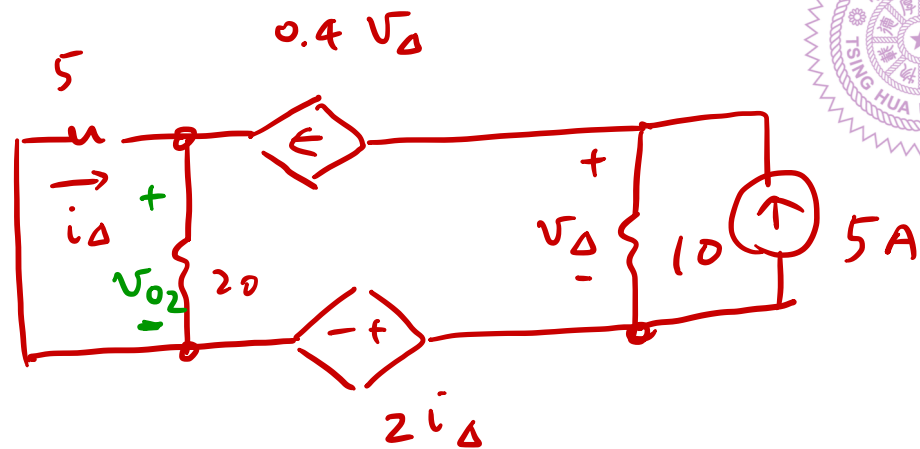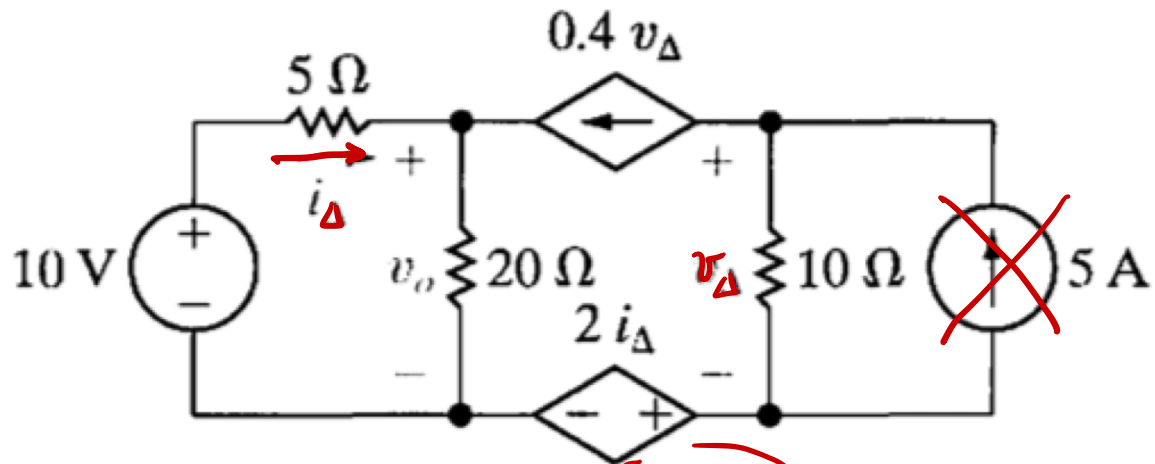

$$\frac{v_{\Delta}}{10} + 0.4 v_{\Delta} = 5 \Rightarrow v_{\Delta} = 10 \text{ V}$$

$$0.4 v_{\Delta} = \frac{v_{02}}{20} + \frac{v_{02}}{5} \Rightarrow v_{02} = 16 \text{ V}$$

$$v_0 = v_{01} + v_{02} = 8 + 16 = 24 \text{ V}$$

$$i_{\Delta} + 0.4 v_{\Delta} = \frac{v_{01}}{20} \Rightarrow i_{\Delta} = \frac{v_{01}}{20}$$

$$-\frac{v_{\Delta}}{10} = 0.4 v_{\Delta} \Rightarrow v_{\Delta} = 0 \text{ V}$$

$$i_{\Delta} = \frac{10 - v_{01}}{5} = \frac{v_{01}}{20} \Rightarrow$$


$$40 - 4 v_{01} = v_{01}$$

$$40 = 5 v_{01}, v_{01} = 8 \text{ V}$$



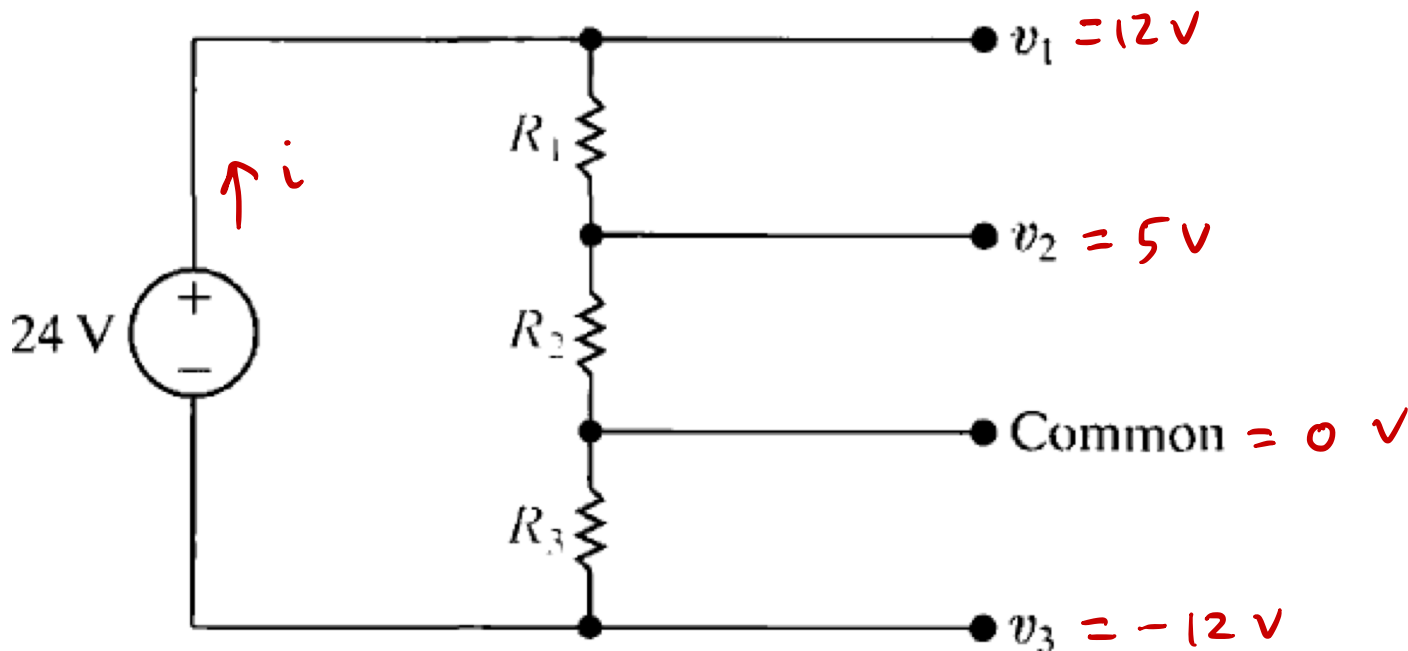Q6

- Determine the values of the resistors R_1 , R_2 , and R_3 such that $v_1 = 12$ V, $v_2 = 5$ V, $v_3 = -12$ V, and the total power dissipated by the circuit by the 24 V source is 80 W in the following figure. Assume the “Common” node is at 0 V of voltage potential. (10%)



$$P = 80 = 24 \cdot i \quad i = \frac{80}{24} \text{ A}$$

$$R_1 = \frac{12 - 5}{i} = 2.1 \Omega$$

$$R_2 = \frac{5 - 0}{i} = 1.5 \Omega$$

$$R_3 = \frac{0 - (-12)}{i} = 3.6 \Omega$$