
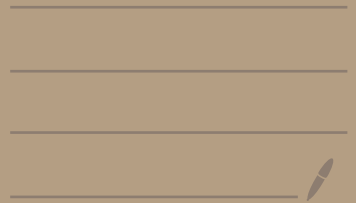


EE2210 Electric circuits Quiz 2 Ans.

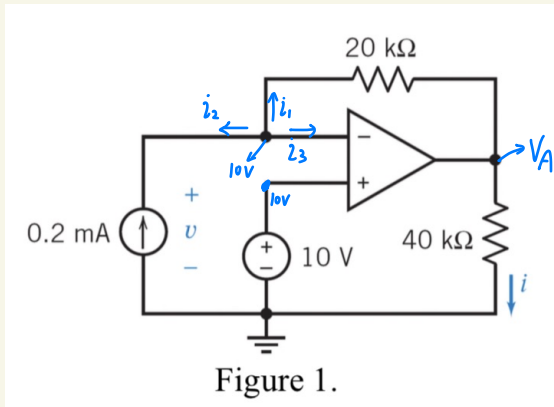

1.



The voltages at the input nodes of an ideal OP amplifier are equal!

$$\therefore V = 10 \text{ (V)} \quad \#$$

Apply KCL at inverting input node of OP


$$i_1 + i_2 + i_3 = 0$$

$$\frac{10 - V_A}{20 \times 10^3} + (-0.2 \times 10^{-3}) + 0 = 0 \quad \therefore V_A = 6 \text{ (V)}$$

$$i = \frac{V_A}{40 \text{ k}} = \frac{6}{40000} = \underline{0.15 \text{ (mA)}} \quad \#$$

$$2. V_0 = V_1 + 2V_2$$

By noninverting summing amplifier

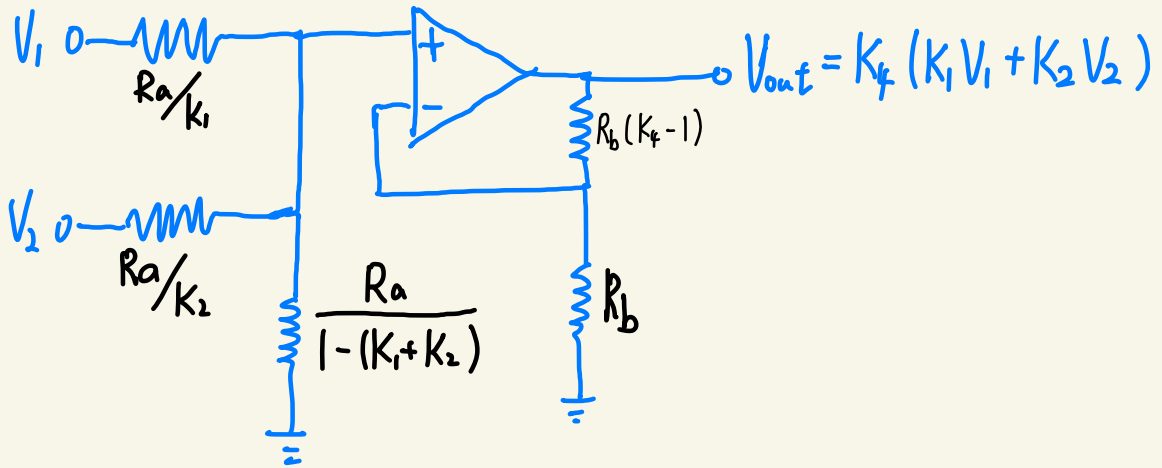

Design: $K_1 = 0.1$, $K_2 = 0.2$, $K_f = 10$,

R_a, R_b : arbitrary (Ex: $R_a = 1k\Omega$, $R_b = 1k\Omega$)

3. if V_i is step function, $V_i = 10$ when $t > 0$, $V_i = 0$ when $t < 0$

$$t \ll 0, i = 0$$

$$t \gg 0, i = 1$$

$$\tau = \frac{L}{R} = \frac{0.4}{10} = \frac{1}{25}$$

$$i(t) = 1 - e^{-25t}$$

consider V_i is ramp function

$$i(t) = \int_{-\infty}^t (1 - e^{-25t'}) dt'$$

$$= t' + \frac{1}{25} e^{-25t'} \Big|_0^t$$

$$= t + \frac{1}{25} (e^{-25t} - 1) \quad (A) \quad \text{for } t \geq 0$$

4. if V_i is step function, $V_i = u(t)$


$$t \ll 0, V_o = 0$$

$$t \gg 0, V_o = 1$$


$$\tau = RC = 10k \cdot 1\mu = 10^{-2}, \quad V_o(t) = 1 - e^{-100t}$$

consider V_i is impulse function
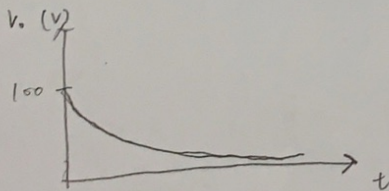
$$V_o(t) = \frac{d}{dt} (1 - e^{-100t}) = 100 e^{-100t} \quad (V) \quad \text{for } t \geq 0$$



5.

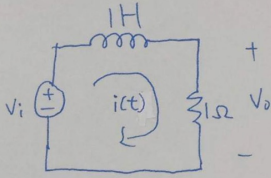

$$v_i(t) = L \frac{di(t)}{dt} + R i(t)$$

$$\Rightarrow v_i(t) = \frac{di(t)}{dt} + i(t)$$

$$\Rightarrow \frac{di(t)}{dt} + i(t) = 20, \text{ for } t \geq 5$$


$$\Rightarrow i(t) = 20 + A e^{-t}$$

$$\because i_L(0) = 0 = i(0) = 20 + A$$


$$\therefore A = -20$$

$$\Rightarrow i(t) = 20(1 - e^{-t})$$
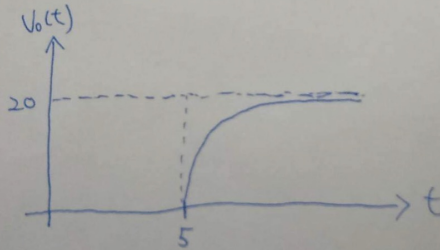
$$V_o(t) = \begin{cases} 0 \text{ V}, & \text{for } 0 \leq t < 5 \\ 20(1 - e^{-(t-5)}) \text{ V}, & \text{for } t \geq 5 \end{cases} \#$$



6.

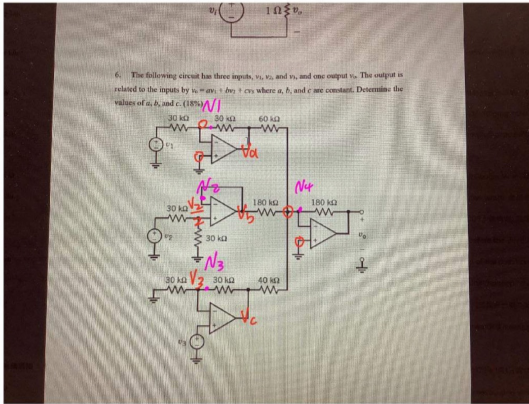

$$N_1 \left\{ \begin{aligned} 0 - V_1 + \frac{0 - V_a}{30k} + \frac{0 - V_a}{30k} &= 0 & V_a &= -V_1 \\ N_2 & V_b = \frac{V_2}{2} \\ N_3 & \frac{V_3 - 0}{30k} + \frac{V_3 - V_c}{30k} = 0 & V_c &= 2V_3 \end{aligned} \right.$$

$$N_4 \quad \frac{0 - V_o}{180k} = \frac{V_a}{60k} + \frac{V_b}{180k} + \frac{V_c}{40k}$$

$$= \frac{-V_1}{60k} + \frac{V_2/3}{180k} + \frac{2V_3}{40k}$$

$$V_o = \underbrace{3V_1}_a - \underbrace{\frac{1}{2}V_2}_b - \underbrace{9V_3}_c$$