

EE2210 Electric circuits
QUIZ3 Ans.

1.

Quiz 3

$$1. \quad 0 < t < \frac{T}{2}: \quad V_o(t) = 0 + (0 - V_s) e^{-\frac{t}{R_{on}C_L}}$$

$$E_1 = \int_0^{\frac{T}{2}} \frac{V_o^2}{R_{on}} dt \approx \frac{V_s^2 C_L}{2}$$

$$\frac{T}{2} < t < T: \quad V_o(t) = V_s + (V_s - 0) e^{-\frac{t}{R_{on}C_L}}$$

$$E_2 = \int_{\frac{T}{2}}^T \frac{(V_s - V_o)^2}{R_{on}} dt \approx \frac{V_s^2 C_L}{2}$$


$$E_{total} = E_1 + E_2 = V_s^2 C_L$$

$$\overline{P} = \frac{E_{total}}{T} = V_s^2 C_L f$$

$$\text{Static power} = 0 \text{ W}_{\#}$$

$$\text{Dynamic power} = V_s^2 \times 1f \times 100M = V_s^2 \times 10^{-7} \text{ W}_{\#}$$

2.

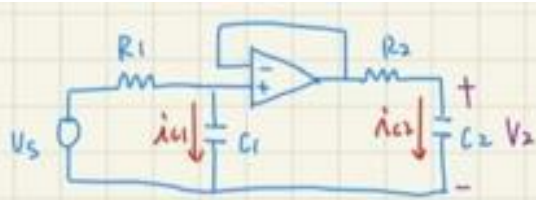

$$\frac{V_s - V_1}{R_1} - i_{c1} = 0 \quad (i_{c1} = C_1 \frac{dV_{c1}}{dt}) \Rightarrow \frac{V_1}{R_1} + C_1 \frac{dV_1}{dt} = \frac{V_s}{R_1} \quad \text{--- ①}$$

$$\frac{V_1 - V_2}{R_2} - i_{c2} = 0 \quad (i_{c2} = C_2 \frac{dV_{c2}}{dt}) \Rightarrow \frac{V_2}{R_2} + C_2 \frac{dV_2}{dt} = \frac{V_s}{R_2}$$

$$\Rightarrow V_1(t) = R_2 C_2 \frac{dV_2}{dt} + V_2 \quad \text{--- ②}$$

将②代入①

$$\frac{R_2 C_2}{R_1} \frac{dV_2}{dt} + \frac{V_2}{R_1} + C_1 \frac{d}{dt} \left[R_2 C_2 \frac{dV_2}{dt} + V_2 \right] = \frac{V_s}{R_1}$$


$$\frac{R_2 C_2}{R_1} V_2' + \frac{1}{R_1} V_2 + R_2 C_1 C_2 V_2'' + C_1 V_2' = \frac{V_s}{R_1} \quad (\text{同乘 } \frac{1}{R_2 C_1 C_2})$$

$$V_2'' + \left(\frac{1}{R_1 C_1} + \frac{1}{R_2 C_2} \right) V_2' + \frac{1}{R_1 R_2 C_1 C_2} V_2 = \frac{1}{R_1 R_2 C_1 C_2} V_s \quad \#$$

3.

Quiz 3.

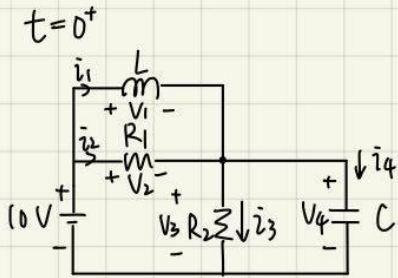3. $V_4(0^+) = 4 \text{ V}$ \Rightarrow capacitor : voltage continuous
 $i_1(0^+) = 2 \text{ A}$ \Rightarrow inductor : current continuous




$$i_2(0^+) = \frac{10 - 4}{R_1} = 3 \text{ A}$$

$$i_3(0^+) = \frac{4}{R_2} = 4 \text{ A}$$

$$i_4(0^+) = i_1 + i_2 - i_3 = 1 \text{ A}$$

$$V_1(0^+) = 10 - 4 = 6 \text{ V} = V_2(0^+)$$
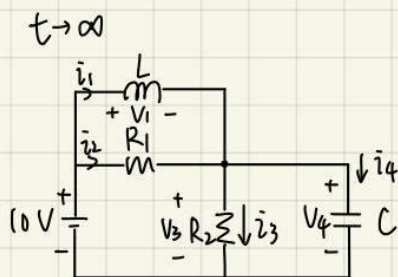
$$V_3(0^+) = V_4(0^+) = 4 \text{ V} \quad \times$$



$$V_4(\infty) = 10 \text{ V} = V_3(\infty)$$

$$V_1(\infty) = 0 \text{ V} = V_2(\infty)$$

$$i_2(\infty) = \frac{10 - 10}{R_1} = 0 \text{ A}$$

$$i_3(\infty) = \frac{10}{R_2} = 10 \text{ A}$$

$$i_4(\infty) = 0 \text{ A}$$

$$i_1(\infty) = i_3 + i_4 - i_2 = 10 \text{ A} \quad \times$$

4.

$$\dot{i}_R + \dot{i}_L + \dot{i}_C = 0$$

$$\frac{V}{R} + \frac{1}{L} \int_0^t v dt + i_L(0) + C \frac{dV}{dt} = 0 \Rightarrow C \frac{d^2V}{dt^2} + \frac{1}{R} \frac{dV}{dt} + \frac{1}{L} V = 0$$

$$\Rightarrow \frac{d^2V}{dt^2} + \frac{1}{RC} \frac{dV}{dt} + \frac{1}{LC} V = 0 \Rightarrow s^2 + 25000s + 10^8 = 0 \Rightarrow s = -20000 / -5000$$

$$\therefore v(t) = A_1 e^{-20000t} + A_2 e^{-5000t}, \quad v(0) = A_1 + A_2 = 15 \quad \text{--- (1)}$$

$$-20000 A_1 - 5000 A_2 = -375000 + 225000 = -150000 \Rightarrow A_1 + 0.25 A_2 = 7.5 \quad \text{--- (2)}$$

$$\text{solve (1), (2)} \Rightarrow A_1 = 5, \quad A_2 = 10, \quad v(t) = 5e^{-20000t} + 10e^{-5000t}$$

5.

$$\begin{aligned} t > 0 \\ \bar{i}_L + 0.2 \frac{dv}{dt} &= 4 \\ (v-1) \frac{di_L}{dt} - 6 \bar{i}_L &= 0 \end{aligned} \quad \left. \vphantom{\begin{aligned} \bar{i}_L + 0.2 \frac{dv}{dt} &= 4 \\ (v-1) \frac{di_L}{dt} - 6 \bar{i}_L &= 0 \end{aligned}} \right\} \frac{d^2v}{dt^2} + 6 \frac{dv}{dt} + 5v = 120$$

$$s^2 + 6s + 5 = 0 \rightarrow v(t) = A_1 e^{-t} + A_2 e^{-5t} + B$$

穩態 $\rightarrow B = 24$

$$\begin{aligned} v(0) &= A_1 + A_2 + 24 = 0 \\ \frac{dv(0)}{dt} &= -A_1 - 5A_2 = 20 \end{aligned} \quad \left. \vphantom{\begin{aligned} v(0) &= A_1 + A_2 + 24 = 0 \\ \frac{dv(0)}{dt} &= -A_1 - 5A_2 = 20 \end{aligned}} \right\} \begin{aligned} A_1 &= -25, A_2 = 1 \\ v(t) &= -25e^{-t} + e^{-5t} + 24 \quad (V) \end{aligned}$$

6.

Quiz 3

b. KVL:

$$\frac{d^2 V_C}{dt^2} + \frac{R}{L} \frac{dV_C}{dt} + \frac{V_C}{LC} = \frac{48}{LC}$$

$$\Rightarrow V_{C,p} = 48$$

$$V_{C,h} = A_1 e^{s_1 t} + A_2 e^{s_2 t}$$

$$\text{characteristic eqn: } s^2 + 2800s + 2.5 \times 10^7 = 0$$

$$\rightarrow s = -1400 \pm 4800j.$$

$$V_C = 48 + e^{-1400t} (K_1 \cos(4800t) + K_2 \sin(4800t))$$

$$K_1 = A_1 + A_2 \quad \text{and} \quad K_2 = jA_1 - jA_2$$

$$\begin{cases} V_C(0) = 48 + K_1 = 0 \\ \dot{V}_C(0) = C \cdot (-1400K_1 + 4800K_2) = 0 \end{cases} \Rightarrow \begin{cases} K_1 = -48 \\ K_2 = -14 \end{cases}$$

$$\Rightarrow V_C(t) = 48 + e^{-1400t} [-48 \cos(4800t) - 14 \sin(4800t)] \text{ (V)}$$

for $t \geq 0$

#