



Electric Circuits

Lecture 10 Damped Second-Order Systems

EE2210, Fall 2022

Jenny Yi-Chun Liu

jennyliu@gapp.nthu.edu.tw



Lecture Outline

- Chapter 9 in the textbook



Review

o 2nd-order Circuits with L, C

1) Write 2nd-order differential equation

2) Particular solution (constant)

3) Homogeneous solution (Ae^{st}), s_1 and s_2


$$\Rightarrow A_1 e^{s_1 t} + A_2 e^{s_2 t}$$

4) Total = 2) + 3) use initial conditions $\Rightarrow A_1, A_2$



Review

Example

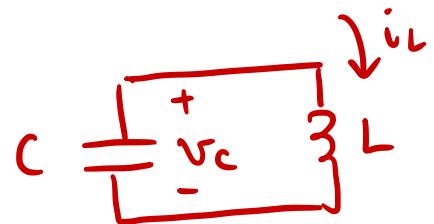

$$C = 1 \mu F, \quad L = 100 \mu H$$

$$i_L(0) = 0, \quad V_C(0) = 1 V.$$

Find i_L and V_C .

$$\omega_0 = \frac{1}{\sqrt{L \cdot C}} = \frac{1}{\sqrt{10^{-4} \cdot 10^{-6}}} = 10^5 \text{ rad/s}$$

$$f_0 = \frac{\omega_0}{2\pi} = \frac{10^5}{2\pi} \text{ Hz}, \quad T_0 = \frac{1}{f_0} = \frac{2\pi}{10^5} \text{ s}.$$

$$V_C(t) = V_C(0) \cdot \cos \omega_0 t = 1 \cdot \cos 10^5 t \text{ V}$$

$$i_L(t) = -i_C(t) = -C \cdot \frac{dV_C}{dt} = 0.1 \cdot \sin 10^5 t \text{ A}$$

Review




Review



R

LC

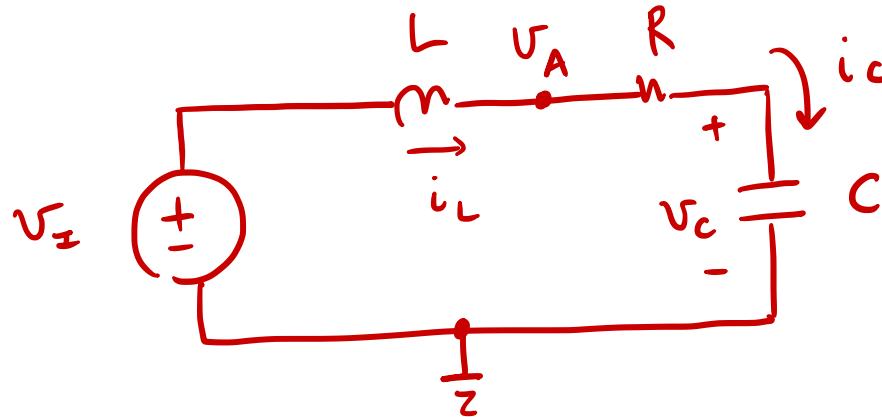Let's Analyze the RLC Network (Damped Oscillator)



Variables : V_C , i_L

$$\text{KCL } @ V_C : \frac{V_A - V_C}{R} = i_C = C \frac{dV_C}{dt} \quad ①$$


$$@ V_A : \frac{1}{L} \int_{-\infty}^t (V_I - V_A) dt = \frac{V_A - V_C}{R} \quad ②$$



Setup the Differential Equation

- Need to get rid of v_A .

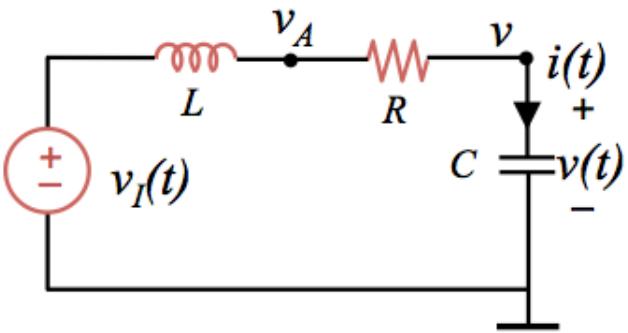From ①, $v_A = RC \cdot \frac{dv_C}{dt} + v_C \quad (3)$



Plug ③ into ②, $\frac{1}{L} \int_{-\infty}^t (v_I - RC \frac{dv_C}{dt} - v_C) dt = C \frac{dv_C}{dt}$


$$\Rightarrow \frac{1}{L} \left(v_I - RC \frac{dv_C}{dt} - v_C \right) = C \frac{d^2 v_C}{dt^2}$$

with only LC (leca)

$$\Rightarrow \frac{d^2 v_C}{dt^2} + \frac{R}{L} \frac{dv_C}{dt} + \frac{1}{LC} v_C = \frac{1}{LC} v_I$$

$$\frac{d^2 v_C}{dt^2} + \frac{1}{LC} v_C = \frac{1}{LC} v_I$$

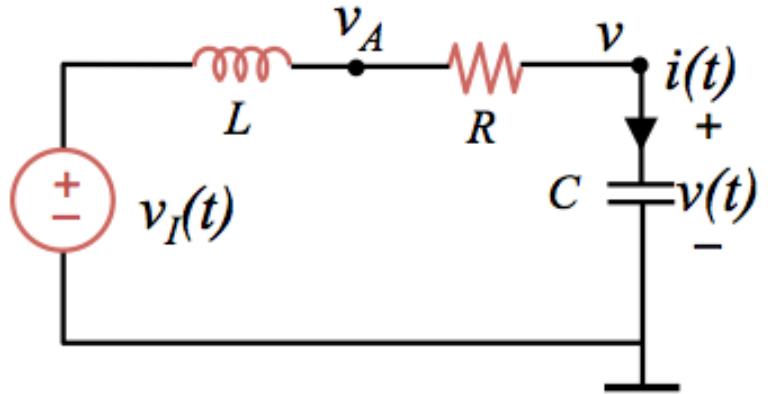Setup the Differential Equation Differently



$$\text{KVL: } v_I = v_C + v_R + v_L = v_C + R \cdot i + L \cdot \frac{di}{dt} \quad ①$$

$$i = C \frac{dv_C}{dt} \quad ②$$

$$\text{use } ② \text{ into } ① \Rightarrow v_I = LC \frac{d^2v_C}{dt^2} + RC \frac{dv_C}{dt} + v_C$$



Method of Particular and Homogeneous Solutions

□ Four-step procedure

1. Find the particular solution $v_P(t)$

2. Find the homogeneous solution $v_H(t)$ Ae^{st} , s_1, s_2

▪ Four-step procedure

$$A_1 e^{s_1 t} + A_2 e^{s_2 t}$$

3. The total solution is the sum of the particular solution and homogeneous solution.

4. Use initial conditions to solve for the remaining constraints.

$$(A_1, A_2)$$

$$\frac{d^2v}{dt^2} + \frac{R}{L} \frac{dv}{dt} + \frac{1}{LC} v = \frac{1}{LC} v_I$$



Let's Solve

$$\frac{d^2v}{dt^2} + \frac{R}{L} \frac{dv}{dt} + \frac{1}{LC} v = \frac{1}{LC} v_I$$

- Given $v_I(t) = V_I \cdot u(t)$, $v(t=0) = 0, i(t=0) = 0$. Find $v(t)$ for $t > 0$.

$$v(t=0) = 0, i(t=0) = 0$$



1. Particular Solution

$$\frac{d^2v}{dt^2} + \frac{R}{L} \frac{dv}{dt} + \frac{1}{LC} v = \frac{1}{LC} v_I$$

Assume $v_{cp} = K$ ↑

$$\Rightarrow \frac{1}{LC} \cdot K = \frac{1}{LC} \cdot V_I$$

$$\Rightarrow v_{cp} = V_I$$



2. Homogeneous Solution

$$\frac{d^2v(t)}{dt^2} + \frac{R}{L} \frac{dv(t)}{dt} + \frac{1}{LC} v(t) = 0$$

① Assume $V_{CH} = Ae^{st}$ ↑

② $A \cdot s^2 \cdot e^{st} + \frac{R}{L} \cdot A \cdot s \cdot e^{st} + \frac{1}{LC} \cdot A e^{st} = 0$

$$\Rightarrow Ae^{st} \left(s^2 + \frac{R}{L}s + \frac{1}{LC} \right) = 0$$

$$\Rightarrow s^2 + \frac{R}{L}s + \frac{1}{LC} = 0 \quad \text{characteristic equation}$$



2. Homogeneous Solution

$$\frac{d^2v(t)}{dt^2} + \frac{R}{L} \frac{dv(t)}{dt} + \frac{1}{LC} v(t) = 0$$

$$s^2 + \frac{R}{L}s + \frac{1}{LC} = 0$$

Assume $\omega_0 = \frac{1}{\sqrt{LC}}$, $\alpha = \frac{R}{2L}$, rewrite $s^2 + 2\alpha s + \omega_0^2 = 0$

③ Solve the characteristic equation, two roots s_1 and s_2 .

$$s_1 = -\alpha + \sqrt{\alpha^2 - \omega_0^2}$$

$$s_2 = -\alpha - \sqrt{\alpha^2 - \omega_0^2}$$

$$④ V_{CH} = A_1 e^{s_1 t} + A_2 e^{s_2 t} = A_1 e^{(-\alpha + \sqrt{\alpha^2 - \omega_0^2})t} + A_2 e^{(-\alpha - \sqrt{\alpha^2 - \omega_0^2})t}$$



3. Total Solution

$$V_C = V_I + A_1 e^{(-\alpha + \sqrt{\alpha^2 - \omega_0^2})t} + A_2 e^{(-\alpha - \sqrt{\alpha^2 - \omega_0^2})t}$$

4. Find unknowns from initial conditions

$$V_C(t=0) = 0 = V_I + A_1 + A_2$$

$$i(t=0) = 0 = C \cdot \frac{dV_C}{dt}(t=0) = C \cdot A_1 \cdot (-\alpha + \sqrt{\alpha^2 - \omega_0^2}) + C \cdot A_2 \cdot (-\alpha - \sqrt{\alpha^2 - \omega_0^2})$$

$$\Rightarrow A_1, A_2$$



Let's Stare at the Total Solution for a While Longer

$$v(t) = V_I + A_1 e^{-\alpha t} e^{\left(\sqrt{\alpha^2 - \omega_0^2}\right)t} + A_2 e^{-\alpha t} e^{\left(-\sqrt{\alpha^2 - \omega_0^2}\right)t}$$


- There are 3 possible cases:

1) $\alpha > \omega_0$, s_1, s_2 : real, overdamped

2) $\alpha < \omega_0$, s_1, s_2 : complex conjugate $(-\alpha + j\beta, -\alpha - j\beta)$, under-damped

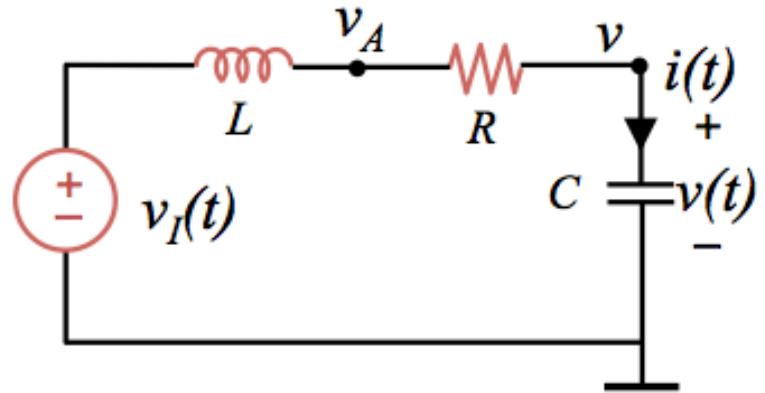3) $\alpha = \omega_0$, $s_1 = s_2$, critically damped

Over-Damped ($\alpha > \omega_0$, $\frac{R}{2L} > \frac{1}{\sqrt{LC}} \Rightarrow R > 2\sqrt{\frac{L}{C}}$)



$$\underline{v_c(t)} = V_I + A_1 e^{s_1 t} + A_2 e^{s_2 t} \quad \checkmark$$

$$s_1 = -\alpha + \sqrt{\alpha^2 - \omega_0^2} \quad \checkmark$$

$$s_2 = -\alpha - \sqrt{\alpha^2 - \omega_0^2} \quad \checkmark$$

Considering $\alpha \gg \omega_0$

$$v_c(t) = V_I + A_1 e^{-\alpha_1 t} = V_I + A_1 e^{-\frac{\omega_0^2}{2\alpha} t}, \quad i = C \frac{d v_c}{d t} = C \cdot A_1 \cdot \left(\frac{-1}{2} \frac{\omega_0^2}{\alpha} \right) \cdot e^{-\frac{\omega_0^2}{2\alpha} t}$$

- $\overset{\omega_0 > \alpha}{\text{use Taylor series}}, \sqrt{1-x^2} = 1 - \frac{1}{2}x^2 - \frac{1}{8}x^4 + \dots$ when $|x^2| \leq 1$

$$\begin{aligned}\alpha_1 = -s_1 &= \alpha - \sqrt{\alpha^2 - \omega_0^2} = \alpha \cdot \left(1 - \sqrt{1 - \left(\frac{\omega_0}{\alpha}\right)^2} \right) \\ &\approx \alpha \cdot \left(1 - 1 + \frac{1}{2} \left(\frac{\omega_0}{\alpha}\right)^2 + \frac{1}{8} \left(\frac{\omega_0}{\alpha}\right)^4 - \dots \right) \\ &\approx \alpha \cdot \frac{1}{2} \left(\frac{\omega_0}{\alpha}\right)^2 = \underbrace{\frac{\omega_0^2}{2\alpha}}\end{aligned}$$

$$\begin{aligned}\alpha_2 = -s_2 &= \alpha + \sqrt{\alpha^2 - \omega_0^2} = \alpha \left(1 + \sqrt{1 - \left(\frac{\omega_0}{\alpha}\right)^2} \right) \\ &\approx \alpha \left(1 + 1 - \frac{1}{2} \left(\frac{\omega_0}{\alpha}\right)^2 - \frac{1}{8} \left(\frac{\omega_0}{\alpha}\right)^4 + \dots \right) \\ &\approx \alpha \left(2 - \frac{1}{2} \left(\frac{\omega_0}{\alpha}\right)^2 \right) \approx \underbrace{\alpha \cdot 2}\end{aligned}$$

$$\alpha_2 > \alpha_1, \quad V_{CH} = \underbrace{A_1 e^{-\alpha_1 t}} + \underbrace{A_2 e^{-\alpha_2 t}} \approx \underbrace{A_1 e^{-\alpha_1 t}}$$