

★ Quiz 3: 12/26 (Wed) 8 am - 9:50 am

Under-Damped

$\alpha < \omega_0$ ($R < 2\sqrt{\frac{L}{C}}$), s_1, s_2 : complex conjugate



$$V_C(t) = V_I + A_1 e^{-\alpha t} e^{j\sqrt{\omega_0^2 - \alpha^2} t} + A_2 e^{-\alpha t} e^{-j\sqrt{\omega_0^2 - \alpha^2} t}$$

Assume $\omega_d = \sqrt{\omega_0^2 - \alpha^2}$, ω_d : natural frequency, $\omega_d \leq \omega_0$

$$V_C(t) = V_I + A_1 e^{-\alpha t} e^{j\omega_d t} + A_2 e^{-\alpha t} e^{-j\omega_d t}$$


use $k_1 = A_1 + A_2$
 $k_2 = jA_1 - jA_2$

$$= V_I + A_1 e^{-\alpha t} (\cos \omega_d t + j \sin \omega_d t) + A_2 e^{-\alpha t} (\cos \omega_d t - j \sin \omega_d t)$$
$$= V_I + e^{-\alpha t} (k_1 \cos \omega_d t + k_2 \sin \omega_d t)$$

exp.
decay

sinusoids, frequency $\omega_d/2\pi$ (Hz)

Under-damped

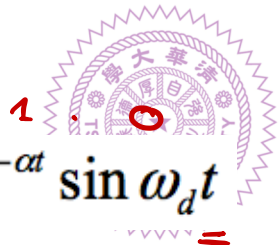

$$v_c(t) = \underline{V_I} + \underline{K_1} e^{-\alpha t} \cos \omega_d t + \underline{K_2} e^{-\alpha t} \sin \omega_d t$$

□ Furthermore, $v(0) = 0$ and $i(0) = 0$

$$1) v_c(0) = V_I + K_1 + K_2 \cdot 0 = 0 \quad \Rightarrow \quad K_1 = -V_I$$

$$2) i(0) = 0 \quad \Rightarrow \quad C \cdot \frac{dV_c(t=0)}{dt} = C \cdot K_1 \cdot (-\alpha) + C \cdot K_2 \cdot \omega_d = 0$$


$$\Rightarrow K_2 = -\frac{\alpha}{\omega_d} \cdot V_I$$

$$\text{Total solution } v_c(t) = V_I - V_I e^{-\alpha t} \cos \omega_d t - \frac{\alpha}{\omega_d} V_I \cdot e^{-\alpha t} \sin \omega_d t$$

Under-damped


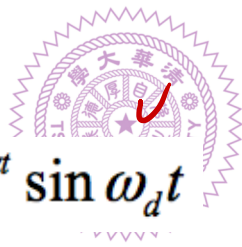
$$v(t) = V_I + K_1 e^{-\alpha t} \cos \omega_d t + K_2 e^{-\alpha t} \sin \omega_d t$$



- Scaled sum of sines (of the same frequency) are also sines (Appendix B.7).

Use $a_1 \cos \omega_d t + a_2 \sin \omega_d t$

$$= \sqrt{a_1^2 + a_2^2} \cos\left(\omega_d t - \tan^{-1} \frac{a_2}{a_1}\right) y(t)$$


$$v_c(t) = V_I + e^{-\alpha t} \cdot V_I \cdot \frac{\omega_0}{\omega_d}$$

$$\cos\left(\omega_d t - \tan^{-1} \frac{\alpha}{\omega_d}\right)$$

α : damping factor

Q : Q factor, quality factor
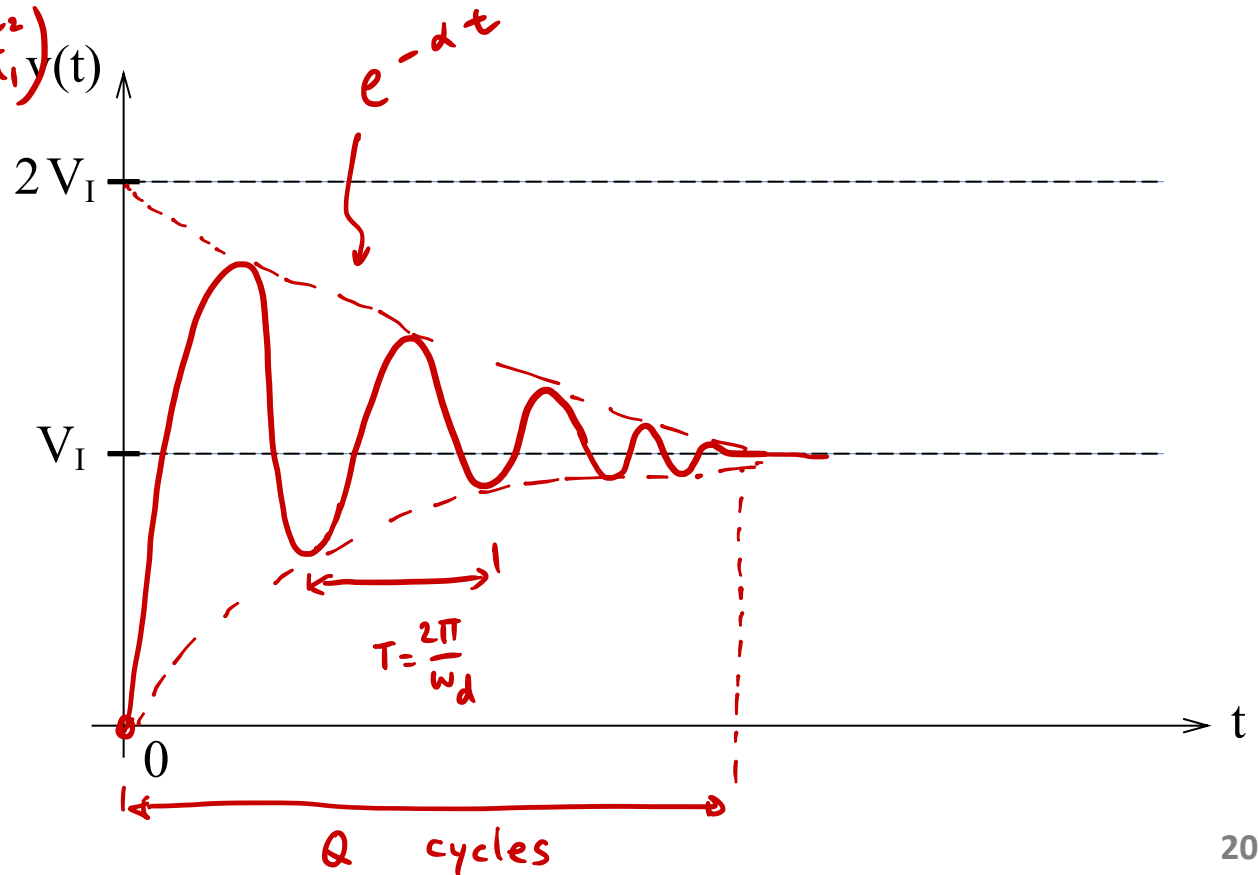
$$Q = \frac{\omega_0}{2\alpha} = \frac{1}{R} \sqrt{\frac{L}{C}}$$




Critically-Damped

$$\alpha = \omega_0, \quad s_1 = s_2 = -\alpha$$






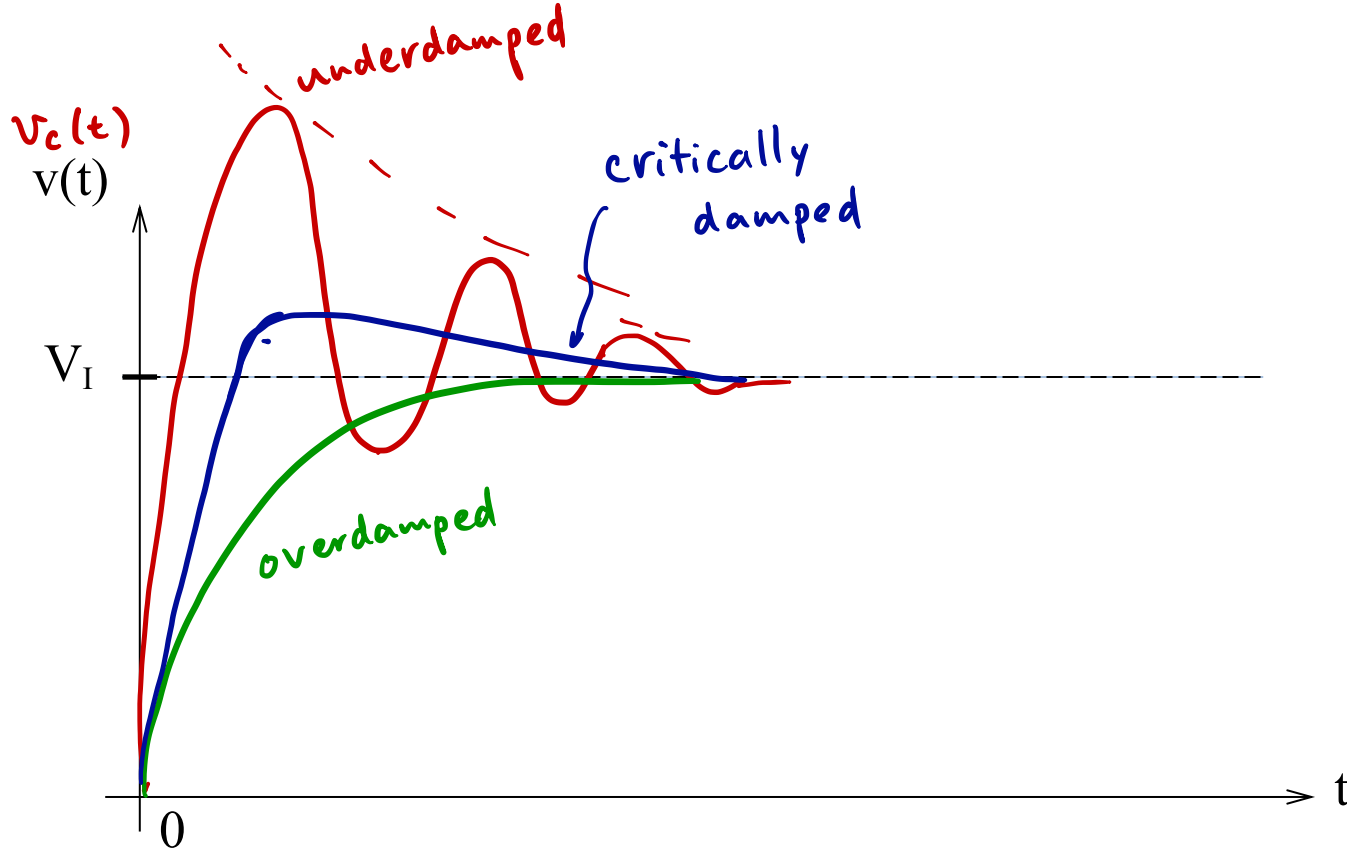□ Total solution will be in the form of $v_c = v_I + A_1 e^{-\alpha t} + A_2 t e^{-\alpha t}$



Remember This?

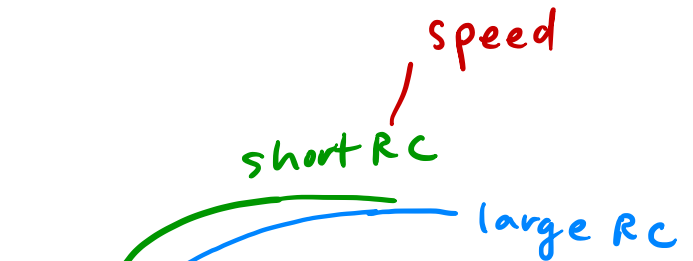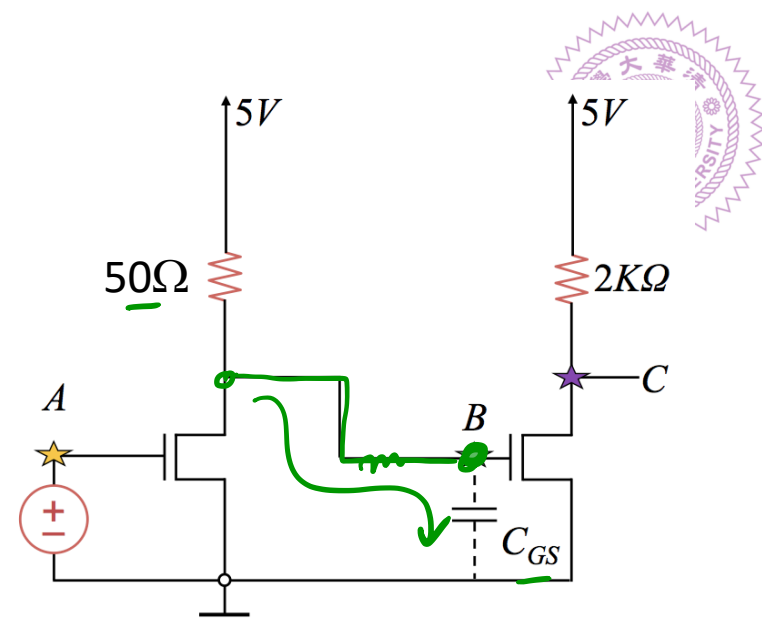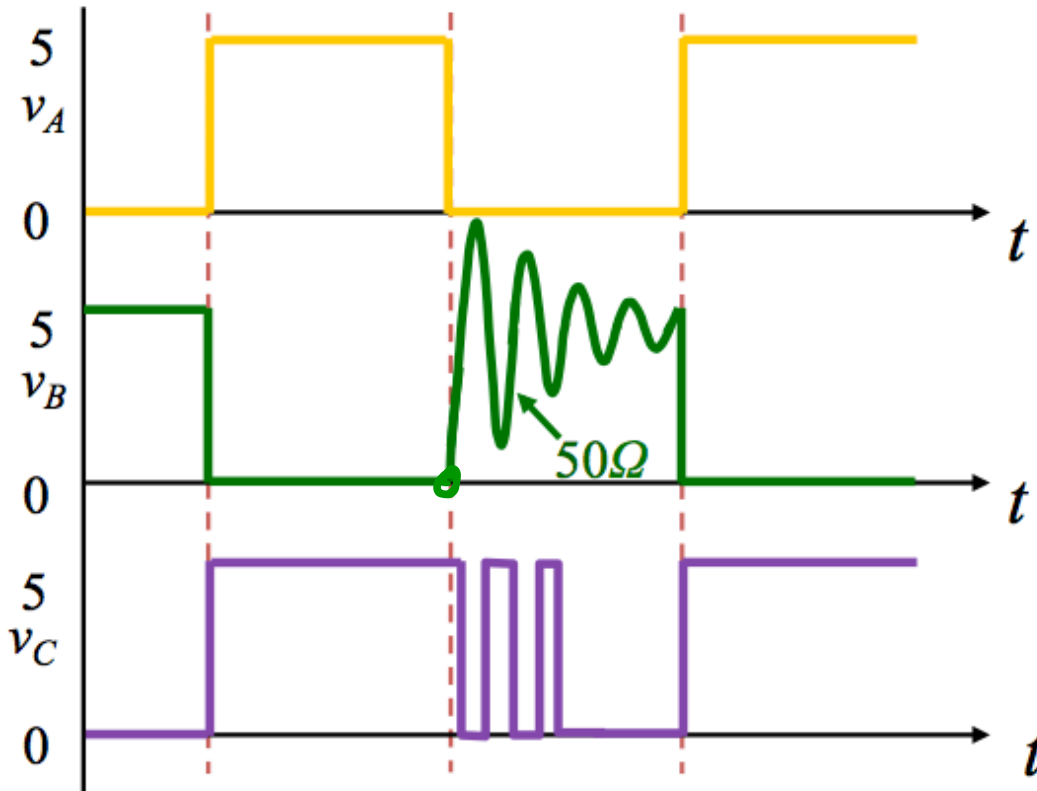- With 50Ω load resistor, hoping to speed up the pull up.



Speed \longleftrightarrow stability
correctness

Particular solution

Excitation

$$k$$

$$k \cdot t$$

$$k \cdot t^2$$

$$k \cdot \sin \omega t$$

$$k \cdot e^{-\alpha t}$$

Assumed response

$$A$$



$$At + B$$

$$At^2 + Bt + C$$

$$A \sin \omega t + B \cos \omega t$$

$$A \cdot e^{-\alpha t}$$

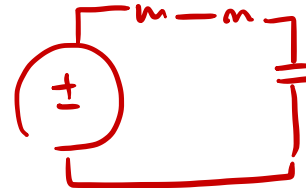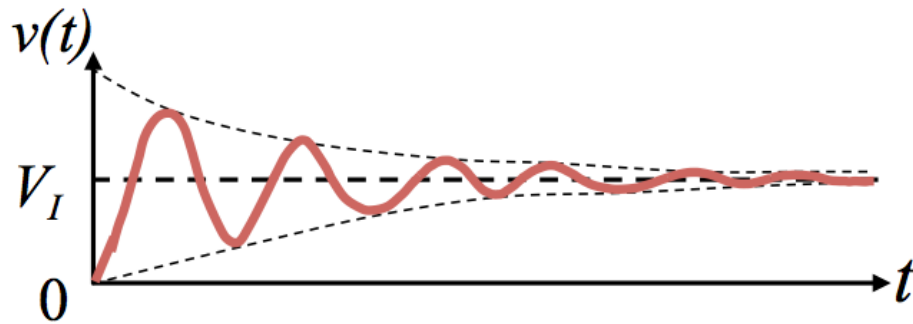Easy Way: Characteristic Equation Tells the Whole Story



□ For series RLC circuit:

characteristic equation: $s^2 + \frac{R}{L}s + \frac{1}{LC} = 0$


$$s^2 + 2\alpha s + \omega_0^2 = 0$$

Intuitive Analysis


$$i = C \frac{dv}{dt} < 0$$

□ What if $v(0) > 0$ and $i(0) < 0$?

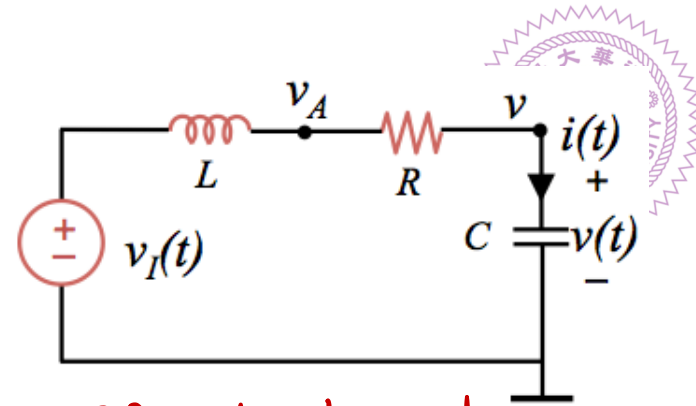- 1) $v_c(0)$ v_{final} 2) α, ω_0 , determine under-damped
over damped
critically damped



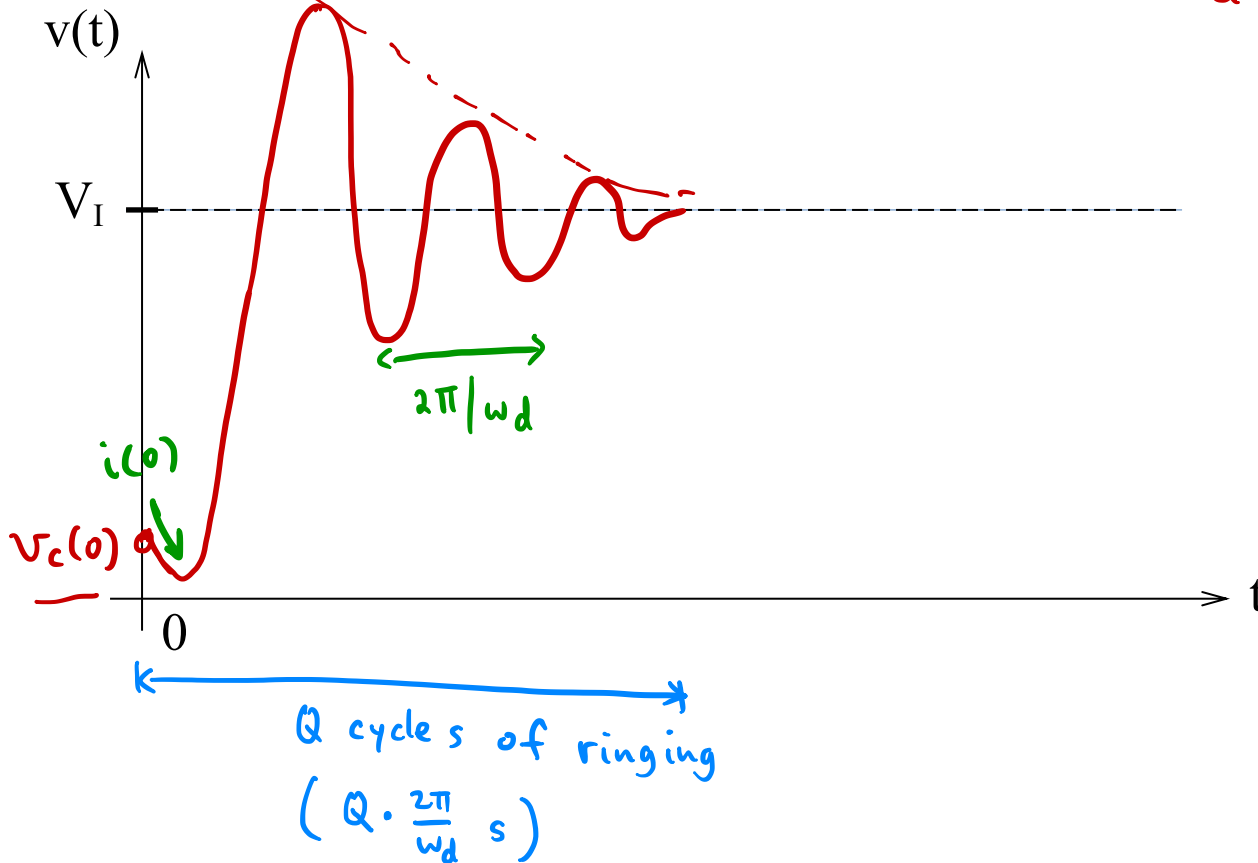
$$Q = \frac{\omega_0}{2\alpha}, \omega_d = \sqrt{\omega_0^2 - \alpha^2}$$





What about Other Variables?

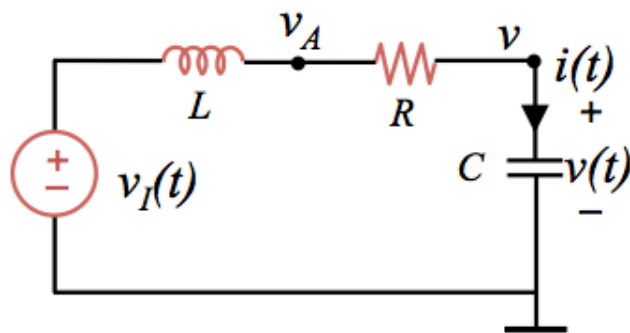

$$i = C \frac{dv}{dt}$$


$$v_R = i \cdot R$$

$$v_L = v_I - v_C - v_R = L \cdot \frac{di}{dt}$$



Parallel RLC – Characteristic Equation Says It All

Practice

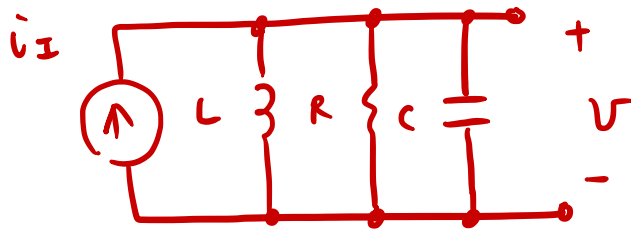

$$\text{From KCL: } i_I = C \frac{dV}{dt} + \frac{V}{R} + \frac{1}{L} \int V dt$$

$$\text{Characteristic equation: } s^2 + \frac{1}{RC} s + \frac{1}{LC} = 0$$

$$s^2 + 2\alpha s + \omega_0^2 = 0$$

$$\Rightarrow \alpha, \omega_0$$

$$\alpha = \frac{1}{2RC}$$

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

Series RLC


characteristic equation

$$s^2 + \frac{R}{L} s + \frac{1}{LC} = 0$$

$$\alpha = \frac{R}{2L}$$


$$\omega_0 = \frac{1}{\sqrt{LC}}$$

Two-Capacitor Circuits

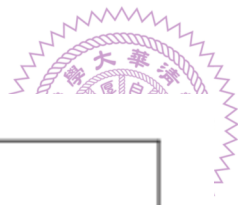

For Node #1 $C_1 \frac{dv_1(t)}{dt} + \frac{1}{R_1} v_1(t) + \frac{1}{R_3} (v_1(t) - v_2(t)) = 0$

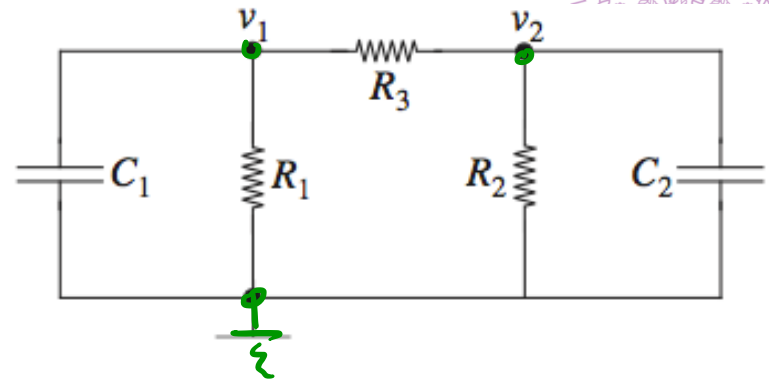For Node #2 $C_2 \frac{dv_2(t)}{dt} + \frac{1}{R_2} v_2(t) + \frac{1}{R_3} (v_2(t) - v_1(t)) = 0$



Express $v_2(t)$ in terms of $v_1(t)$ $v_2(t) = R_3 C_1 \frac{dv_1(t)}{dt} + \left(1 + \frac{R_3}{R_1}\right) v_1(t)$


Differential equation of $v_1(t)$ $\checkmark \frac{d^2 v_1(t)}{dt^2} + \left(\frac{1}{R_1 C_1} + \frac{1}{R_2 C_2} + \frac{1}{R_3 C_1} + \frac{1}{R_3 C_2} \right) \frac{dv_1(t)}{dt} + \left(\frac{1}{R_1 R_2 C_1 C_2} + \frac{1}{R_1 R_3 C_1 C_2} + \frac{1}{R_2 R_3 C_1 C_2} \right) v_1(t) = 0.$

$$v_1 = A_1 e^{s_1 t} + A_2 e^{s_2 t}$$

$$\Rightarrow s^2 + 2\alpha s + \omega_0^2 = 0$$

- Circuits with only resistors and capacitors have characteristic equations with only real non-positive roots.

Example 1:

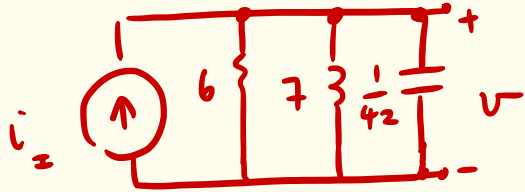

$i_1 = 8 \cdot e^{-2t}$, Find $v(t)$

$$\text{KCL: } i_1 = i_R + i_L + i_C = \frac{v}{R} + \frac{1}{L} \int v dt + C \frac{dv}{dt}$$

$$\frac{d}{dt} \rightarrow \frac{di_1}{dt} = \frac{1}{R} \frac{dv}{dt} + \frac{v}{L} + C \frac{d^2v}{dt^2} = -16 \cdot e^{-2t}$$

① Particular, $v_p = A \cdot e^{-2t}$

$$-16 \cdot e^{-2t} = \frac{1}{6} (-2) \cdot A \cdot e^{-2t} + \frac{1}{7} \cdot A e^{-2t} + \frac{1}{42} A \cdot 4 \cdot e^{-2t}$$

$$\Rightarrow A = 168, \quad \Rightarrow v_p = 168 e^{-2t}$$

(2) Homogeneous. Assume $v_H = B \cdot e^{st}$

$$\frac{1}{6} \frac{dv_H}{dt} + \frac{v_H}{7} + \frac{1}{42} \frac{d^2 v_H}{dt^2} = 0 \Rightarrow \text{characteristic equation } s^2 + 7s + 6 = 0$$


$$\alpha = \frac{7}{2}, \omega_0 = \sqrt{6}$$

$$s_1, s_2 = -1, -6$$

over damped


$$(3) v = 168e^{-2t} + B_1 e^{-t} + B_2 e^{-6t}$$

Example 2.

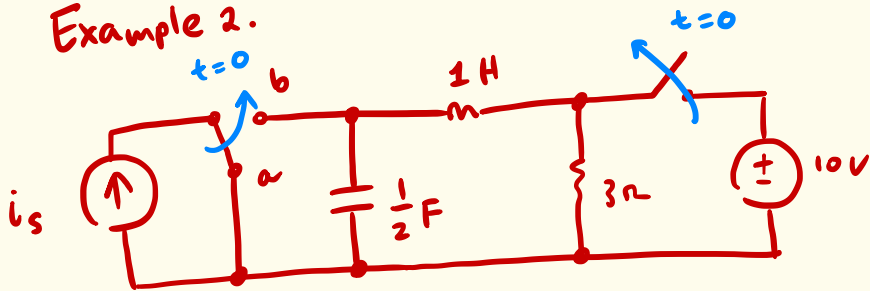


$i_s = 2e^{-3t}$, Find $v(t)$.

At $t < 0$

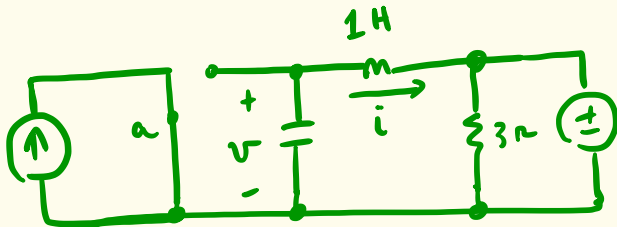


initial conditions

$$i(0) = 0 \text{ A}$$

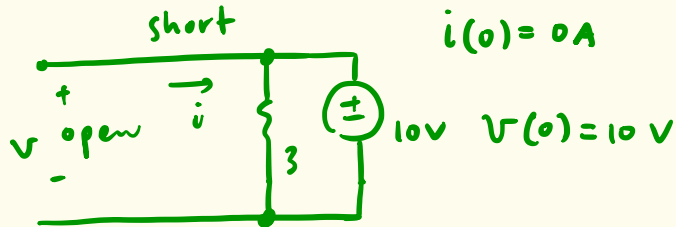

$$v(0) = 10 \text{ V}$$

At $t \geq 0$

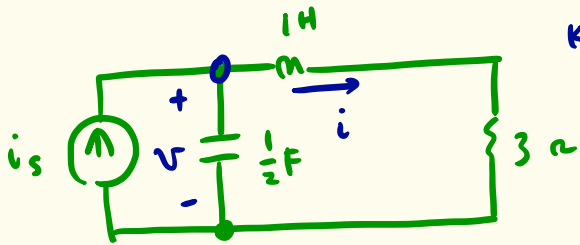

$$\text{KCL: } i_s = i + \frac{1}{2} \frac{dV}{dt} \quad (1)$$

$$\text{KVL: } V = L \frac{di}{dt} + 3i \quad (2)$$

$$\Rightarrow i_s = i + \frac{3}{2} \frac{di}{dt} + \frac{1}{2} \frac{d^2 i}{dt^2}$$

Practice

$$i = 2e^{-3t} - 14e^{-2t} + 12e^{-t} \quad A$$

$$V = \frac{di}{dt} + 3i$$