



# Electric Circuits

## Lecture 1 Introduction

EE2210, Fall 2022



Jenny Yi-Chun Liu

[jennyliu@gapp.nthu.edu.tw](mailto:jennyliu@gapp.nthu.edu.tw)


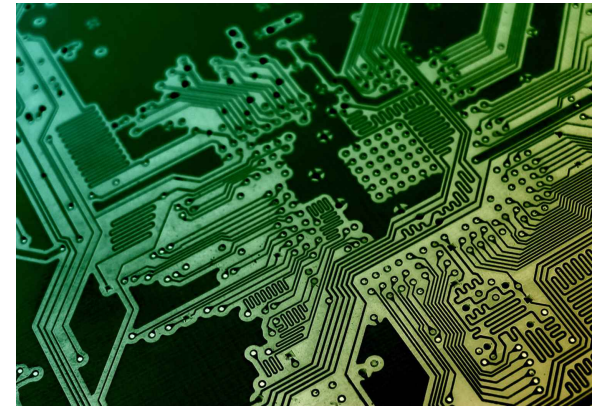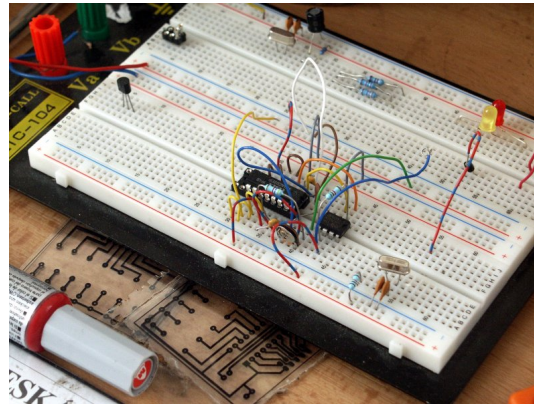
# Lecture Outline

- ❑ Course introduction
- ❑ Electric circuit variables (Chapter 1 in the textbook)
  - Voltage and current.
  - Power and energy.
- ❑ Circuit elements (Chapter 2 in the textbook)





# Course Info

- Instructor: Jenny Yi-Chun Liu 劉怡君
- Email: jennyliu@gapp.nthu.edu.tw
- Time & location: Mon 10:10am-12pm, Wed 9-9:50am @ Delta 215
  - Starting from the 2<sup>nd</sup> week (Sept. 21<sup>st</sup>), remote classes on every Wednesday (temporarily).
- Office hours: by appointment
- Course website: iLMS (notes and videos)
- TAs: 曾柏勳, 陳志育, 王柏翰, 郭施謙, 李孟儒, 羅偉倫
- TA session: Thur 6-8pm @ EECS 518
- Feedback anytime!



# What is this class all about?

- This course introduces the fundamental circuit concepts and circuit analysis techniques.
- Main topics include resistive networks, circuit laws and analytical techniques, linear circuit analysis, energy storage elements, first-order and second-order circuits, sinusoidal steady state, and MOSFET amplifiers.



# Course Goals

- ❑ Understand the basic circuit principles on which the design of electronic systems is based.
- ❑ Analyze and design simple electronic circuits in time and frequency domains.
- ❑ Analyze the circuits with energy storage elements.
- ❑ Understand the concept of employing models to represent nonlinear and active elements.

# Weekly Schedule (Tentative)



Week	Date	Lecture
1	Sept 12	Introduction
	Sept 14	Resistive circuits
2	Sept 19	
	Sept 21	
3	Sept 26	Circuit theorems
	Sept 28	
4	Oct 3	First-order circuits
	Oct 5	
5	Oct 10	Holiday
	Oct 12	First-order circuits
6	Oct 17	
	Oct 19	
7	Oct 24	Operational amplifiers
	Oct 26	
8	Oct 31	Review
	Nov 2	Midterm
9	Nov 7	Second-order circuits
	Nov 9	

Week	Date	Lecture
10	Nov 14	Second-order circuits
	Nov 16	No class (sports day)
11	Nov 21	Second-order circuits
	Nov 23	
12	Nov 28	Sinusoidal steady state
	Nov 30	
13	Dec 5	Energy and power
	Dec 7	
14	Dec 12	Frequency response
	Dec 14	
15	Dec 19	Impedance
	Dec 21	
16	Dec 26	Holiday
	Dec 28	
17	Jan 2	Review
	Jan 4	Final exam
18	Jan 9	



# Course Materials

## □ Textbooks

- Lecture notes (will be posted online)
- Richard C. Dorf and James A. Svoboda, *Introduction to Electric Circuits*, Wiley.

## □ Reference materials

- James W. Nilsson and Susan A. Riedel, *Electric Circuits*, Pearson Prentice Hall.
- Anant Agarwal and Jeffrey H. Lang, *Foundations of Analog and Digital Electronic Circuits*, Morgan Kaufmann Publisher, Elsevier.
- Others available on course website.



# Course Grading

- Four items make the final grade.
  - Homework: 20%
  - Quizzes: 20% (In-class)
  - Midterm: 30%
  - Final: 30%
  - For all quizzes/exams: calculator allowed. Closed book.
- Please comply with the honor code.
  - Cheating leads to 0%.





# Chapter 1

## Electric Circuit Variables




# Introduction

- ❑ Circuits: various electrical elements connected together in a closed form so that an electric current may flow continuously.
- ❑ Electrical power sources have mobility and flexibility.
- ❑ Applications of circuits:
  - Generation, transmission, and consumption of electric power and energy.
  - Encoding, decoding, storage, retrieval, transmission, and processing of information.



# Electric Circuit and Current

two-terminal (node)

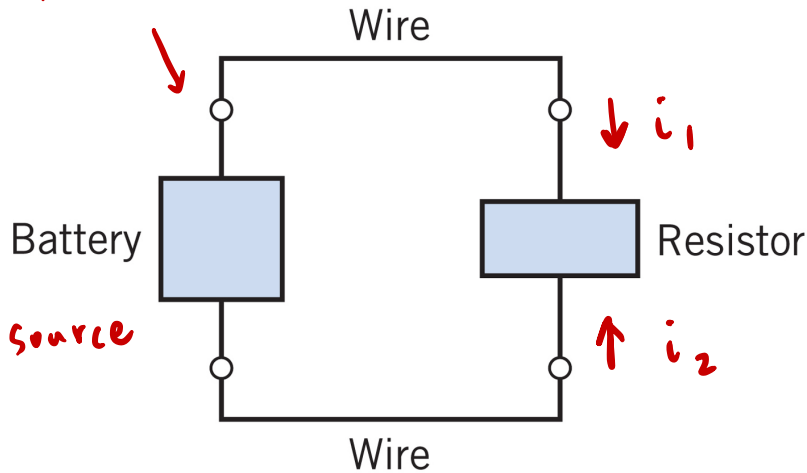

$$i_1 = -i_2$$

- Current: time rate of change of electric charges  $q$  past a given point.


$$i = \frac{dq}{dt} \text{ (ampere, A)}$$

$q$ : coulomb, C


$t$ : second, S




# Forms of Electric Current

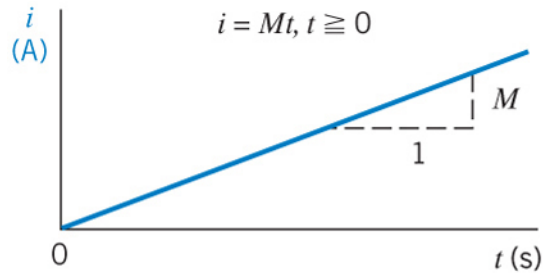

ramp (a)

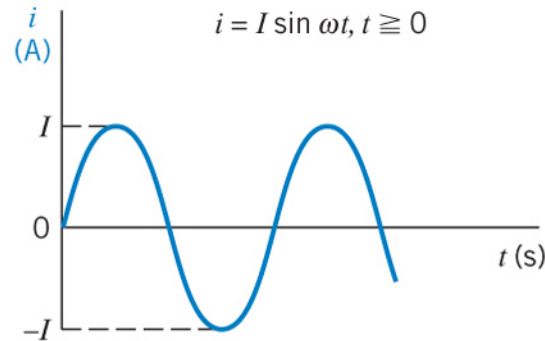

(b) sinusoidal

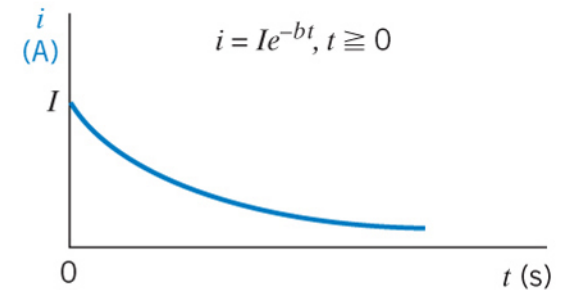

(c) exponential

• direct current (dc) : current with a constant magnitude


• alternating current (ac) : time-varying current

• From  $i = \frac{dq}{dt} \Rightarrow q(t) = \int_{-\infty}^t i(\tau) d\tau = \int_0^t i(\tau) d\tau + q(t=0)$


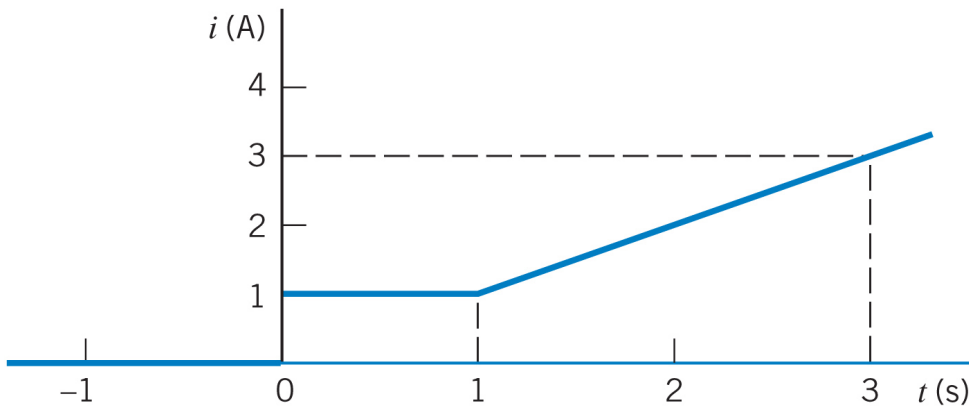
## Example 1.2-2

- Find the charge that has entered the terminal of an element for  $t = 0$  to  $t = 3$  s when the current entering the element is shown in the figure.




$$i(t) = \begin{cases} 0 & , t < 0 \\ 1 & , 0 \leq t \leq 1 \\ t & , t > 1 \end{cases}$$

$$\begin{aligned} \Rightarrow q(t=3) - q(t=0) &= \int_0^3 i(\tau) d\tau \\ &= \int_0^1 1 dt + \int_1^3 t dt = 5 \text{ C} \end{aligned}$$



# Voltage

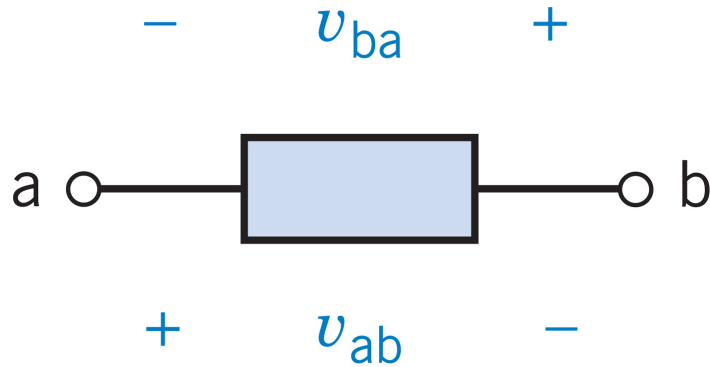

$$v_{ba} = -v_{ab}$$

• Voltage across an element = energy required to move a unit positive charge from "-" terminal to "+" terminal.

$$v = \frac{dw}{dq} \text{ (volt, V)}$$

w: energy (joule, J)

q: C




# Power and Energy

° Power: time rate of energy

$$P = \frac{dw}{dt} = \frac{dw}{dq} \cdot \frac{dq}{dt} = v \cdot i$$

$P$ : watts, W

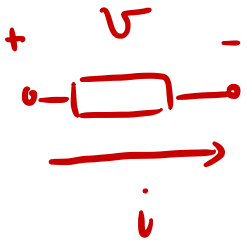

$$w = \int_{-w}^t P(\tau) d\tau$$



## Chapter 2

# Circuit Elements

- Linearity
- Active and passive components
- Resistors
- Independent sources
- Open circuits and short circuits
- Voltmeters and ammeters
- Dependent sources





# Linearity


- Linear components: the element's excitation and response satisfy the linearity principle.
  - Principle of superposition. *and homogeneity.*

1. Superposition:

$$v_1 \rightarrow i_1$$

$$v_2 \rightarrow i_2$$

$$v_1 + v_2 \rightarrow i_1 + i_2$$

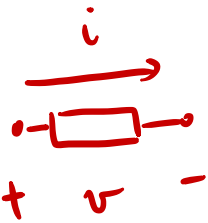

2. Homogeneity:  $v_1 \rightarrow i_1$

$$k \cdot v_1 \rightarrow k \cdot i_1$$

$k$ : constant

element / component / device



## Example 2.2-2

- Consider an element with the following expression:  $v = i^2$

$i$ : excitation,  $v$ : response

$$\text{Given } i_1 \Rightarrow v_1 = i_1^2 \quad \checkmark$$

$$i_2 \Rightarrow v_2 = i_2^2 \quad \checkmark$$


$$i_1 + i_2 \Rightarrow v_3 = (i_1 + i_2)^2 \neq i_1^2 + i_2^2$$

$\therefore$  nonlinear component



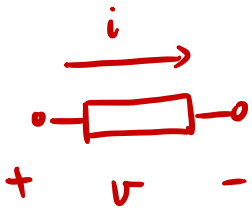
# Active and Passive Elements

- Passive elements: absorb energy to the circuits.
  - Example: resistors, capacitors, inductors.
- Active elements: provide energy to the circuits.
  - Example: battery, generators, transistors.



$w \geq 0$  passive


$w < 0$  active

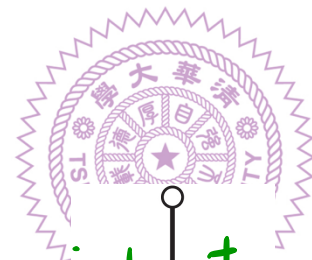
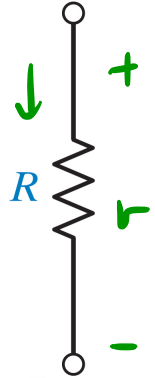
# Resistors

□ Resistor: a passive two-terminal element that has electrical resistance.

- Resistivity  $\rho$  resists the flow of current.
- Resistivity: largely depend on the materials. Insulator has high resistivity and metal has low resistivity.



• Resistance  $R = \rho \cdot \frac{L}{A}$  (ohm,  $\Omega$ )


L: length

A: cross-section area

•  $G = \frac{1}{R}$  (siemens, S,  $\Omega^{-1}$ )

Conductance

$v = R \cdot i$  linear component

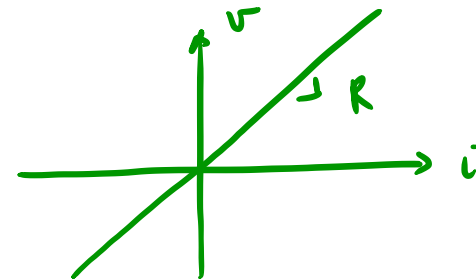


• Power delivered to R =  $v \cdot i = v \cdot \frac{v}{R} = \frac{v^2}{R}$   
 $= R \cdot i \cdot i = R \cdot i^2$


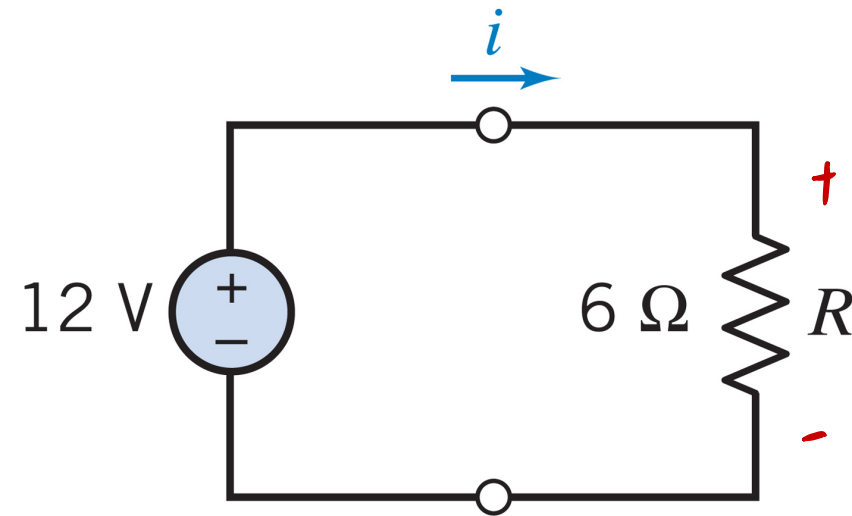
## Example 2.4-1

- Find the current, power and energy supplied by the electric source to the resistor.



$$v = 12 \text{ V}$$

$$i = \frac{12}{6} = 2 \text{ A}$$




$$p = v \cdot i = 24 \text{ W}$$

$$w = \int_0^t 24 \cdot dt = 24t \text{ J}$$


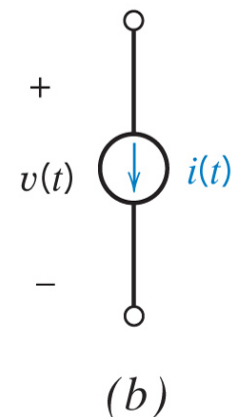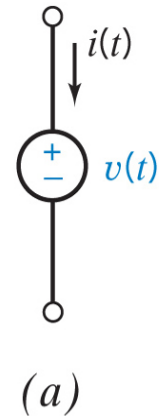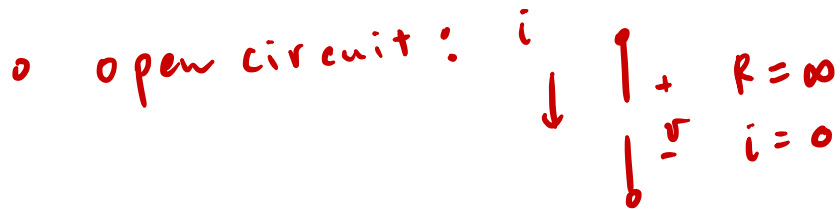
# Independent Sources




- Independent source: voltage or current generator that supplies voltage or current independent of other circuit variables.





# Voltmeters and Ammeters

- Measure the dc voltage and current.

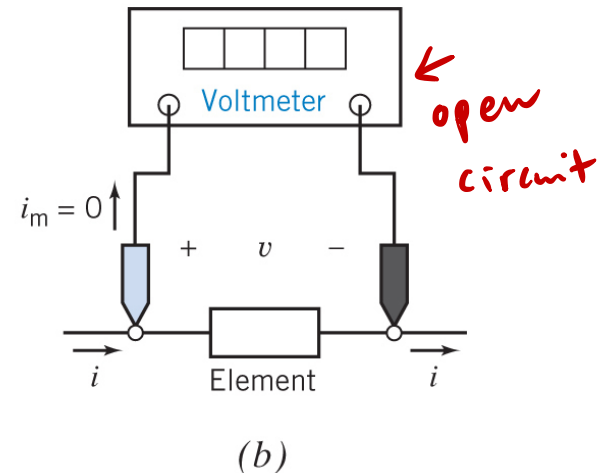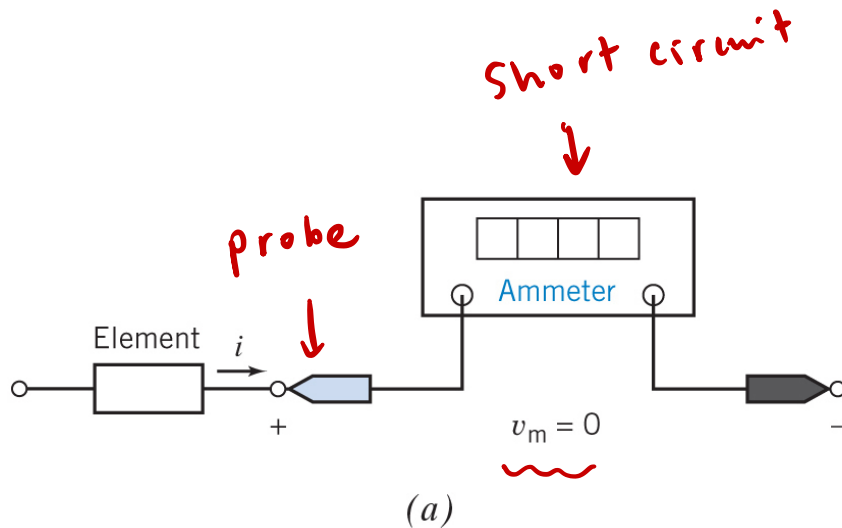
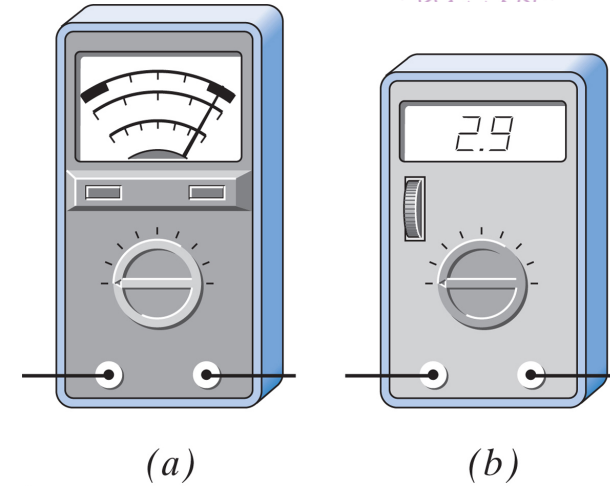




# Dependent Sources

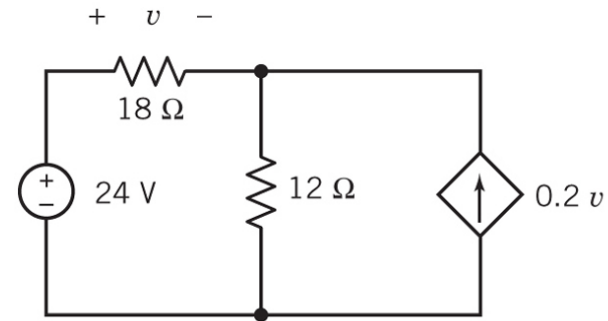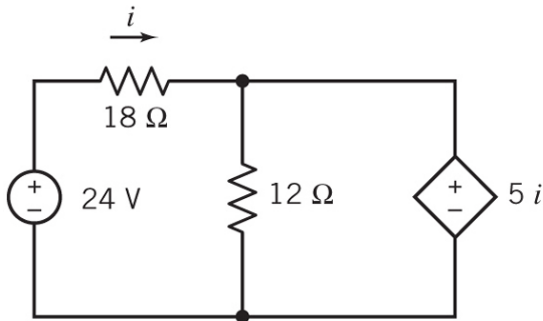Example: transistors,  
amplifiers.



- Dependent sources model the situation where the voltage or current of one circuit element is dependent on the voltage or current of the second circuit element.









# Types of Dependent Sources

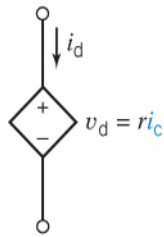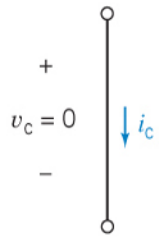



1. CCVS

unit  
 $r: V/A$

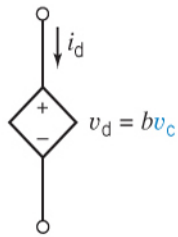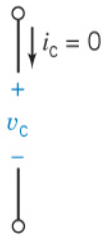



2. VCVS

$b: V/V$

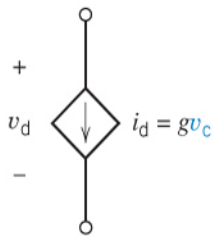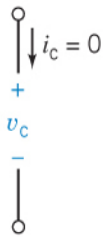

3. VCCS

$g: A/V$

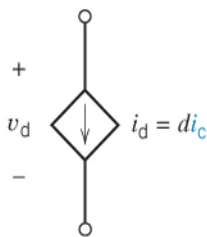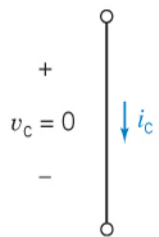

4. CCCS

$d: A/A$