



# Electric Circuits

## Lecture 2 Resistive Circuits

EE2210, Fall 2022

Jenny Yi-Chun Liu

[jennyliu@gapp.nthu.edu.tw](mailto:jennyliu@gapp.nthu.edu.tw)



# Lecture Outline

- Review
- Chapter 3 in the textbook
  - Kirchoff's laws (KCL, KVL)
  - Voltage and current dividers
  - Series and parallel simplification
  - Circuit analysis examples



# Review

1) current  $i = \frac{dq}{dt}$  (A)

2) voltage,  $v = \frac{dw}{dq}$  (V)

3) Power,  $P = v \cdot i$  (W)

Energy,  $w = \int P dt$  (J)

4) Linearity: superposition, homogeneity,


5) Active vs. passive (R, L, C)

6) Resistors,  $R = \rho \cdot \frac{L}{A}$  ( $\Omega$ )

7)

Independent  
Dependent

Sources

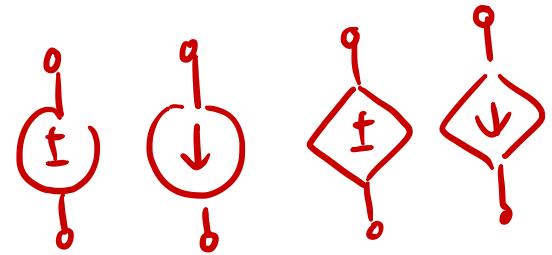



# Example 1 –

## Terminal Variables and Power into a Resistor


- A resistor (10 Ohms) is connected to an arbitrary circuit at points x and y. Assume the current flowing into the network at node x is 2 A. Find  $i$ ,  $v$ ,  $P$ .

$$i = -2 \text{ A}$$

$$v = i \cdot R = (-2) \cdot 10 = -20 \text{ V}$$

$$P = v \cdot i = (-20) \cdot (-2) = 40 \text{ W} > 0$$

passive

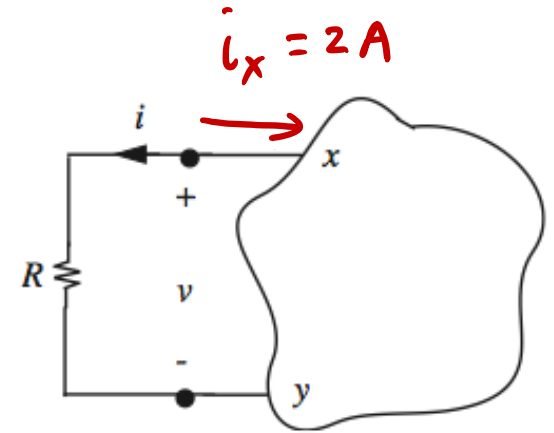



## Example 2 – Power Supplied by a Battery


- The same example but replaced with a 3-V battery.

$$i = -2 \text{ A}$$


$$V = 3 \text{ V}$$

$$P = 3 \cdot (-2) = -6 \text{ W}$$

Active

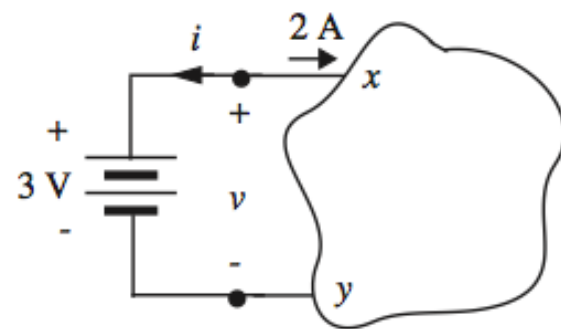
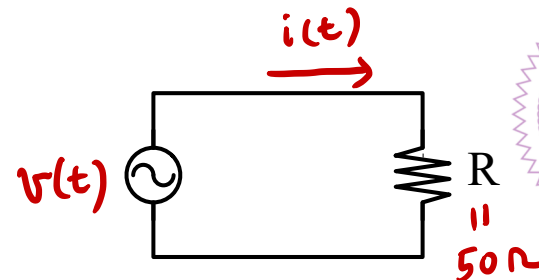
# Example 3 – AC (alternating current) Power



- 110-V 60-Hz AC voltage

$$V_{rms} = 110 \text{ V}$$

$$V_{amp} = \sqrt{2} \cdot 110 \text{ V}$$

$$V_{p-p} = 2 \cdot \sqrt{2} \cdot 110 \text{ V}$$

(peak-to-peak)

$$v(t) = \sqrt{2} \cdot 110 \cdot \sin(2\pi \cdot 60 t) \text{ V}$$

$$\text{Frequency} = 60 \text{ Hz}$$


$$\text{Period} = 1/60 \text{ s}$$

\* What is the period of  $p(t)$ ?

$$i(t) = \frac{v(t)}{50} = \frac{\sqrt{2} \cdot 110}{50} \sin(2\pi \cdot 60 t) \text{ A}, \quad p(t) = v(t) \cdot i(t) = \frac{110^2}{50} [1 - \cos(2\pi \cdot 120 t)] \text{ W}$$

- What would be the power dissipated by the resistor if the voltage was a constant value of 110 V?
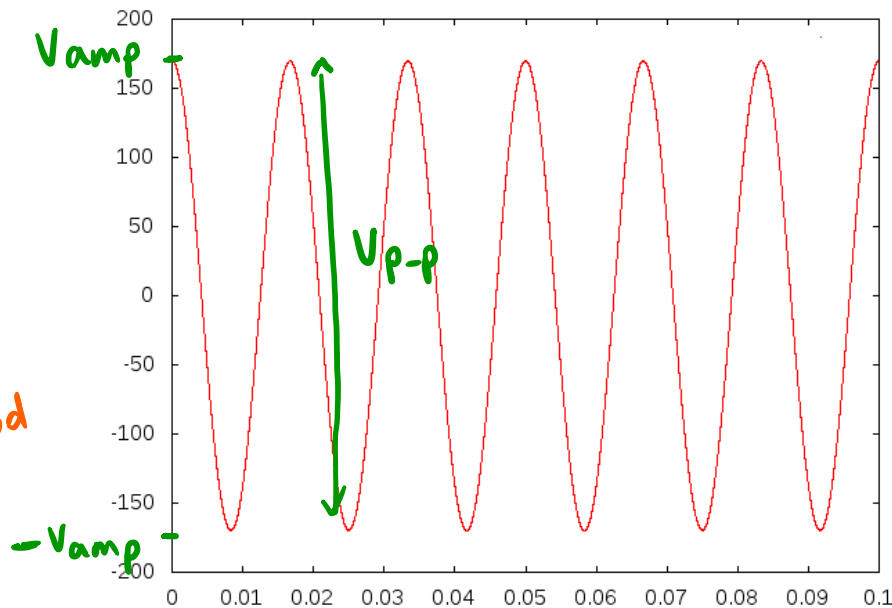
$$P = 110 \cdot \frac{110}{50} = \frac{110^2}{50} \text{ W}$$






## Chapter 3 Resistive Circuits



# Terminology
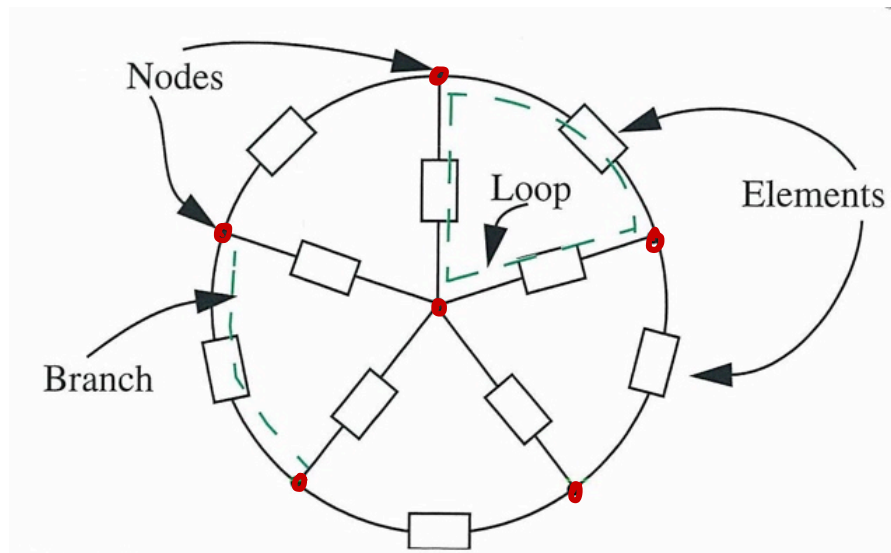
## Component

- ❑ Element is accessed through its terminals.
- ❑ Node: the junction point where the terminals of two or more elements are connected.
- ❑ Branch: the connection between nodes.
- ❑ Loop: a closed path through a circuit along its branches.







# Kirchhoff's Law




- Kirchhoff's Law: from conservation of charge and conservation of energy.
  - Kirchhoff's current law (KCL): the algebraic sum of the current into a node at any instant is zero.
  - Kirchhoff's voltage law (KVL): the algebraic sum of the voltage around any loop in a circuit is zero at all time.



# Basic KVL/KCL Method of Circuit Analysis

- Analyzing a circuit means to find out all the element v's and i's.

o 6 elements, 12 unknowns (v, i)

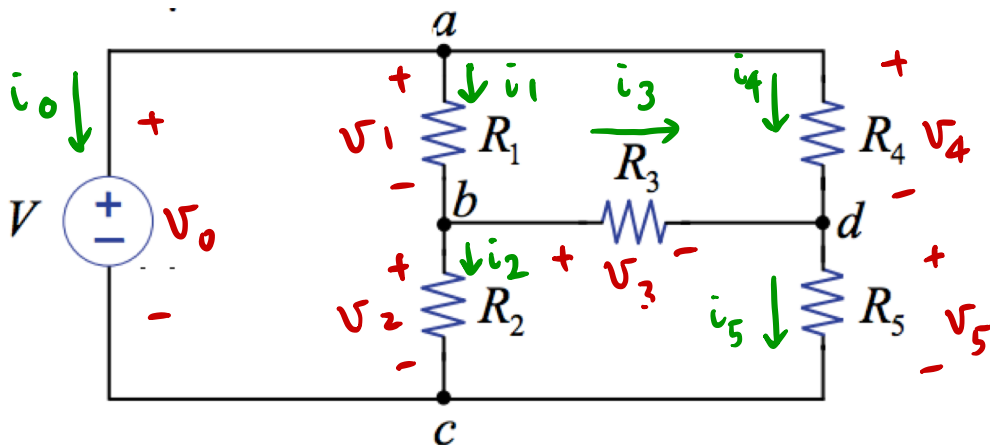


1. Label all elements' v's and i's.
  2. Write element v-i relationship.
  3. Write KCL for all nodes.
  4. Write KVL for all loops.
- Basically lay out all equations...


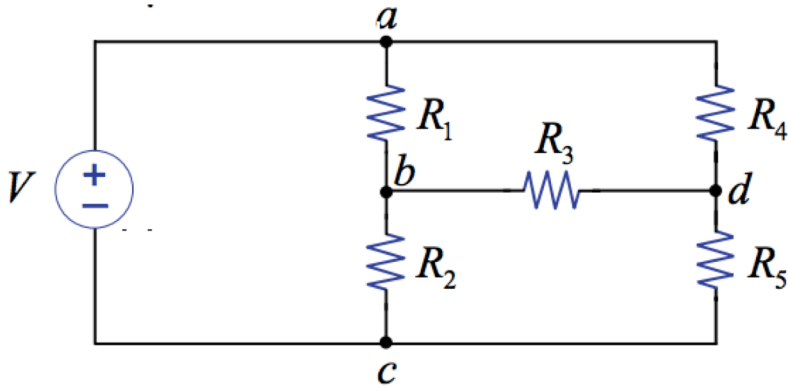
# Basic KVL/KCL Method of Circuit Analysis

- Goal: find out all element v's and i's (12 unknowns).
- Step 2: Write v-i relation for all elements.



$$V_0 = V$$

$$V_1 = i_1 \cdot R_1$$

$$V_2 = i_2 \cdot R_2$$

$$V_3 = i_3 \cdot R_3$$

$$V_4 = i_4 \cdot R_4$$


$$V_5 = i_5 \cdot R_5$$

6 independent equations


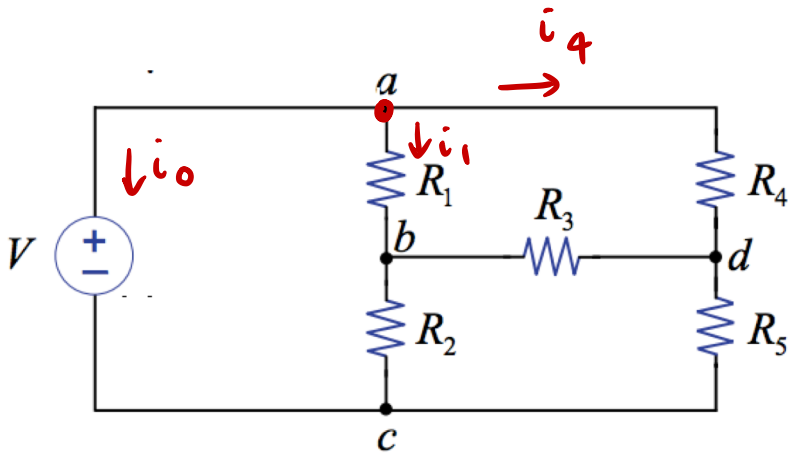
# Basic KVL/KCL Method of Circuit Analysis

- Goal: find out all element v's and i's (12 unknowns).
- Step 3: Apply KCL at the nodes.



node a:  $-i_0 - i_1 - i_4 = 0$

node b:  $i_1 - i_2 - i_3 = 0$

node c:  $i_0 + i_2 + i_5 = 0$


node d:  $i_3 + i_4 - i_5 = 0$

3 independent equations


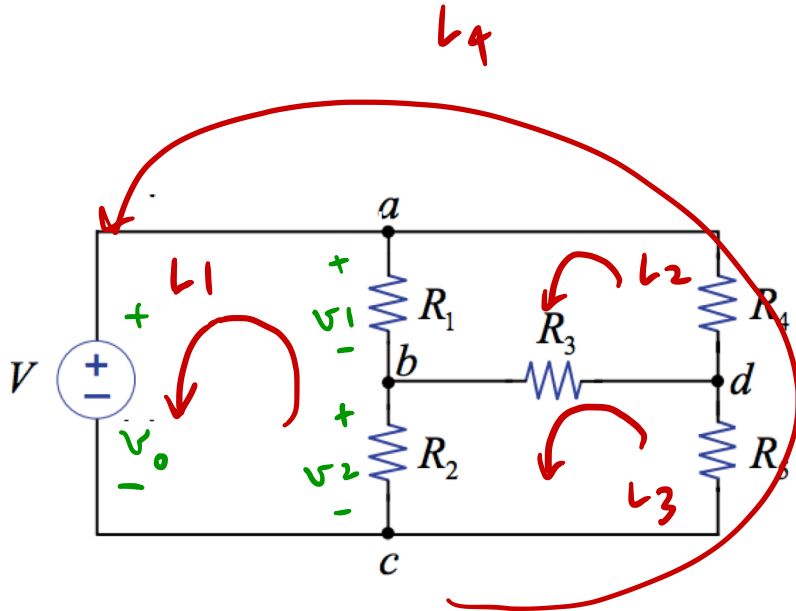
# Basic KVL/KCL Method of Circuit Analysis

- Goal: find out all element v's and i's (12 unknowns).
- Step 4: Apply KVL for the loops



$$L_1: V_1 + V_2 - V_0 = 0$$

$$L_2: V_4 - V_3 - V_1 = 0$$

$$L_3: V_5 - V_2 + V_3 = 0$$

$$L_4: V_4 + V_5 - V_0 = 0$$

3 independent equations

# Basic KVL/KCL Method of Circuit Analysis




## □ 12 equations for 12 unknown

### ■ 1. Element $v$ - $i$ relationships

$$v_0 = V_0 \quad v_3 = i_3 \cdot R_3$$

$$v_1 = i_1 \cdot R_1 \quad v_4 = i_4 \cdot R_4$$
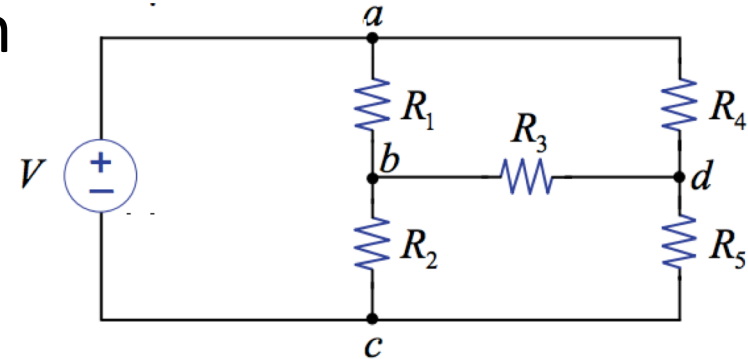
$$v_2 = i_2 \cdot R_2 \quad v_5 = i_5 \cdot R_5$$



### ■ 2. KCL at the nodes

$$a: \quad i_0 + i_1 + i_4 = 0$$

$$b: \quad i_2 + i_3 - i_1 = 0$$

$$c: \quad i_5 - i_3 - i_4 = 0$$

$$(d: \quad -i_0 - i_2 - i_5 = 0)$$

### 3. KVL for the loops

$$L1: \quad -v_0 + v_1 + v_2 = 0$$

$$L2: \quad v_1 + v_3 - v_4 = 0$$

$$L3: \quad v_3 + v_5 - v_2 = 0$$

$$(L4: \quad -v_0 + v_4 + v_5 = 0)$$