



# Electric Circuits

## Lecture 3 Circuit Analysis Methods and Theorems

EE2210, Fall 2022

Jenny Yi-Chun Liu


[jennyliu@gapp.nthu.edu.tw](mailto:jennyliu@gapp.nthu.edu.tw)



# Lecture Outline

- Review
  - KCL, KVL (method 1)
  - Element combination (method 2)
- Chapter 4 in the textbook
  - Node analysis (method 3)
  - Mesh analysis (method 4)
- Chapter 5 in the textbook
  - Superposition (method 5)
  - Thévenin and Norton (method 6 and 7)

Example 1.

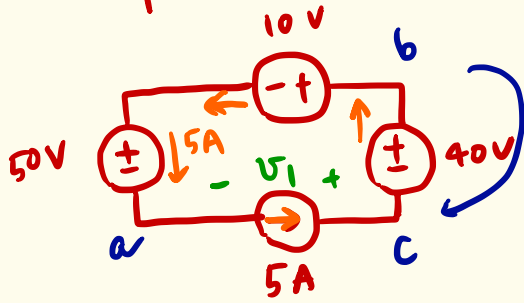

Is the circuit valid? Yes

What is  $V_1$ ? KVL

Power of each source?


$$V_1 = 50 + 10 - 40 = 20 \text{ V}$$

$$P_{50\text{V}} = 50 \times 5 = 250 \text{ W}$$

$$P_{10\text{V}} = 10 \times 5 = 50 \text{ W}$$


$$P_{40\text{V}} = 40 \times (-5) = -200 \text{ W}$$

$$P_{5\text{A}} = 20 \times (-5) = -100 \text{ W}$$

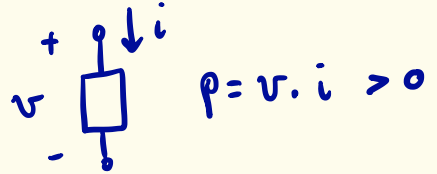

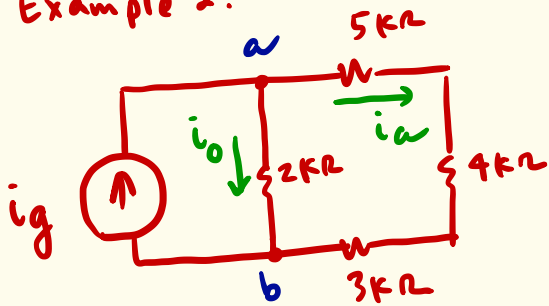Example 2.

Assume  $i_a = 2 \text{ mA}$ . Find  $i_o$  and  $i_g$ .



$$\text{KCL: } i_g - i_o - i_a = 0 \quad (1)$$


$$\text{KVL: } 2\text{k} \cdot i_o - 5\text{k} \cdot i_a - 4\text{k} \cdot i_a - 3\text{k} \cdot i_a = 0 \quad (2)$$

$$\text{From (2), } i_o = 6i_a = 12 \text{ mA}$$

$$(1), \quad i_g = i_a + i_o = 14 \text{ mA}$$

Example 3.

Find  $V_o$

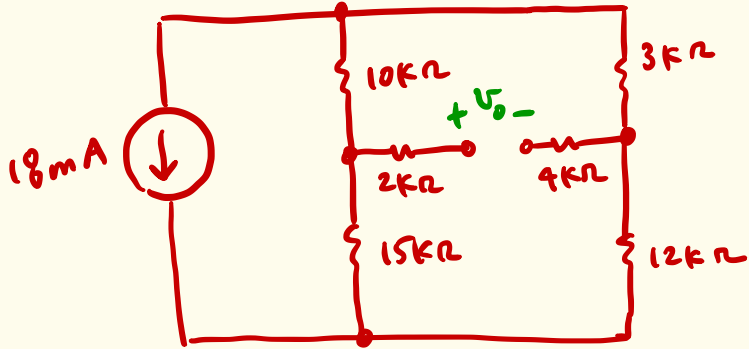



# Chapter 4 Methods of Analysis of Resistive Circuits



# Node Voltage



- Node voltage: the potential difference between the given node and a reference node, which is usually ground (zero V).
  - Current flows from the node with higher potential to the node with lower potential.
  - It is common to choose the node that has the maximum number of elements connected to it as the reference node.



# Example – Reference Node

ground (0V)

$\perp \downarrow \perp$

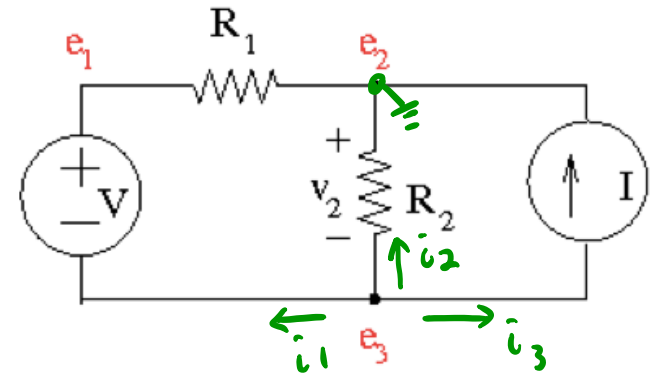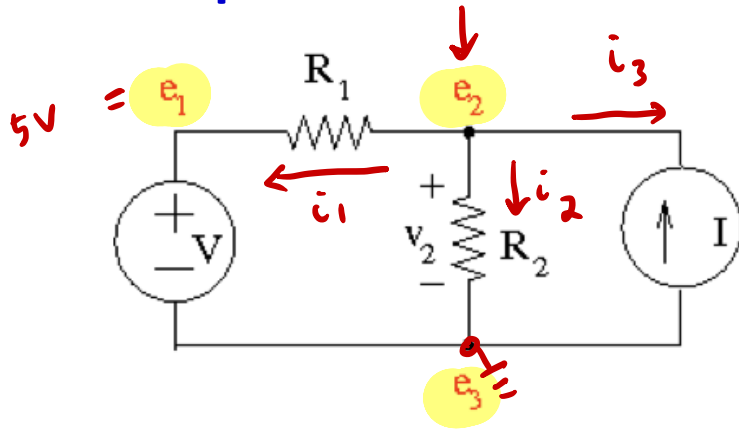

Given  $V = 5\text{ V}$ ,  $I = 3\text{ A}$ ,  $R_1 = 3\ \Omega$ ,  $R_2 = 5\ \Omega$ .

Case 1. Set  $e_3$  as reference node.

Case 2. Set  $e_2$  as reference node.

$$\text{KCL @ } e_2: i_1 + i_2 + i_3 = 0$$

$$\Rightarrow \frac{e_2 - e_1}{R_1} + \frac{e_2}{R_2} - I = 0$$

$$\Rightarrow e_2 = 8.75\text{ V}$$

$$\text{KCL @ } e_3: i_1 + i_2 + i_3 = 0$$

$$\Rightarrow \frac{e_3 + V - e_2}{R_1} + \frac{e_3}{R_2} + I = 0$$

$$e_1 = e_3 + V$$

$$\Rightarrow e_3 = -8.75\text{ V}$$






# Method 3: Node Analysis

- The most efficient utilization of KCL and circuit elements' laws to solve for the voltages and currents of all elements of a given circuit.
  1. Select a node as a reference (ground) node.
  2. Label node voltages to the remaining nodes with respect to ground.
    - These are the primary unknowns.
  3. Apply KCL to all but the ground node.  
Use device laws to express the branch currents in terms of node voltages.
  4. Solve the  $n - 1$  equations for node voltages.
  5. Calculate all branch voltages and currents based on elements' laws.



# Example – Using Node Method

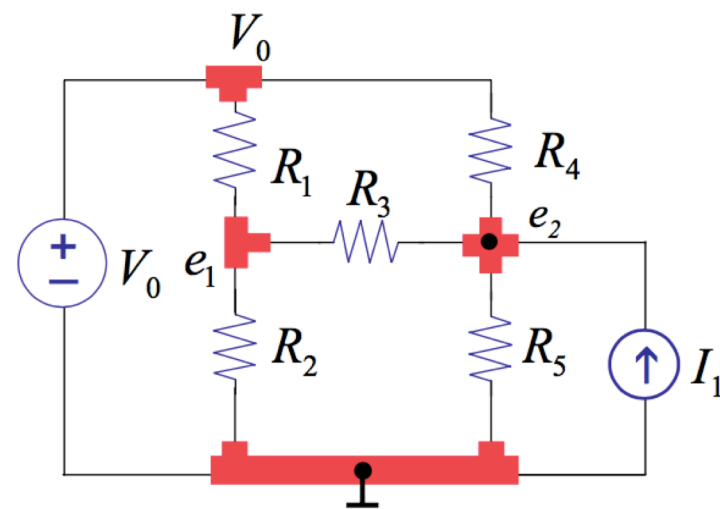1. Select a node as a reference (ground) node.
2. Label node voltages to the remaining nodes with respect to ground.






# Example – Using Node Method

3. Apply KCL to all but the ground node. Use device laws to express the branch currents in terms of node voltages.

- For convenience, write  $G_i = \frac{1}{R_i}$
- To avoid mistakes use convention:  
e.g., always sum currents leaving a node

$$\text{KCL @ } e_1: \frac{e_1 - V}{R_1} + \frac{e_1 - e_2}{R_3} + \frac{e_1}{R_2} = 0 \quad (1)$$
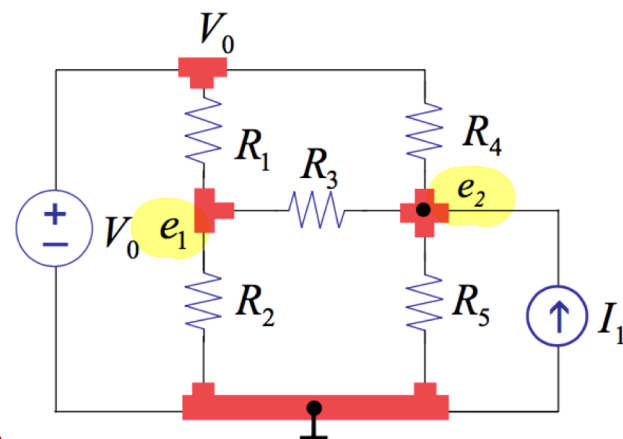
$$\text{KCL @ } e_2: \frac{e_2 - V}{R_4} + \frac{e_2 - e_1}{R_3} + \frac{e_2}{R_5} - I = 0 \quad (2)$$



From (1) and (2), express  $e_1$  and  $e_2$  as functions of  $V$ ,  $I$ ,  $R_1$ ,  $R_2$ ,  $R_3$ ,  $R_4$ ,  $R_5$   
(known variables)




# Example – Using Node Method

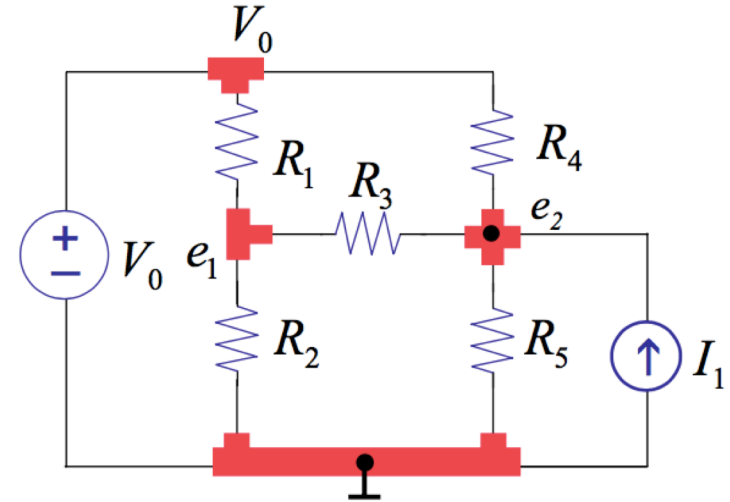4. Solve the  $n - 1$  equations for node voltages

$$\text{KCL at } e_1 \quad (e_1 - V_0)G_1 + (e_1 - e_2)G_3 + (e_1 - 0)G_2 = 0$$

$$\text{KCL at } e_2 \quad (e_2 - e_1)G_3 + (e_2 - V_0)G_4 + (e_2 - 0)G_5 - I_1 = 0$$





# Example – Using Node Method


5. Calculate all branch voltages and currents based on elements' laws.

For example

$$\bar{i}_2 = \frac{e_1 - 0}{R_2}$$

$$\bar{i}_3 = \frac{e_1 - e_2}{R_3}$$

⋮

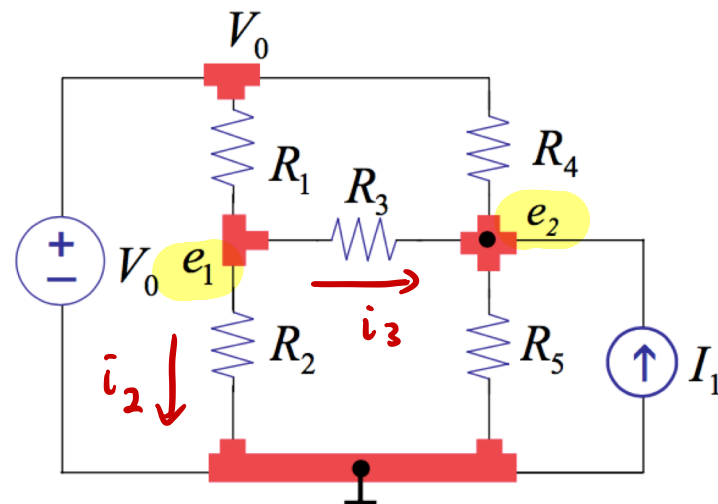



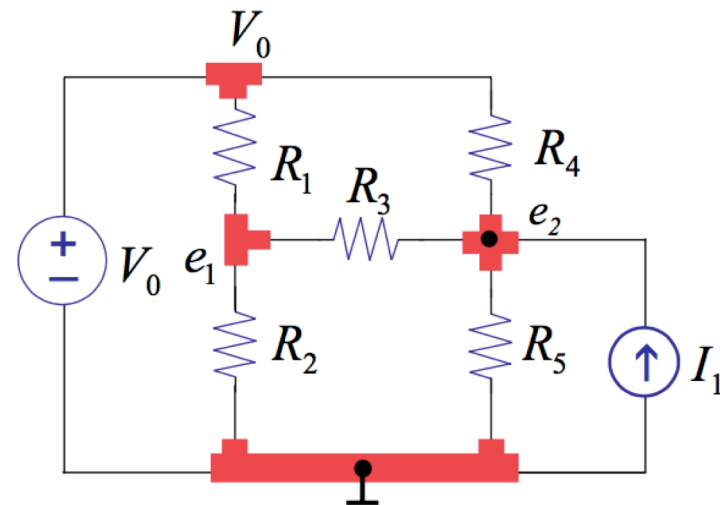
# Revisit Step 4

$$e_1(G_1 + G_2 + G_3) + e_2(-G_3) = V_0(G_1)$$

$$e_1(-G_3) + e_2(G_3 + G_4 + G_5) = V_0(G_4) + I_1$$



$$\left[ \begin{array}{c|c} G_1 + G_2 + G_3 & -G_3 \\ \hline -G_3 & G_3 + G_4 + G_5 \end{array} \right] \begin{bmatrix} e_1 \\ e_2 \end{bmatrix} = \begin{bmatrix} G_1 V_0 \\ G_4 V_0 + I_1 \end{bmatrix}$$

conductivity matrix      unknown node voltages      sources




# Revisit Step 4

$$\left[ \begin{array}{c|c} G_1 + G_2 + G_3 & -G_3 \\ \hline -G_3 & G_3 + G_4 + G_5 \end{array} \right] \begin{bmatrix} e_1 \\ e_2 \end{bmatrix} = \begin{bmatrix} G_1 V_0 \\ G_4 V_0 + I_1 \end{bmatrix}$$

$$e_1 = \frac{(G_3 + G_4 + G_5)(G_1 V_0) + (G_3)(G_4 V_0 + I_1)}{G_1 G_3 + G_1 G_4 + G_1 G_5 + G_2 G_3 + G_2 G_4 + G_2 G_5 + G_3 G_4 + G_3 G_5}$$

$$e_2 = \frac{(G_3)(G_1 V_0) + (G_1 + G_2 + G_3)(G_4 V_0 + I_1)}{G_1 G_3 + G_1 G_4 + G_1 G_5 + G_2 G_3 + G_2 G_4 + G_2 G_5 + G_3 G_4 + G_3 G_5}$$

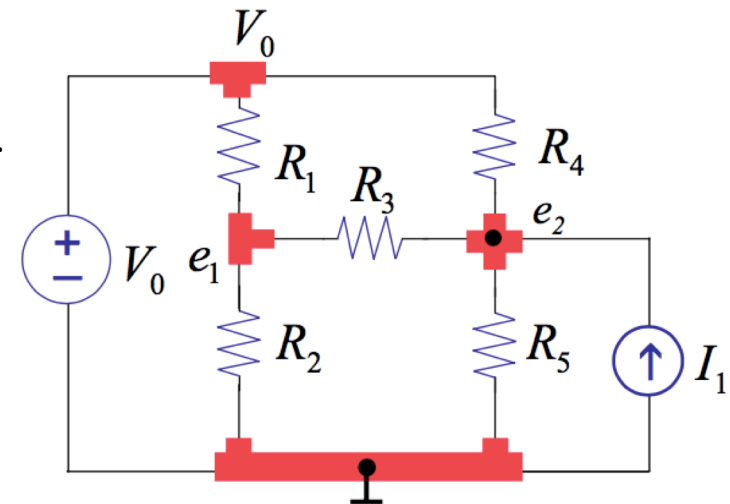
- The same denominator for  $e_1$  and  $e_2$ .
- No negative terms in denominator.
- Linear in  $V_0$  and  $I_1$ .





# More Example – Node Method

- Determine the current  $i$ .

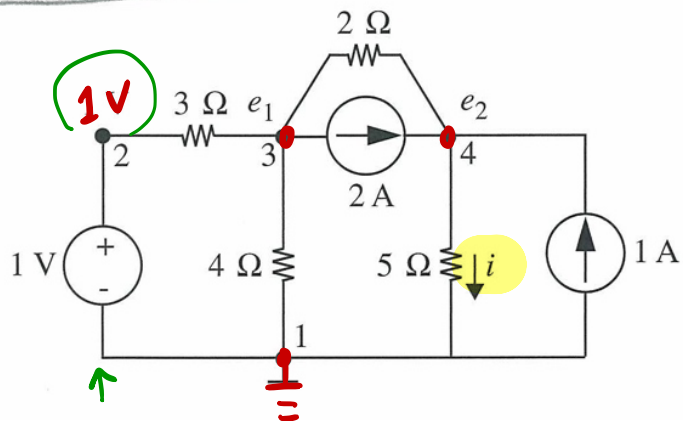

1. Choose node 1 as ref. node
2. Label all other unknowns ( $e_1, e_2$ )
3. KCL @  $e_1$ :  $\frac{e_1 - 1}{3} + \frac{e_1}{4} + \frac{e_1 - e_2}{2} + 2 = 0$   
KCL @  $e_2$ :  $-2 + \frac{e_2 - e_1}{2} + \frac{e_2}{5} - 1 = 0$


$$\Rightarrow e_1 = 0.65V, \quad e_2 = 4.75V$$

$$i = \frac{e_2 - 0}{5} = 0.95A$$





# Floating Independent Sources

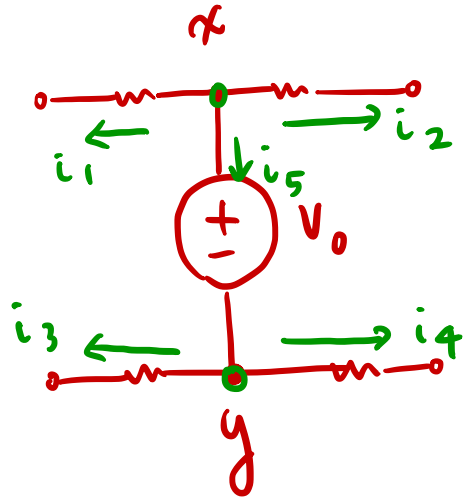

$$\text{KCL @ } x: i_1 + i_5 + i_2 = 0$$

$$\text{KCL @ } y: i_3 - i_5 + i_4 = 0$$

---

$$i_1 + i_2 + i_3 + i_4 = 0$$

$x, y$ : supernode




# Example 4.3-2

- Determine  $v_a$  and  $v_b$ .

$a, b$  : supernode

$$v_b = v_a + 12 \quad (1)$$

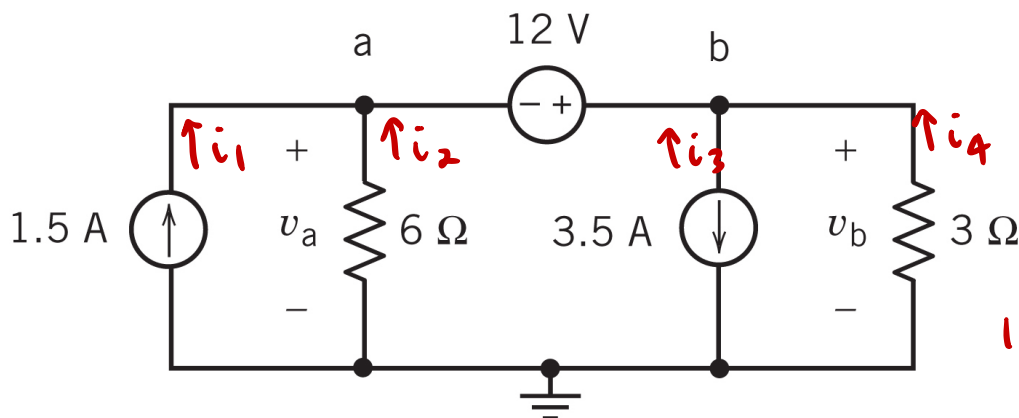

KCL @ supernode :  $i_1 + i_2 + i_3 + i_4 = 0$


$$1.5 + \frac{-v_a}{6} - 3.5 + \frac{-v_b}{3} = 0 \quad (2)$$

From (1) and (2),  $v_a = -12\text{ V}$   
 $v_b = 0\text{ V}$



# Exercise 4.3-2

- Determine  $v_a$  and  $v_b$ .

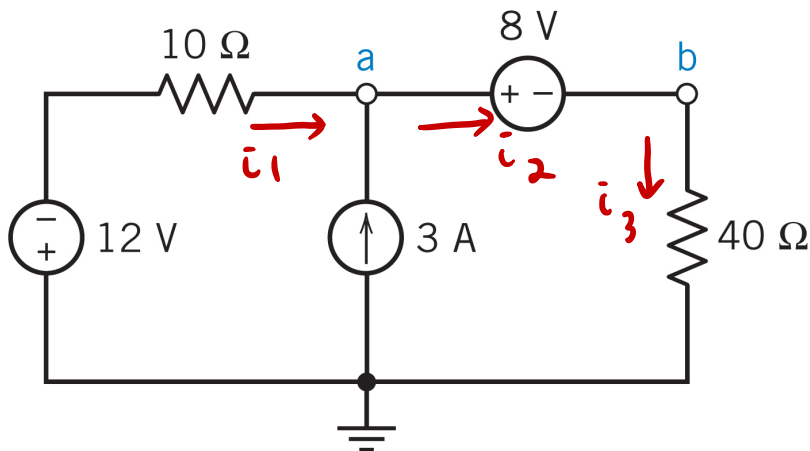

$a, b$ : supernode

$$\text{KCL @ } a: i_1 + 3 - i_2 = 0 \quad (1)$$

$$\text{KCL @ } b: i_2 - i_3 = 0 \quad (2)$$

$$v_a = v_b + 8$$

$$(1) + (2)$$

$$\Rightarrow i_1 + 3 - i_3 = 0$$

$$\text{From (1), } \frac{-12 - v_a}{10} + 3 - i_2 = 0$$


$$\text{From (2), } i_2 = i_3 = \frac{v_b}{40}$$

$$\Rightarrow v_a = 16 \text{ V, } v_b = 8 \text{ V}$$



# Exercise 4.4-1

□ Determine  $v_b$ .

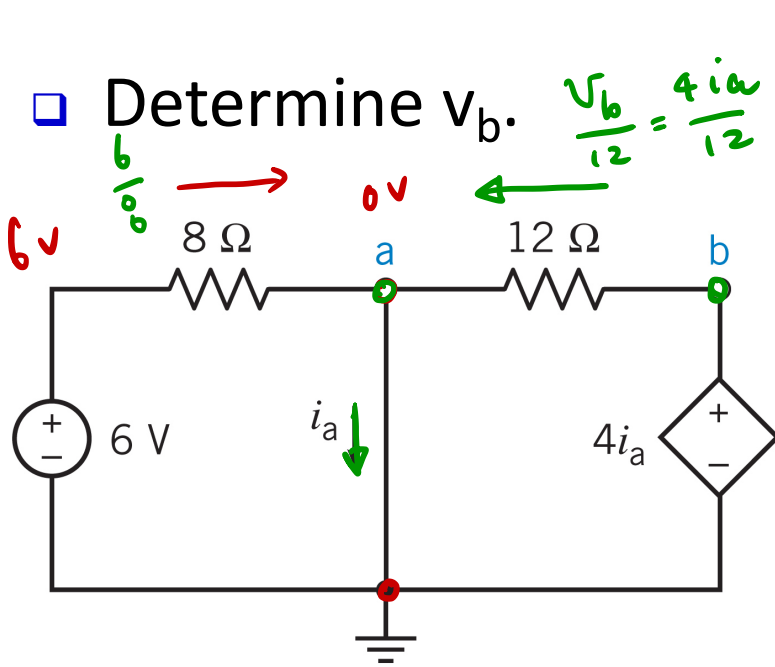

KCL @ a:  $\frac{6}{8} - i_a + \frac{4i_a}{12} = 0$

$\Rightarrow i_a = \frac{9}{8} \text{ A}$

$v_b = 4i_a = \frac{9}{2} \text{ V}$





# Method 4: Mesh Analysis

□ Mesh: a loop that does not contain any other loops within it.

□ Mesh analysis

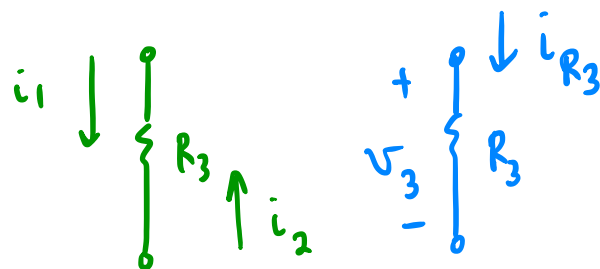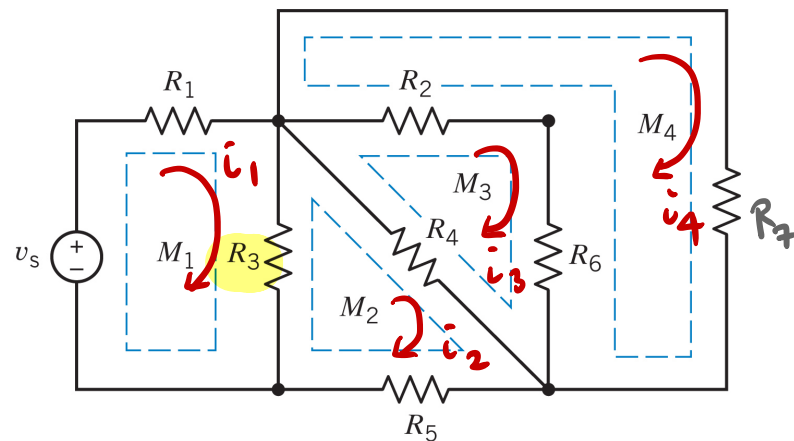- Write element voltages as functions of mesh currents.
- Apply KVL to each mesh of the circuit.




$$i_{R3} = i_1 - i_2$$

$$v_3 = i_{R3} \cdot R_3$$



# Mesh Equations

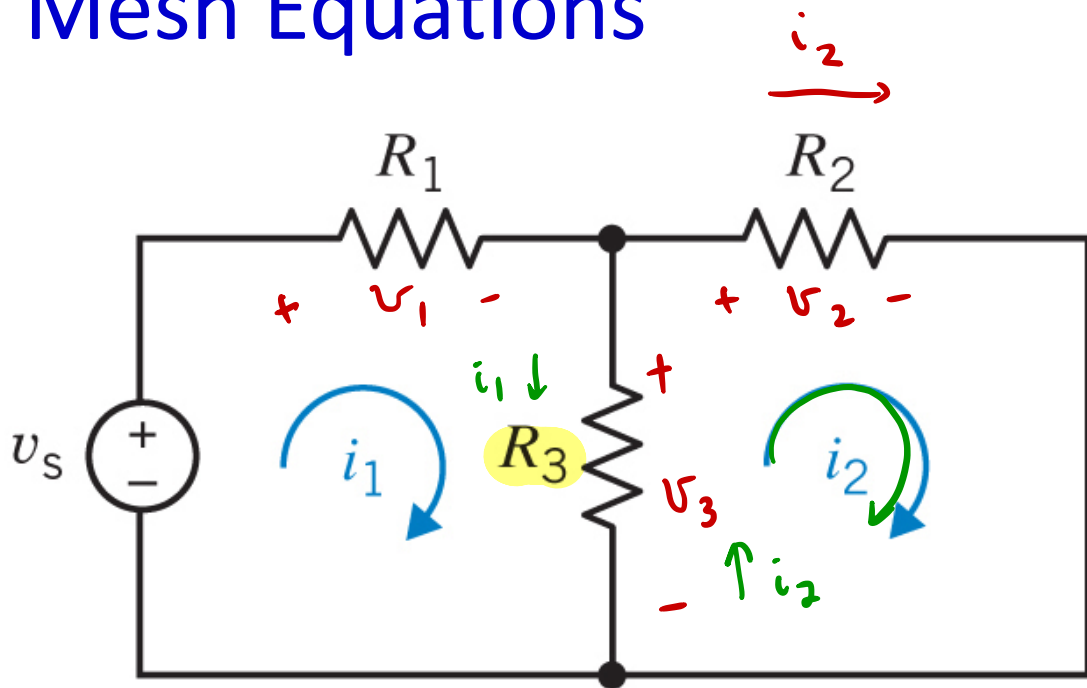

$$\text{KVL mesh 1: } v_s - v_1 - v_3 = 0$$

$$\text{mesh 2: } v_3 - v_2 = 0$$

$$v_1 = i_1 \cdot R_1$$

$$v_3 = (i_1 - i_2) \cdot R_3$$

$$v_2 = i_2 \cdot R_2$$