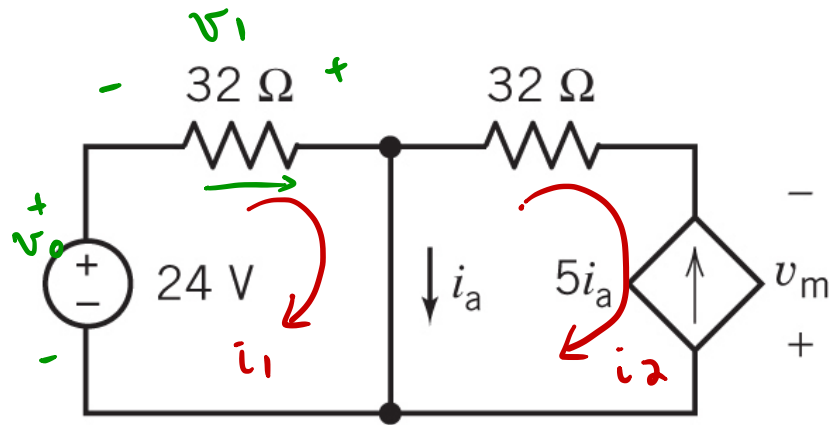




Example 4.7-1

- Determine v_m .



KVL

mesh 1: $v_0 + v_1 = 0$

$$24 - i_1 \cdot 32 = 0 \Rightarrow i_1 = \frac{24}{32} = \frac{3}{4} \text{ A}$$

mesh 2: $-32i_2 + v_m = 0$ ✓


$$5i_a = -i_2 = 5(i_1 - i_2)$$

$$\Rightarrow 4i_2 = 5i_1$$

$$\Rightarrow i_2 = \frac{5}{4} i_1 = \frac{15}{16} \text{ A}$$

$$v_m = 32i_2 = 30 \text{ V}$$

Example.

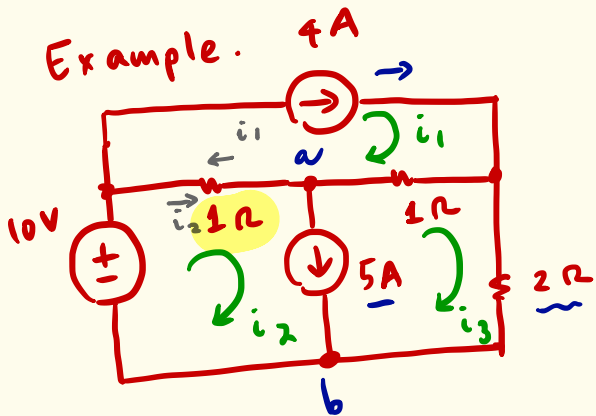

$$i_1 = 4A \quad \checkmark$$

$$i_2 - i_3 = 5A \quad \checkmark \quad (1)$$

$$V_{ab} = V_a - V_b$$

KVL

$$\text{mesh 2: } 10 - (i_2 - i_1) \cdot 1 - V_{ab} = 0 \quad (2)$$

$$\text{mesh 3: } V_{ab} - (i_3 - i_1) \cdot 1 - i_3 \cdot 2 = 0 \quad (3)$$

From (1), (2), (3)

$$\Rightarrow i_2 = \frac{33}{4} A$$

$$i_3 = \frac{13}{4} A$$




Chapter 5 Circuit Theorems

*linear
networks*

- Superposition
- Thevenin's
- Norton's

Linearity

□ Consider this circuit

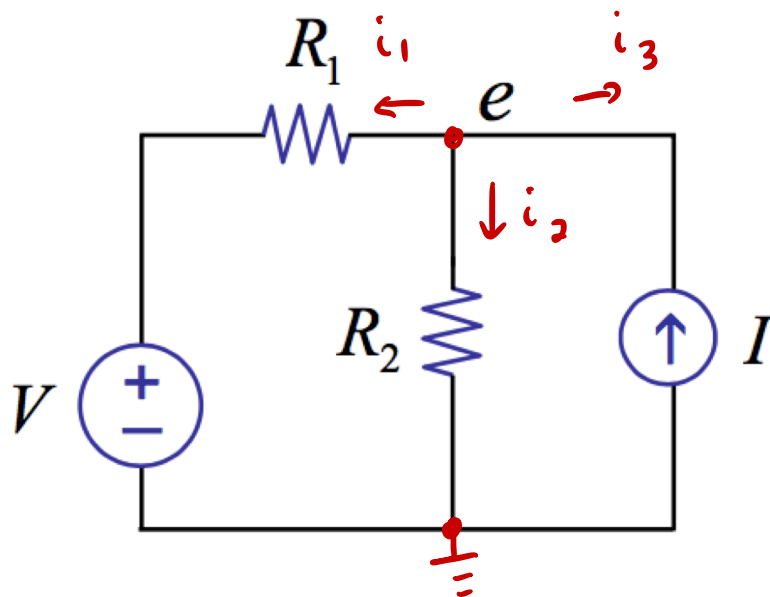

□ Write node equation.




Linearity

□ Node equation

$$\frac{e-V}{R_1} + \frac{e}{R_2} - I = 0 \quad \text{linear in } e, V, I$$

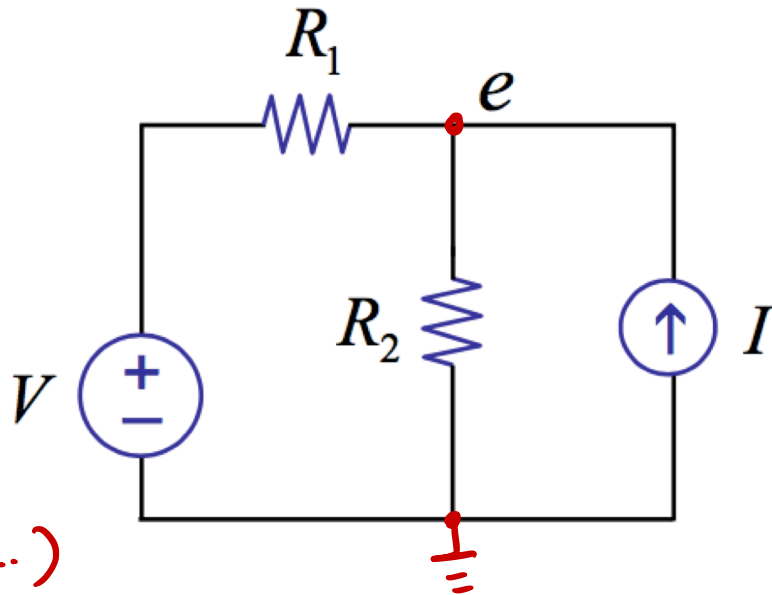(no $e^2, V^2, \sqrt{e}, e \cdot I, \exp I, \dots$)



$$\Rightarrow e = \frac{\frac{V}{R_1} + I}{\frac{1}{R_1} + \frac{1}{R_2}} = \frac{R_2}{R_1 + R_2} \cdot V + \frac{R_1 \cdot R_2}{R_1 + R_2} I = a \cdot V + b \cdot I$$

where a, b constant

Linearity

□ Linearity

- ✓ ■ Homogeneity
- ✓ ■ Superposition






Method 5: Superposition

1. Find the partial responses of the circuit to each source acting along.
 2. Sum the individual responses.
- Dependent sources remain active at all time. Only the independent sources are turned ON and OFF.




★ Each Source Acting Alone Means...


□ Voltage source

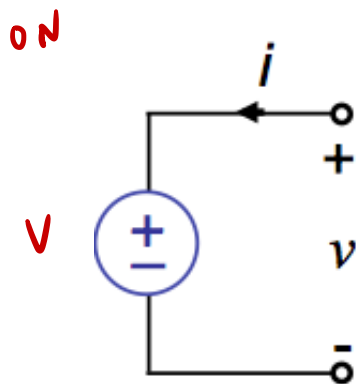


OFF

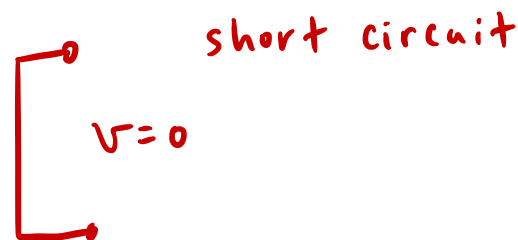

□ Current source

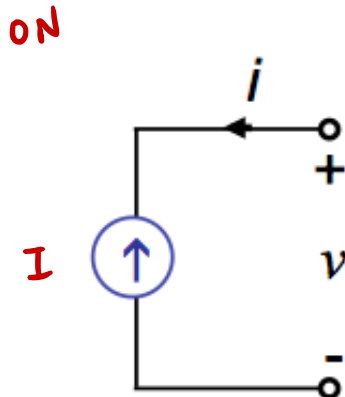


OFF

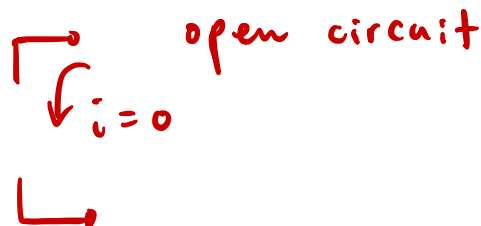




Example – Analysis Using Superposition


- Superposition – with V acting alone

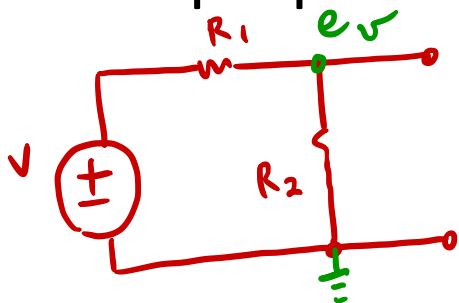
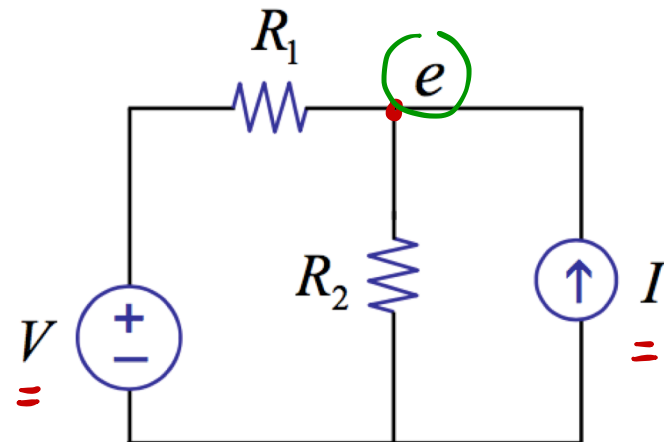
$$(I=0) \quad e_v = \frac{R_2}{R_1 + R_2} \cdot V$$



- Superposition – with I acting alone

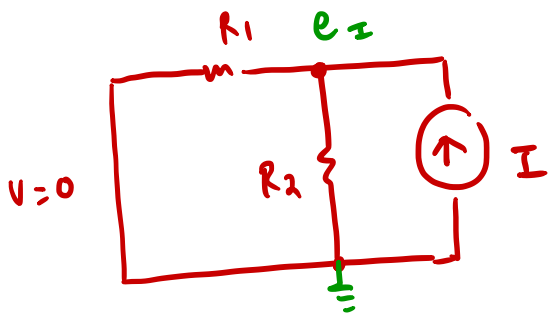


$$e_I = I \cdot (R_1 \parallel R_2) = \frac{R_1 \cdot R_2}{R_1 + R_2} \cdot I$$

- Sum two partial responses



$$\text{Total response} = e_v + e_I = \frac{R_2}{R_1 + R_2} \cdot V + \frac{R_1 \cdot R_2}{R_1 + R_2} \cdot I$$



Example – Resistive Adder Circuit

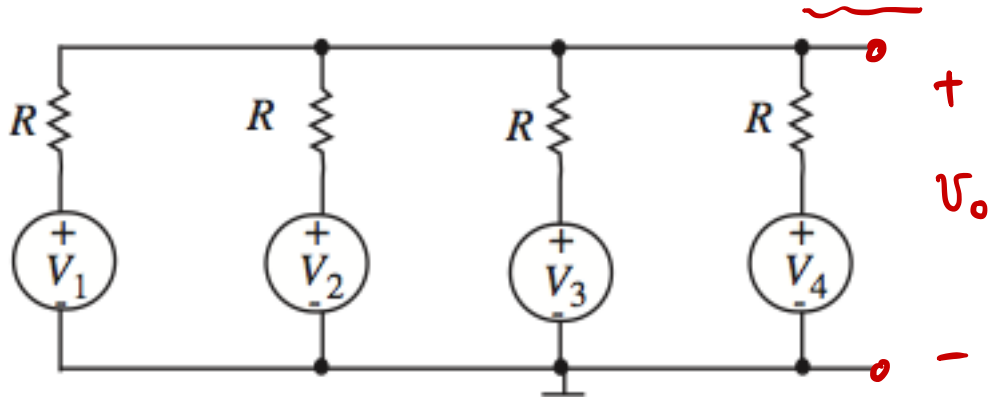


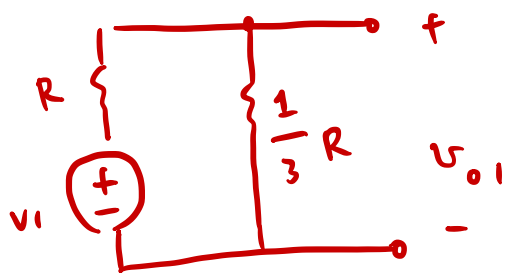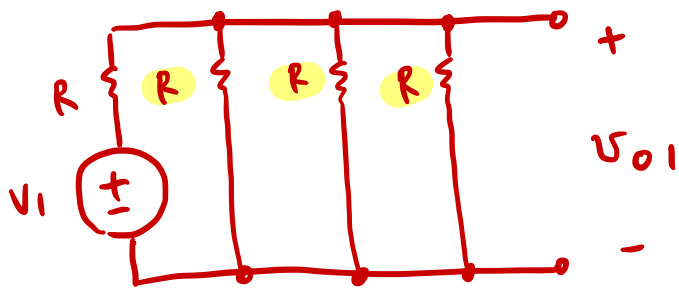1) Partial response due to V_1 ($V_2 = V_3 = V_4 = 0$)



$$V_{01} = \frac{\frac{1}{3} R}{R + \frac{1}{3} R} \cdot V_1 = \frac{1}{4} V_1$$

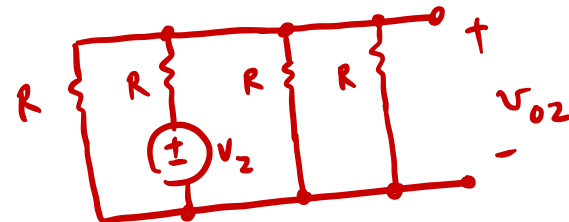2) Partial response due to V_2 , $V_{02} = \frac{1}{4} V_2$



3) $V_{03} = \frac{1}{4} V_3$

4) $V_{04} = \frac{1}{4} V_4$

Total $V_0 = V_{01} + V_{02} + V_{03} + V_{04}$

$$= \frac{1}{4} (V_1 + V_2 + V_3 + V_4)$$



Yet Another Method?


□ Arbitrary network

$$v = \sum_m \alpha_m V_m + \sum_n \beta_n I_n + Ri$$

depends only on the network N.
independent of i .

α : no unit

β : Ω

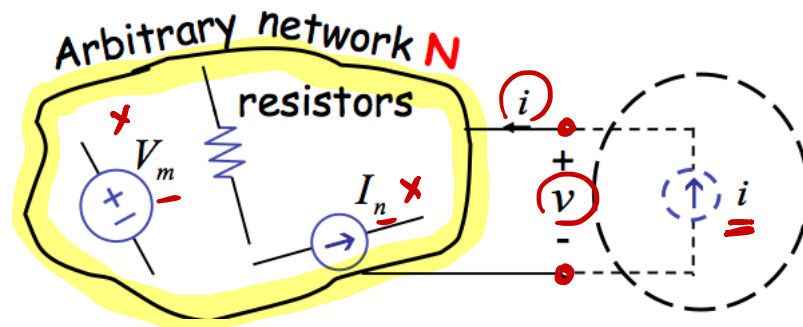

where all $V_m = 0, I_n = 0$


1. Independent of external excitation and behave like a voltage.
 - Let's call it ' v_{TH} '
2. Independent of external excitation and behave like a resistor.
 - Let's call it ' R_{TH} '



Arbitrary Network

$$v = \sum_m \alpha_m V_m + \sum_n \beta_n I_n + Ri$$
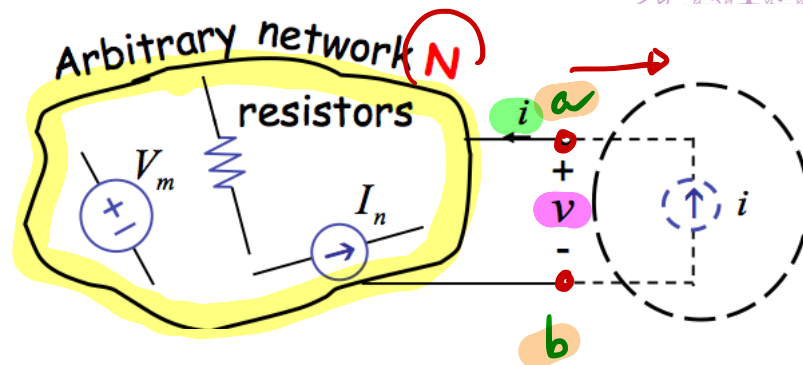
$$v = \underbrace{V_{TH} + R_{TH} \cdot i}$$



- In other words, as far as the external world is concerned (for the purpose of the $i-v$ relation), 'arbitrary network N ' is indistinguishable from:

