
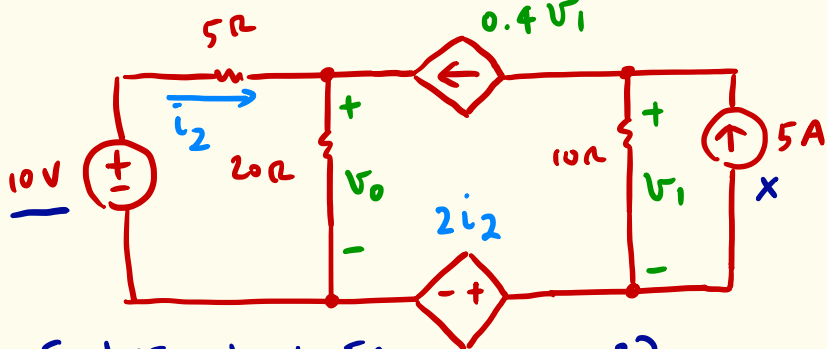


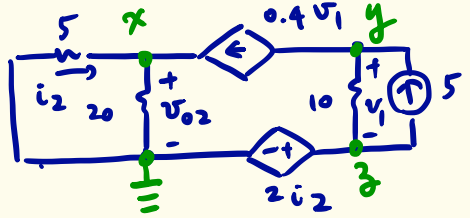- Example. Use superposition. Find  $V_o$ .



- 2) Find  $V_{o2}$  due to 5A source.




KCL @ x:  $\frac{V_x}{5} + \frac{V_x}{20} - 0.4V_1 = 0$

@ y:  $0.4V_1 + \frac{V_1}{10} - 5 = 0$


$V_3 = 2i_2 = 2 \cdot \frac{-V_x}{5} \Rightarrow V_{o2} = 16V$

- 3) Total response  
 $V_o = V_{o1} + V_{o2}$   
 $= 8 + 16$   
 $= 24V$

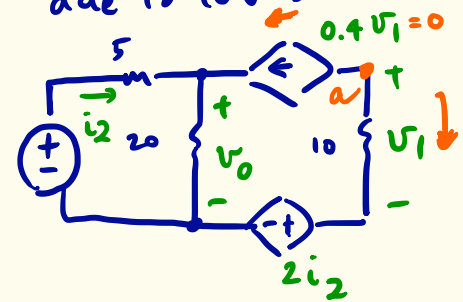- 1) Find partial response  $V_{o1}$  due to 10V source.



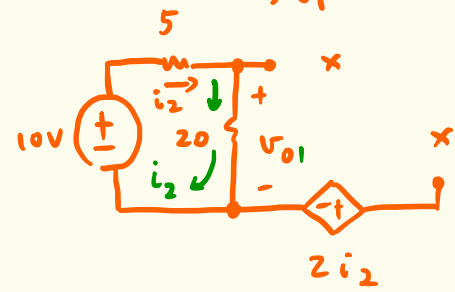KCL @ a:  $0.4V_1 + \frac{V_1}{10} = 0$   
 $\Rightarrow V_1 = 0$



$i_2 = \frac{10}{(5+20)} = 0.4A$ ,  $V_{o1} = 0.4 \times 20 = 8V$



# Yet Another Method?


□ Arbitrary network

$$v = \sum_m \alpha_m V_m + \sum_n \beta_n I_n + Ri$$

depends only on the network N.  
independent of  $i$ .

$\alpha$  : no unit

$\beta$  :  $\Omega$

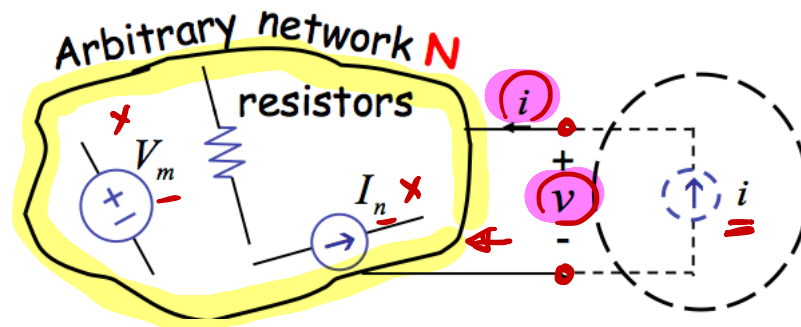

where all  $V_m = 0, I_n = 0$


1. Independent of external excitation and behave like a voltage.
  - Let's call it ' $v_{TH}$ '
2. Independent of external excitation and behave like a resistor.
  - Let's call it ' $R_{TH}$ '



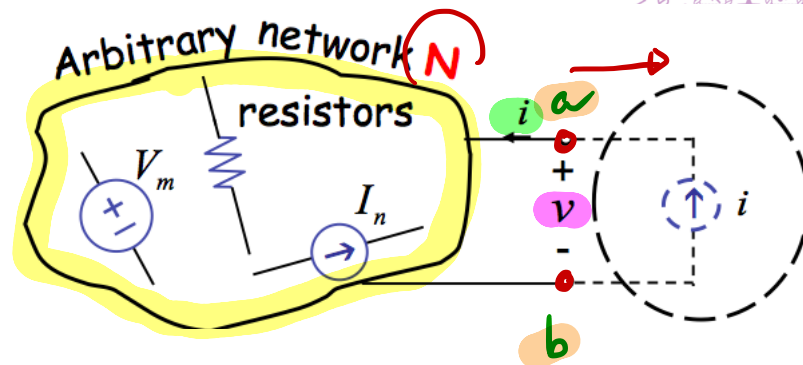
# Arbitrary Network

$$v = \sum_m \alpha_m V_m + \sum_n \beta_n I_n + Ri$$

$$v = \underbrace{V_{TH} + R_{TH} \cdot i}$$




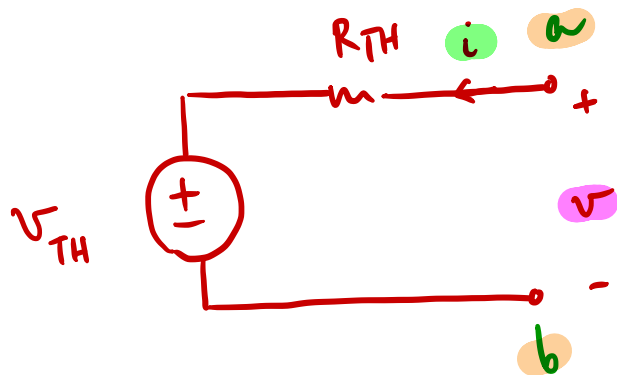
- In other words, as far as the external world is concerned (for the purpose of the  $i-v$  relation), 'arbitrary network  $N$ ' is indistinguishable from:





# Arbitrary Network

$$v = v_{TH} + R_{TH} \cdot i$$

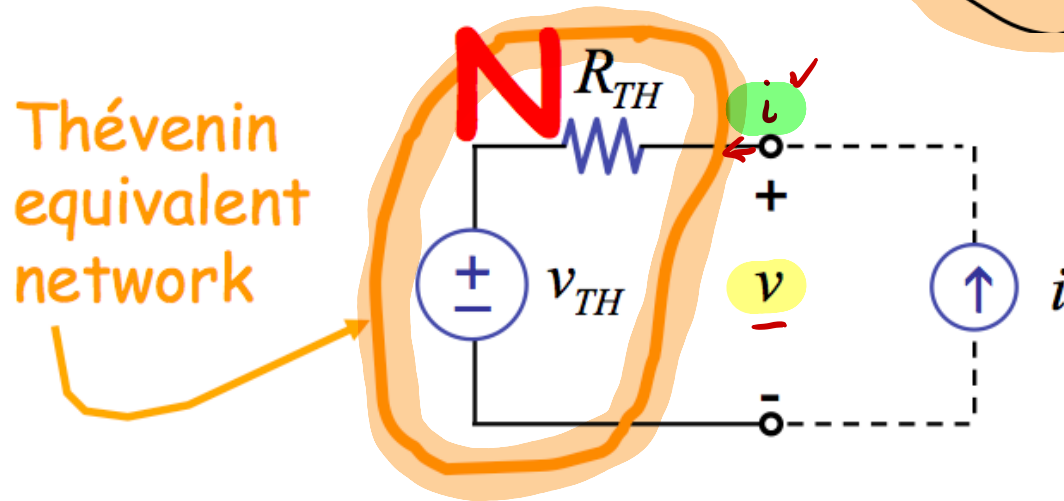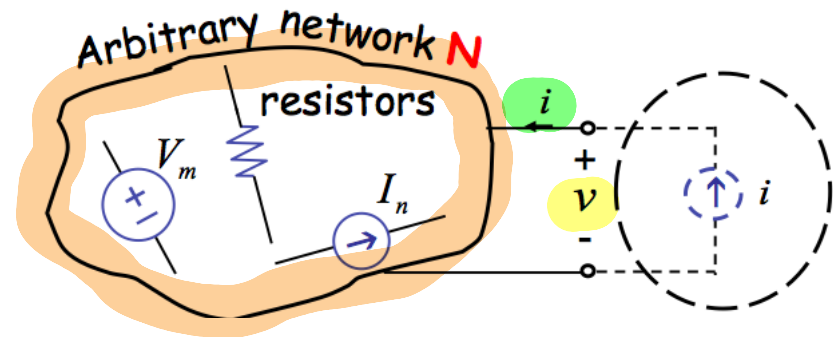


$$v_{TH} = v_{open}, \quad i = 0$$

- How to derive  $v_{TH}$  and  $R_{TH}$ ?
- $v_{TH} \rightarrow$  Open circuit voltage seen at terminal pair (aka port).
- $R_{TH} \rightarrow$  Resistance of network seen from port (with  $V_m$ 's and  $I_n$ 's set to 0).

$$R_{TH} = \frac{v}{i} \text{ when independent sources} = 0$$




# Method 6: The Thévenin Method

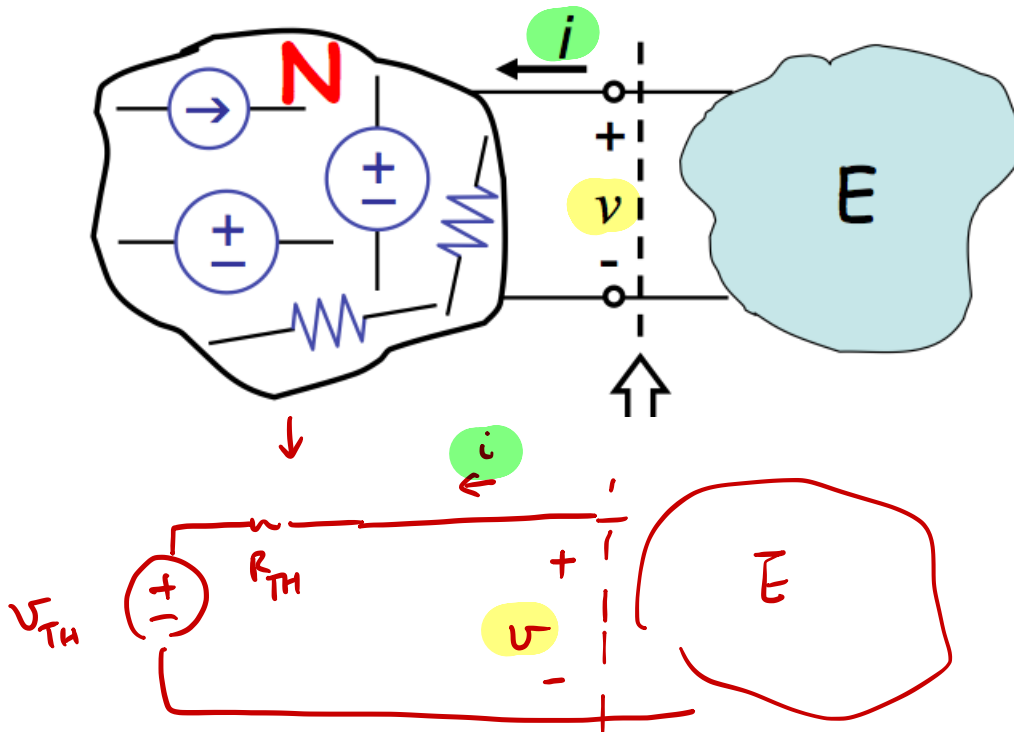


- Replace network  $N$  with its Thévenin equivalent
- Solve with external network  $E$




# Example – Using Thévenin Method

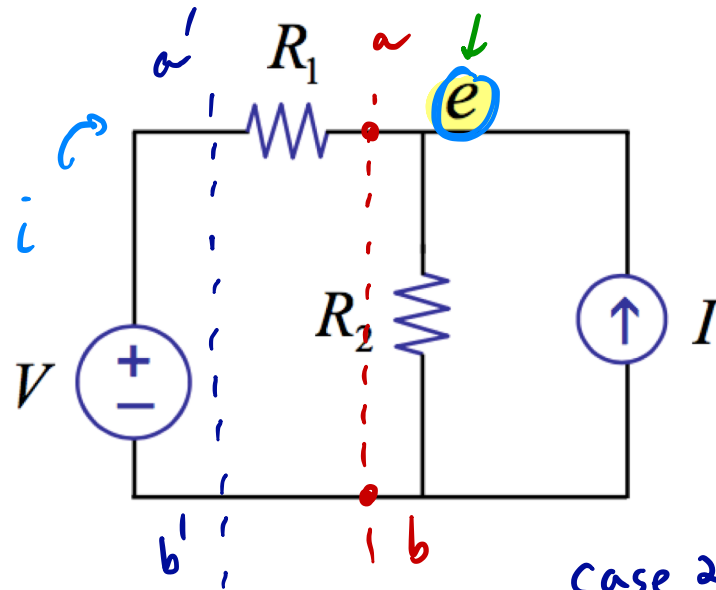

Case 1.

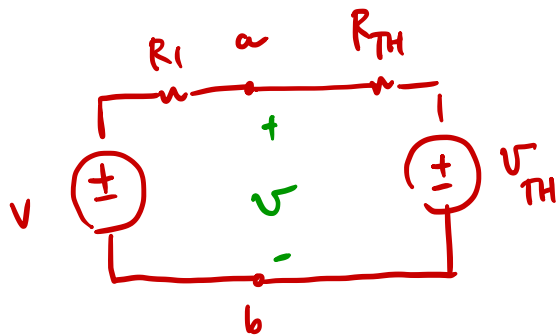


Case 2

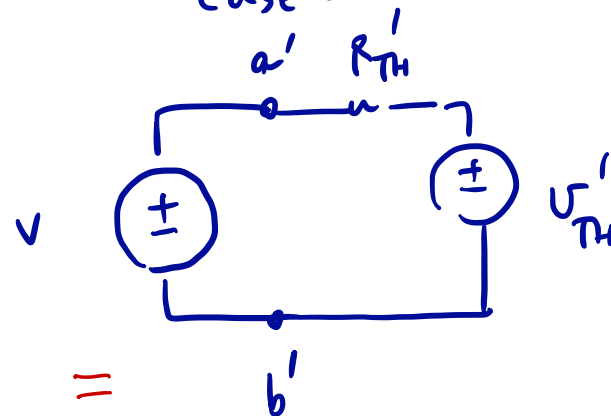




# Example – Using Thévenin Method


## Case 1

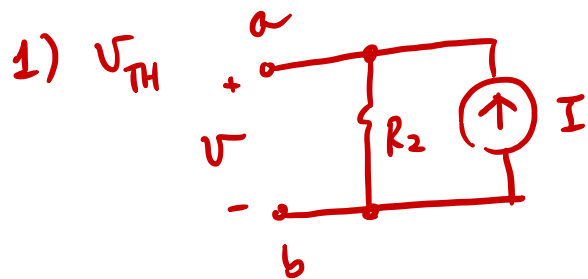


$$V_{TH} = I \cdot R_2$$

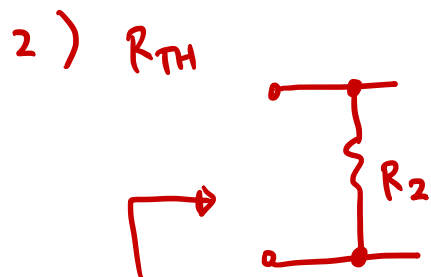

$$R_{TH} = R_2$$

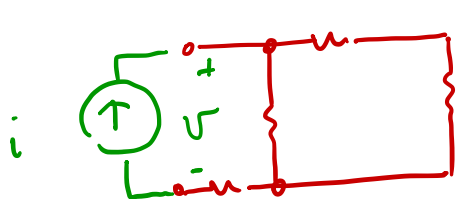

$$\frac{V}{i} = R_{TH}$$

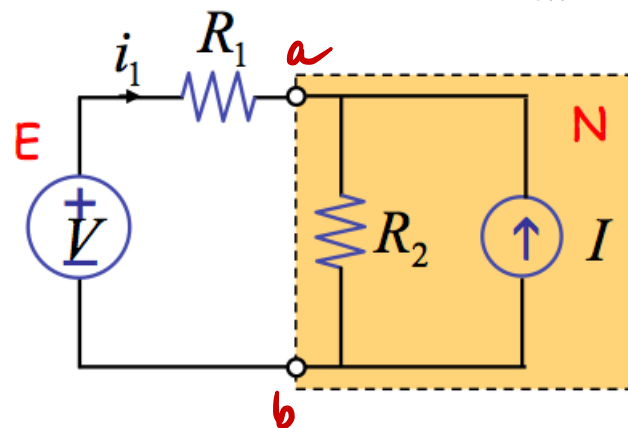


$$V_{TH} = IR_2$$
$$R_{TH} = R_2$$




# Example – Using Thévenin Method

## Case 2

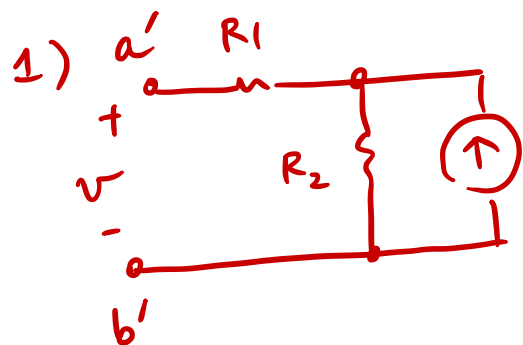


$$V'_{TH} = R_2 \cdot I$$

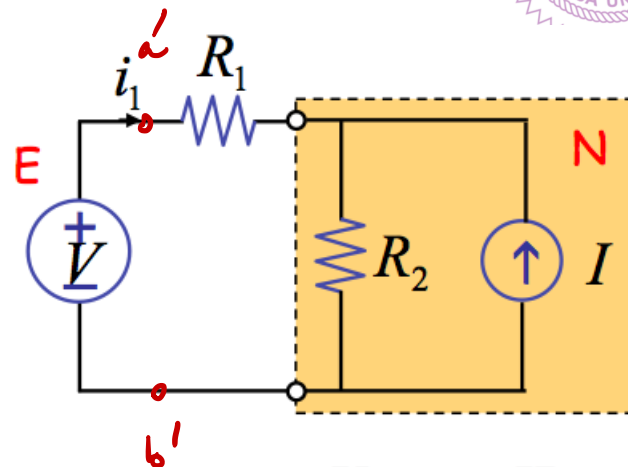

~~$$V_{TH} = IR_2$$~~  
~~$$R_{TH} = R_2$$~~

2)  $R_{TH} = R_1 + R_2$

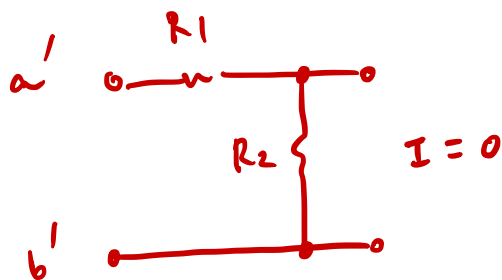







# Example – Using Thévenin Method

- Solve with external network E

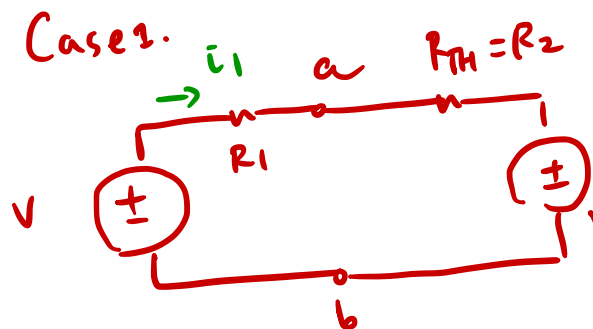


$$i_1 = \frac{V - V_{TH}}{R_1 + R_{TH}} = \frac{V - I \cdot R_2}{R_1 + R_2}$$

$$V_a = V - i_1 \cdot R_1$$

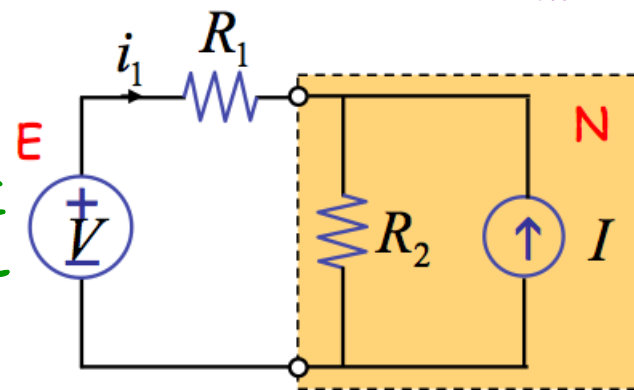

$$V_{TH} = I R_2$$

$$R_{TH} = R_2$$

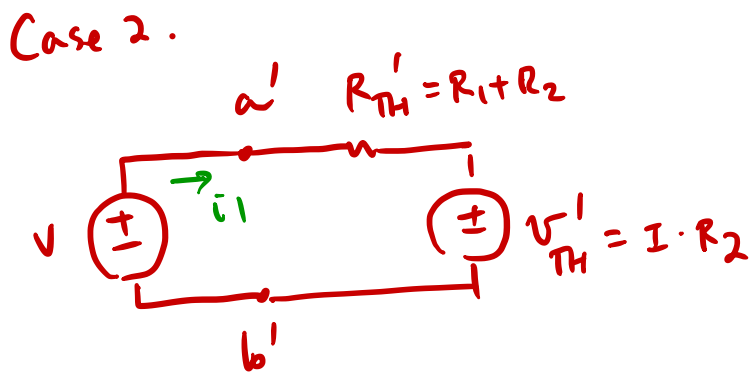


$$i_1 = \frac{V - V'_{TH}}{R'_{TH}} = \frac{V - I \cdot R_2}{R_1 + R_2}$$




# Example – Using Thévenin Method

- Graphically...

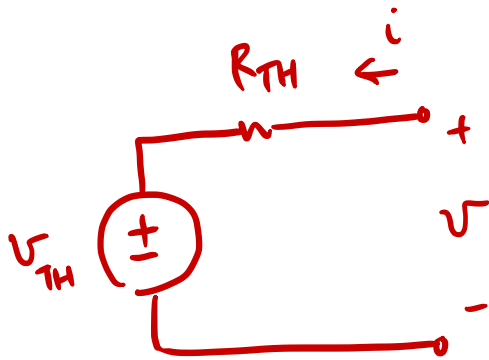


$$V = V_{TH} + R_{TH} \cdot i$$

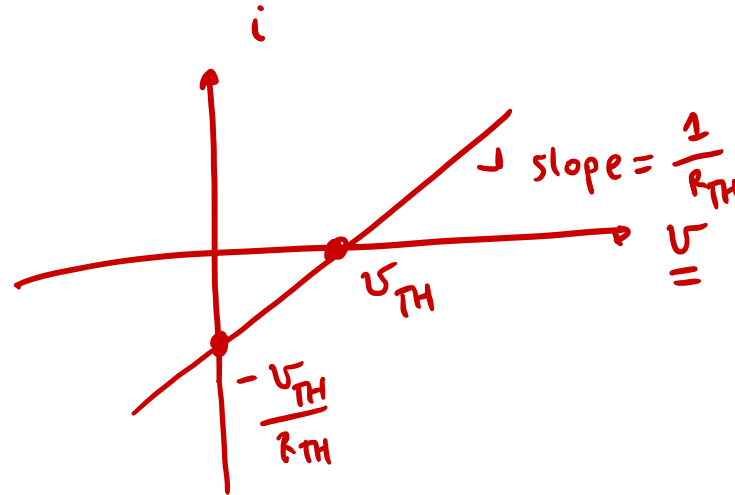

*i - V characteristic*



# Method 7: The Norton Method

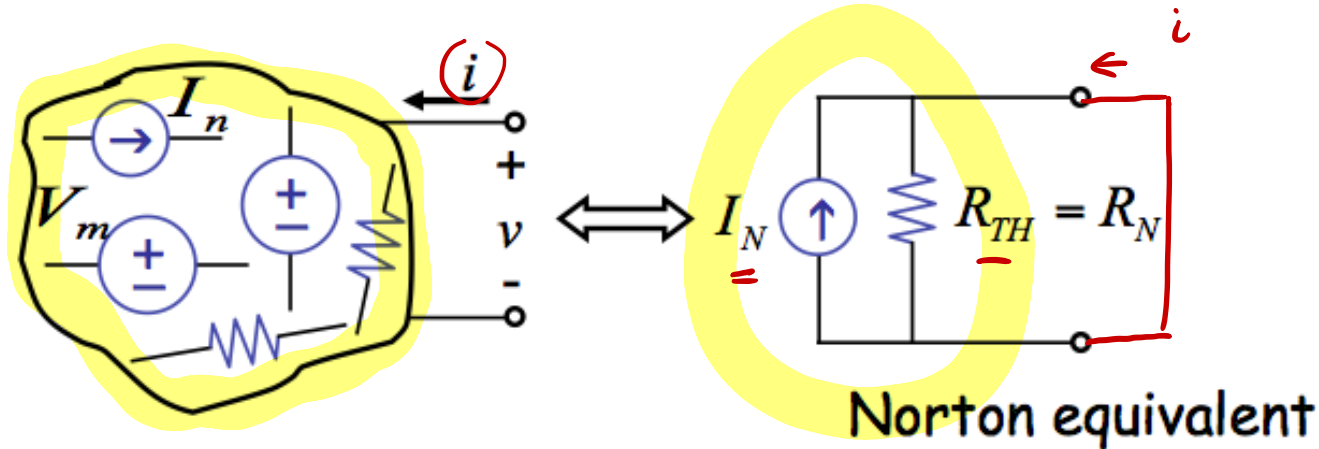



•  $I_N$ : short circuit current,  $I_N = -i$

•  $R_N = R_{TH}$

Resistance of network seen from the port when all independent sources = 0.



# Thévenin and Norton

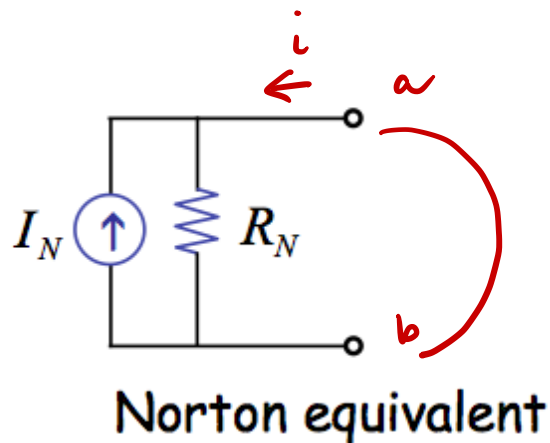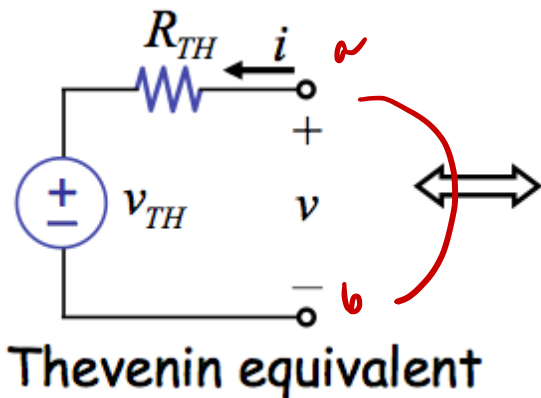

Equivalent  
resistance

$$R_{TH}$$

$$= R_N$$

open-circuit  
voltage,  $V_{oc}$

$$V_{TH}$$

$$= I_N \cdot R_N$$

Short-circuit  
current,  $i_{sc}$



$$-\frac{V_{TH}}{R_{TH}}$$

$$= -I_N$$


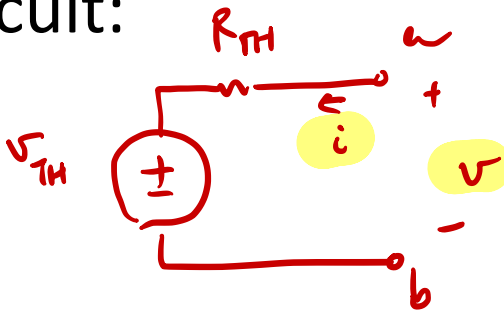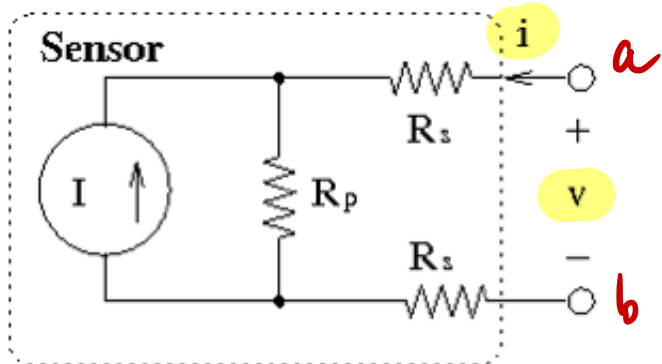
# Example – Thévenin and Norton


- A light sensor is modeled as a current source that produces a current proportional to the intensity of light.
  - Leakage through the sensor is modeled as  $R_p$ .
  - Resistance in the contacts (wires) is modeled as  $R_s$ .
- Thévenin equivalent circuit:



$$V_{TH} = I \cdot R_p$$

$$R_{TH} = 2R_s + R_p$$


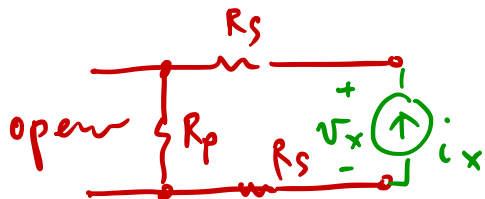
$$V_x = i_x (R_s + R_p + R_s) \Rightarrow R_{TH} = \frac{V_x}{i_x}$$






# Example – Thévenin and Norton

- Norton equivalent circuit:

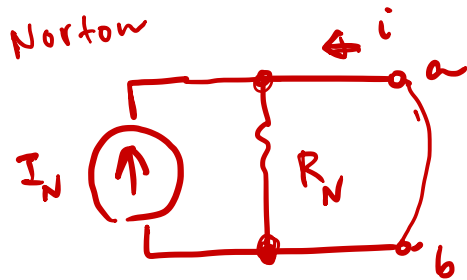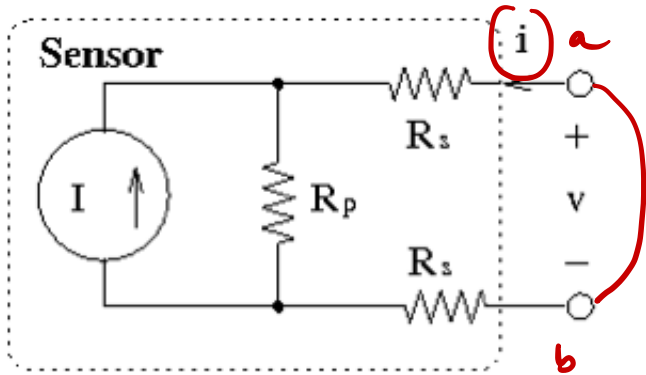

$$I_N = -i = -I \cdot \frac{R_p}{R_p + 2R_s}$$

$$R_N = 2R_s + R_p$$

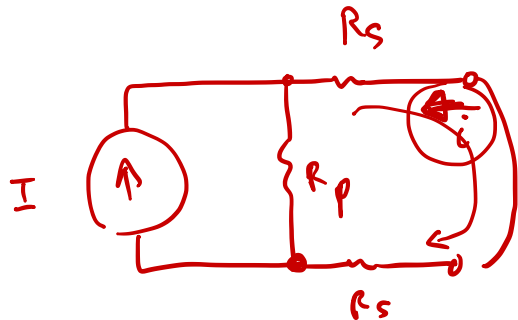



# Summary


## □ Basic circuit analysis methods

- KCL, KVL
  - Element combination rules
  - Node method
  - Mesh method
  - Superposition
  - Thévenin
  - Norton
- For all circuits*
- For linear circuits only*


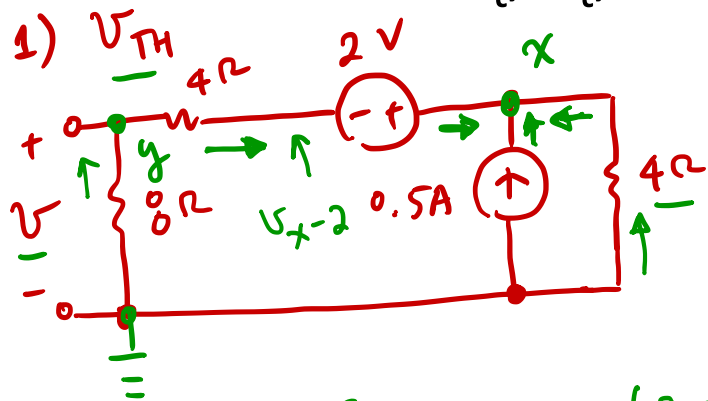
# Problem 5.2-1



□ Determine  $R_t$ ,  $v_t$ , and  $i_a$ .




KCL @ x: 
$$\frac{-v_x}{4} + 0.5 + \frac{v_{TH} - (v_x - 2)}{4} = 0$$

@ y: 
$$\frac{v_{TH}}{8} + \frac{v_{TH} - (v_x - 2)}{4} = 0$$
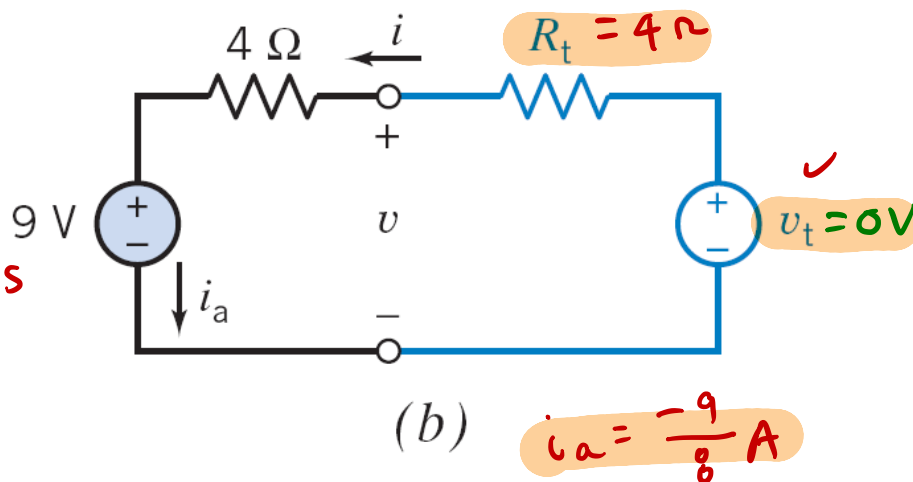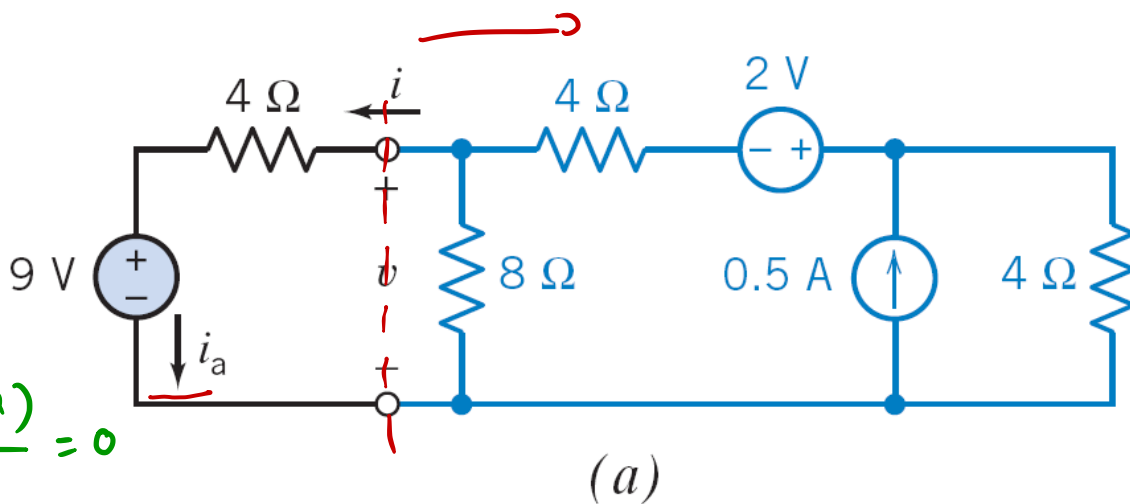
$$\Rightarrow v_x = 2V, v_y = v_{TH} = 0V$$



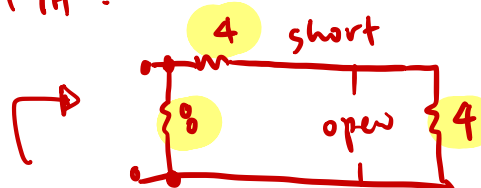2)  $R_{TH}$ : turn OFF all independent sources



$$R_{TH} = (4+4) \parallel \infty = 4\Omega$$