



Inductor i - v Behaviors

- Its voltage v depends on the time-varying rate of current i .

$$v = L \cdot \frac{di}{dt}$$

- Steady state characteristics

- The inductor is a short circuit to DC signal at steady state.

$$\frac{di}{dt} = 0, \quad v = 0$$

- The inductor is an open circuit to high frequency signals at steady state.

$$\frac{di}{dt} \rightarrow \infty, \quad v \rightarrow \infty$$


Assume

$$i_L = I_0 \cdot \sin \omega t, \quad v = L \cdot \omega \cdot I_0 \cdot \cos \omega t$$

As $\omega \rightarrow \infty, v \rightarrow \infty$

similar to an open circuit

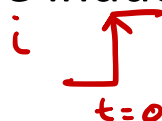- The current through an inductor does not change abruptly.
 - A discontinuous change of the inductor current requires an infinite voltage.



Summary


i_L



	R	C	L
$v - i$	$v_R = i_R \cdot R$	$v_C = v_C(t_0) + \frac{1}{C} \int_{t_0}^t i_C \cdot dt$	$v_L = L \frac{di}{dt}$
$i - v$	$i_R = \frac{v_R}{R}$	$i_C = C \frac{dv}{dt}$	$i_L = i_L(t_0) + \frac{1}{L} \int_{t_0}^t v_L \cdot dt$
Power, Energy	$P_R = i_R^2 \cdot R = \frac{v_R^2}{R}$	$E_C = \frac{1}{2} C \cdot v_C^2$	$E_L = \frac{1}{2} L \cdot i_L^2$
Series	$R_{eq} = \sum R_k$	$\rightarrow \frac{1}{C_{eq}} = \sum \frac{1}{C_k}$	$L_{eq} = \sum L_k$
<u>Parallel</u>	$\frac{1}{R_{eq}} = \sum \frac{1}{R_k}$	$C_{eq} = \sum C_k$	$\frac{1}{L_{eq}} = \sum \frac{1}{L_k}$
DC steady state	(same)	open-circuit $\frac{dv}{dt} = 0, i = 0$	short-circuit $\frac{di}{dt} = 0, v = 0$
High freq. HF steady state	(same)	short-circuit $\frac{dv}{dt} \rightarrow \infty, i \rightarrow \infty$	open-circuit $\frac{di}{dt} \rightarrow \infty, v \rightarrow \infty$
Continuity	(no restriction)	v_C	i_L

Series and Parallel Inductors

$$v = L \cdot \frac{di}{dt}$$

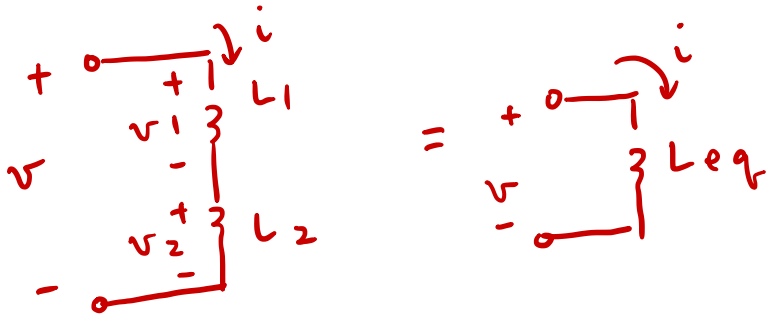


$$v = v_1 + v_2$$

$$= L_1 \frac{di}{dt} + L_2 \frac{di}{dt}$$

$$= (L_1 + L_2) \frac{di}{dt} = L_{eq} \cdot \frac{di}{dt}$$

$$\Rightarrow L_{eq} = L_1 + L_2$$

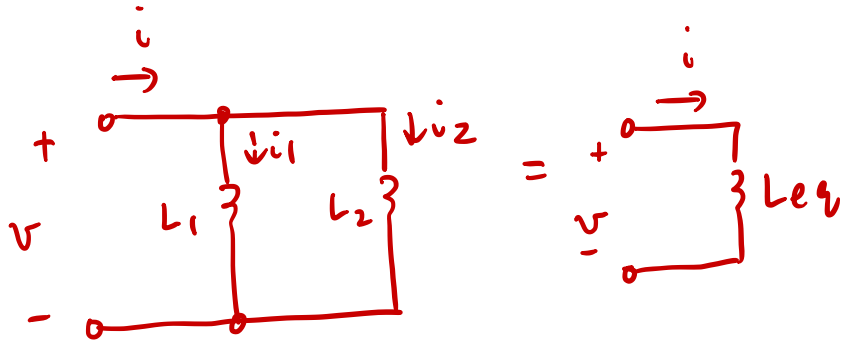

$$v = L_{eq} \cdot \frac{di}{dt} = L_{eq} \frac{d(i_1 + i_2)}{dt}$$

$$= L_{eq} \left(\frac{v}{L_1} + \frac{v}{L_2} \right)$$

$$\Rightarrow L_{eq} = \frac{1}{\frac{1}{L_1} + \frac{1}{L_2}}$$