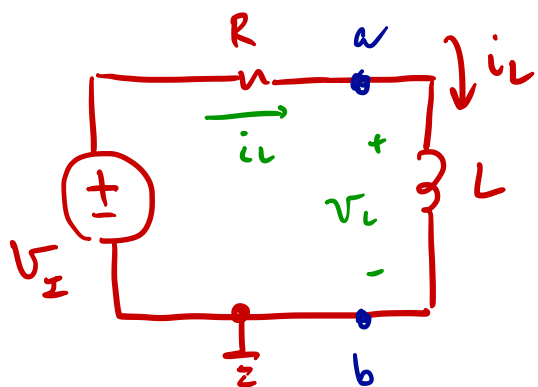




# RL Circuit in Series with a Voltage Source



Given  $V_I(t) = V_I u(t) = \begin{cases} V_I, & t \geq 0 \\ 0, & t < 0 \end{cases}$

$i_L(t=0) = 0A$

Find  $i_L(t)$  for  $t \geq 0$ .

KVL:  $V_I - i_L \cdot R - L \cdot \frac{di_L}{dt} = 0$

1) Particular: assume  $i_{L,p} = K$ ,  $V_I - K \cdot R - L \cdot 0 = 0$

$\Rightarrow K = \frac{V_I}{R}$

2) Homogeneous: assume  $i_{L,h} = A \cdot e^{st}$

$Ae^{st} \cdot R + L \cdot A \cdot s \cdot e^{st} = 0 \Rightarrow R + L \cdot s = 0 \Rightarrow s = -\frac{R}{L}$

$i_{L,h} = A e^{-R/L \cdot t}$

3) Total solution  $i_L = \frac{V_I}{R} + A e^{-R/L \cdot t}$

$i_L(t=0) = 0 = \frac{V_I}{R} + A \Rightarrow A = -\frac{V_I}{R}$

$i_L(t) = \frac{V_I}{R} - \frac{V_I}{R} e^{-R/L \cdot t}$

$i_L(t=0) = 0A$

$i_L(t \rightarrow \infty) = \frac{V_I}{R}$

$L \rightarrow$  short

$i_L(t) = \frac{V_I}{R} + \left[0 - \frac{V_I}{R}\right] \cdot e^{-t/\tau}$

$\tau = L/R$

o RC, RL

$$\checkmark x(t) = \underline{x(\infty)} + \left[ \underline{x(0) - x(\infty)} \right] \cdot e^{-t/\tau}$$

$\tau$ : time constant


$$\tau = R \cdot C, \quad \frac{L}{R}$$

Examples.


Given  $i_L = 20t e^{-2t}$  A for  $t > 0$

$$i_L(0) = 0$$

Find  $V_L$ , power, energy.

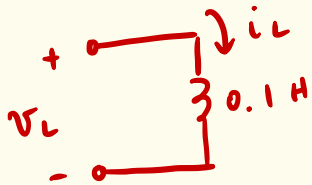

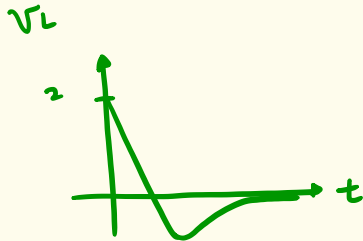
$$V_L = 0.1 \frac{di_L}{dt} = 0.1 \cdot 20 (-2te^{-2t} + e^{-2t}) = 2e^{-2t}(1-2t)$$



$$\begin{aligned} P &= i_L \cdot V_L = 20t e^{-2t} \cdot 2e^{-2t}(1-2t) \\ &= 40t \cdot e^{-4t} \cdot (1-2t) \text{ W, } t > 0 \end{aligned}$$

$$\begin{aligned} \text{Energy} &= \frac{1}{2} \cdot L \cdot i^2 = \frac{1}{2} \cdot 0.1 \cdot 400t^2 \cdot e^{-4t} \\ &= 20t^2 \cdot e^{-4t} \text{ J, } t > 0 \end{aligned}$$

Example 2.

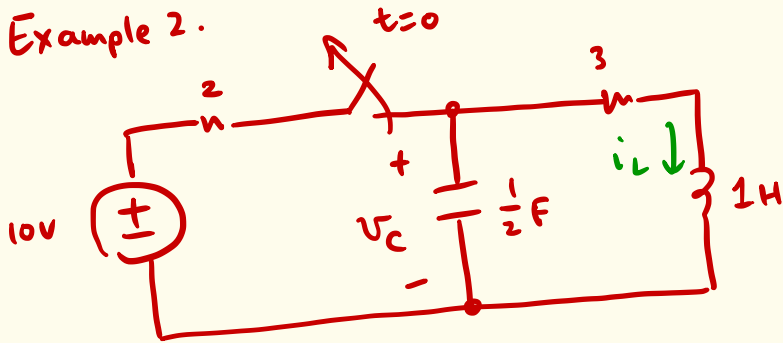


Find  $i_L(t^+)$ ,  $V_C(t^+)$

$$i_L(t^+) = i_L(t^-) \checkmark$$

$$V_C(t^+) = V_C(t^-) \checkmark$$

$t < 0$

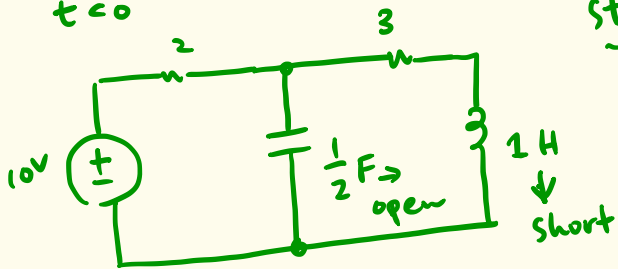


Steady-state for  $t < 0$

$$\frac{dV_C}{dt} = 0, \quad \frac{di_L}{dt} = 0$$



$$i_L(t^-) = \frac{10}{2+3} = 2 \text{ A} = i_L(t^+)$$
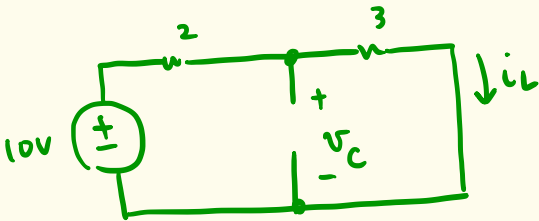
$$V_C(t^-) = \frac{10}{2+3} \times 3 = 6 \text{ V} = V_C(t^+)$$



Example.  $V_C(t=0) = -20V$ , Find  $V_C(t)$  at  $t = 1ms, 2ms, 5ms$ . ✓

Power, energy

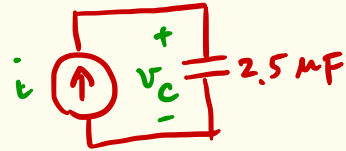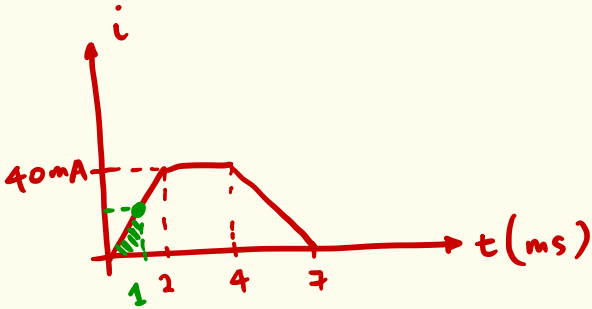


$$V_C(t) = V_C(0) + \frac{1}{C} \cdot \int_0^t i(\tau) d\tau = -20 + \frac{1}{2.5 \times 10^{-6}} \cdot \underbrace{\int_0^t i(\tau) d\tau}_{\text{area}}$$


$$V_C(t=1ms) = -20 + \frac{1}{2.5 \times 10^{-6}} \times \frac{1}{2} \times 1m \times 20m$$
$$= -16V$$

Example 4. Practice


\* Series / parallel of R, L, C

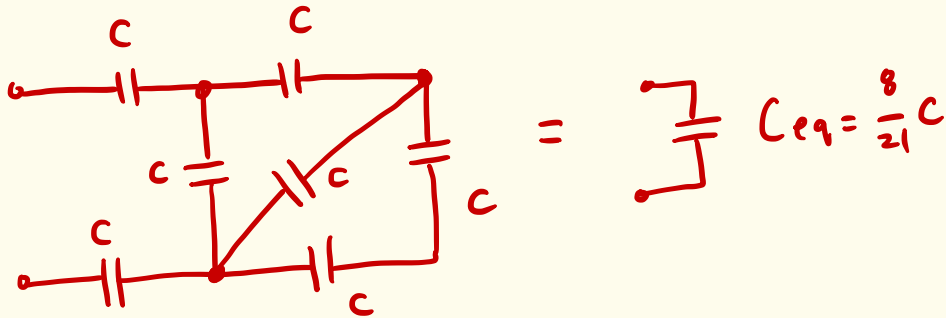

Example 5.

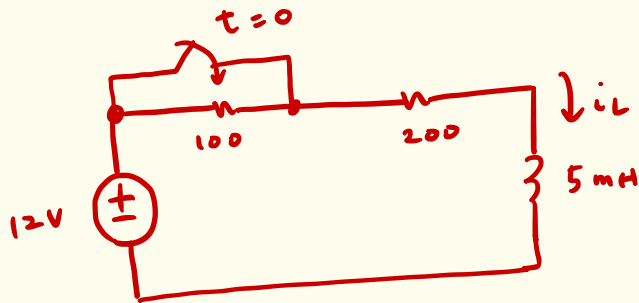

Find  $i_L(t)$  for  $t > 0$ .

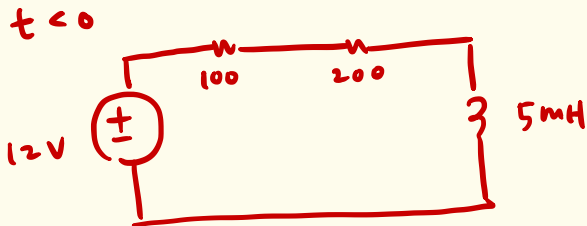


$$V_L = 0$$

$$i_L = \frac{12}{100 + 200} = 40 \text{ mA}$$

$$i_L(0^-) = i_L(0^+) = \underline{40 \text{ mA}}$$

$t > 0$

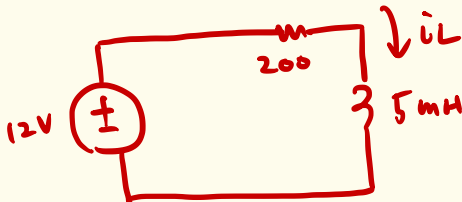

$$\text{KVL: } V_L + i_L \cdot 200 = 12, \quad V_L = 5 \text{ m} \cdot \frac{di_L}{dt}$$

$$\Rightarrow 5 \text{ m} \cdot \frac{di_L}{dt} + 200 \cdot i_L = 12$$

$$i_L(t \rightarrow \infty) = \frac{12}{200} = 60 \text{ mA}$$

$$5 \text{ m} \cdot \frac{di_L}{dt} + 200 i_L = 12 \quad \checkmark$$

① Particular: assume  $i_{L,p} = K$ ,  $5 \text{ m} \cdot 0 + 200 \cdot K = 12$ ,  $\Rightarrow i_{L,p} = \frac{12}{200} = 0.06$

② Homogeneous, assume  $i_{L,h} = A e^{st}$ ,  $5 \text{ m} \cdot A \cdot s \cdot e^{st} + 200 \cdot A e^{st} = 0$

$$5 \text{ m} \cdot s + 200 = 0 \Rightarrow s = -40000$$

③ Total solution  $i_L = 0.06 + A e^{-40000t}$

$$i_L(t=0^+) = 40 \text{ m} = 0.06 + A \Rightarrow A = -0.02$$

$$i_L(t) = 0.06 - 0.02 \cdot e^{-40000t} \quad A$$


$$i_L(t) = 0.06 + (0.04 - 0.06) \cdot e^{-t/\tau}$$

$$\tau = \frac{L}{R} = \frac{5 \text{ m}}{200}$$



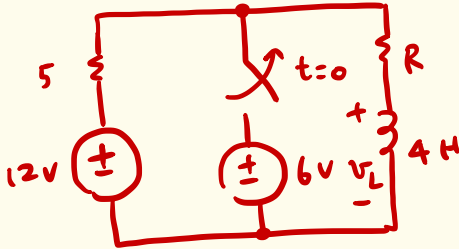Example 6.

Given  $v_L$ , Find  $v_L$ ,  $R$ ,  $i_L$




①

$$v_L = \begin{cases} 0 & t < 0 \\ 4e^{-at}, & t \geq 0 \end{cases} \checkmark$$

$$2 = 4e^{-a \cdot 0.14} \Rightarrow a = 5$$



②  $t > 0$

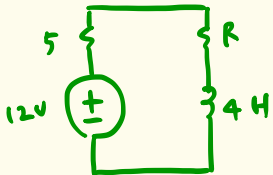

$$v_L = 0 + (4 - 0) \cdot e^{-t/\tau}, \quad \tau = \frac{4}{5+R} = \frac{1}{5} \Rightarrow R = 15$$

$$i_L(t) = i_L(\infty) + [i_L(0) - i_L(\infty)] \cdot e^{-t/\tau}$$

$$\tau = \frac{L}{R}$$

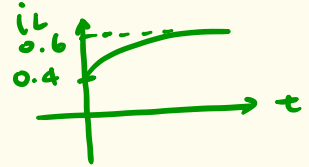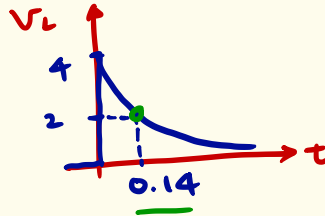

$$\begin{aligned} \textcircled{3} \quad i_L &= \frac{1}{L} \int_0^t v_L dt + i(0) \\ &= \frac{1}{4} \int_0^t 4e^{-5t} dt + 0.4 \\ &= \underline{0.6 - 0.2e^{-5t}} \end{aligned}$$

Practice  $i_L(0)$   
 $i_L(\infty)$