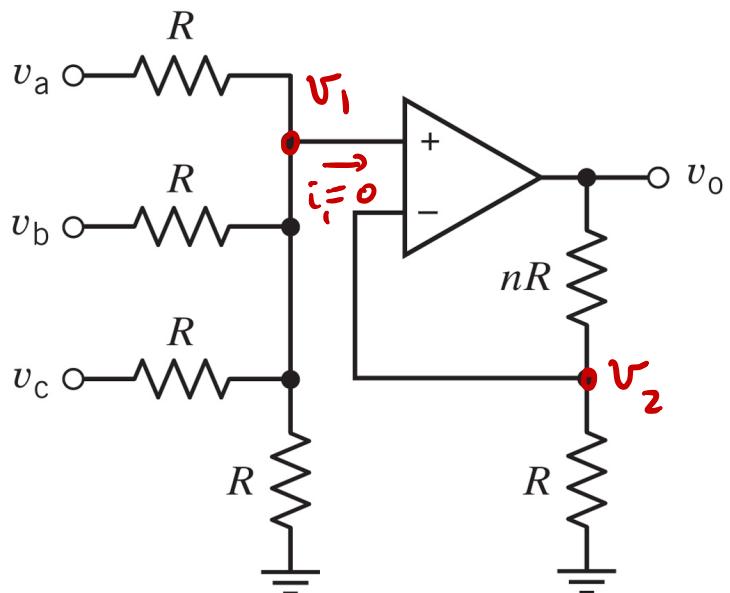





Voltage Summer

From
 $v_1 = v_2$



FCL @ v_1
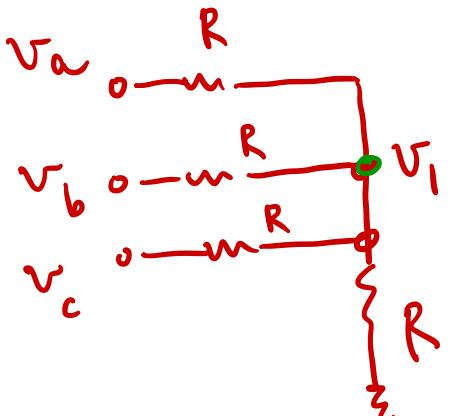
$$\frac{v_a - v_1}{R} + \frac{v_b - v_1}{R} + \frac{v_c - v_1}{R} = \frac{v_1}{R}$$




$$\Rightarrow v_0 = \left(\frac{1}{4} v_a + \frac{1}{4} v_b + \frac{1}{4} v_c \right) (n+1)$$

$$\text{FCL: } \frac{v_0 - v_2}{nR} + \frac{0 - v_2}{R} = 0$$

$$\Rightarrow v_0 = v_2 (n+1)$$

$$= v_1 (n+1)$$

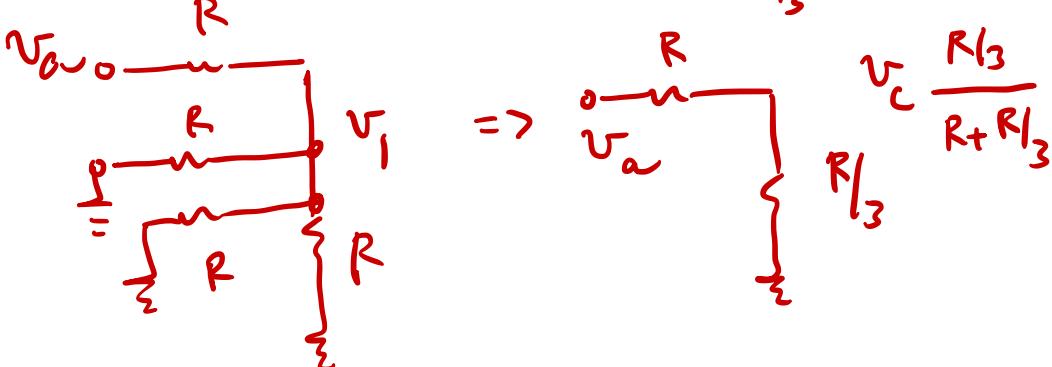
Use superposition: $v_1 = v_a \frac{R_{l3}}{R+R_{l3}} + v_b \frac{R_{l3}}{R+R_{l3}} + v_c \frac{R_{l3}}{R+R_{l3}}$



$$v_1 = \frac{1}{4} v_a + \frac{1}{4} v_b + \frac{1}{4} v_c$$

Example 1

□ Find v_o and i_o .

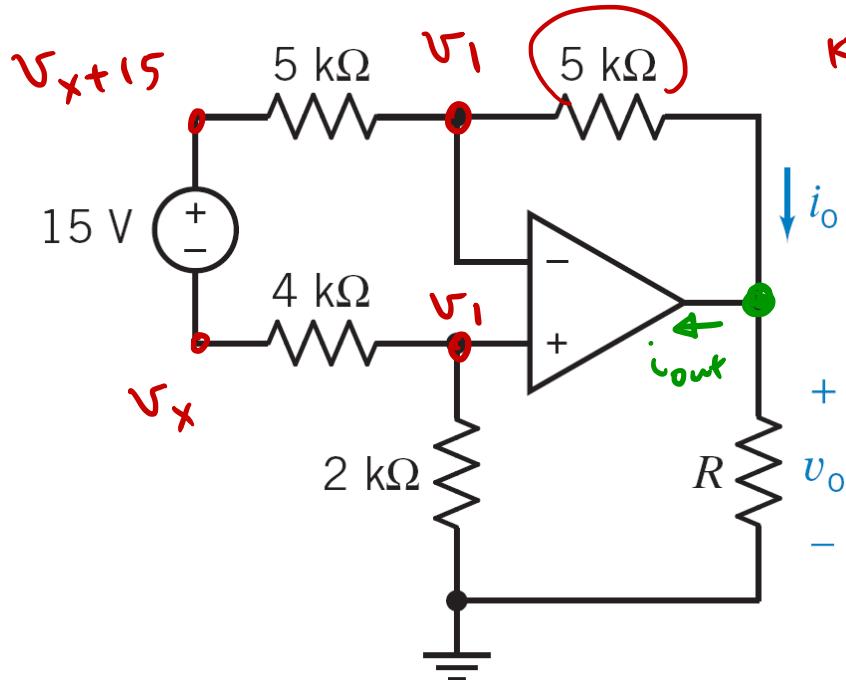

$$\text{KCL at } V_+: \frac{V_x - V_1}{4\text{k}} + \frac{0 - V_1}{2\text{k}} = 0$$

$$\Rightarrow V_x = 3V_1$$

$$\text{KCL at } V_-: \frac{V_x + 15 - V_1}{5\text{k}} + \frac{V_o - V_1}{5\text{k}} = 0$$

$$\Rightarrow V_o = -V_1 - 15$$

@ 15V
 Superode: $\frac{V_1 - V_x - 15}{5\text{k}} + \frac{0 - V_1}{2\text{k}} = 0$


$$\Rightarrow V_1 = \frac{-10}{3} \text{ V}, V_o = -\frac{-10}{3} - 15 = -11.6 \text{ V}$$

$$i_o = \frac{V_1 - V_o}{5\text{k}} = 1.67 \text{ mA}$$

$$i_{out} = i_o + \frac{-V_o}{R}$$

Example 2

- Find v_o and i_o .

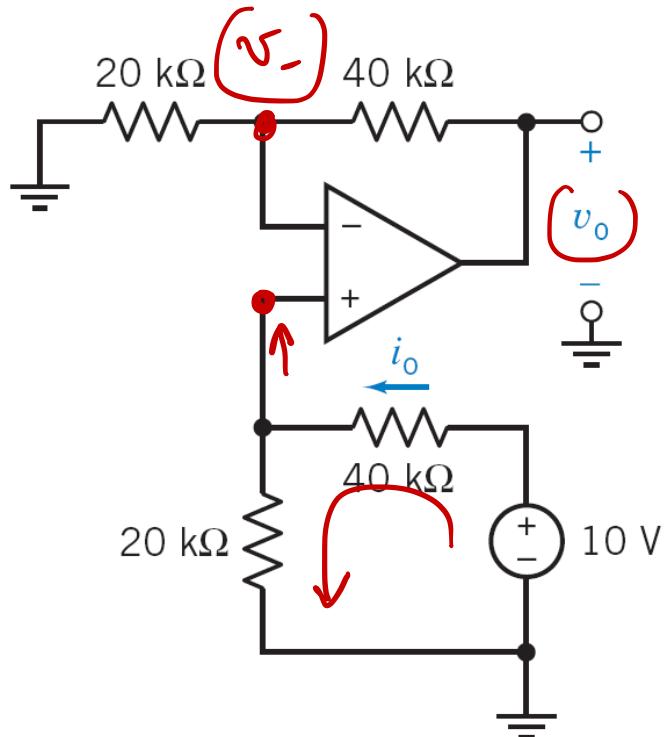

$$i_o = \frac{10}{20\text{k} + 40\text{k}} = 0.167 \text{ mA}$$

$$V_f = V_- = 10 \times \frac{20\text{k}}{20\text{k} + 40\text{k}} = \frac{10}{3} \text{ V}$$

KCL:

$$\frac{v_o - V_-}{40\text{k}} + \frac{0 - V_-}{20\text{k}} = 0$$



$$\Rightarrow v_o = 5 \cdot V_- = 10 \text{ V}$$



Design Example 1

- Design the operational amplifier such that $v_{out} = \underline{\underline{30}}$
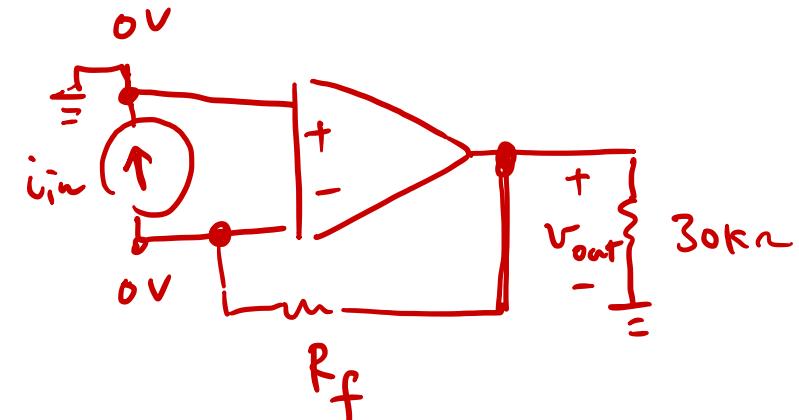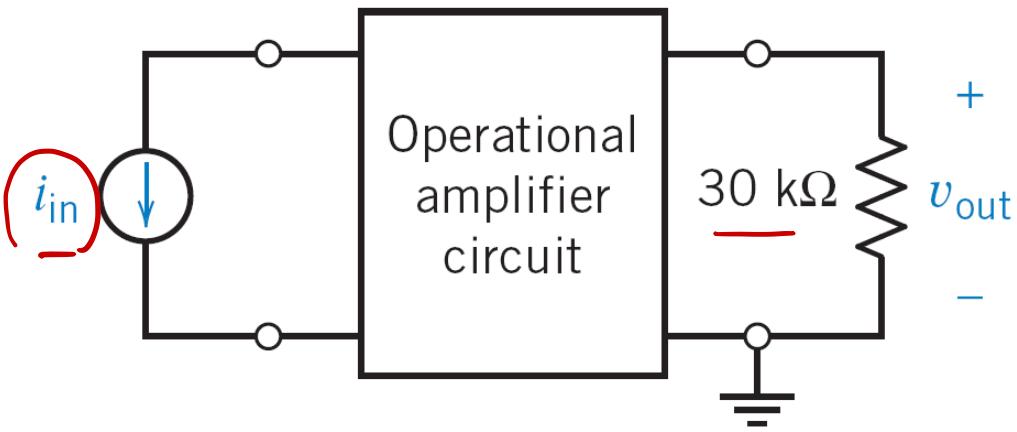
$$V/mA * i_{in} = 30 \times 10^3 \frac{V}{A} \cdot i_{in}$$



$$i_{in} = \frac{v_{out} - 0}{R_f} \Rightarrow \frac{v_{out}}{i_{in}} = R_f = 30\text{ k}\Omega$$



Design Example 2

- Design the operational amplifier such that $v_{out} = \underline{5*v_1 + 2*v_2}$.

