



Electric Circuits

Lecture 7 Impulses, Steps, and Ramps

EE2210, Fall 2022

Jenny Yi-Chun Liu

jennyliu@gapp.nthu.edu.tw



Lecture Outline


- RC and RL (Chapter 7 and 8 in the textbook)
 - Steps
 - Impulses
 - Ramp




A Step Function

unit step function


$$v_I(t) = u(t)$$

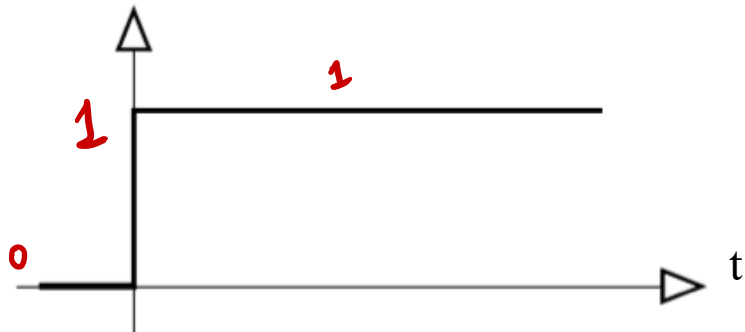




$$V(t) = A \cdot u(t)$$

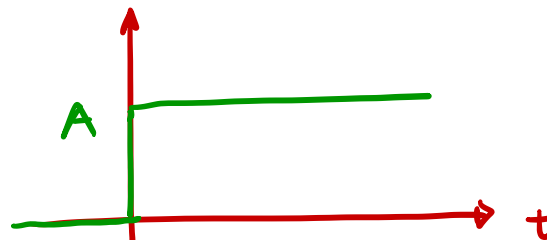

$$v_I(t) = u(t - t_0)$$

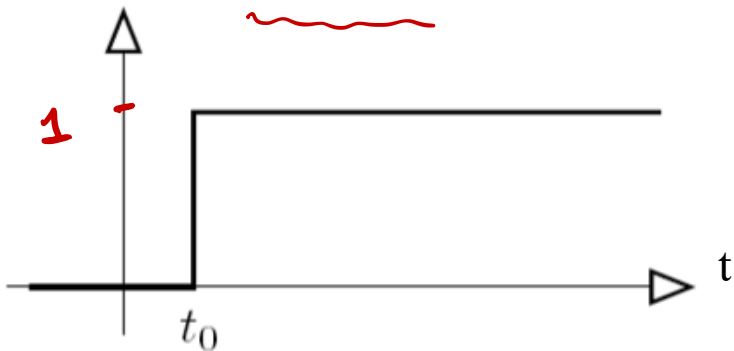


$$V(t) = A(1 - u(t + t_0))$$

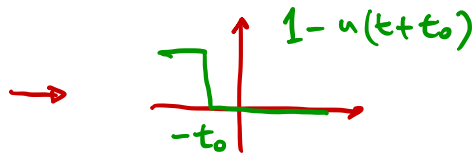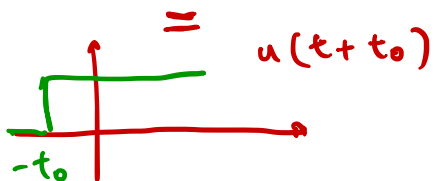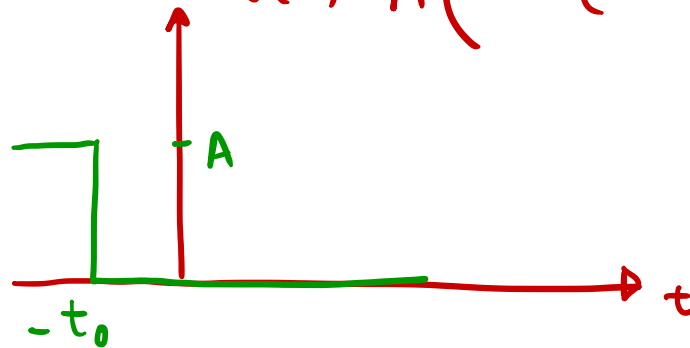




Rising Step Response of RC Circuit

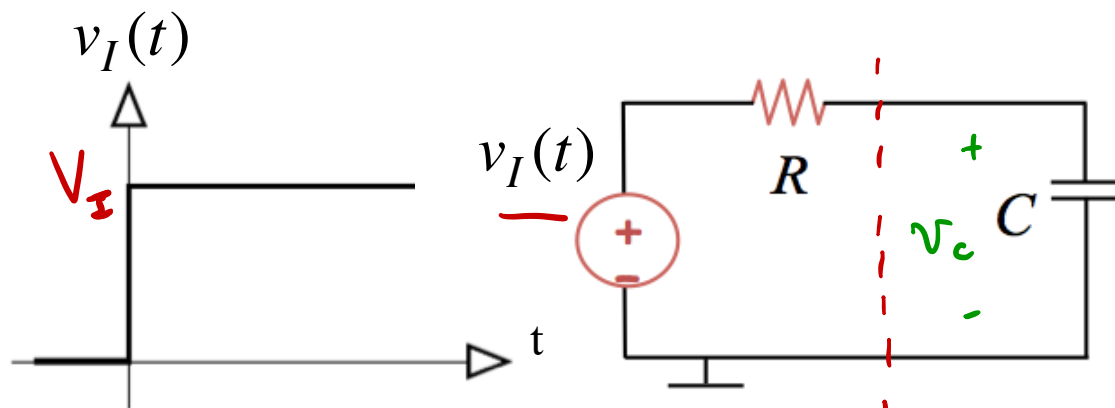




Given $v_I(t)$ or $i_I(t)$
 and $v_C(t=0) = 0$,
 then
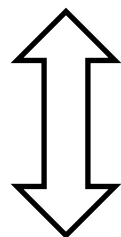
$$v_C(t) = V_I \cdot (1 - e^{-t/RC})$$
 for $t > 0$.



Thévenin form
 Norton form

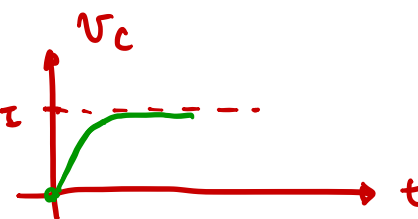
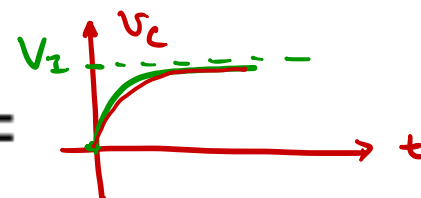
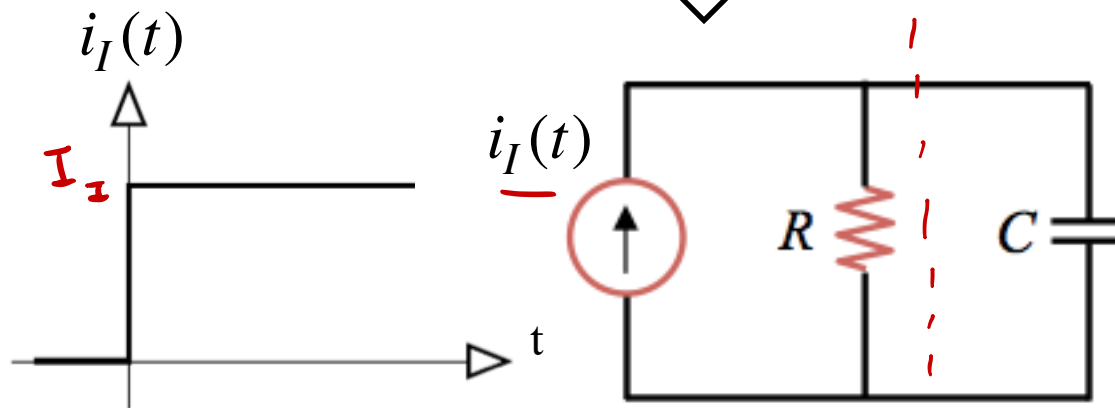
$$\left(\begin{array}{l} v_{C,f} = V_I \quad \tau = RC \\ v_{C,i} = 0 \\ v_C = V_I + (0 - V_I) \cdot e^{-t/RC} \end{array} \right)$$



• Both are zero-state response for $t > 0$ (initial value, $v_C(0) = 0$)
 $I_I \cdot R = V_I$



Falling Step Response of RC Circuit

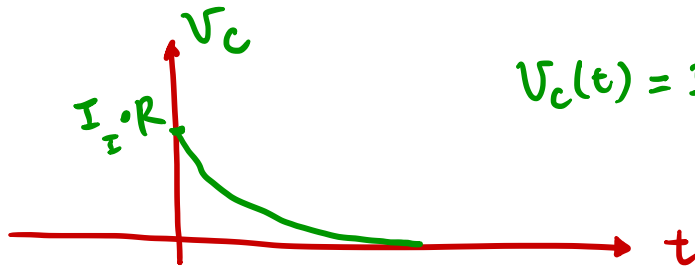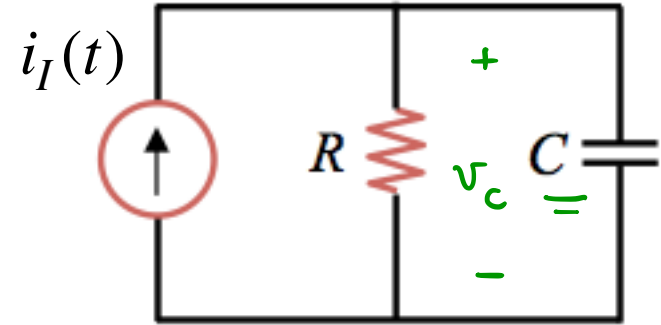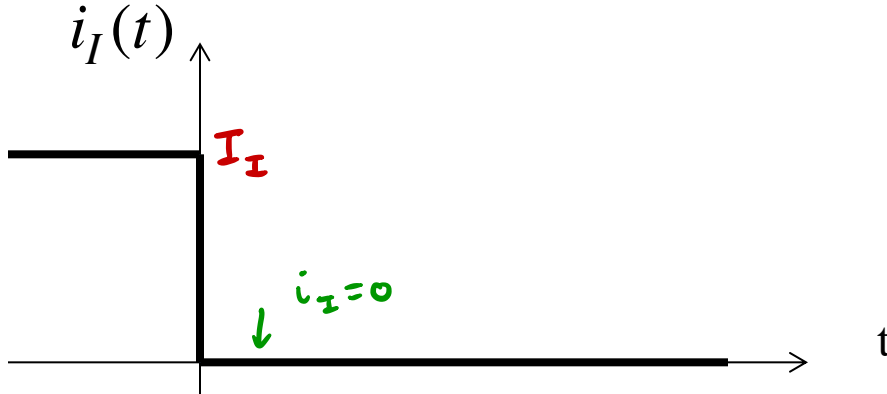




$$V_C(t) = \underline{I_I \cdot R} \cdot e^{-t/RC}, \quad t > 0$$

- zero-input response for $t > 0$
($i_I(t) = 0$ for $t > 0$)



Pulse Input for RC Circuit

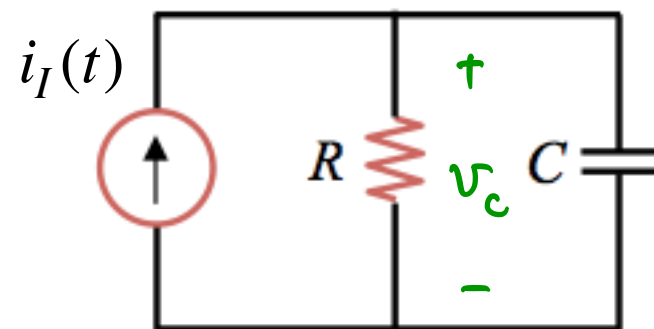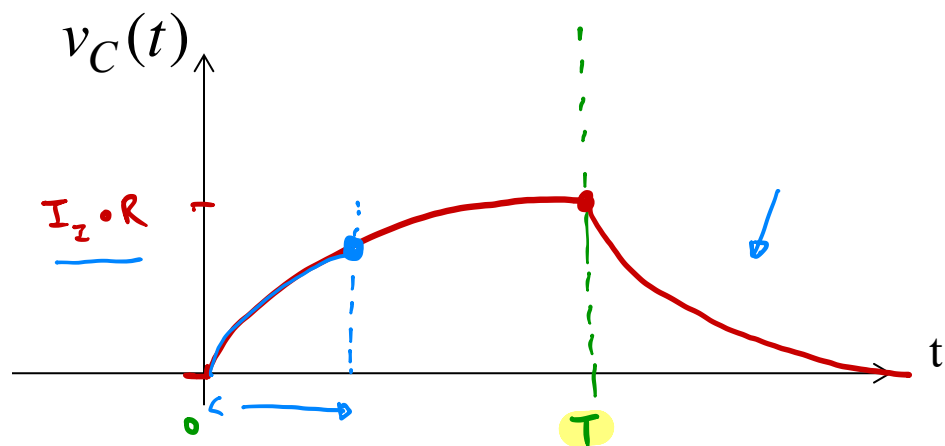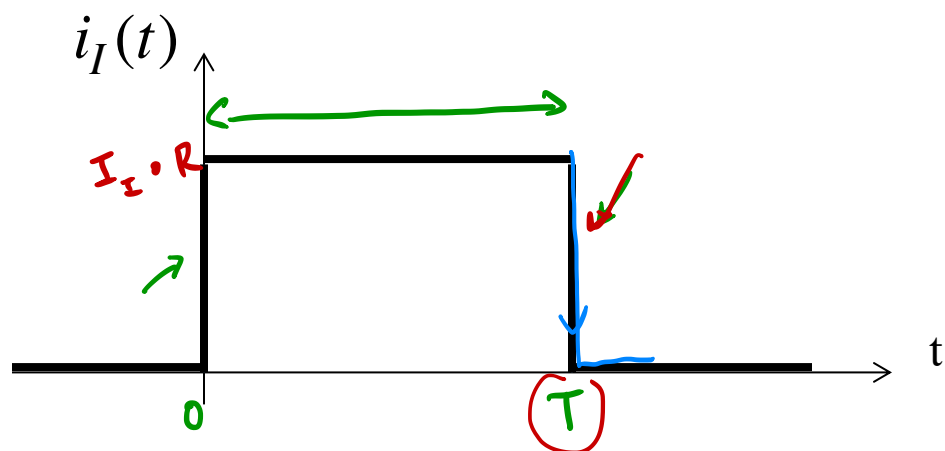- Rising step followed by falling step (much later)!
- Pulse width T much larger than time constant RC .



$$v_C(t) = 0, \quad t < 0$$




$$v_C(t) = I_2 \cdot R \cdot (1 - e^{-t/RC}), \quad 0 \leq t < T$$

$$v_C(t) = I_2 \cdot R \cdot e^{-(t-T)/RC}, \quad t \geq T$$



Short Pulse Input to RC Circuit

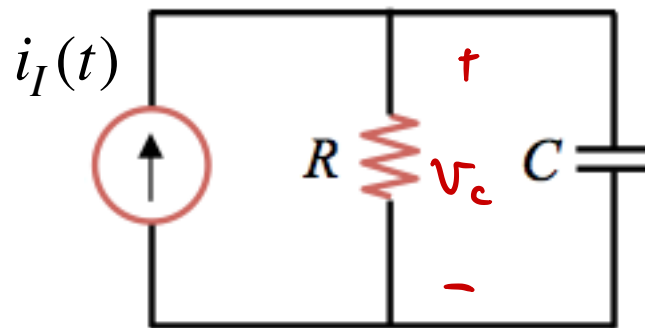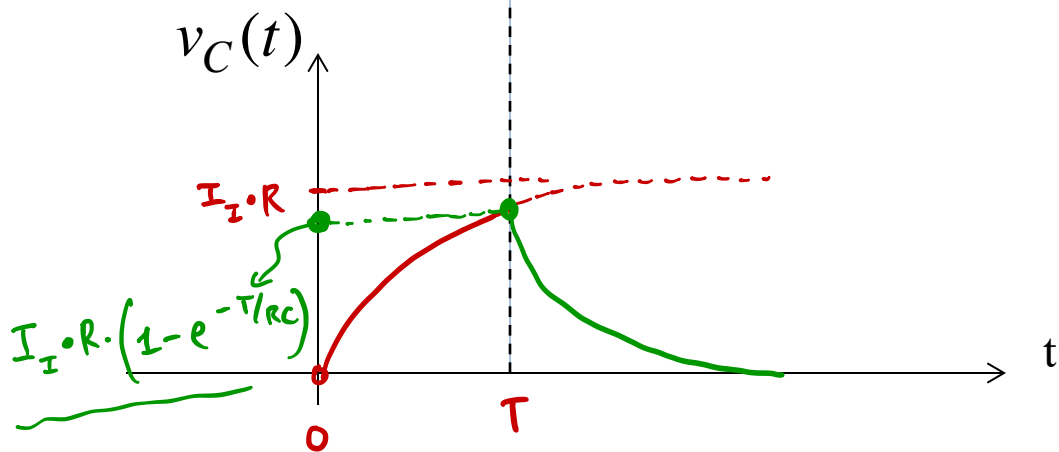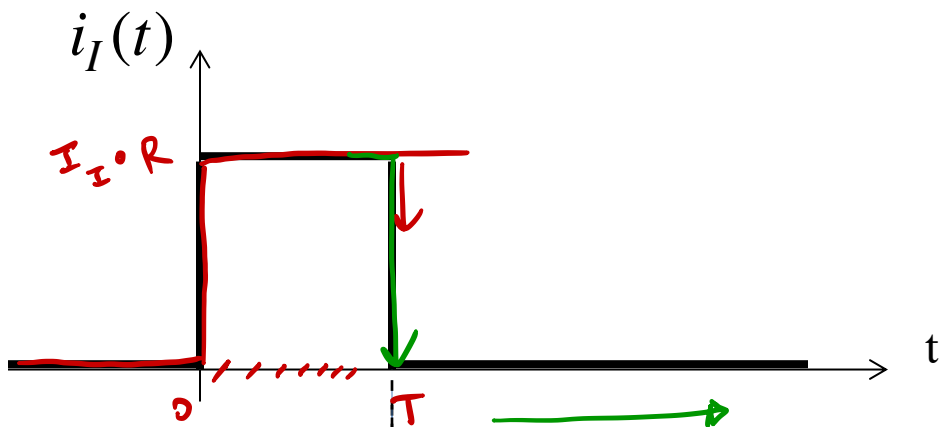- Rising step followed by falling step (shortly thereafter)!



$$v_C(t) = 0, \quad t < 0$$

$$v_C(t) = I_I \cdot R \cdot (1 - e^{-t/RC})$$

$$0 \leq t < T,$$

$$v_C(t) = I_I \cdot R \cdot (1 - e^{-T/RC}) \cdot e^{-(t-T)/RC}$$



initial condition at $t=T$




Let's Stare at Current Pulse

- Current pulse delivers charges.

$$Q = I_2 \cdot T$$

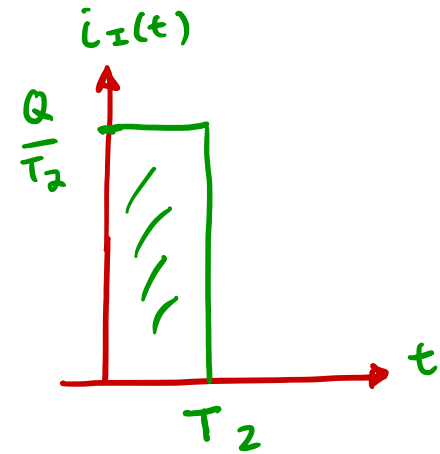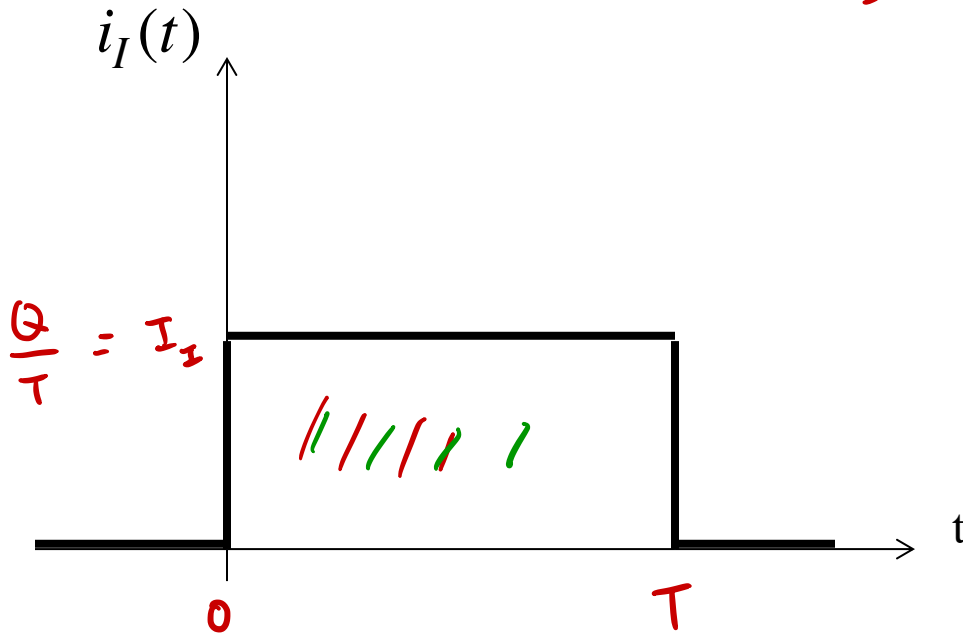
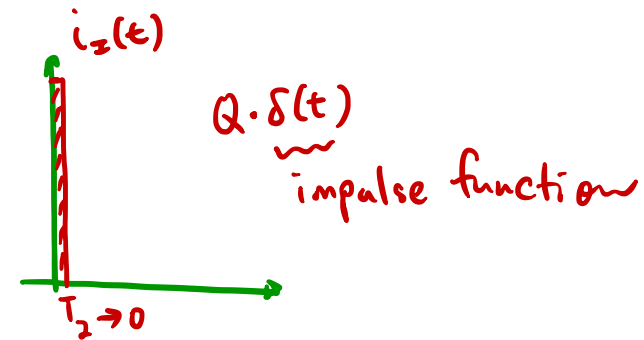
$$T_2 \rightarrow 0 \quad \frac{Q}{T_2} \rightarrow \infty$$





- Pulse becomes impulse as $T \rightarrow 0$

- Denoted as $Q \cdot \delta(t)$




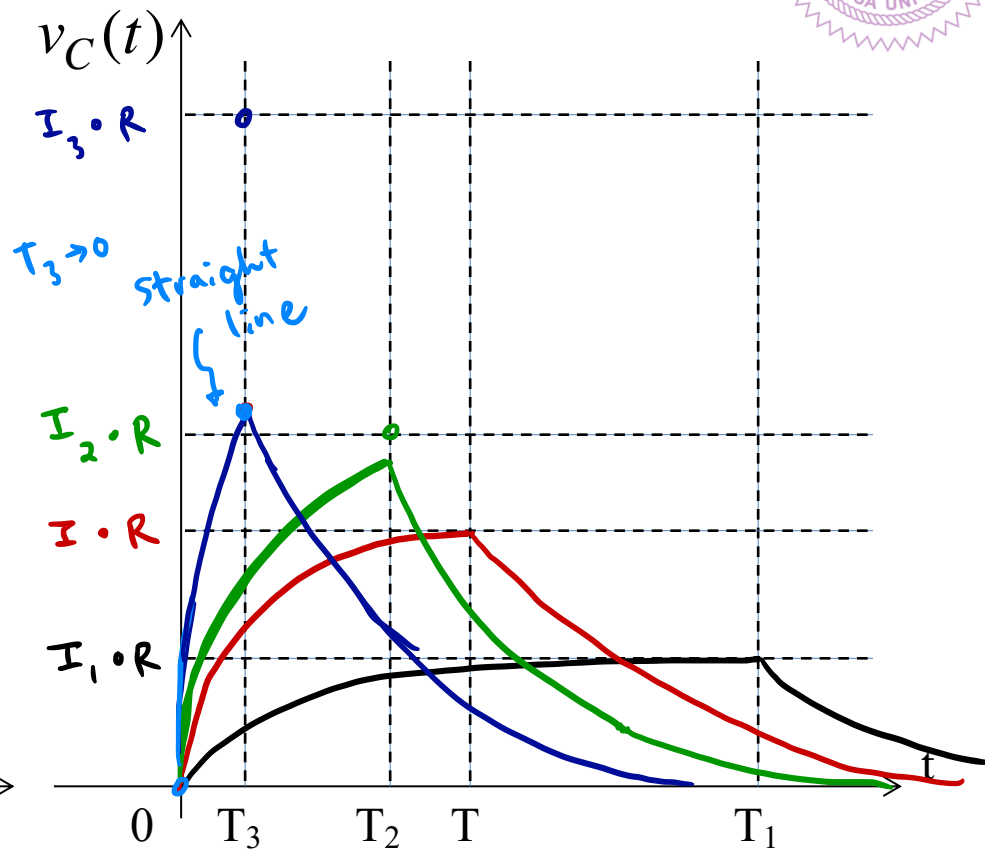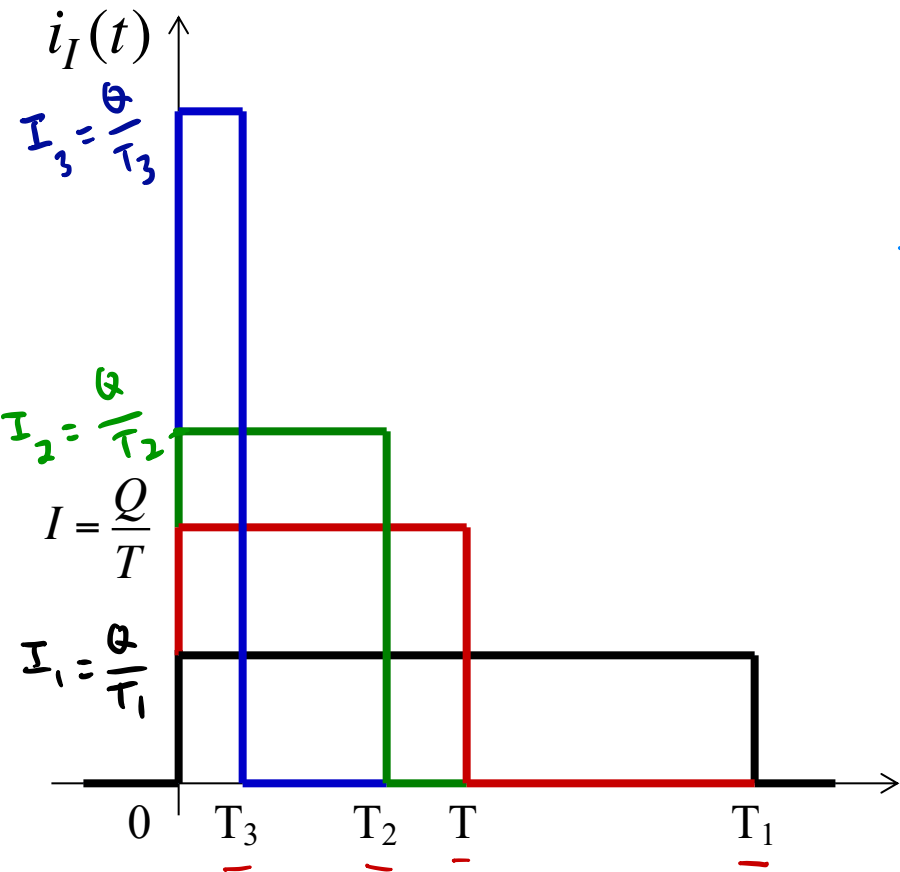As the Pulse Gets Narrower \rightarrow Impulse




□ As $\lim T \rightarrow 0$, pulse becomes impulse

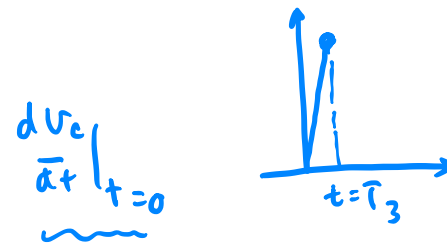- Denoted by $\delta(t)$
- Impulse is an important signal type.





Response to Impulse – Limit Case

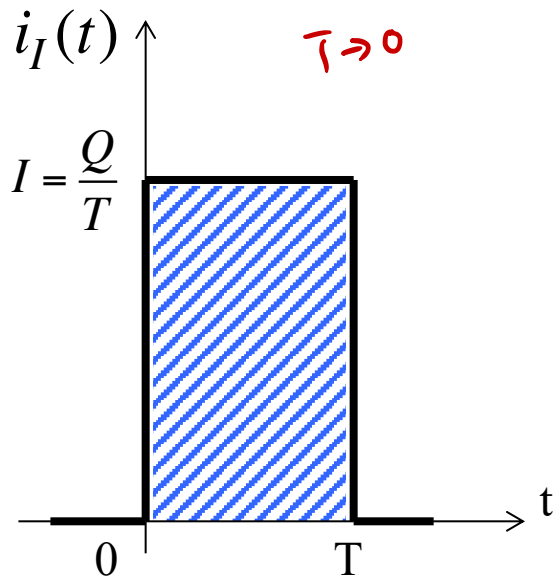

$$v_C(t) = 0, \quad t < 0$$

$$v_C(t) = \frac{Q}{T} \cdot R \cdot (1 - e^{-t/RC}), \quad 0 \leq t < T$$

$$v_C(t) = v_C(T) \cdot e^{-(t-T)/RC}, \quad t > T$$

$$\text{where } v_C(T) = \frac{Q}{T} \cdot R \cdot (1 - e^{-T/RC})$$

Now consider $T \rightarrow 0$, $v_C(T) = ?$

① $\frac{dv_C(t)}{dt} \Big|_{t=0} = \frac{Q}{T} \cdot R \cdot \frac{1}{RC} = \frac{Q}{TC}$, then



$$v_C(T) \approx \frac{Q}{TC} \cdot T = \frac{Q}{C}$$

② Taylor expansion, $v_C(t) = v_C(0) + v_C'(0) \cdot (t-0) + \dots$

$$v_C(T) = 0 + v_C'(0) \cdot T + \dots = \frac{Q}{C}$$

$$\left\{ \frac{Q}{C} \cdot e^{-t/RC} \right.$$

impulse response


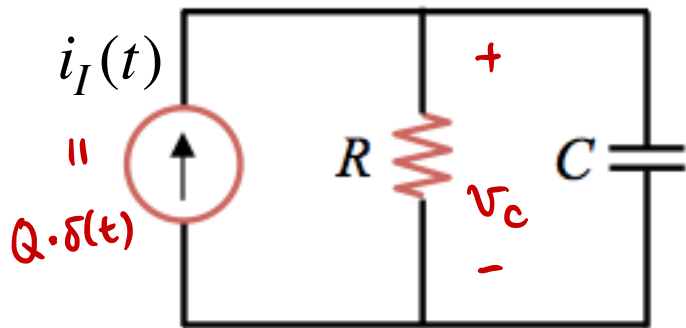
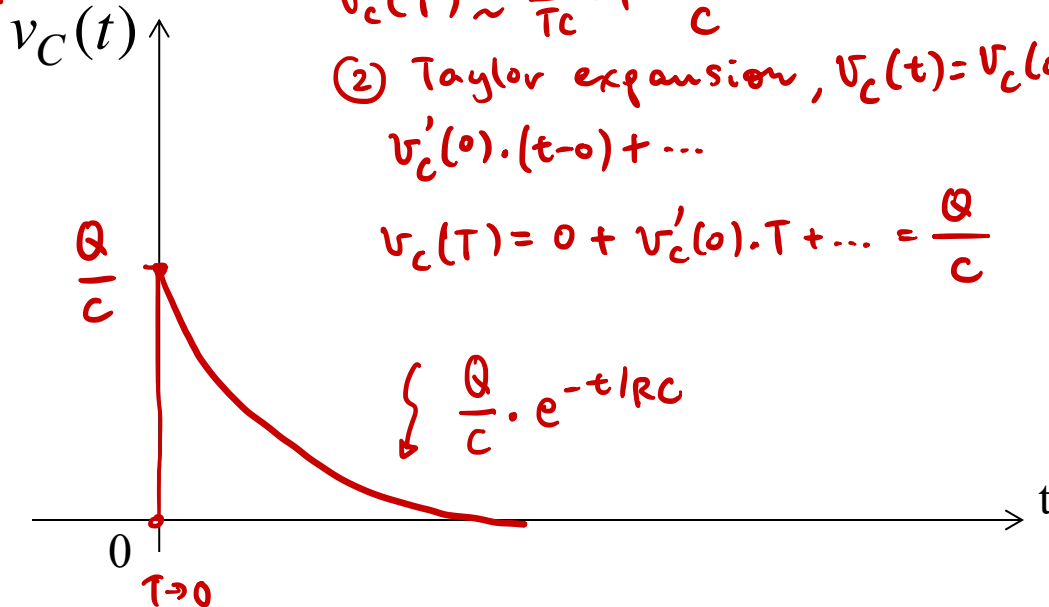




Response to Impulse



Impulse response
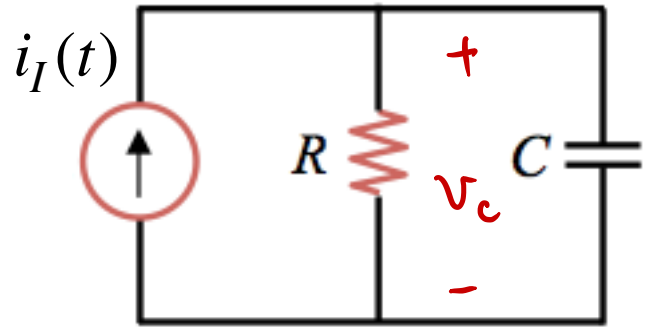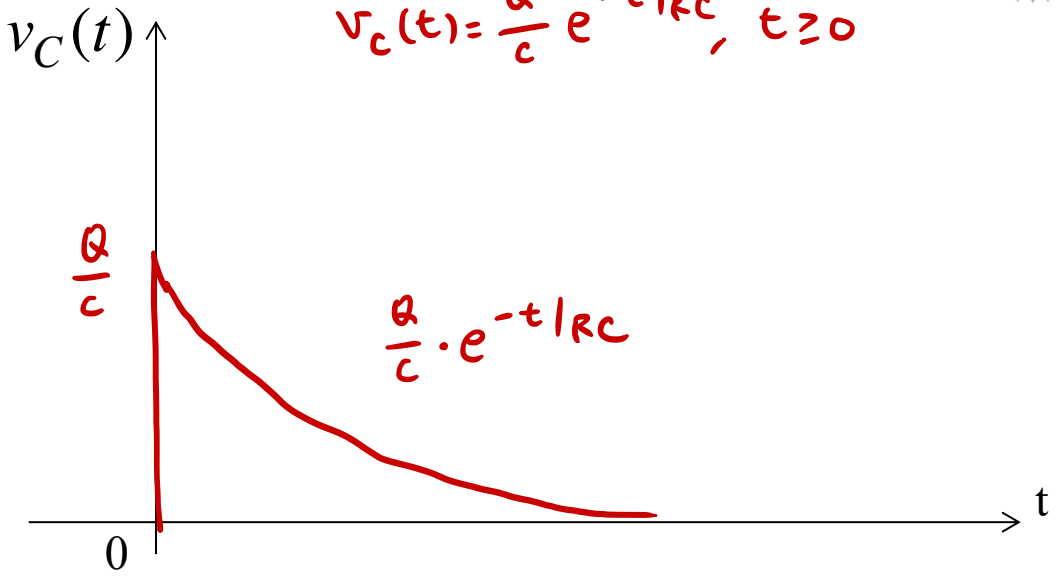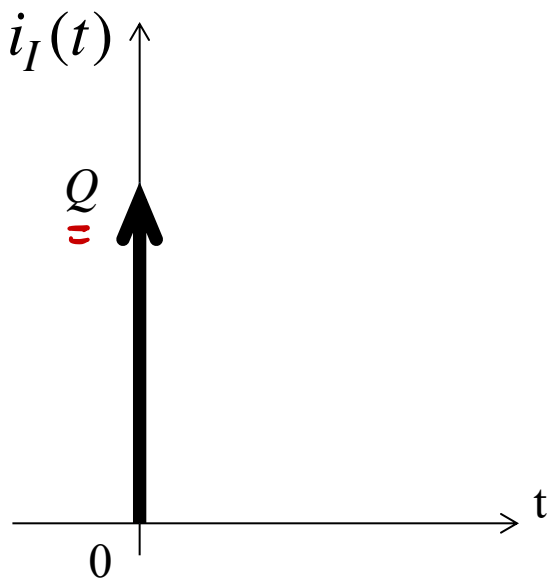
$$v_C(t) = \frac{Q}{C} e^{-t/RC}, t \geq 0$$







Response to Impulse

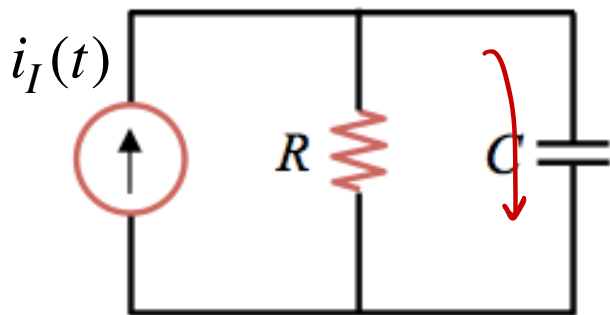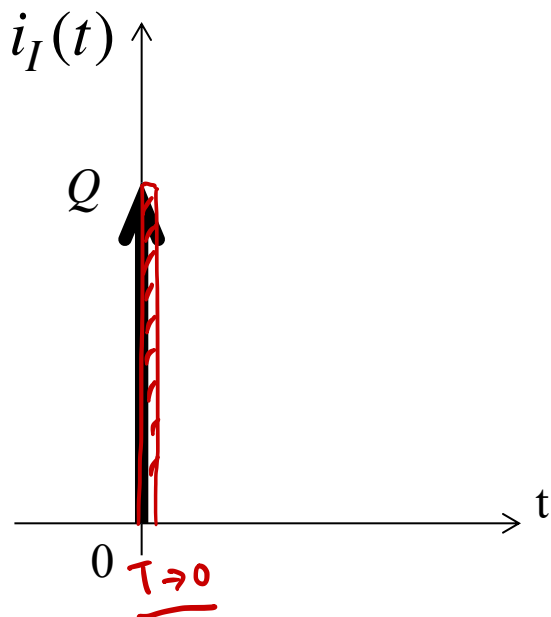




- $v_C(t)$ is largely independent of T or details of the pulse.
 - During delivery, shape of pulse does not matter.
- Capacitor behaves like a short circuit for changes that are much faster than the time constant RC .
- All charge Q gets delivered to capacitor.
 - Recall that, for capacitor, $v = \frac{Q}{C}$
- Impulse sets up initial condition on capacitor.



Current and Voltage Impulses

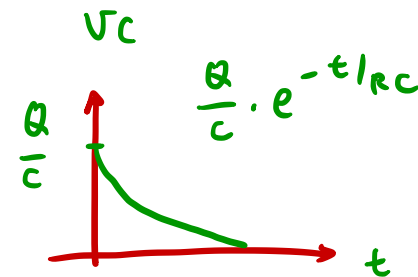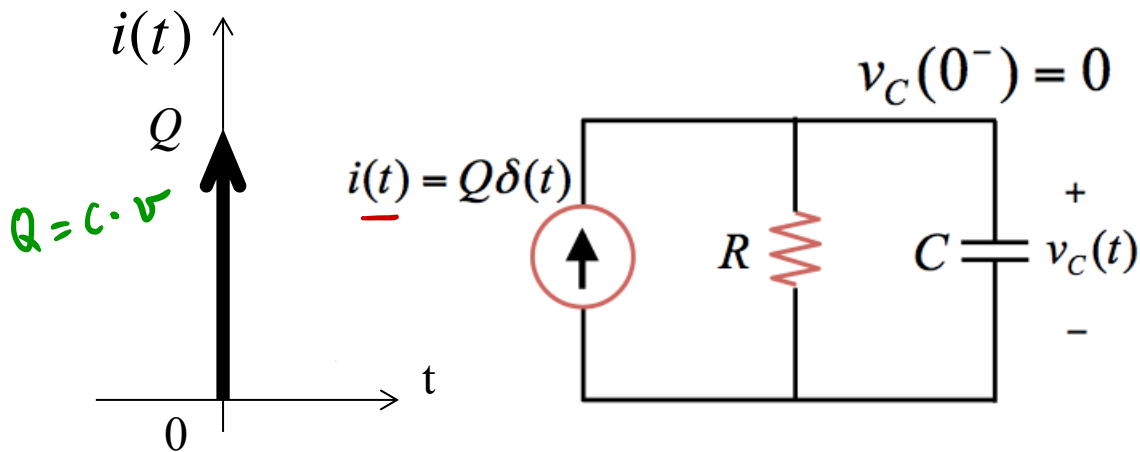

- Current impulse delivers charge Q .

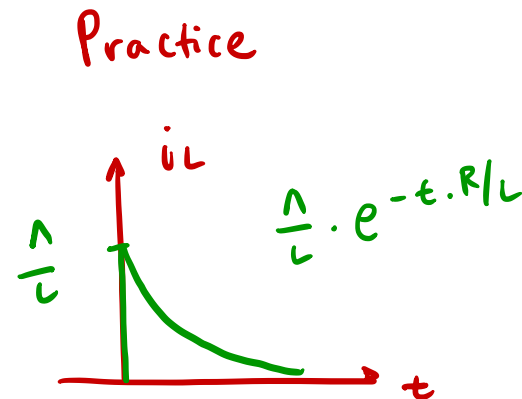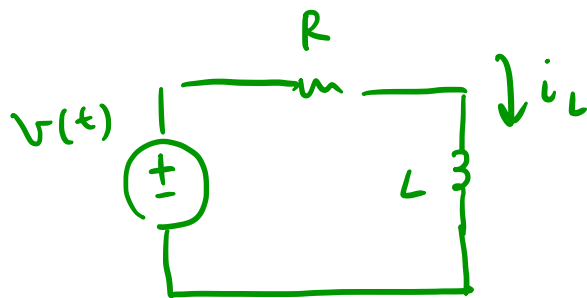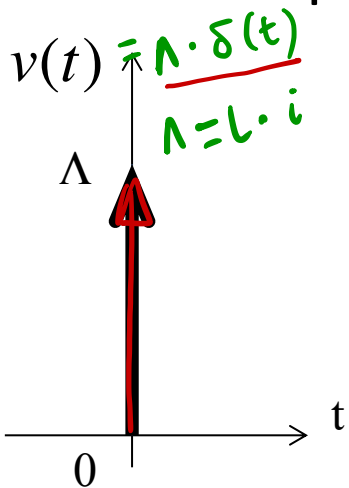

- Voltage impulse delivers flux linkage.