





Superposition with Initial Conditions and Sources

- Note that superposition does NOT apply when initial condition exists.
- Superposition does apply when initial conditions are zero.
- One way of solving circuits with multiple sources and multiple initial conditions
 - Treat initial conditions like sources.
 - Find response to each source or each initial condition acting alone.
 - Sum all the partial responses for total response.


$$\underline{V_c(t)} = \underbrace{f(V_1) + f(V_2) + f(i_1) + \dots}_{\text{zero-state response, } V_c(t=0)=0} + \underbrace{f(V_{c,0})}_{\substack{\text{zero-input response} \\ \text{initial condition}}} \quad 14$$




Impulses, Steps, and Ramps

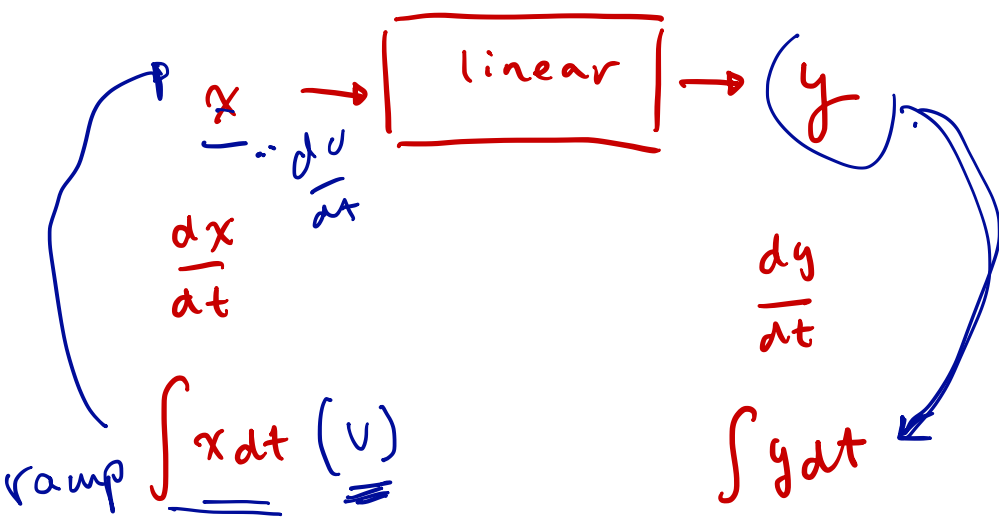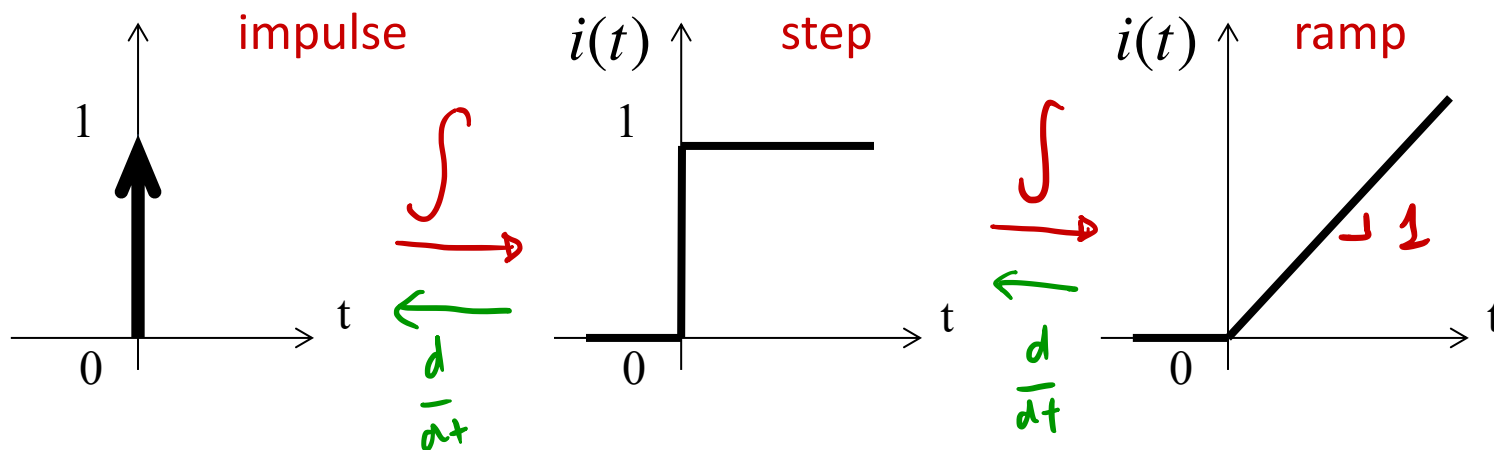


Ramp Input to RC Circuit

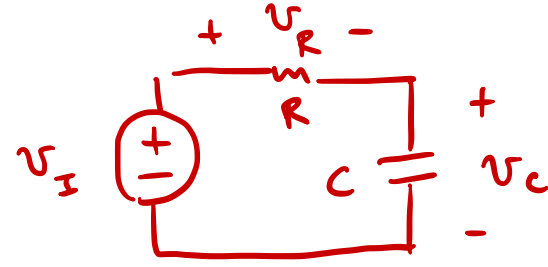

□ Recall step response

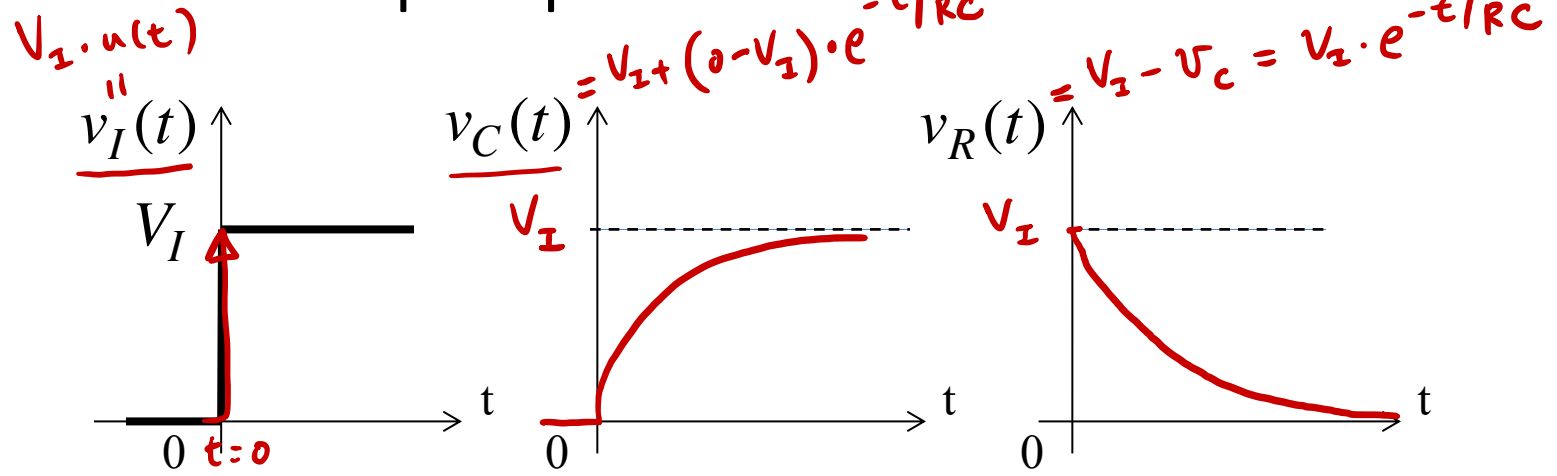

□ With ramp input

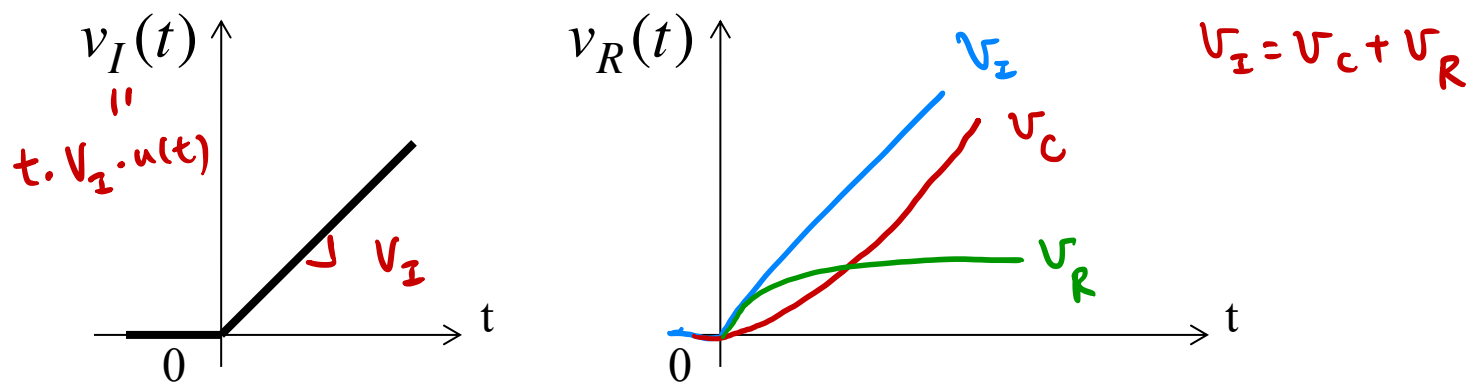

• Ramp response

$$\begin{aligned}V_c(t) &= \int_{-\infty}^t V_I (1 - e^{-t/RC}) dt \\&= V_c(0^-) + \int_0^t V_I (1 - e^{-t/RC}) dt \\&= V_c(0^-) + V_I (t + RC \cdot e^{-t/RC}) \Big|_0^t \\&= 0 + V_I (t - 0 + RC \cdot e^{-t/RC} - RC) \\&= V_I (t + RC \cdot e^{-t/RC} - RC), \quad t > 0\end{aligned}$$

$$V_R(t) = \int_{-\infty}^t V_I \cdot e^{-t/RC} dt = V_I \cdot (-RC) \cdot e^{-t/RC} \Big|_0^t = V_I \cdot RC \cdot (1 - e^{-t/RC}), \quad t > 0$$

Check that $V_c + V_R = V_I$