



Electric Circuits

Lecture 8 Energy and Power

EE2210, Fall 2022

Jenny Yi-Chun Liu

jennyliu@gapp.nthu.edu.tw




Why Worry about Energy?

- Portable devices

- How long will the battery last?
 - In standby mode
 - In active mode

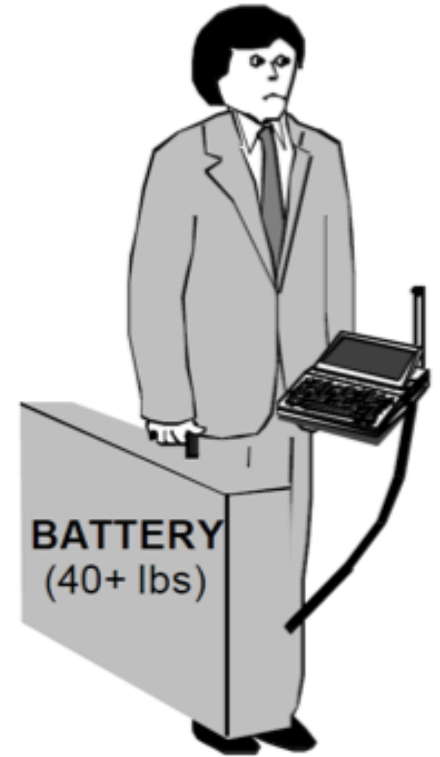
- Will the chip overheat and self-destruct?





Static and Dynamic Power

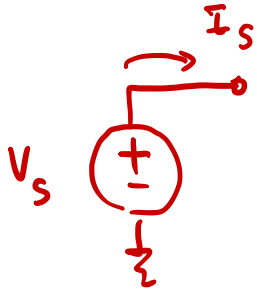- Static power: power loss due to static current drawn from the power supply.






$$P_s = V_s \cdot I_s$$

- Dynamic power: power loss due to the switching current required to charge and discharge capacitors.



Energy Dissipation in MOSFET Gates


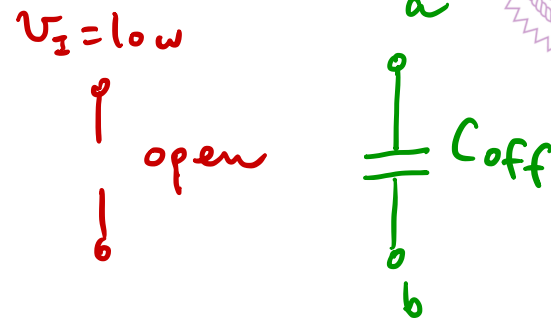
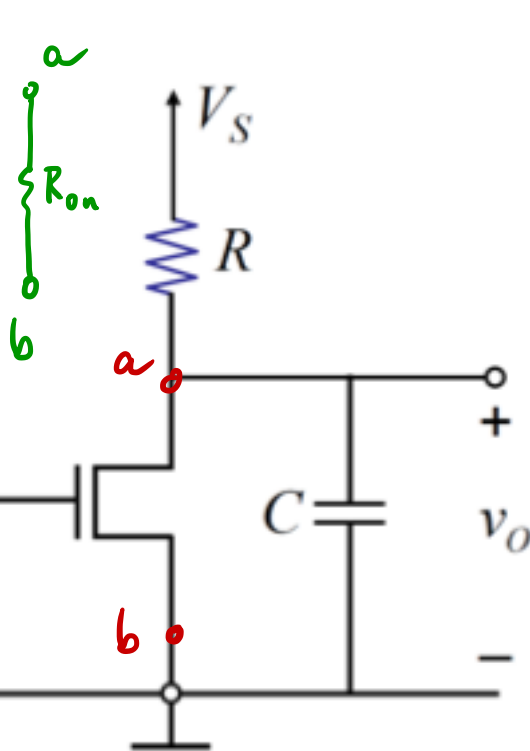
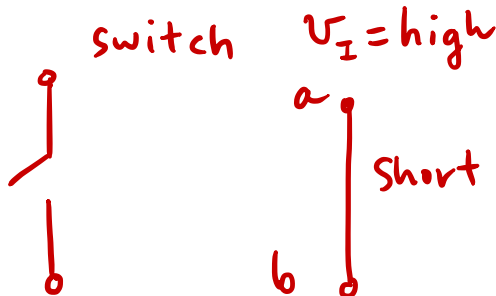


ideally, $R_{on} \rightarrow 0$

R_{on} : on resistance

ideally $C_{off} \rightarrow 0$
 2) when $V_I = V_S$ (High)
 ($V_I \geq V_{TH}$ $0.3V \sim 1V$
 V_{TH} : threshold voltage)



1) when $V_I = 0$ (Low)

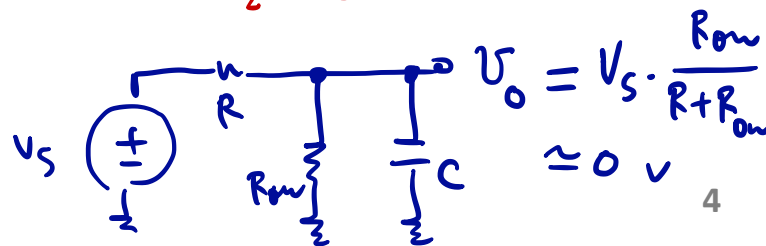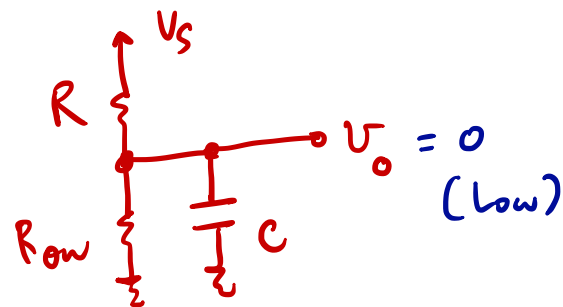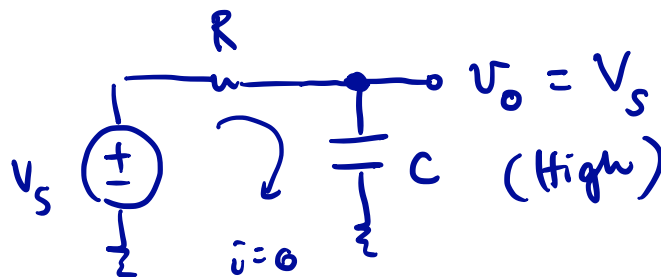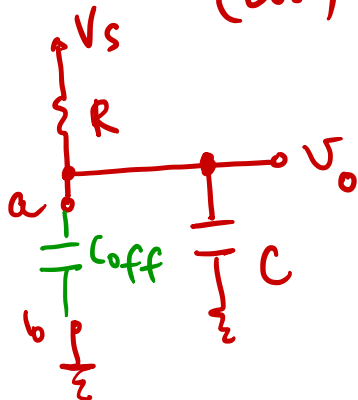

First Example

- The power consumed by R
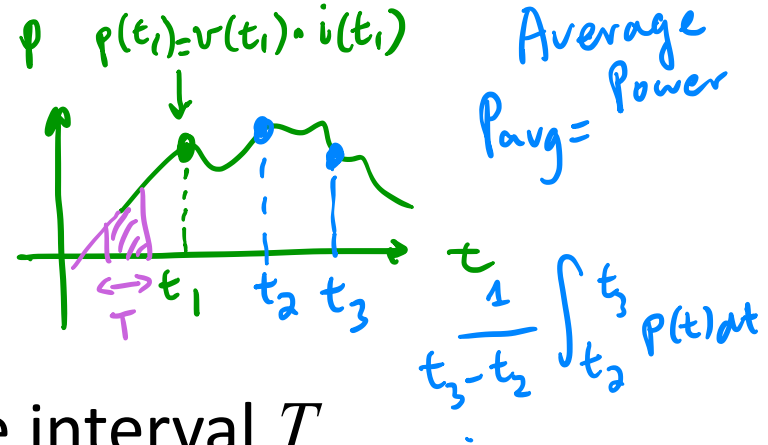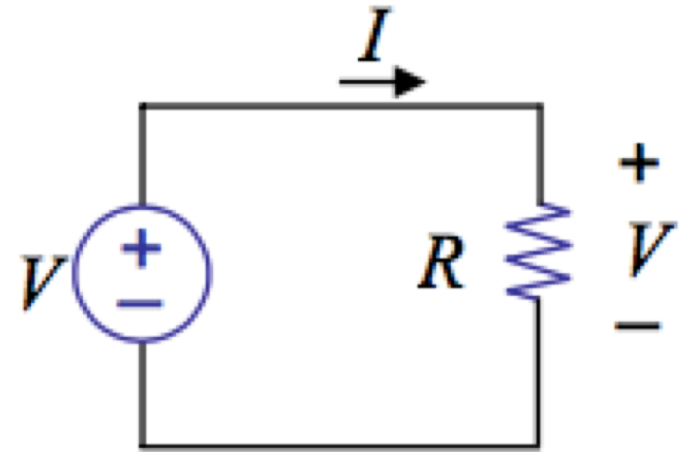
$$P = v \cdot i = V \cdot \frac{V}{R} = I^2 \cdot R \quad (\text{W})$$



- The energy dissipated during time interval T

$$E = \int_T p dt = P \cdot T \quad (\text{J})$$

$$\text{Energy} = \int_T p(t) dt$$




Steady-state

Apply to Our Gate for Static Power


□ When the gate is not switching

1) When $V_{i2} = \text{low}$

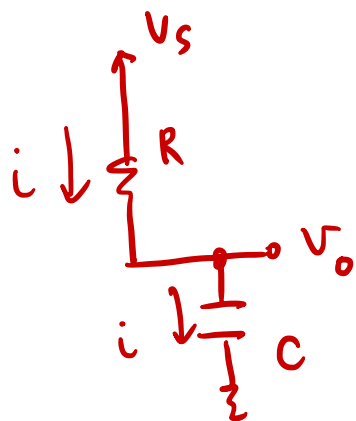


$$i = 0$$
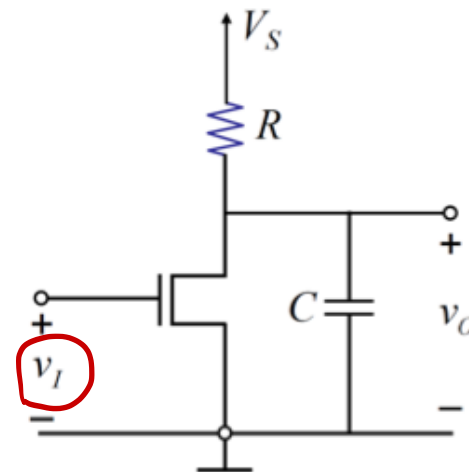
$$P = V_s \cdot i = V_s \cdot 0 = 0 \text{ W}$$



2) When $V_{i2} = \text{high}$

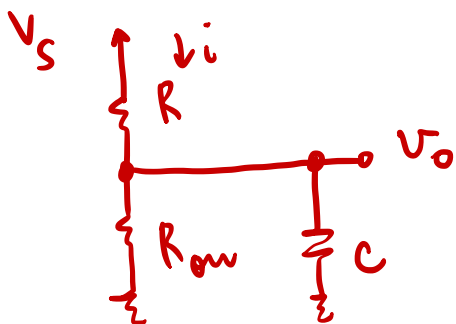


$$P = V_s \cdot i = V_s \cdot \frac{V_s}{R + R_{on}} = \frac{V_s^2}{R + R_{on}} \text{ W}$$





Example

Find the max. static power.

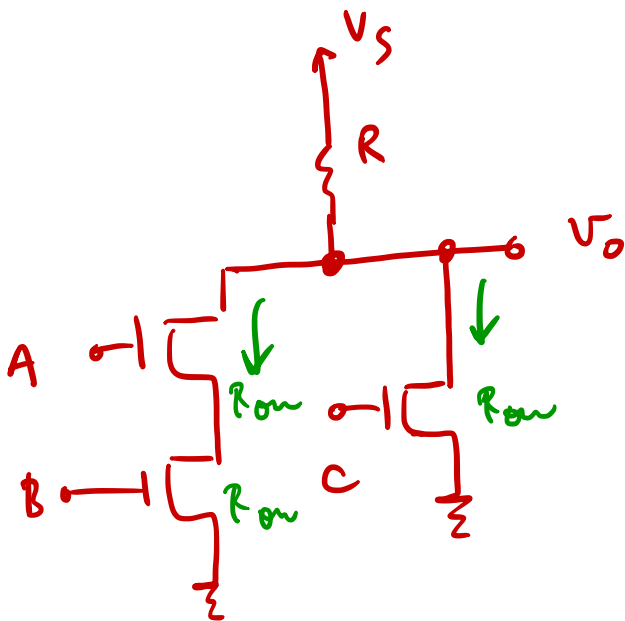

$$P_{\text{static}} = V_s \cdot i = V_s \cdot \frac{V_s}{R + R_{\text{eq}}} = V_s \cdot \frac{V_s}{R + \frac{2}{3} R_{\text{on}}}$$



\Rightarrow Min. Req. A, B, C = High

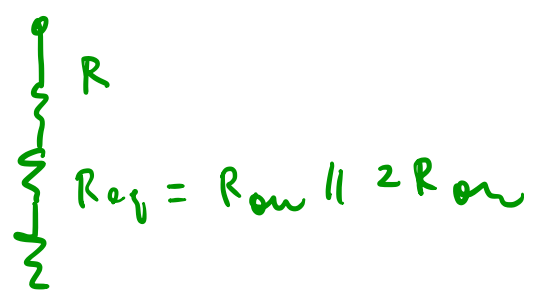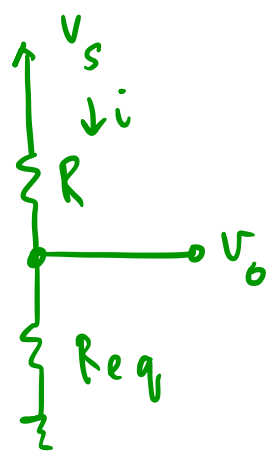

Second Example





□ Consider

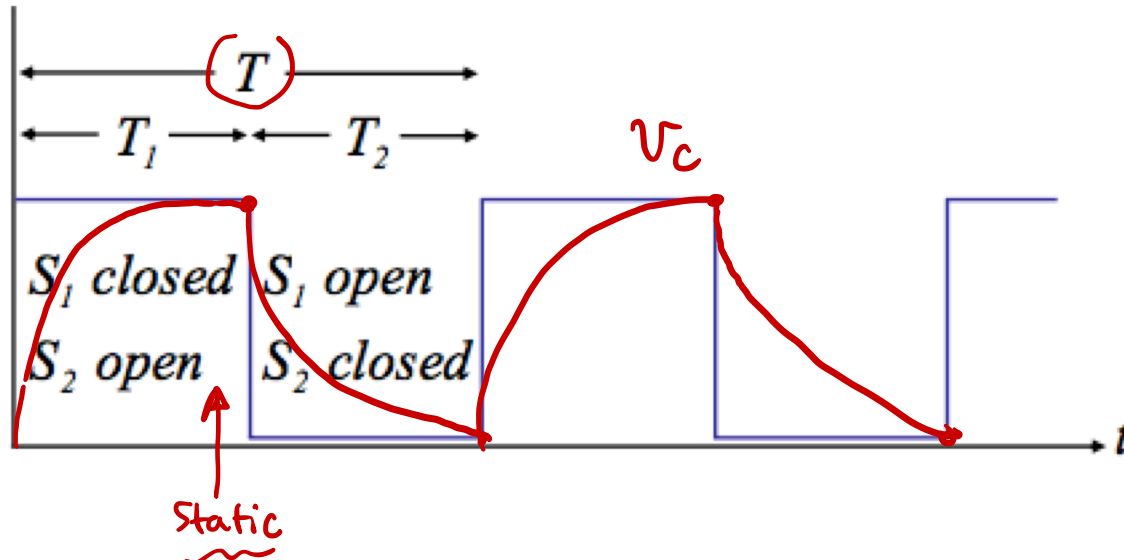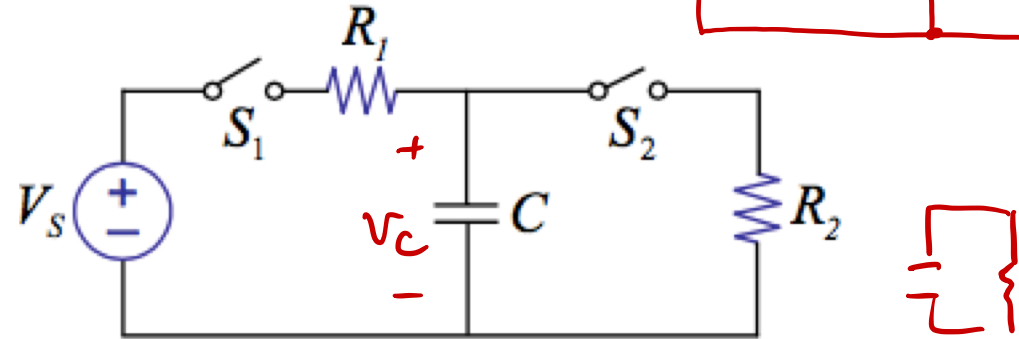

- Find energy dissipated in each cycle.
- Find average power.

Second Example

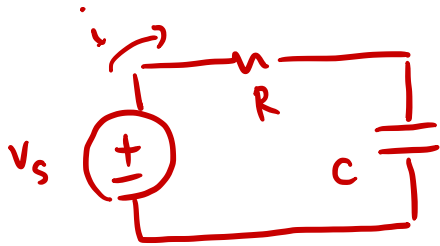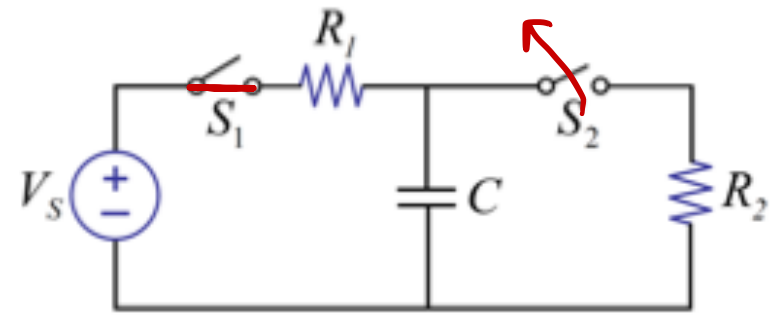
- During T_1 :
 S_1 is closed and S_2 is open.



$i_{static} = 0$

$$i_c = C \cdot \frac{dV}{dt} = \frac{V_R}{R} = \frac{V_s - V_c}{R}$$

$$V_c = V_s \cdot (1 - e^{-t/RC})$$

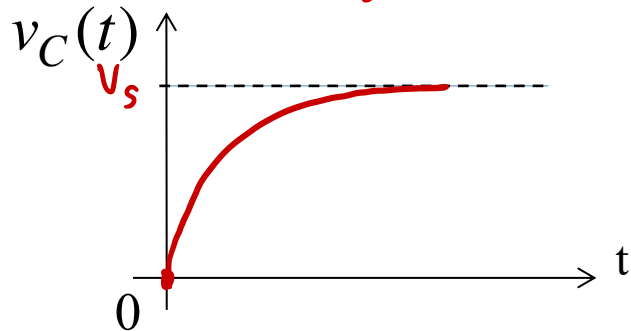

$$i_c = \frac{V_s}{R_1} \cdot e^{-t/RC}$$

