



Electric Circuits

Lecture 8 Energy and Power

EE2210, Fall 2022

Jenny Yi-Chun Liu

jennyliu@gapp.nthu.edu.tw




Why Worry about Energy?

- Portable devices

- How long will the battery last?
 - In standby mode
 - In active mode

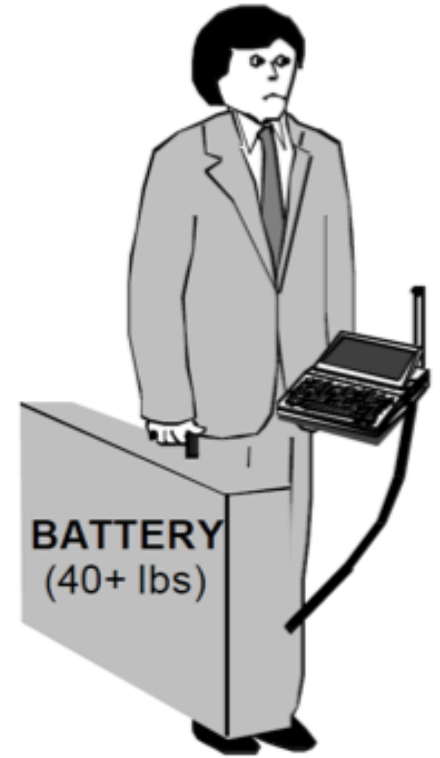
- Will the chip overheat and self-destruct?





Static and Dynamic Power

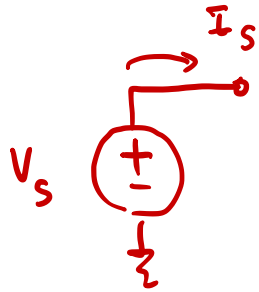- Static power: power loss due to static current drawn from the power supply.





$$P_s = V_s \cdot I_s$$

- Dynamic power: power loss due to the switching current required to charge and discharge capacitors.




Energy Dissipation in MOSFET Gates

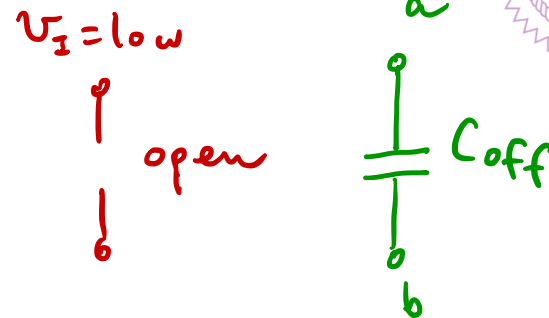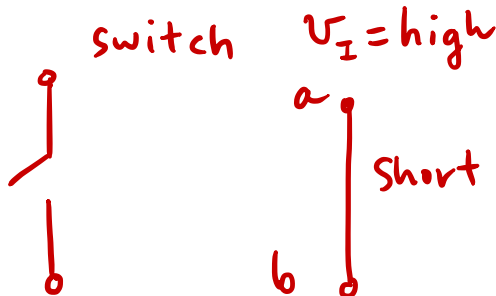





ideally, $R_{on} \rightarrow 0$

R_{on} : on resistance

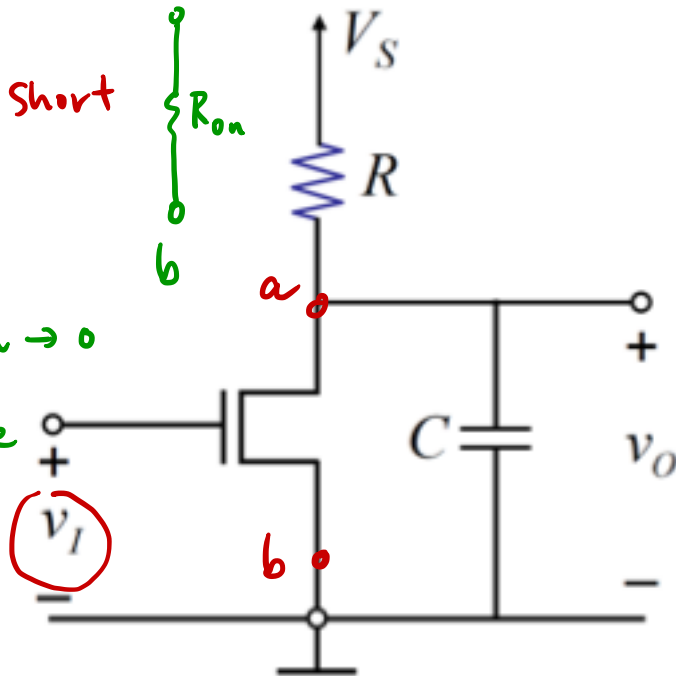

ideally $C_{off} \rightarrow 0$
 2) when $V_I = V_S$ (High)
 ($V_I \geq V_{TH}$ $0.3V \sim 1V$
 V_{TH} : threshold voltage)



1) when $V_I = 0$ (Low)

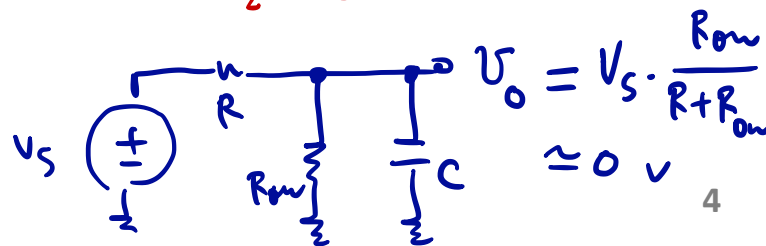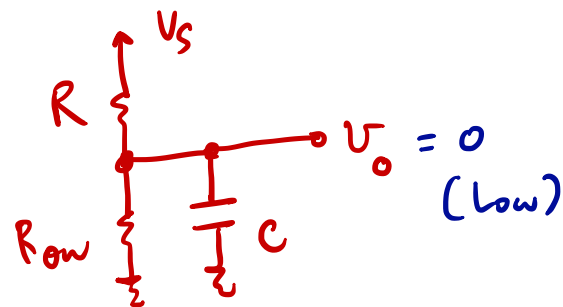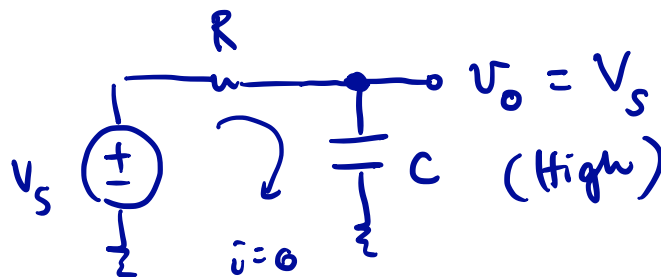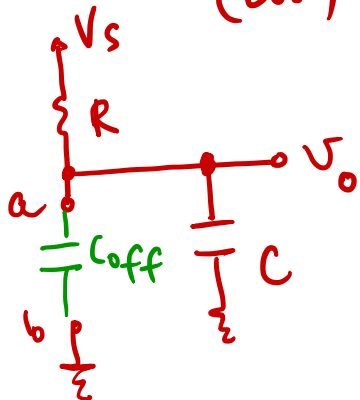

First Example

- The power consumed by R
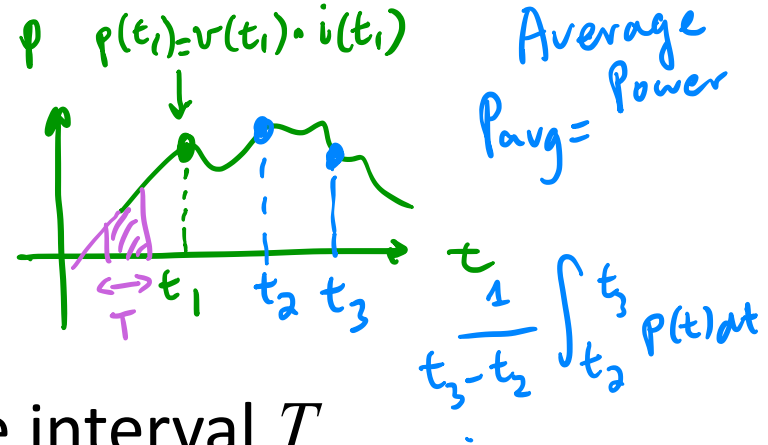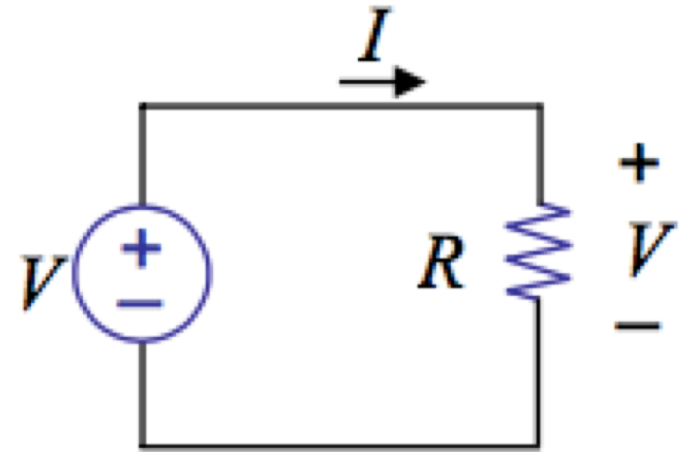
$$P = v \cdot i = V \cdot \frac{V}{R} = I^2 \cdot R \quad (\text{W})$$



- The energy dissipated during time interval T

$$E = \int_T p dt = P \cdot T \quad (\text{J})$$

$$\text{Energy} = \int_T p(t) dt$$




Steady-state

Apply to Our Gate for Static Power


□ When the gate is not switching

1) When $V_{in} = \text{low}$

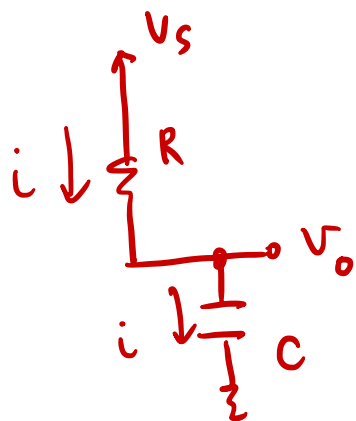


$$i = 0$$
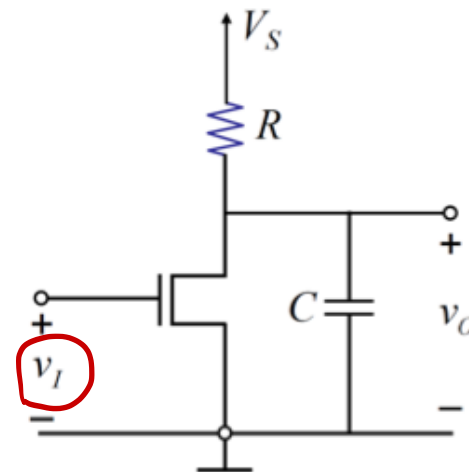
$$P = V_s \cdot i = V_s \cdot 0 = 0 \text{ W}$$



2) When $V_{in} = \text{high}$

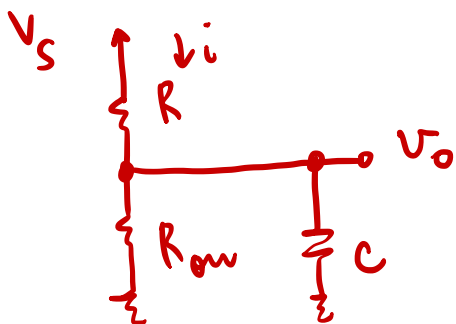


$$P = V_s \cdot i = V_s \cdot \frac{V_s}{R + R_{ow}} = \frac{V_s^2}{R + R_{ow}} \text{ W}$$





Example

Find the max. static power.

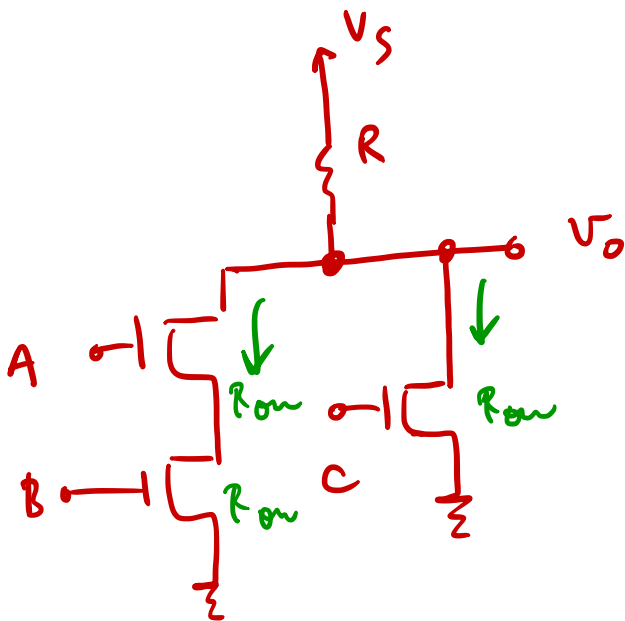

$$P_{\text{static}} = V_s \cdot i = V_s \cdot \frac{V_s}{R + R_{\text{eq}}} = V_s \cdot \frac{V_s}{R + \frac{2}{3} R_{\text{on}}}$$



\Rightarrow Min. Req. A, B, C = High

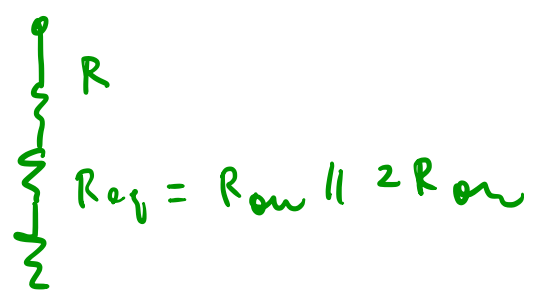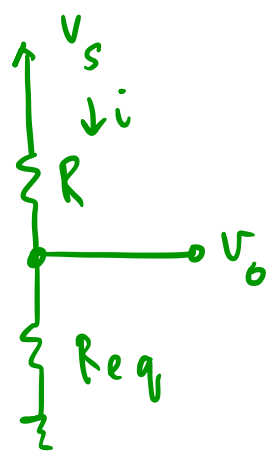

Second Example





□ Consider

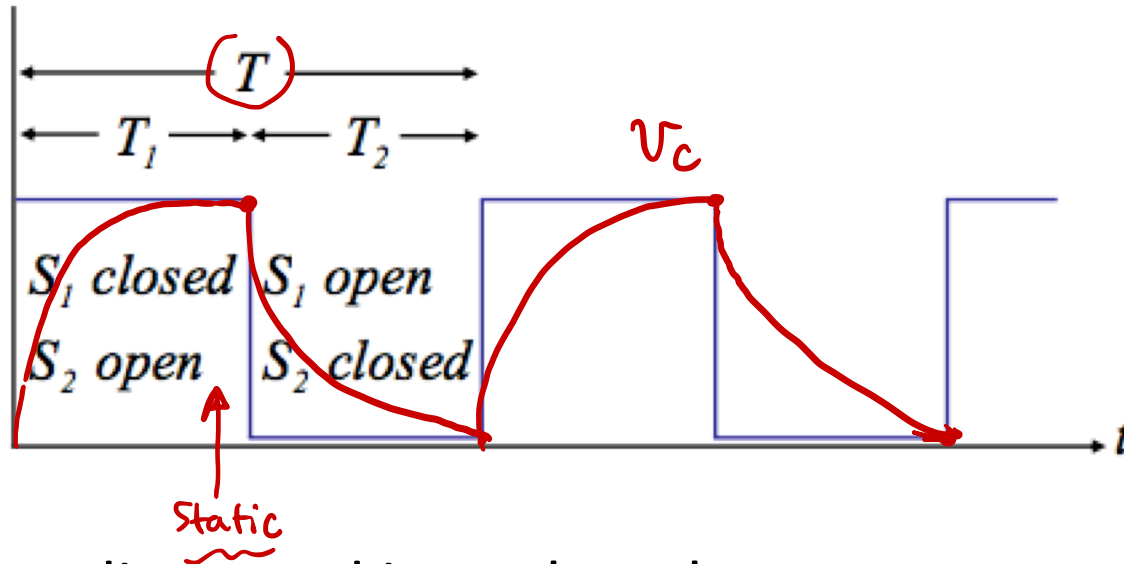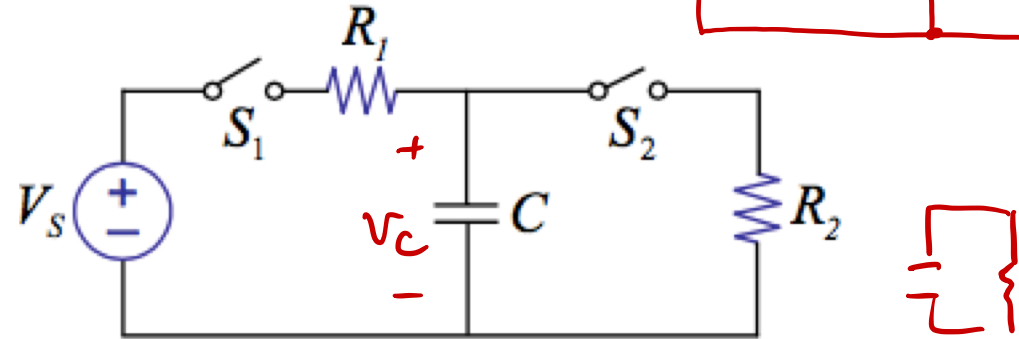

- Find energy dissipated in each cycle.
- Find average power.

Second Example

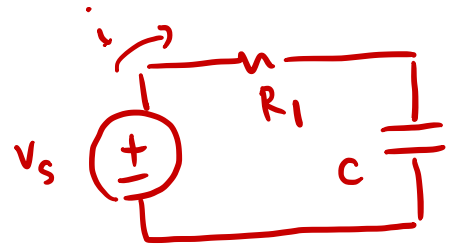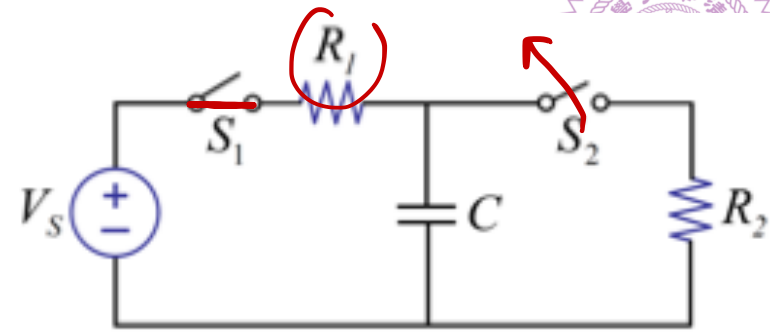- During T_1 :
 S_1 is closed and S_2 is open.




$P_{static} = 0$


$$i_c = C \cdot \frac{dV}{dt} = \frac{V_R}{R}$$

$$= \frac{V_s - V_c}{R}$$

$$V_c = V_s \cdot (1 - e^{-t/RC})$$

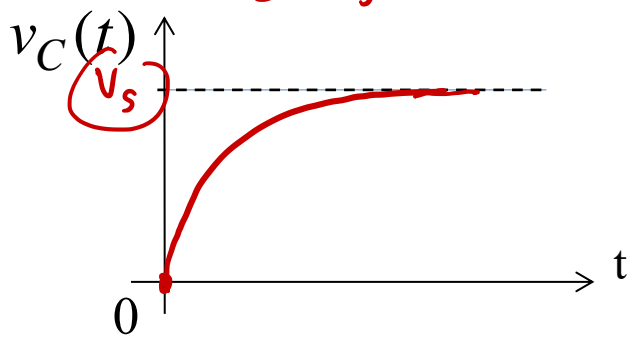
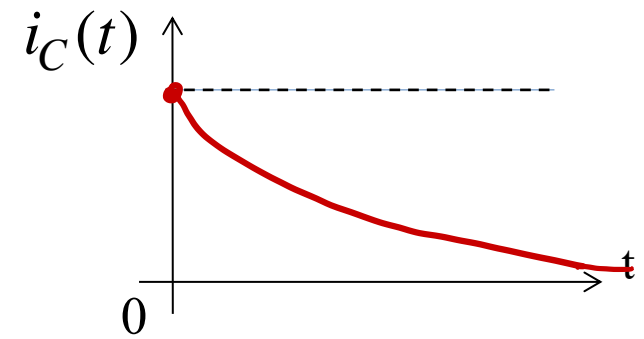
$$i_c = \frac{V_s}{R_1} \cdot e^{-t/RC}$$






Total Energy Provided by Source During T_1

Total energy provided by V_s (to R_1, C)

$$E = \int_0^{T_1} v \cdot i \, dt = \int_0^{T_1} \underline{V_s \cdot i} \, dt$$
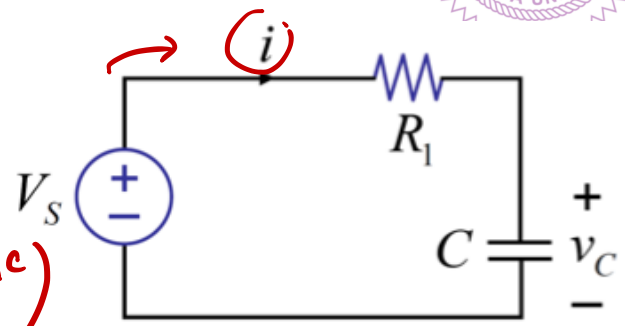
$$= \int_0^{T_1} V_s \cdot \frac{V_s}{R_1} e^{-t/R_1 C} \, dt = V_s^2 \cdot C \cdot (1 - e^{-T_1/R_1 C})$$



If $T_1 \gg R_1 C$, $e^{-t/R_1 C}$ can be ignored

$$E_1 \approx \underline{V_s^2 \cdot C}$$



Practice :

✓ Energy stored on capacitor $C = ? \frac{1}{2} V_s^2 \cdot C$

✓ Energy dissipated in $R_1 = ? \frac{1}{2} V_s^2 \cdot C = \int_0^{T_1} (V_s - v_c) \cdot i_c \, dt$

Second Example

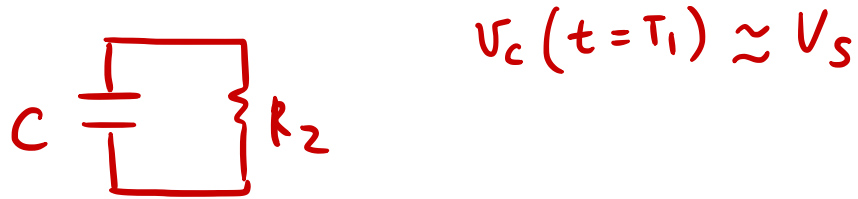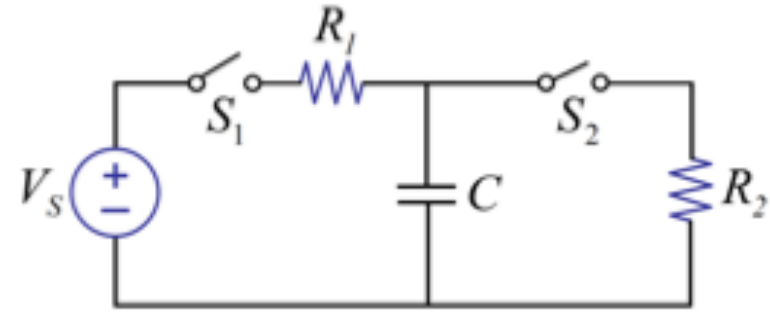
- During T_2 :
 S_2 is closed and S_1 is open.



- Initially, $V_c = V_s$
 - Energy stored on capacitor is $\frac{1}{2} C V_s^2$
- Assume $T_2 \gg R_2 \cdot C$
- Capacitor discharges more or less fully during T_2 .
- ✓ □ Energy dissipated in R_2 during T_2 is $\frac{1}{2} C \cdot V_s^2 = E_2$
- E_2 is also independent of R_2 .

Practice

Putting the Two Together

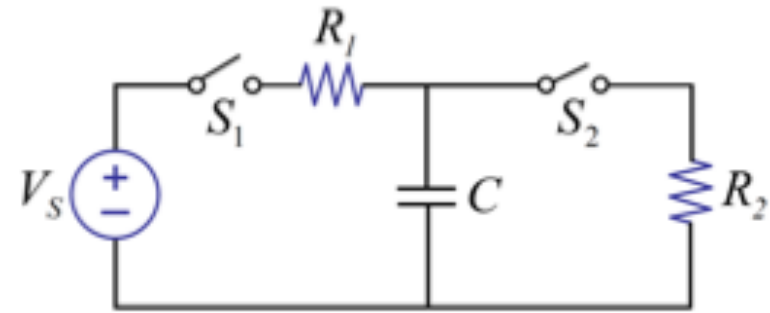

- Total energy dissipated in each cycle

$$E_{\text{total}} = E_{R_1} + E_{R_2} = \underbrace{\frac{1}{2} C V_s^2}_{R_1} + \underbrace{\frac{1}{2} C V_s^2}_{R_2} = \underbrace{C V_s^2}_{\text{provided by } V_s}$$

- The energy dissipated in charging and discharging the capacitor C .
- Assume C charges and discharges fully. ($T_1 \gg R_1 C$, $T_2 \gg R_2 C$)


- The average power is

$$P = \frac{E_{\text{total}}}{T_1 + T_2} = \frac{C V_s^2}{T_1 + T_2} = \frac{C V_s^2}{T} = C V_s^2 \cdot f$$

f : frequency ($1/s$, Hz)




Back to Our Inverter

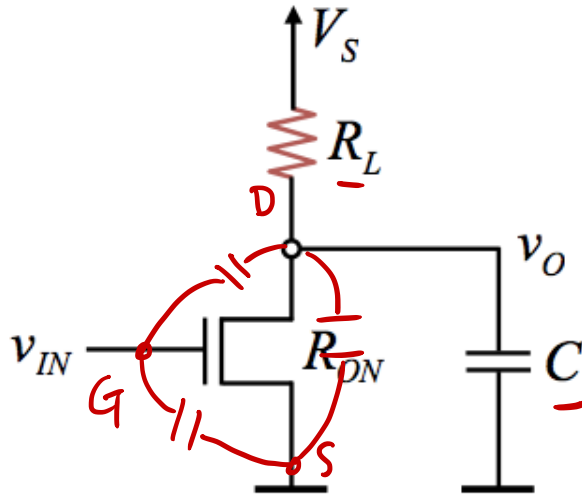


C includes wire capacitance C_W and gate capacitance C_{GS} of the following gates.

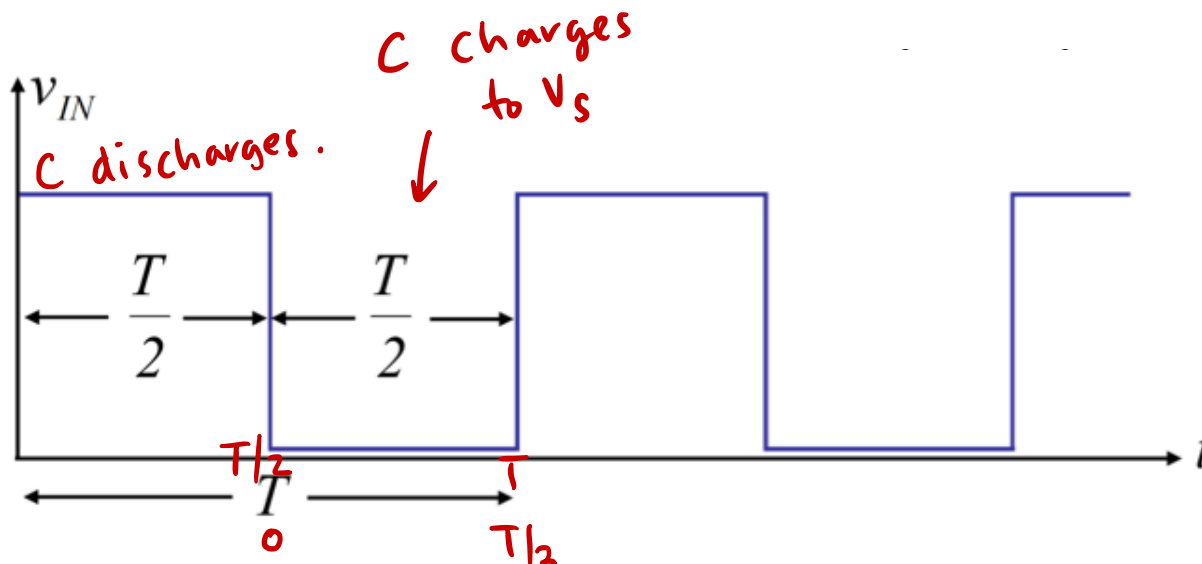- What is \bar{P} with the following input pattern?








Equivalent Circuit

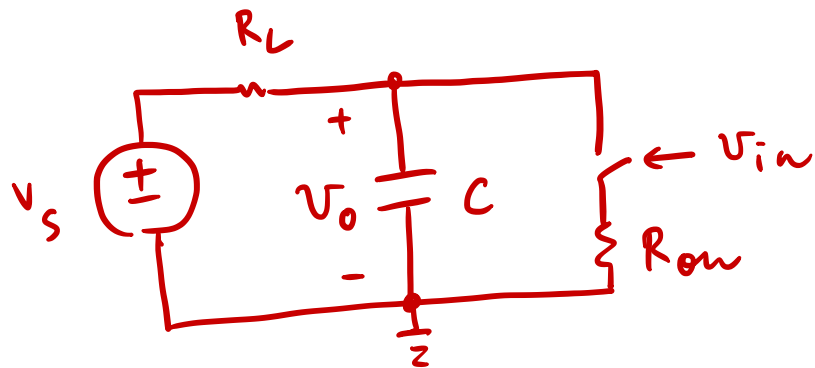

1) When V_{in} is high, discharging C.

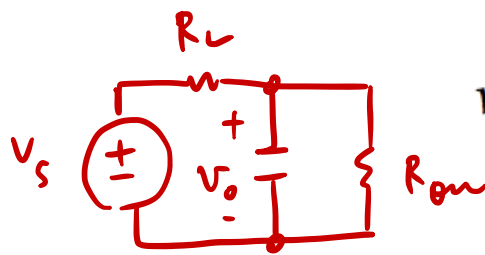

$t \rightarrow \infty$

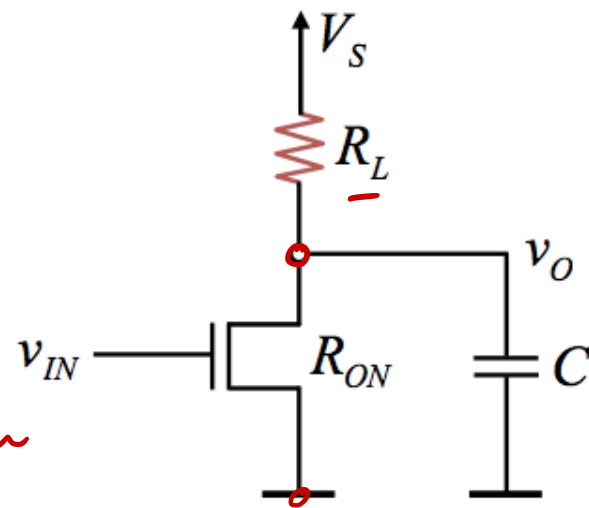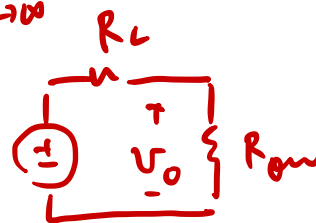

$$V_{O,initial} = V_S, \quad V_{O,final} = \frac{R_{ON}}{R_L + R_{ON}} \cdot V_S$$

$$V_O(t) = V_S \cdot \frac{R_{ON}}{R_L + R_{ON}} + \left(V_S - \frac{R_{ON}}{R_L + R_{ON}} V_S \right) \cdot e^{-t/\tau}$$

$$V_{O,final} = V_S \cdot \frac{R_{ON}}{R_L + R_{ON}}$$

$$\tau = (R_L \parallel R_{ON}) \cdot C$$

$$E_1 = \int_0^{T/2} \left(\frac{(V_S - V_O)^2}{R_L} + \frac{V_O^2}{R_{ON}} \right) dt = \frac{V_S^2}{R_L + R_{ON}} \cdot \frac{T}{2} + \frac{C \cdot V_S^2 \cdot R_L^2}{2(R_L + R_{ON})^2}, \quad \text{assuming } \frac{T}{2} \gg \tau$$



$$\bar{P}_1 = \frac{E_1}{T/2} = \frac{V_S^2}{R_L + R_{ow}} + \frac{C V_S^2 \cdot R_L^2}{(R_L + R_{ow})^2} \cdot 2f$$

2) when V_{in} is low, C charging


$$V_{0, initial} = V_S \cdot \frac{R_{ow}}{R_L + R_{ow}} \quad (\rightarrow 0 \text{ when } R_{ow} \rightarrow 0)$$

$$V_{0, final} = V_S$$

$$V_0(t) = V_S + \left(V_S \frac{R_{ow}}{R_L + R_{ow}} - V_S \right) \cdot e^{-t / R_L \cdot C}$$

$$E_2 = \int_0^{T/2} \frac{(V_S - V_0)^2}{R_L} dt = \frac{C V_S^2 \cdot R_L^2}{2(R_L + R_{ow})^2}$$
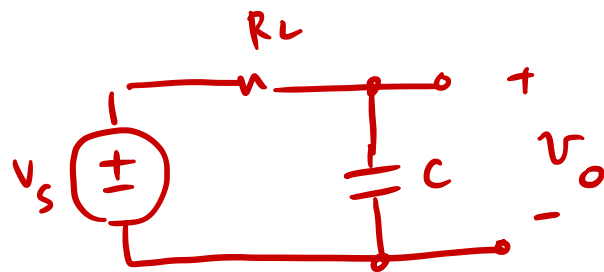
$$\bar{P}_2 = \frac{E_2}{T/2} = \frac{C V_S^2 \cdot R_L^2}{2(R_L + R_{ow})^2} \cdot 2f$$



$$e^{-(t - T/2) / R_L \cdot C}$$

$$\int_{T/2}^T$$






What is \bar{P} for the Gate?

$$\bar{P} = \frac{V_S^2}{2(R_L + R_{ON})} + CV_S^2 f \frac{R_L^2}{(R_L + R_{ON})^2}$$

■ with

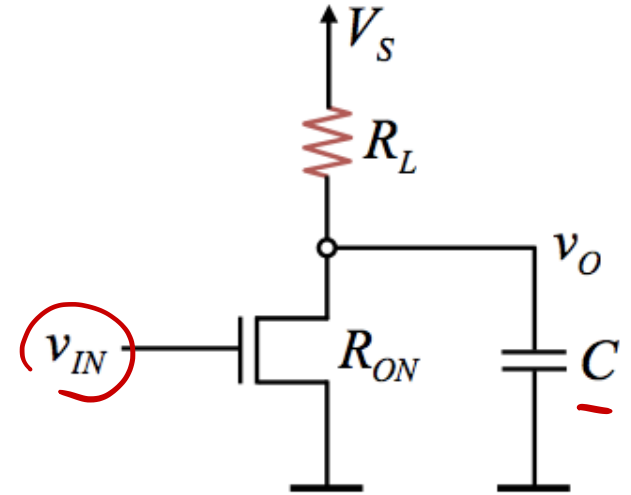$R_L \gg R_{ON}$, $\bar{P} = \underbrace{\frac{V_S^2}{2R_L}}_{\text{Static}} + \underbrace{CV_S^2 \cdot f}_{\text{dynamic}}$



- During active mode, the circuit consumes static power and dynamic power.
 - The first term is called the **static power dissipation**.
 - In both standby mode and active mode.
 - Independent of frequency f .
 - The MOSFET is ON half of the time.
 - The second term is called **dynamic power dissipation**.
 - Proportional to frequency f and capacitance C .
- \bar{P}
of V_{in}



Some Numbers

- A chip with 5 million gates running at 3 GHz. *frequency*

Assume $V_S = 5V$, $R_L = 10k\Omega$, $R_{on} \rightarrow 0\Omega$, $C = 1fF$

$$\bar{P} = \left(\frac{V_S^2}{2R_L} + CV_S^2 \cdot f \right) \cdot 5 \times 10^6$$


$$= \left(\frac{25}{2 \times 10^4} + 10^{-15} \times 25 \times 3 \times 10^9 \right) \times 5 \times 10^6$$

$$= \underbrace{6.25 \text{ kW}}_{\text{static}} + \underbrace{375 \text{ kW}}_{\text{dynamic}}$$




How to Get Rid of Static Power Dissipation?

□ Intuition:

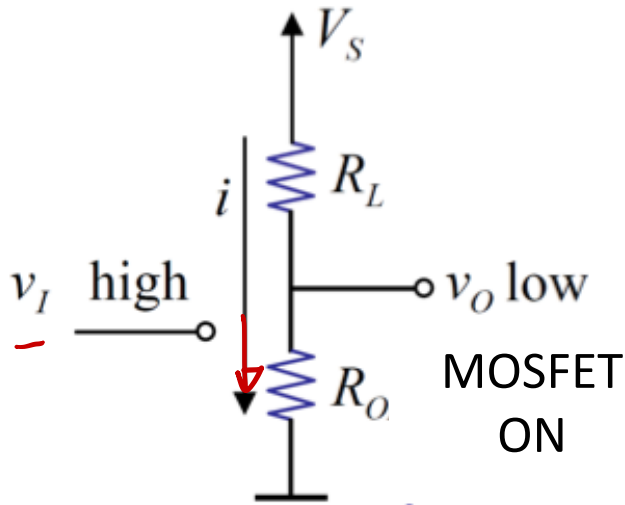


Problem case!!

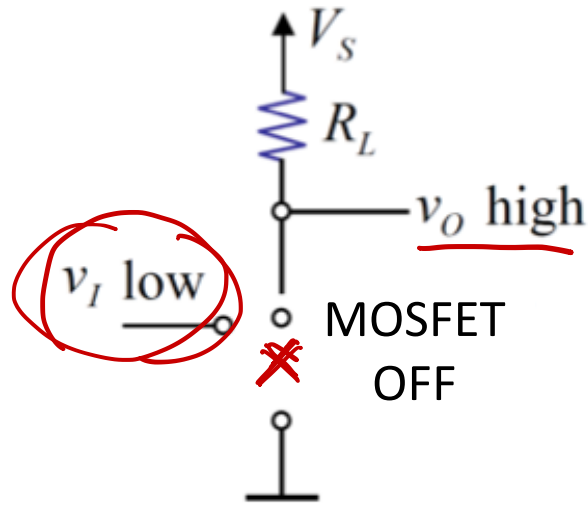

no problem

v_I high

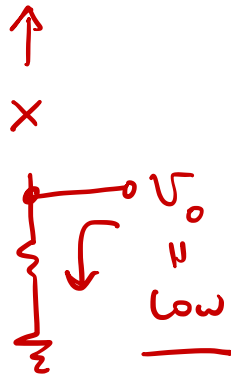


no dc path $\Rightarrow P_{static} = 0$



PMOS

CMOS : NMOS + PMOS
complementary


□ N-channel MOSFET (NMOS)

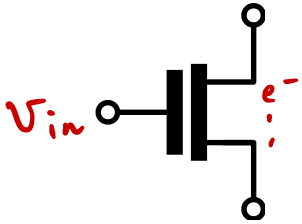

V_{in} high, NMOS turns on (Ron)

V_{in} low, NMOS turns off. (open, Coff)

□ P-channel MOSFET (PMOS)

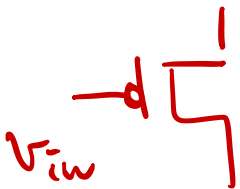


V_{in} high, PMOS turns off (open, Coff)

V_{in} low, PMOS turns on (Ron)






Consider This Circuit

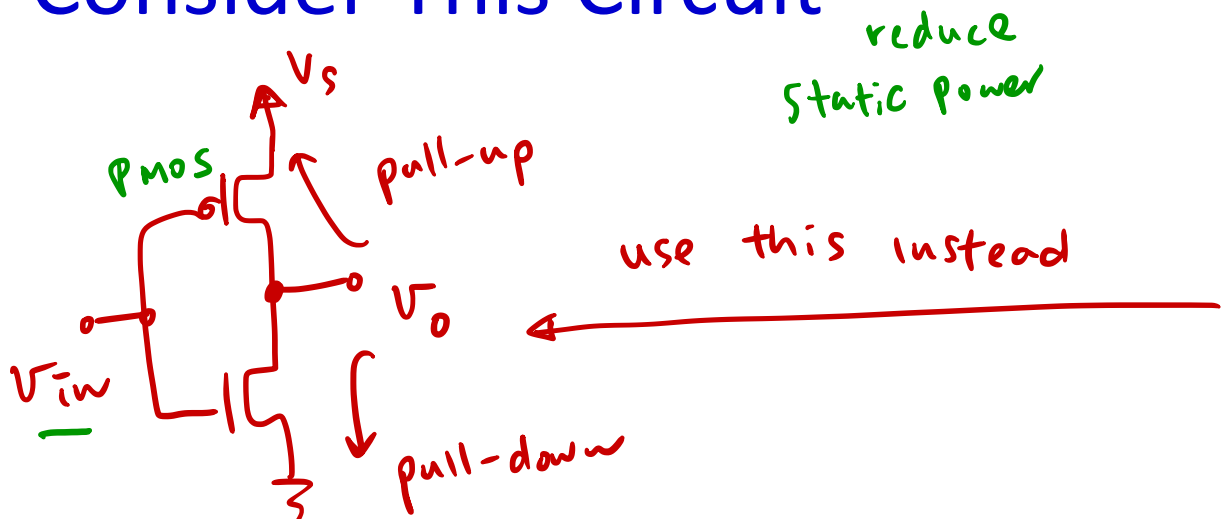

reduce static power

use this instead

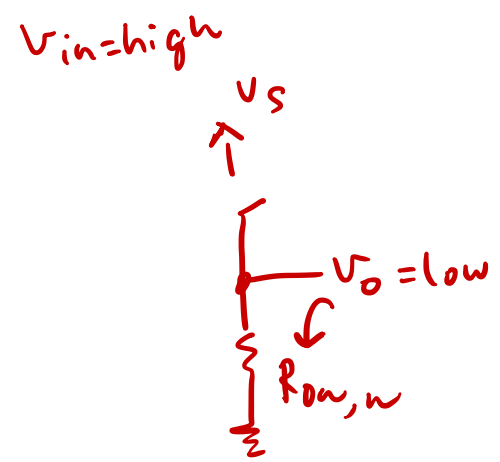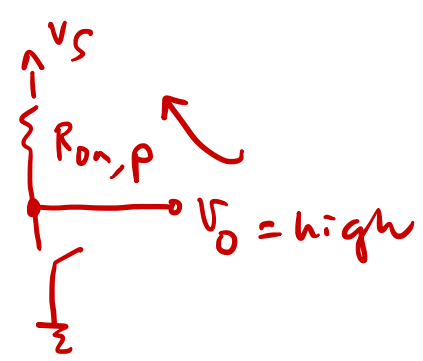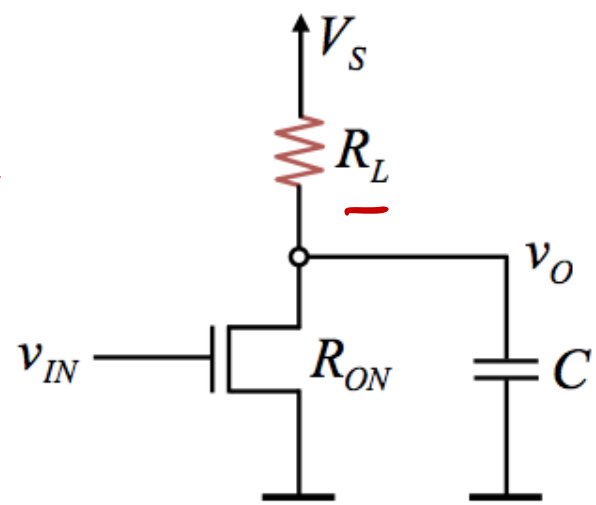

$$R_{on,p} \neq R_{on,n}$$

- When v_I high, pull-up path should behave like open circuit.

Behavior of the Circuit

□ Input HIGH

$$v_I = 5 \text{ V}$$

NMOS on

PMOS off

$$V_o = 0 \text{ V}$$


Input LOW

$$v_I = 0 \text{ V}$$

NMOS off

PMOS on

$$V_o = 5 \text{ V}$$

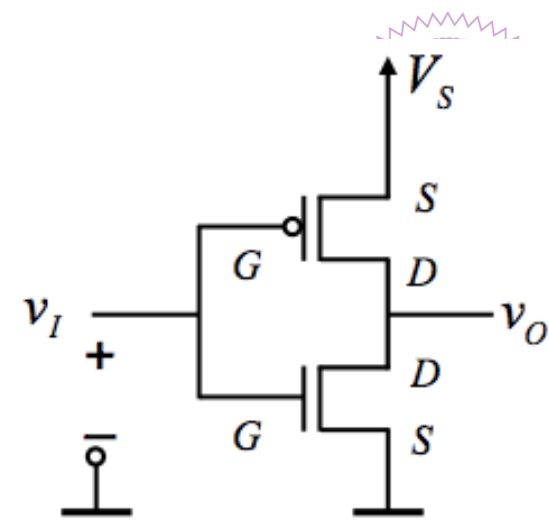

(optional)

(■ Assume $V_{TN} = 1 \text{ V}$ and $V_{TP} = -1 \text{ V}$)

 (

 NMOS on

 $V_{in} \geq V_{TH,n}$

 NMOS off

 $V_{in} < V_{TH,n}$

 PMOS on

 $V_{in} \leq V_{TH,p}$

 PMOS off

 $V_{in} \geq V_{TH,p}$
)


□ Never a path from V_S to ground.

□ Called complementary MOS, 'CMOS' logic.



Power

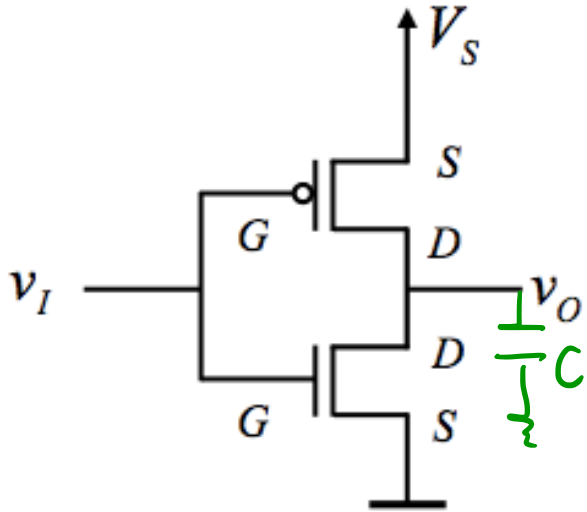
- **Key:** no path from V_S to ground, no static power!



$$P_{\text{dynamic}} = C \cdot V_S^2 \cdot f$$

Practice $V_o = ?$

How

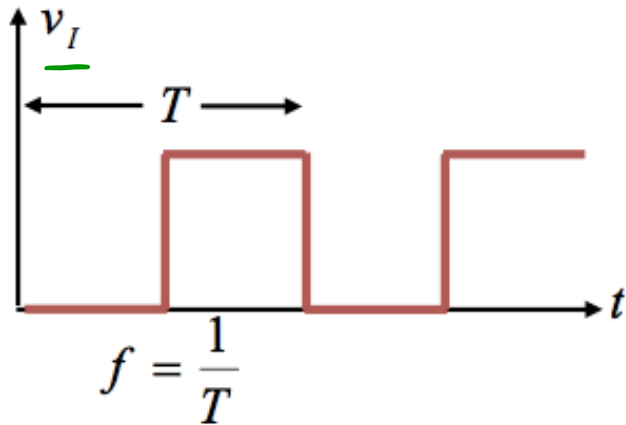



Our Previous Example

- 5 million gates running at 3 GHz
 - With $V_s = 5 \text{ V}$, $C = 1 \text{ fF}$
- Scaling up
 - Increase frequency and number of gates

# Gates	f	\bar{P}
10^6	100 MHz	~2.5 W
2×10^6	300 MHz	~15 W
2×10^6	600 MHz	~30 W
5×10^6	3 GHz	~375 W
25×10^6	3 GHz	~1875 W



How to Reduce Power

o Reduce C (layout, advanced technology)

□ Reduce \bar{V}_S . 1. 降低

□ Turn OFF circuit and/or clock when not in use.

■ Sleep mode, clock gating.

□ Change V_S depending on need.

□ Use multicore to reduce f without sacrificing speed of circuits.

technology $\propto C \cdot V_S^2 \cdot f$

tsmc 0.35um
0.25um
0.18um
90nm


65nm

40nm

28nm

22nm, 16nm/14nm, 10nm,

(3D) FinFET

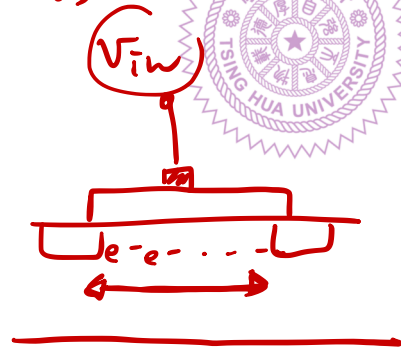

7nm
5nm



3nm
...

# Gates	f	\bar{P}	
2.5×10^6	66 MHz	15 W	Intel Pentium, 0.7 μm , 1993
7.5×10^6	400 MHz	35 W	Intel PII, 0.35 μm , 1997
44×10^6	1 GHz	15 W	Intel PIII, 0.18 μm , 1999
120×10^6	3 GHz	75 W	Intel PIV, 0.13 μm , 2001
615×10^6	0.7 GHz	20 W	Tilera 64-core, 90 nm, 2007
2300×10^6	3.6 GHz	75 W	Intel Nehalem, 8-core, 45 nm, 2011




o Review of lec 8.

* - Static

* - Dynamic

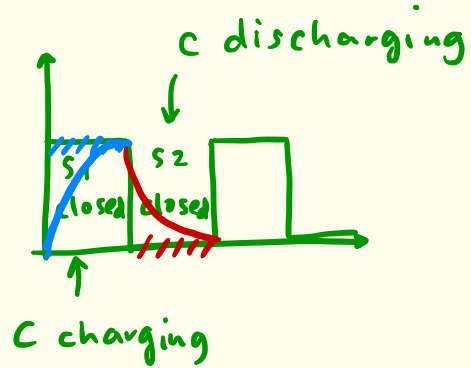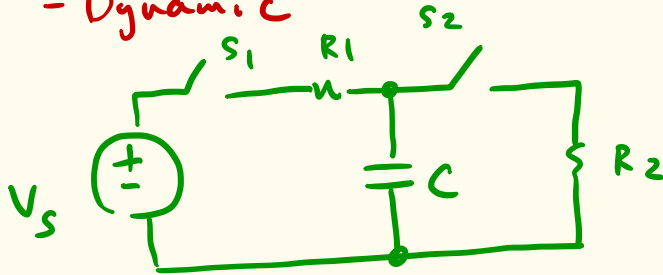

(1) During T_1 , C is charging
(p.10)

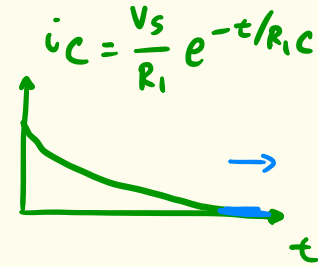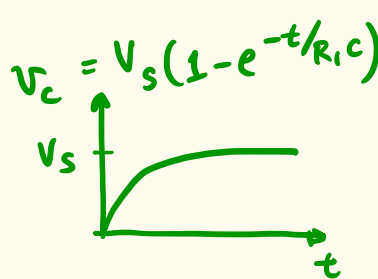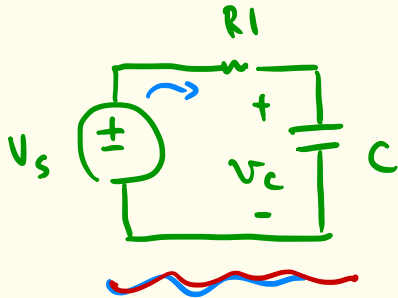


$$P_{\text{static}} = V_s \cdot 0 = 0 \text{ W}$$

$$P_{\text{dynamic}} = P_{\text{cap}} + P_{R_1} = v_c \cdot i_c + (V_s - v_c) \cdot i_c$$

$$= \frac{V_s^2}{R_1} \cdot e^{-t/R_1C}$$

(2) During T_1 to T (total of T_2)

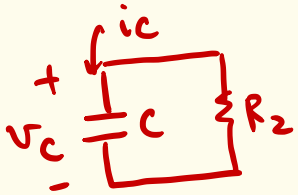


$$P_{\text{static}} = 0$$

$$V_c = V_s e^{-t/R_2 C}, \quad i_c = \frac{-V_c}{R_2}$$

$$\text{Energy dissipated by } R_2 = \int_0^{T_2} V_c \cdot (-i_c) dt$$



$$= \int_0^{T_2} \frac{V_s^2}{R_2} e^{-2t/R_2 C} dt$$
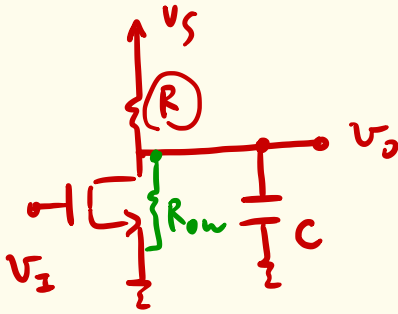
$$= \frac{V_s^2}{R_2} \cdot \frac{1}{2} R_2 C = \frac{V_s^2}{2} C$$



①

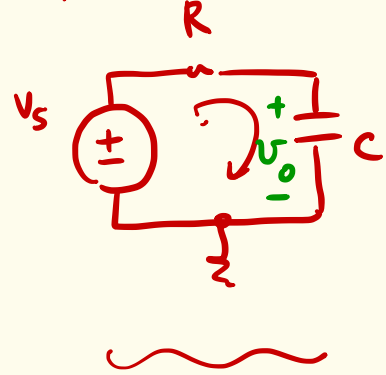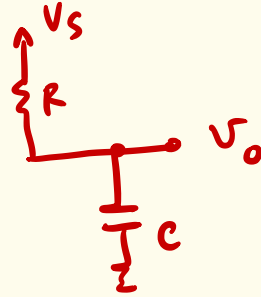$V_I = \text{low}, V_O = \text{high}, C \text{ charging}$



$P_{\text{static}} = 0$

$$V_O = V_S - V_S \frac{R_L}{R_L + R_{ow}} e^{-t/R_L C}$$

$$E_R = \int_0^{T/2} (V_S - V_O) \cdot i_C dt = \int_0^{T/2} \frac{V_S^2}{(R_L + R_{ow})^2} \cdot R_L \cdot e^{-2t/R_L C} dt = \frac{V_S^2 \cdot R_L^2}{(R_L + R_{ow})^2} \cdot \frac{C}{2}$$

$$= \frac{V_S^2}{2} \cdot C \cdot \frac{R_L^2}{(R_L + R_{ow})^2}$$

(charging)


$$E_{cap} = \int_0^{T/2} V_C \cdot i_C dt$$

$$i_C = C \frac{dV_C}{dt} = i_R = \frac{V_S - V_C}{R}$$


$$= \int_0^{T/2} \left(V_S - V_S \frac{R_L}{R_{on} + R_L} e^{-t/RC} \right) \cdot \left(\frac{V_S}{R_{on} + R_L} \cdot e^{-t/RC} \right) dt$$

$$= \frac{1}{2} C V_S^2 \cdot \frac{R_L^2 + 2R_{on}R_L}{(R_{on} + R_L)^2} = \frac{1}{2} C \cdot V_{C,final}^2 - \frac{1}{2} C \cdot V_{C,initial}^2$$
$$= \frac{1}{2} C \cdot V_S^2 - \frac{1}{2} \cdot C \cdot V_S^2 \left(\frac{R_{on}}{R_L + R_{on}} \right)^2 \quad (2)$$

$t=0$

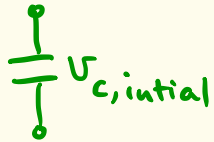


$t=T/2$

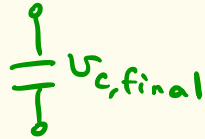

(P.14)

C discharging

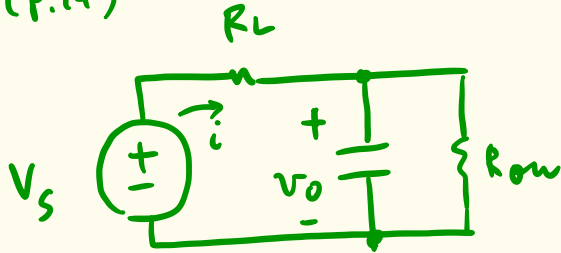

$$V_0 = V_s \frac{R_{0w}}{R_L + R_{0w}} + \left(V_s - V_s \frac{R_{0w}}{R_L + R_{0w}} \right) \cdot e^{-t/\tau}$$

$$\tau = (R_L \parallel R_{0w}) \cdot C$$


$$\text{Energy provided by } V_s = \int_0^{T/2} V_s \cdot i \, dt = \int_0^{T/2} V_s \cdot \frac{V_s - V_0}{R_L} \, dt \quad \checkmark$$

$$= \int_0^{T/2} \frac{V_s^2}{R_L + R_{0w}} (1 - e^{-t/\tau}) \, dt = \frac{V_s^2}{R_L + R_{0w}} \left(t + \tau \cdot e^{-t/\tau} \right) \Big|_0^{T/2}$$

$$= \frac{V_s^2}{R_L + R_{0w}} \left(T/2 - 0 + \tau e^{-T/2\tau} - \tau \right)$$

$$= \frac{V_s^2}{R_L + R_{0w}} \cdot \frac{T}{2} - \frac{V_s^2 \cdot R_L \cdot R_{0w} \cdot C}{(R_L + R_{0w})^2} \quad \textcircled{1}$$
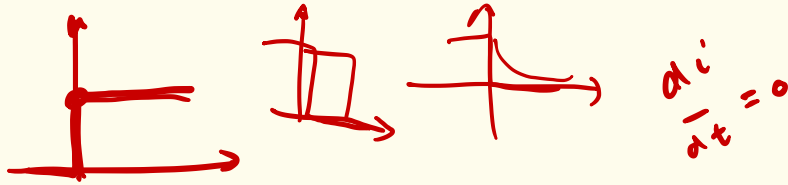
$$\textcircled{1} + \textcircled{2} = \text{P.14}$$



$$V_s + \left(V_s \cdot \frac{R_{on}}{R_L + R_{on}} - V_s \right)$$

