



Electric Circuits

Lecture 9 Second-Order Systems

EE2210, Fall 2022

Jenny Yi-Chun Liu

jennyliu@gapp.nthu.edu.tw


Lecture Outline

- Chapter 9 in the textbook





An Inverter Chain Example

- With C_{GS} of NMOS on node B.

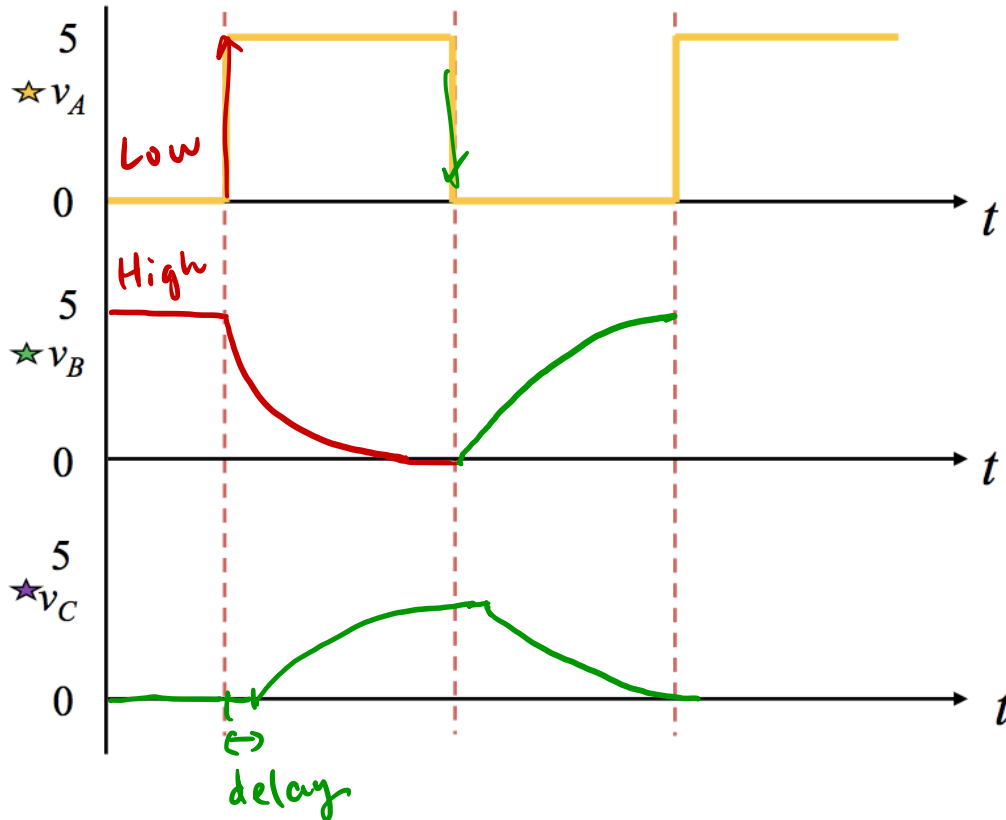

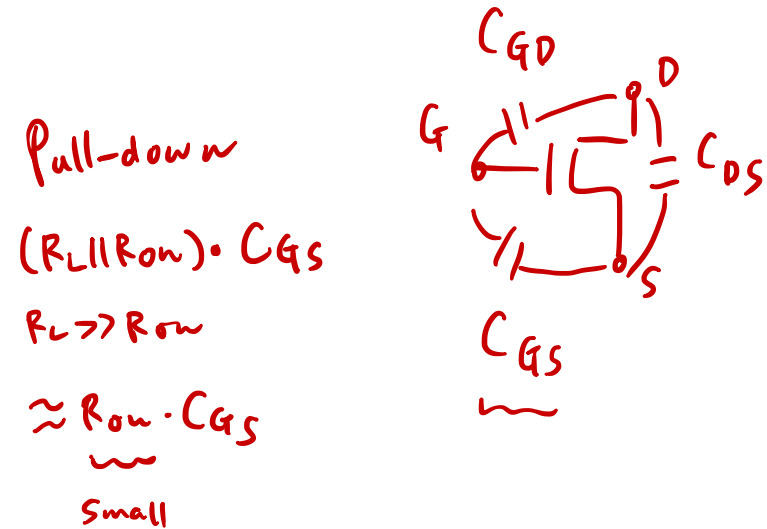
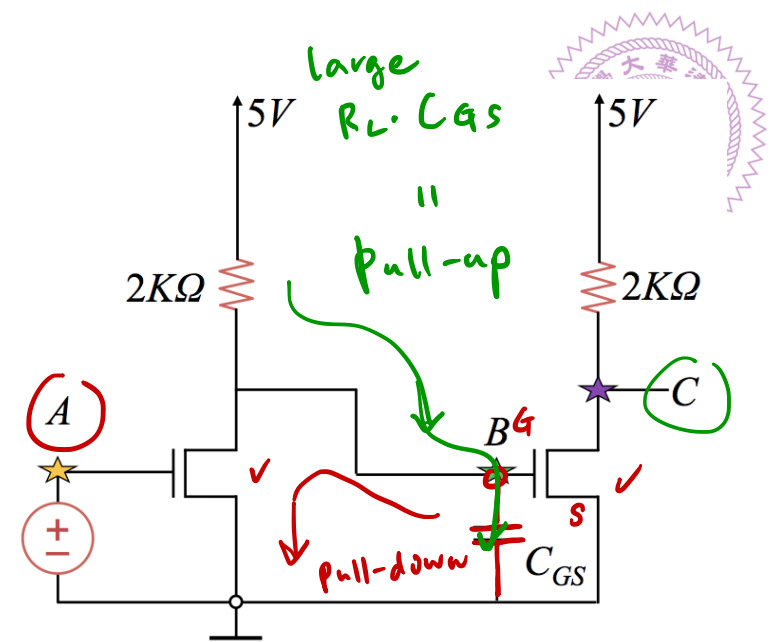
- Slow rise time and delay in signal.
- We can try to increase the speed with a smaller R_L (from 2 k Ω to 50 Ω).





Observed Output – Fast Case

- With C_{GS} of NMOS on node B.

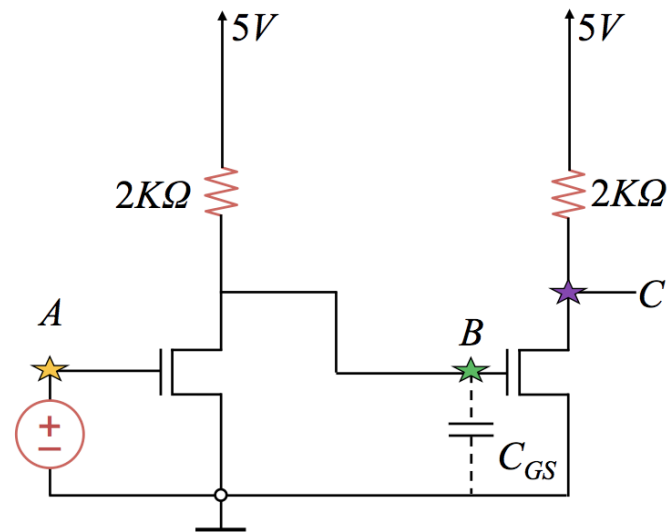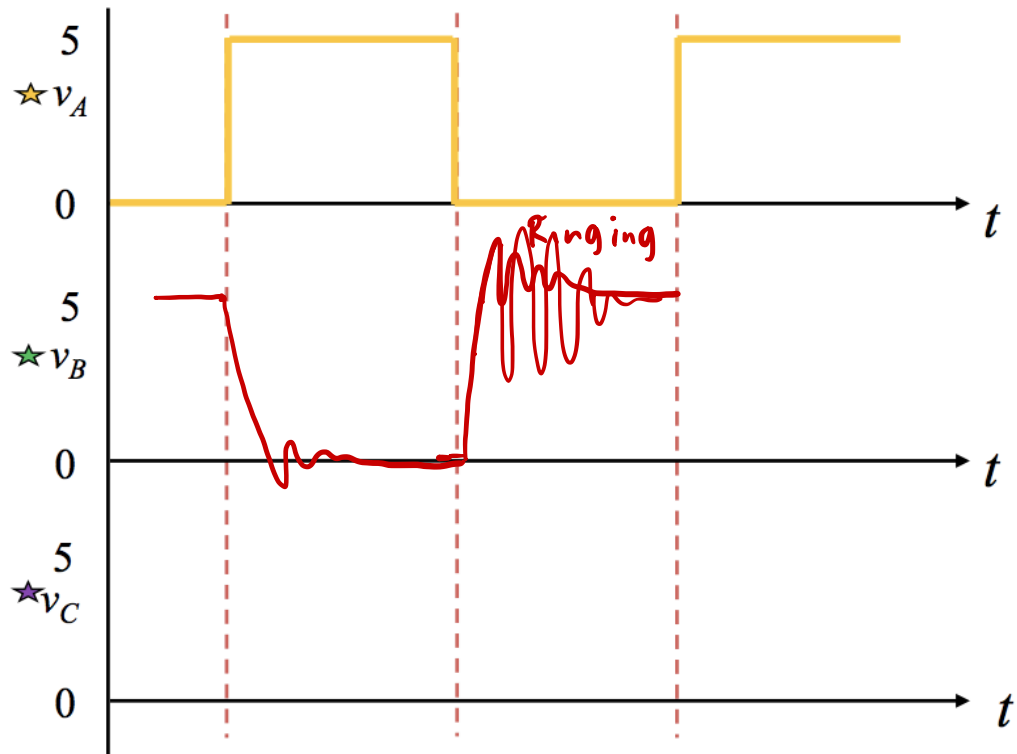



- ringing behavior observed!!




Fast Case – What's Really Going On

寄生

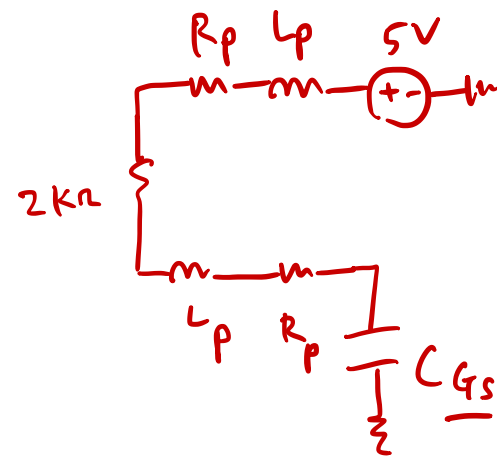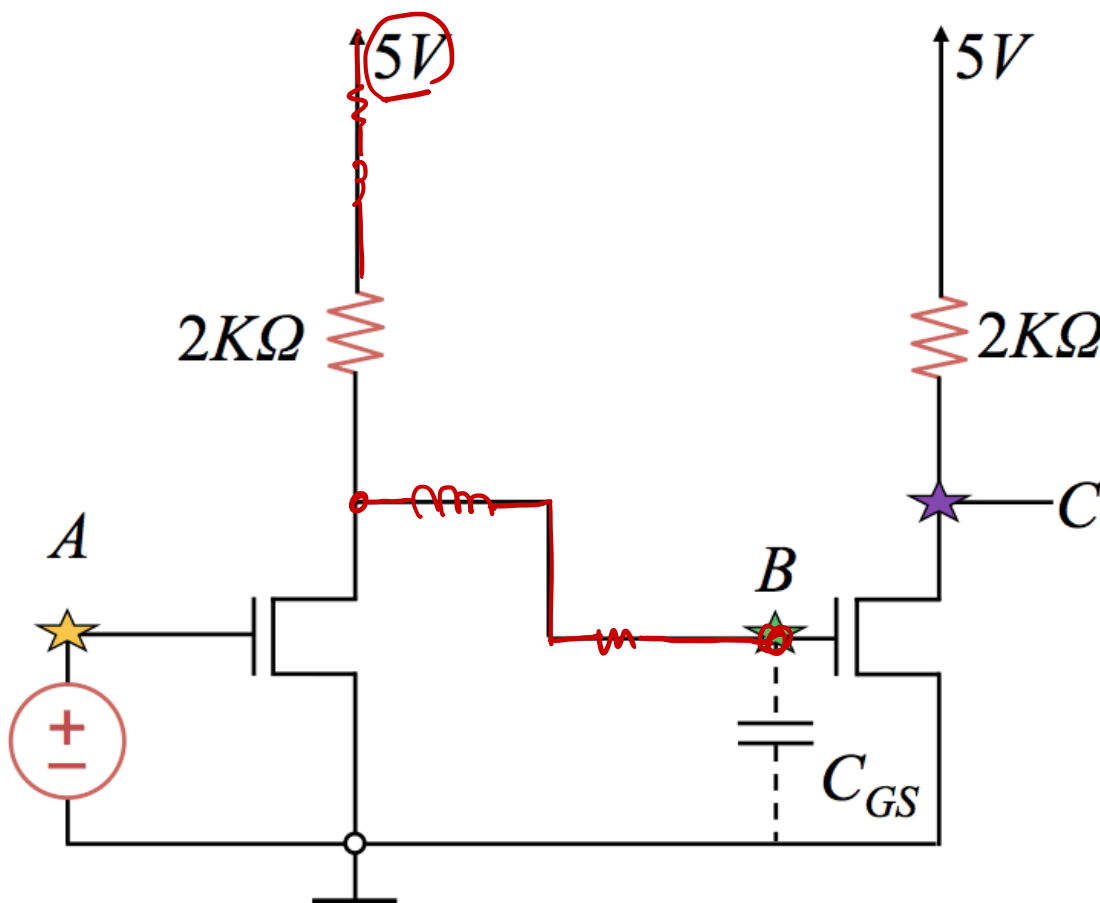
- The parasitic inductance of the wire is included.






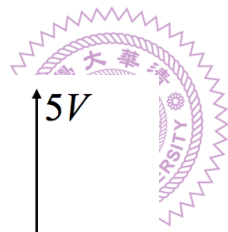


Second-Order Systems

- Involving R, L, C circuit elements.

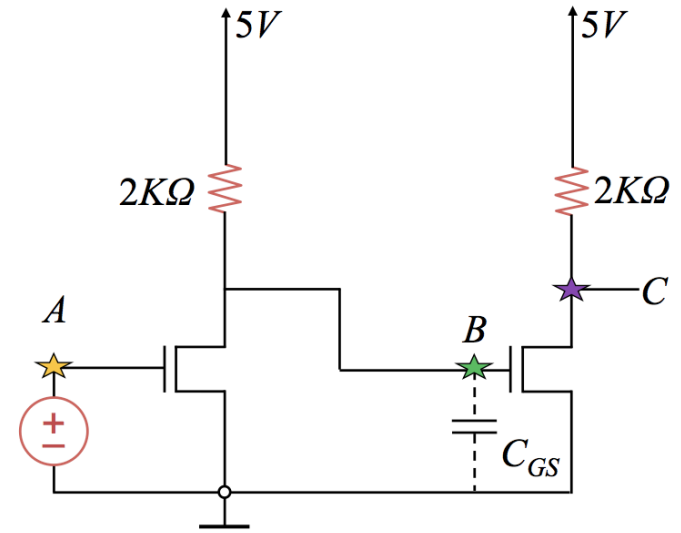

- Relevant circuit model

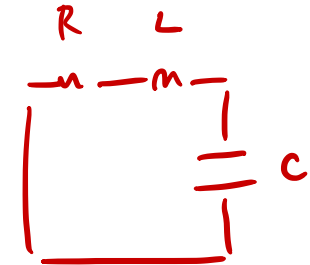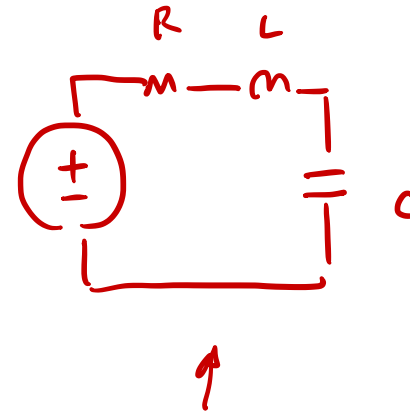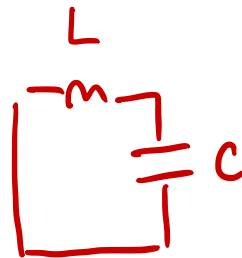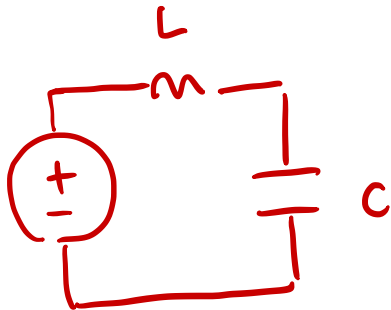


- Two energy-storage elements → second-order system



First, Let's Analyze the LC Network

□ We will introduce R into the circuit later.

□ Node method

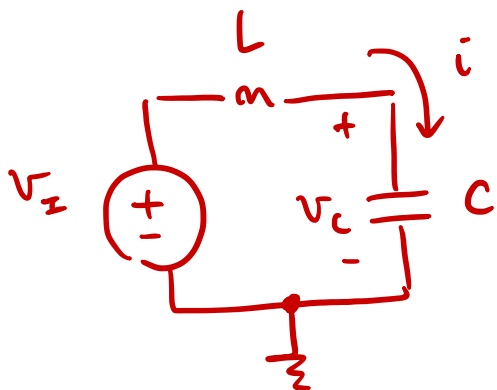

$$i = C \frac{dv_C}{dt} = \frac{1}{L} \int_{-\infty}^t (v_I - v_C) dt$$

$$\frac{d}{dt} \rightarrow C \frac{d^2 v_C}{dt^2} = \frac{1}{L} (v_I - v_C)$$

$$\Rightarrow LC \frac{d^2 v_C}{dt^2} + v_C = v_I$$

Given $v_C(0), v_C'(0)$



Method of Particular and Homogeneous Solutions

□ Four-step procedure


✓
$$LC \frac{d^2 v}{dt} + v = v_I$$

1. Find the particular solution
2. Find the homogeneous solution
 - Four-step procedure
3. The total solution is the sum of the particular solution and homogeneous solution.
4. Use initial condition to solve for the remaining constraints.



Let's Solve

Consider $v_I(t) = V_I \cdot u(t)$

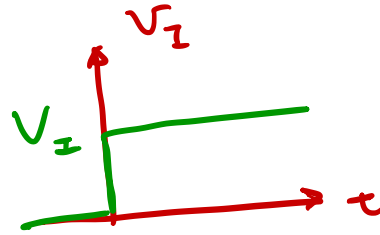

Given $v_c(0) = 0$
initial conditions $i(0) = 0$

$$\left(i = C \frac{dv_c}{dt} \quad \frac{dv_c}{dt}(t=0) = 0 \right)$$

Zero-state response, $v_c(t)$, $t > 0$



1. Particular Solution

$$LC \frac{d^2 v_c}{dt^2} + v_c = V_{\text{I}}$$

Guess that $v_{c,p} = K$

$$LC \cdot 0 + K = V_{\text{I}}$$

$$v_{c,p} = V_{\text{I}}$$



2. Homogeneous Solution

□ Look for solution to $LC \frac{d^2 v_{CH}}{dt^2} + v_{CH} = 0$

□ Four-step method:

1) Assume $v_{CH} = Ae^{st}$

2) $LC \cdot A \cdot s^2 \cdot e^{st} + Ae^{st} = 0$

$\Rightarrow (LCs^2 + 1) e^{st} = 0$

$\Rightarrow LCs^2 + 1 = 0$ characteristic equation

3) $s^2 = \frac{-1}{LC} \Rightarrow s = \pm j \cdot \sqrt{\frac{1}{LC}} \quad j^2 = -1, j = \sqrt{-1}$

$= \pm j \cdot \omega_0$

$\omega_0 = \sqrt{\frac{1}{LC}}$: natural frequency of LC circuit (rad/s)

$\frac{\omega_0}{2\pi} = f_0 = \text{natural frequency (Hz)}$

4) $v_{CH} = A_1 e^{j\omega_0 t} + A_2 e^{-j\omega_0 t}$



3. Total Solution

$$v_c = v_{ch} + v_{cp} = \underbrace{A_1 e^{j\omega_0 t} + A_2 e^{-j\omega_0 t}} + V_I, \quad \omega_0 = \sqrt{\frac{1}{LC}}$$

4. Find unknowns from initial conditions

$$v_c(0) = 0 = A_1 + A_2 + V_I \quad (1)$$

$$i(0) = 0 = C \cdot \frac{dv_c}{dt} \Big|_{t=0} = C \cdot A_1 \cdot j\omega_0 \cdot e^{j\omega_0 t} - C \cdot A_2 \cdot j\omega_0 \cdot e^{-j\omega_0 t} \Big|_{t=0}$$
$$= C j\omega_0 (A_1 - A_2) \quad (2)$$

$$\Rightarrow \begin{cases} A_1 + A_2 = -V_I \\ A_1 - A_2 = 0 \end{cases} \Rightarrow A_1 = A_2 = -\frac{V_I}{2}$$

$$v_c = -\frac{V_I}{2} e^{j\omega_0 t} - \frac{V_I}{2} e^{-j\omega_0 t} + V_I, \quad \omega_0 = \sqrt{\frac{1}{LC}}$$



3. Total Solution

□ Remember Euler relation: $e^{jx} = \cos x + j \sin x$


$$v_C = v_I - v_I \cdot \cos(\omega_0 t)$$

$$i = C \cdot v_I \cdot \omega_0 \cdot \sin(\omega_0 t)$$




Plotting the Total Solution

$$v_c(t) = V_I - V_I \cos \omega_0 t$$

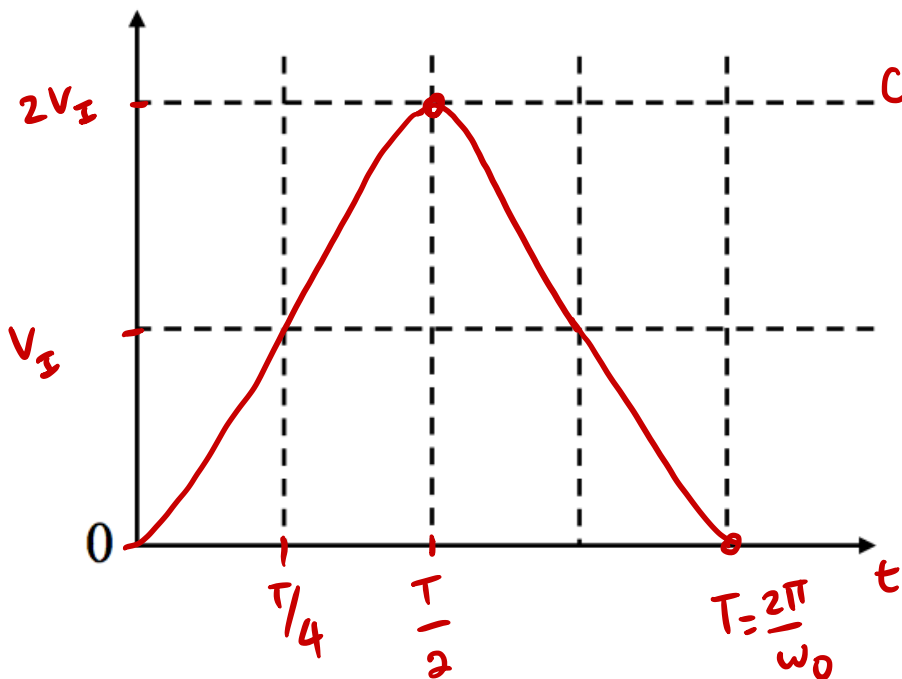
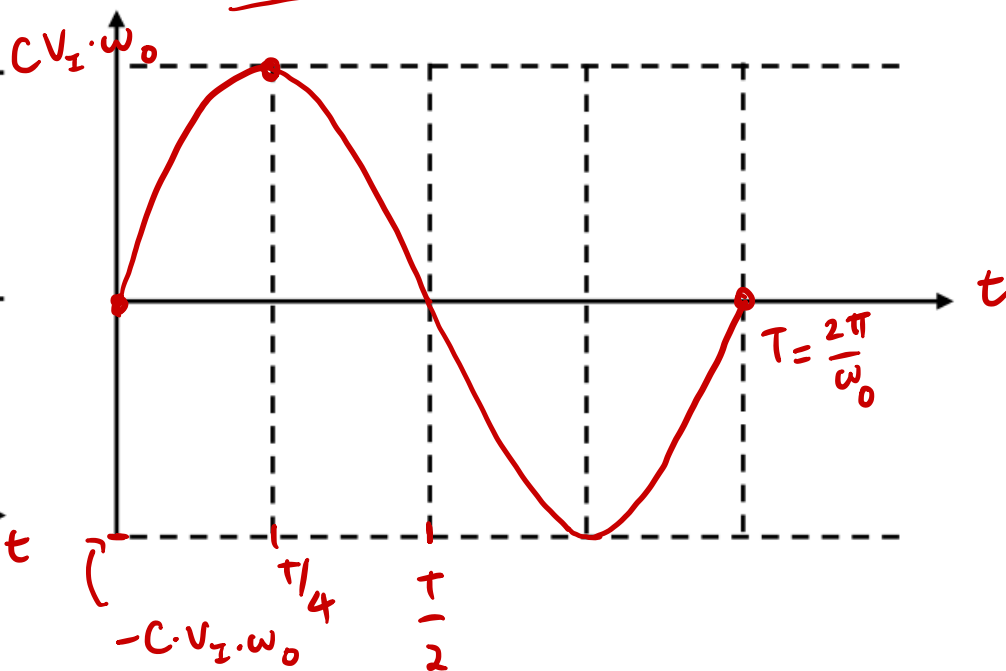
$$i(t) = C \cdot V_I \cdot \omega_0 \cdot \sin \omega_0 t$$



- $i(t)$ leads $v_c(t)$ by $T/4$
- $v_c(t)$ lags $i(t)$ by $T/4$

Practice $V_L = ?$

V_L leads or lags i by ?




Summary of Method

- ✓ 1. Write DE for circuit by applying node method.
2. Find particular solution v_P by guessing and trial & error.
3. Find homogeneous solution v_H .
 - A. Assume solution of the form. Ae^{st}
 - B. Obtain characteristic equation. s^2
 - C. Solve characteristic equation for roots s_i .
 - D. Find v_H by summing $A_i \cdot e^{s_i t}$ terms.
4. Total solution is $v_P + v_H$, then solve for remaining constants using initial conditions.
(A_i)



Example – Undriven LC Network Response

- What if we have:

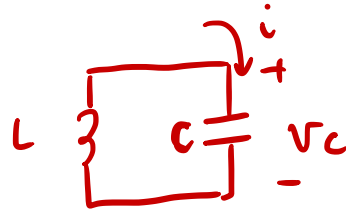

- We can obtain the answer directly from the homogeneous solution (with $v_I = 0$).

$$LC \frac{d^2 v_c}{dt^2} + v_c = 0$$

Given $v_c(0) = V_1$, $i(0) = 0$

$$v_c(t) = A_1 e^{j\omega_0 t} + A_2 e^{-j\omega_0 t}$$

$$\begin{cases} A_1 + A_2 = V_1 \\ CA_1 j\omega_0 - CA_2 j\omega_0 = 0 \end{cases} \Rightarrow A_1 = A_2 = \frac{V_1}{2}$$


$$v_c(t) = \frac{V_1}{2} (e^{j\omega_0 t} + e^{-j\omega_0 t}) = \frac{V_1}{2} \cdot 2 \cos \omega_0 t = V_1 \cdot \cos \omega_0 t$$

(oscillator)
振荡器




Undriven LC Network Response

$$v_c = V_1 \cdot \cos \omega_0 t$$

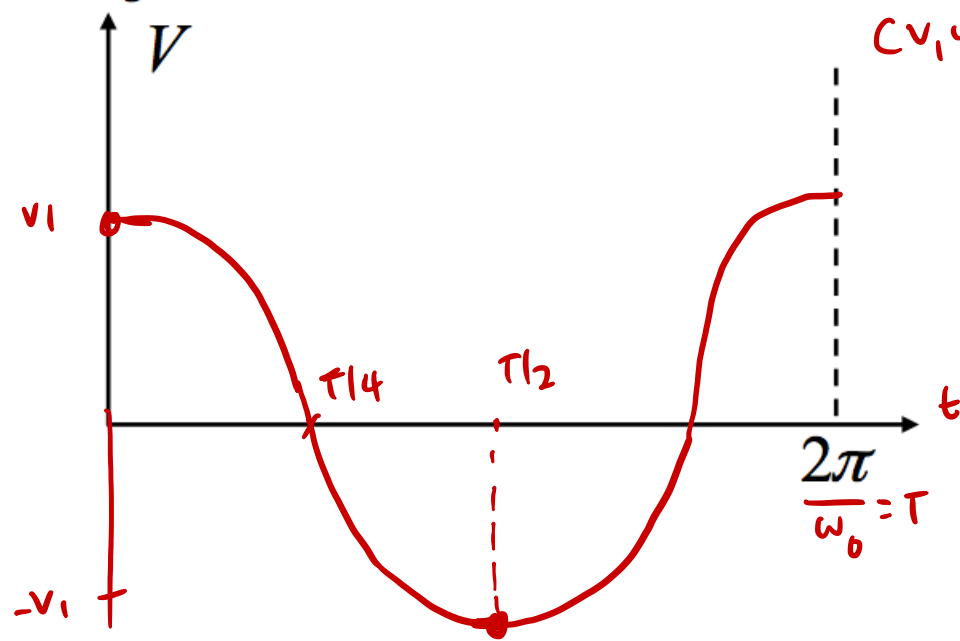
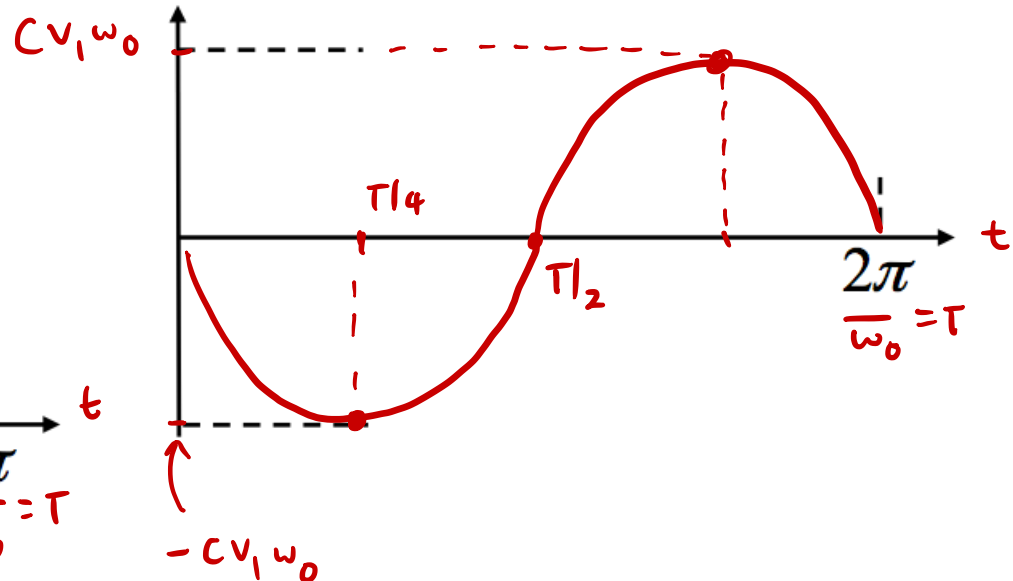
$$i_c = -C \cdot V_1 \cdot \omega_0 \cdot \sin \omega_0 t$$







i_c leads v_c by $\frac{T}{4}$

$$\frac{V_{\text{peak}}}{i_{\text{peak}}} = \sqrt{\frac{V_1}{C V_1 \omega_0}} = \sqrt{\frac{1}{C \omega_0}} = \sqrt{\frac{L}{C}}$$

characteristic impedance of LC
 $\beta \Omega \text{ in}^2$

Energy

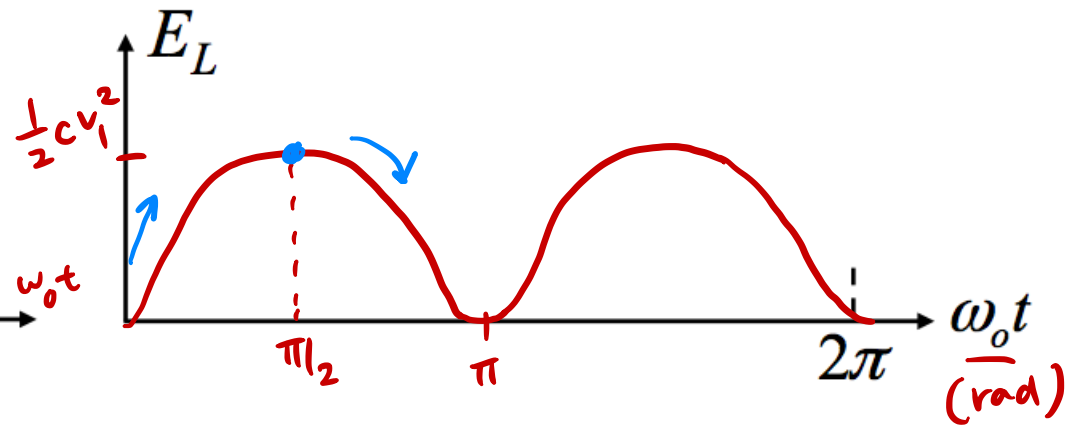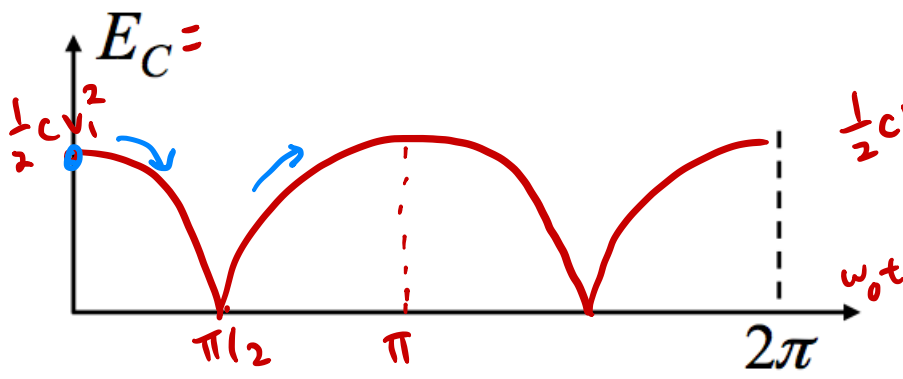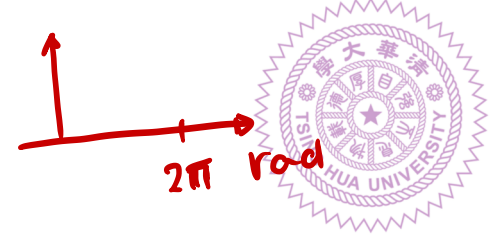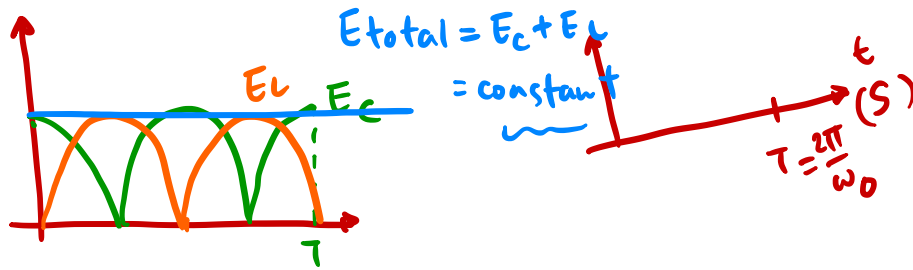

$$E_C = \frac{1}{2} C \cdot v_c^2 = \frac{1}{2} C \cdot (V_1 \cos \omega_0 t)^2$$

$$= \frac{1}{2} C V_1^2 \cos^2 \omega_0 t$$

$$E_{C,max} = \frac{1}{2} C V_1^2$$

$$E_L = \frac{1}{2} L \cdot i^2 = \frac{1}{2} L \cdot (-C V_1 \omega_0 \sin \omega_0 t)^2$$

$$= \frac{1}{2} L \cdot C^2 \cdot V_1^2 \cdot \omega_0^2 \cdot \sin^2 \omega_0 t$$

$$E_{L,max} = \frac{1}{2} L C^2 \cdot V_1^2 \cdot \frac{1}{LC} = \frac{1}{2} C V_1^2$$

$$E_C + E_L = C V_1^2 = \text{constant}$$

- Total energy in the system is a constant, but it goes back and forth between the capacitor and the inductor.