

Analog IC Design Homework 1




學號: 102061112


姓名: 謝博楊

1.

Schematic:

 

Waveform:

 

Comments:

(a) The capacitance is 218fF.


(b) The capacitance is same as (a), 218fF. Since $C_{gs} = C_{ox} \cdot W \cdot L$ proportional to $W \cdot L$, with $W \cdot L = 25 \mu\text{m}^2$. Besides, five capacitors with the same value C parallel with each other is the same as a single capacitor with value $5C$.

(c) The capacitance is slightly smaller, 206fF. Though having the same $W \cdot L$ with that of (a) and (b), from the formula $I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH})^2$, the current proportional to W/L is smaller in case (c), so the depletion region is a little smaller, result in less electrons in inversion layer, so the capacitance is slightly smaller.

(i) When $V_{GS} < 0$, the device is off, and will attract holes to accumulate under the oxide, and can be seen as a capacitor with value C_{ox} per unit area, so $C_{g,total} = C_{ox} WL$. When $V_{GS} < V_{th}$, a depletion region begins to form, so $C_{g,total} = C_{ox} WL$ in series with C_{dep} . When $V_{GS} > V_{th}$, the oxide-silicon interface sustains a channel, so $C_{g,total} = C_{gb} + C_{gd} + C_{gs} = 0 + 1/2 C_{ox} WL + 1/2 C_{ox} WL = C_{ox} WL$.


2.

Schematic:

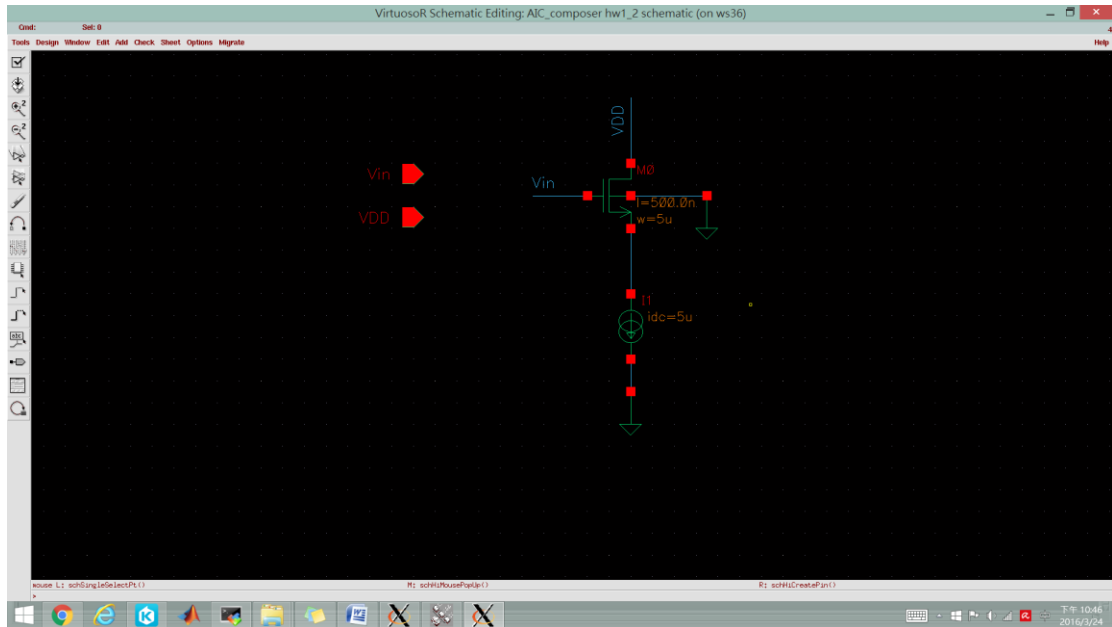

(a)

Waveform:

 

Comments:

(i) From the figure above:

$V_{out}=1.18V$ at $V_{in}=1.8V$.

The slope is 0.873 at $V_{out}/2=590mV$.


The slope within 0.5% variation is about from 0.868 to 0.877.

The linear range: V_{in} is from 1.02V to 1.24V, with the corresponding V_{out} from 492mV to 691mV.

The DC offset is $1.02-0.492=528mV$, and $1.24-0.691=549mV$.

(b)

Waveform:

 

Comments:

(i) From the figure above:

$V_{out}=1.34V$ at $V_{in}=1.8V$.

The slope is 984m at $V_{out}/2=670mV$.

The slope within 0.5% variation is about from 979m to 988m.

The linear range: V_{in} is from 9.96mV to 1.8V, with the corresponding V_{out} from -422mV to 1.34V.


DC offset is $9.96\text{m} + 422\text{m} = 431.96\text{mV}$, and $1.8 - 1.34\text{m} = 460\text{mV}$.

(ii) The DC offset is smaller than that of (a), because with body connected to source node, the body effect is reduced, V_{TH} becomes a little smaller than that of (a), and with I_1 remain the same, $V_{in} - V_{out}$ needs to be a little smaller.

$$(I_1 = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{in} - V_{out} - V_{TH})^2)$$

(c)

Waveform:

 

Comments:

(i) From the figure above:

$V_{out} = 630\text{mV}$ at $V_{in} = 1.8\text{V}$.

The slope is 857m at $V_{out}/2=310mV$.

The slope within 0.5% variation is about from 853m to 900m.

The linear range: (we consider $V_{out}>0$)

V_{in} is from 1.34V to 1.8V, with the corresponding


V_{out} from 232mV to 630mV.

DC offset is $1.34-232m=1.108V$, and $1.8-0.63=1.17V$.

(ii) The DC offset is much bigger than that of (a), because we need to provide a larger $V_{in} - V_{out}$, in order to provide a much larger current I_1 . ($I_1 = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{in} - V_{out} - V_{TH})^2$)

(d)

Waveform:

 

Comments:

(i) From the figure above:

$V_{out}=1.27V$ at $V_{in}=1.8V$.

The slope is 874m at $V_{out}/2=635mV$.

The slope within 0.5% variation is about from 869m to 878m.

The linear range:

V_{in} is from 954mV to 1.19V, with the corresponding


V_{out} from 527mV to 729mV.

DC offset is $954m-527m=427mV$, and $1.19-729m=461mV$.


(ii) The DC offset is smaller than that of (a), because with I_1 remaining the same, W/L becomes bigger, $V_{in} - V_{out}$ must become smaller.

3.

Schematic:

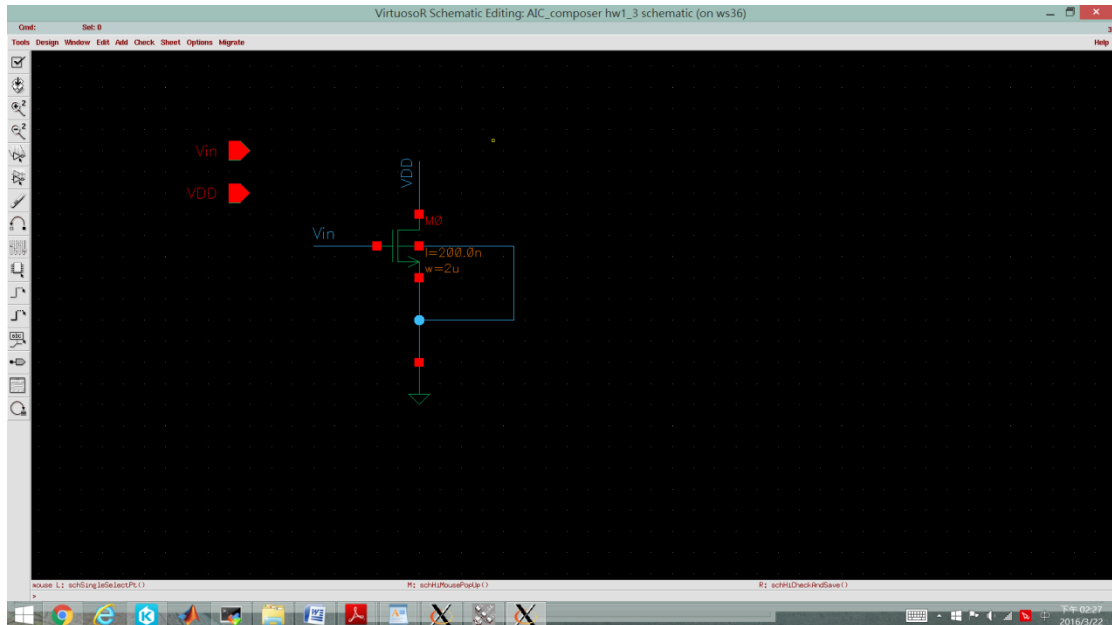

Waveform:

 

Comments: (Channel Modulation Effect)

(i) The actual length of the inverted channel gradually decreases as the potential difference between gate and drain


increases. So to the same device, as V_{GS} increases, the slope in the saturation region will have bigger change.

(ii) $I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH})^2 (1 + \lambda V_{DS})$, and λ is proportional to $\frac{1}{L}$, so with the same V_{GS} , the device with shorter channel length will have higher drain current. As shown in the figure above, the waveform on the top is the device with $W/L = 2\mu\text{m}/0.2\mu\text{m}$, and the one at bottom is the device with $W/L = 2\mu\text{m}/2\mu\text{m}$.


(iii) I_D is proportional to $(V_{GS} - V_{TH})^2$, so with the same channel length, larger V_{GS} means larger I_D .

4.

Schematic:

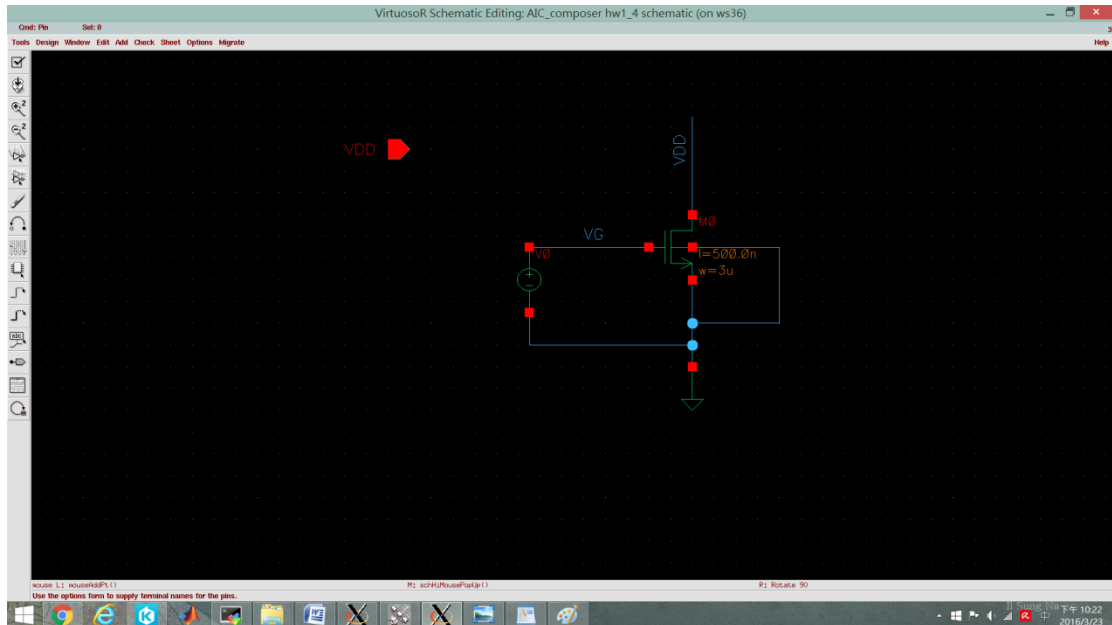

Waveform:

 

Comments:

(i) When the device is off, $C_{GD} = C_{GS} = C_{ov} W$.


(ii) When the device is in saturation region, $C_{GD} = C_{ov}W$. And the potential difference varies from V_{GS} at the source to $V_{GS} - V_{TH}$ at the pinch-off point, resulting in an inhomogeneous electric field, $C_{GS} = C_{ov}W + \frac{2C_{ox}WL}{3}$.

(iii) When the device is in deep triode region, the source and drain voltage are almost the same, and the capacitance between the gate and the channel $C_{ox}WL$ can be separate evenly by source and drain, so


$$C_{GD} = C_{GS} = C_{ov}W + \frac{C_{ox}WL}{2}.$$

5.

Schematic:

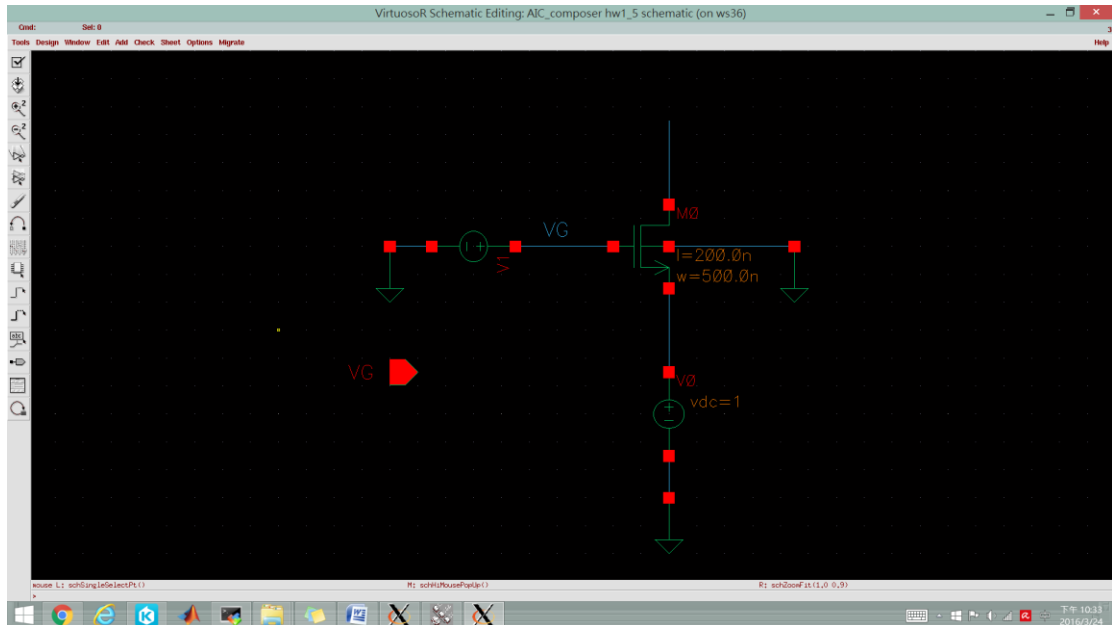

Waveform:

 

Comment:

(i) When $V_{GS} < V_{Th}$, the device is in cutoff region, $I_D = 0$, so

$$R_{on} = \infty$$

(ii) When $V_{GS} > V_{Th}$, if $V_{DS} \ll 2(V_{GS} - V_{Th})$, $R_{on} =$
 $(\mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH}))^{-1}$, so when V_{GS} becomes bigger, R_{on}
will become smaller, as shown in the figure.