

# Analog IC Design Homework 2




學號: 102061112

姓名: 謝博楊


1.

Schematic:


(a)

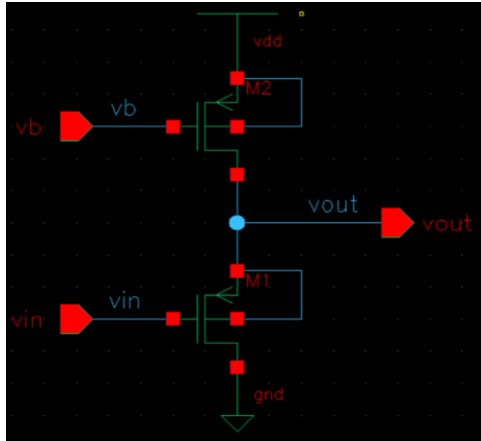


(b)

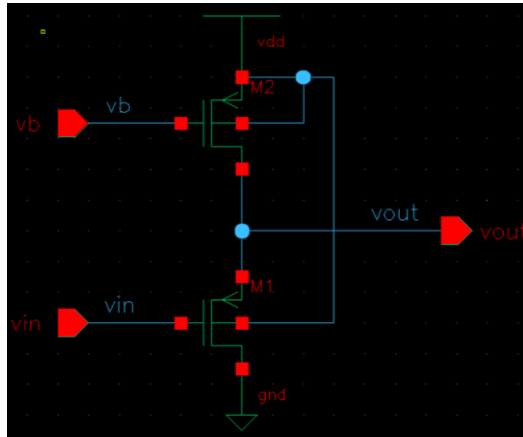

(a) The voltage gain  $> 0.95$ :

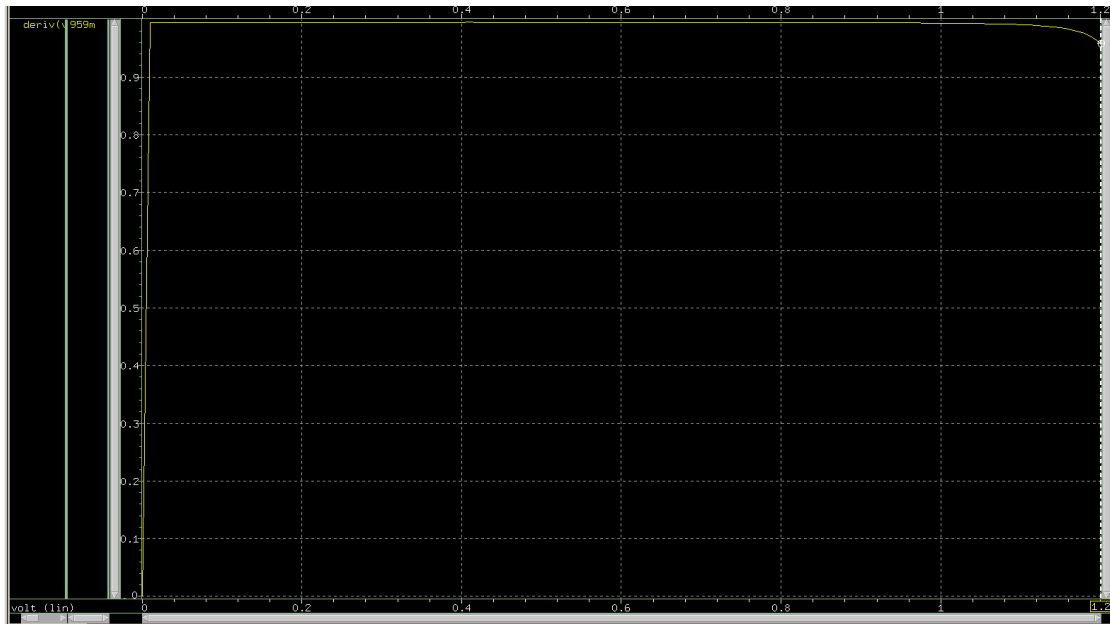


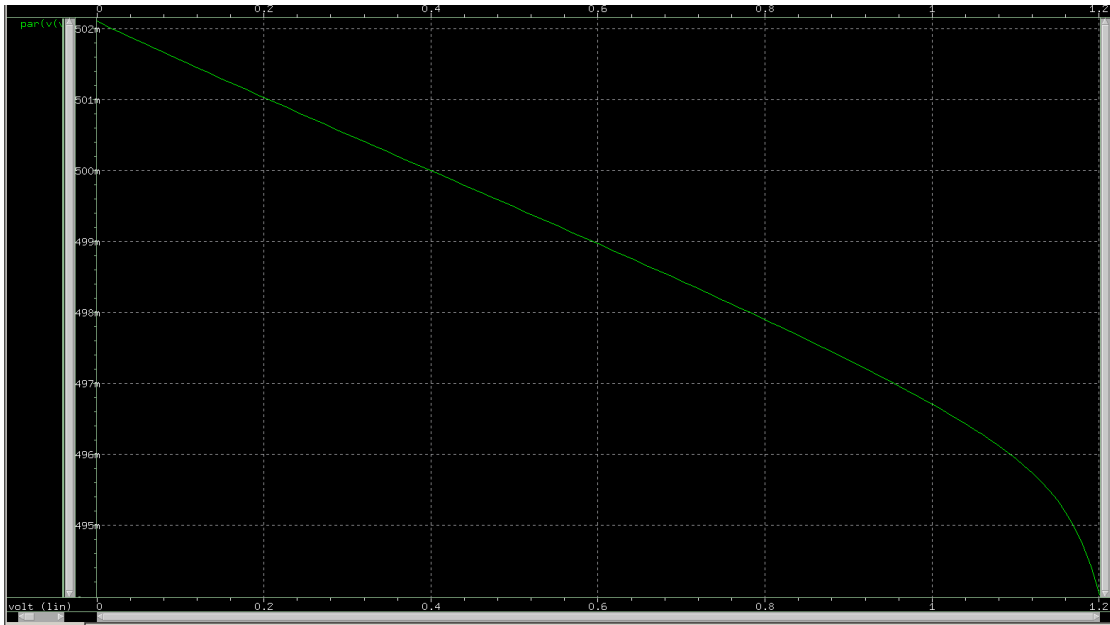The Vout-Vin transfer curve is almost the same for Vin from 0~1.2V:




Level shift is almost the same, because our gain is close to 1.

(b) The voltage gain  $> 0.75$ :

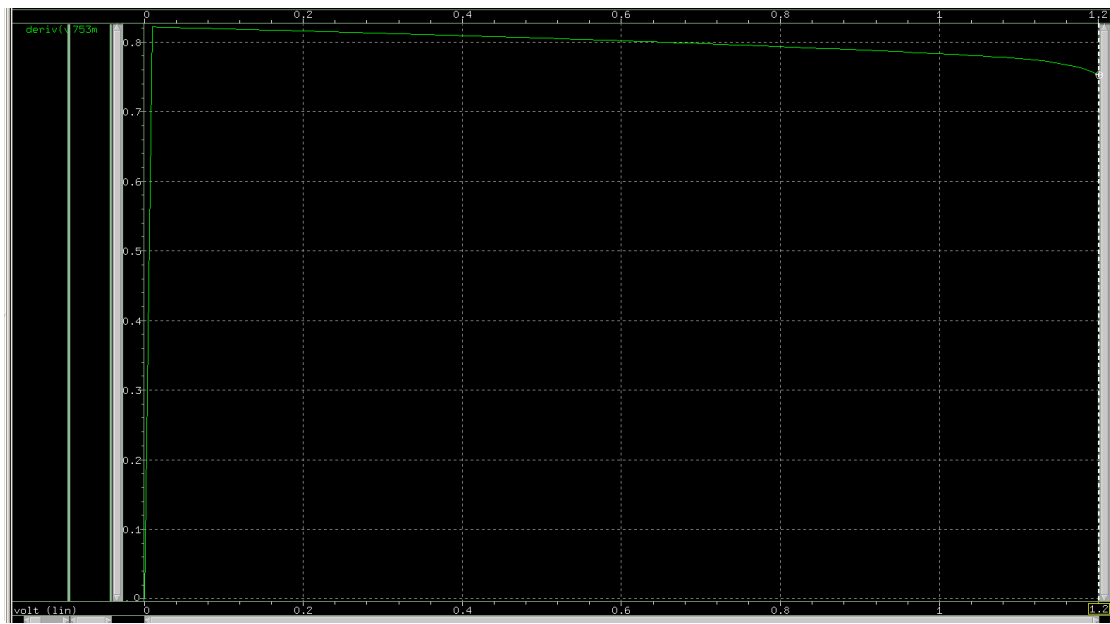

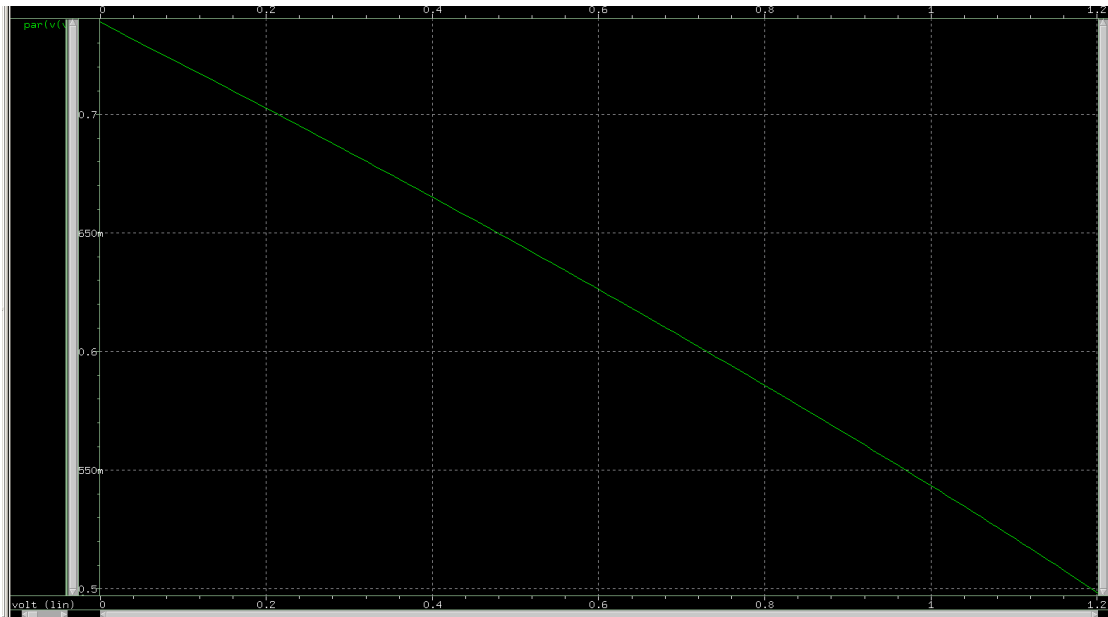The  $V_{out}$ - $V_{in}$  transfer curve:




(c)

case (b) has body effect, so the gain is  $(1/(g_m + g_{nb}))$ , so the gain is smaller than (a)


2.

Schematic:

(a)

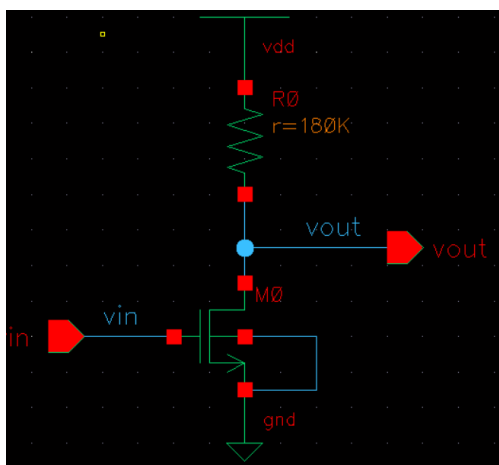


(b)

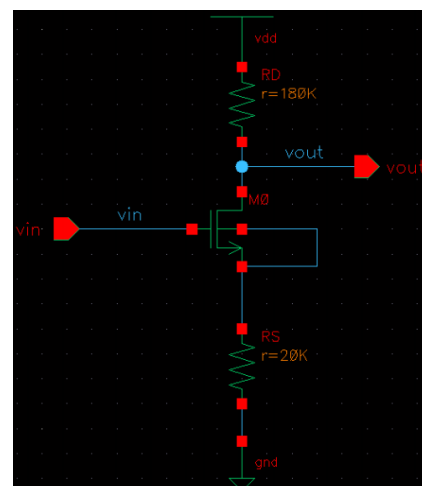

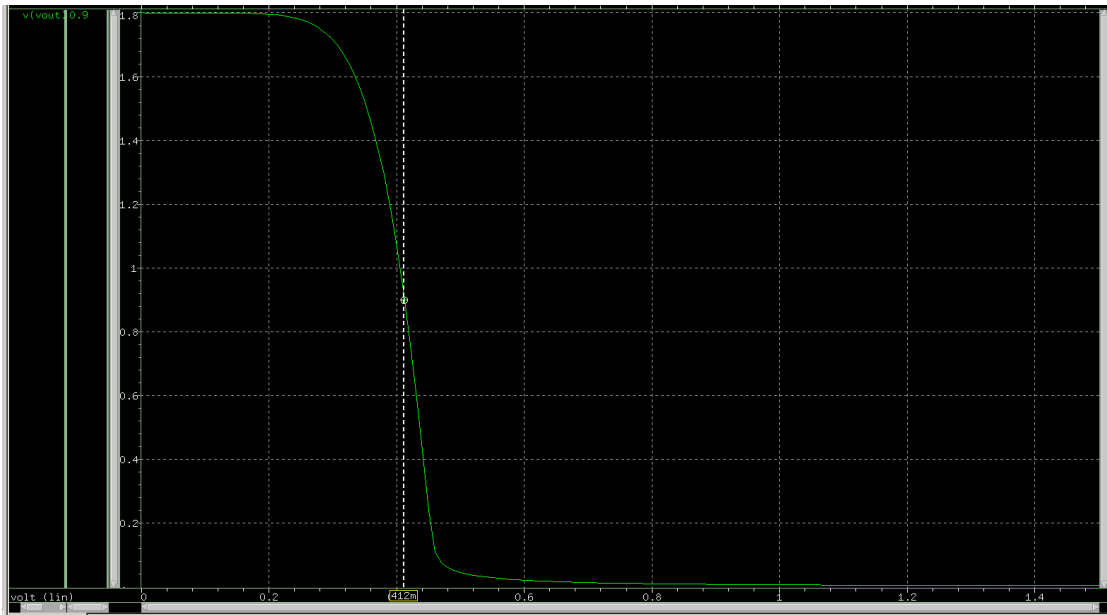
(a) Design:

The size of M1(W/L) = 8.5u/1u,


and when  $V_{in} = 412\text{mV}$ ,  $V_{out} = 0.9\text{V}$ .



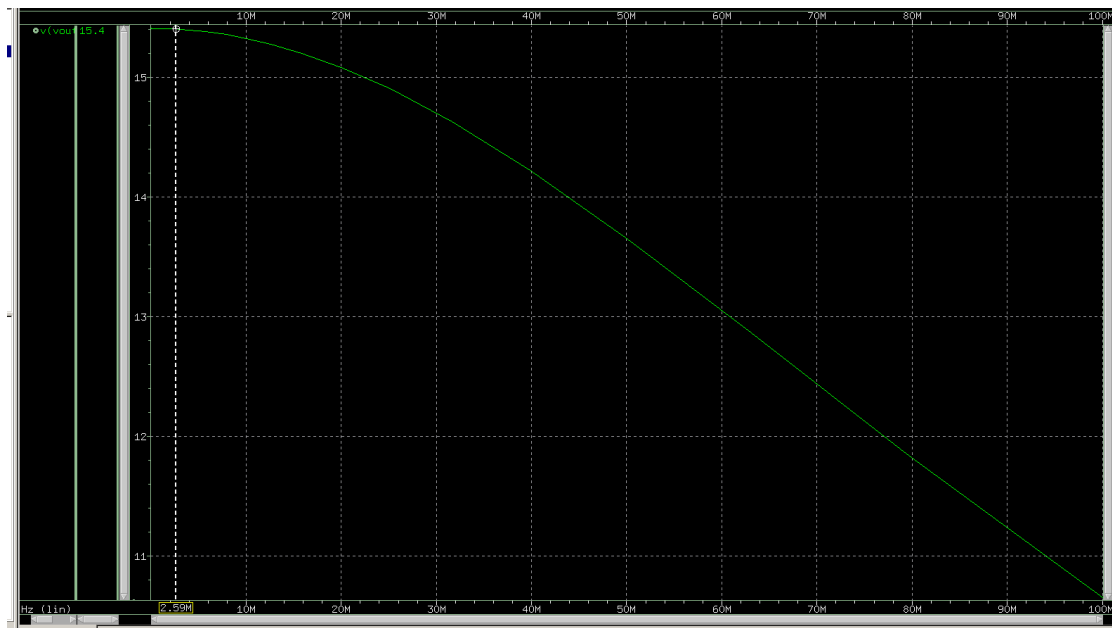
The ac gain is **15.4** > 15 at low frequency:



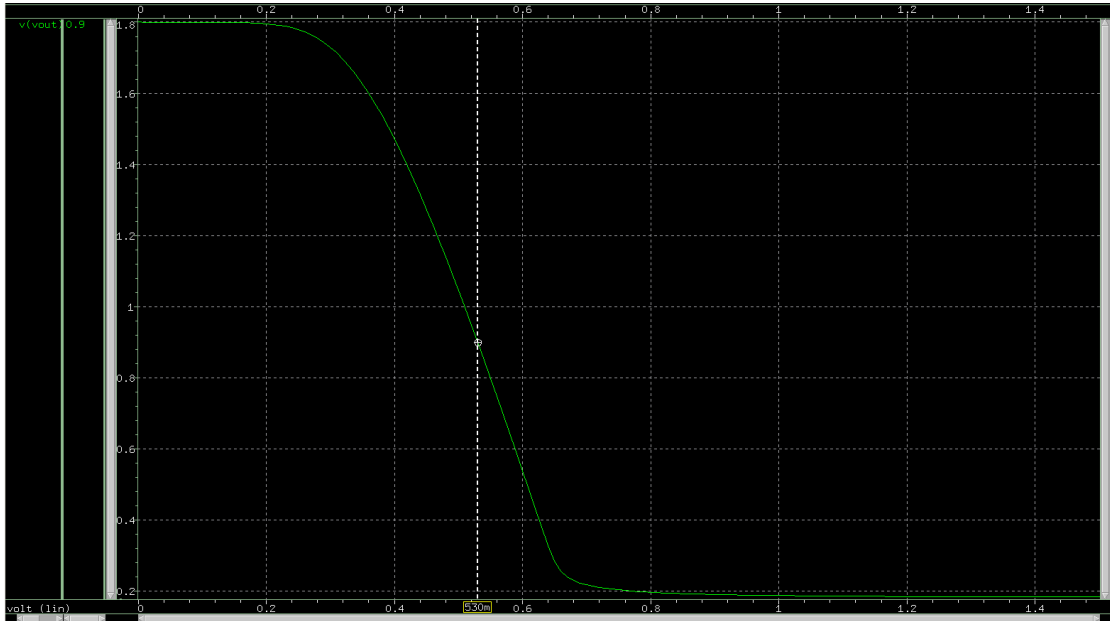(b) Same M1 W/L size of (a), and to have the same output voltage  $V_{out} = 0.9$ , I set dc bias voltage  $V_{in} = 530\text{mV}$ .



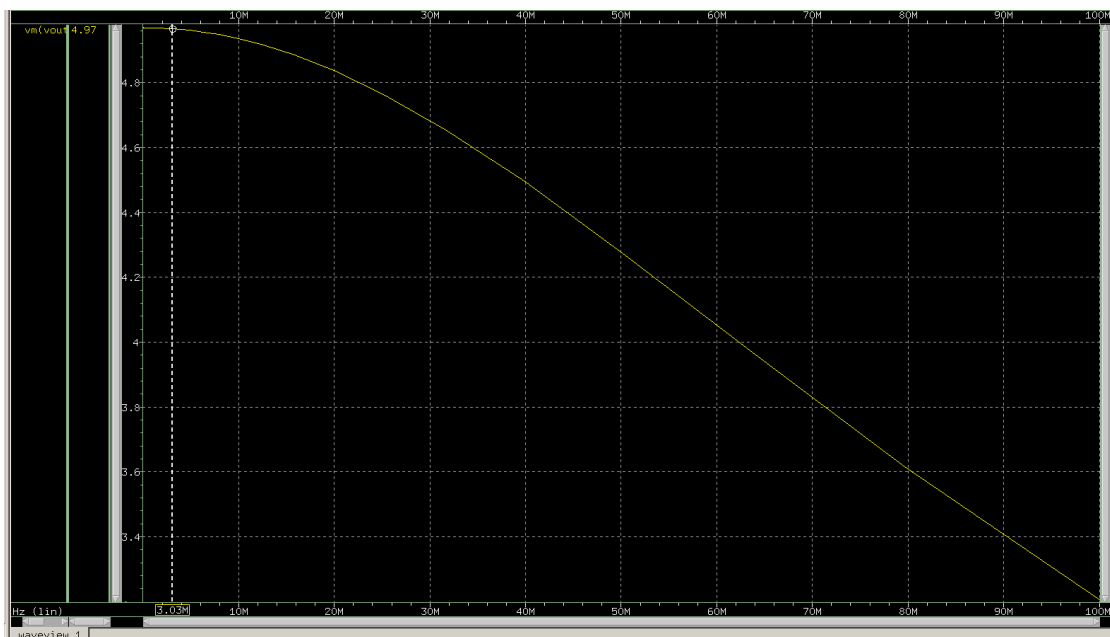The ac gain is **4.97** at low frequency:




Comments:

- (i) When  $V_{in}$  increases,  $I_D$  increases too, and so does the voltage across  $R_S$ , which means some of the voltage between gate and source now drop on  $R_S$ , and thus the **linearity of case (b) improves** in comparison with cases without source

degeneration like (a).

(ii) Although the linearity of (b) increases, we actually **sacrifice the gain**. (Gain from  $A_v = -g_m R_D$  to  $A_v = -\frac{g_m R_D}{1+g_m R_S}$  )

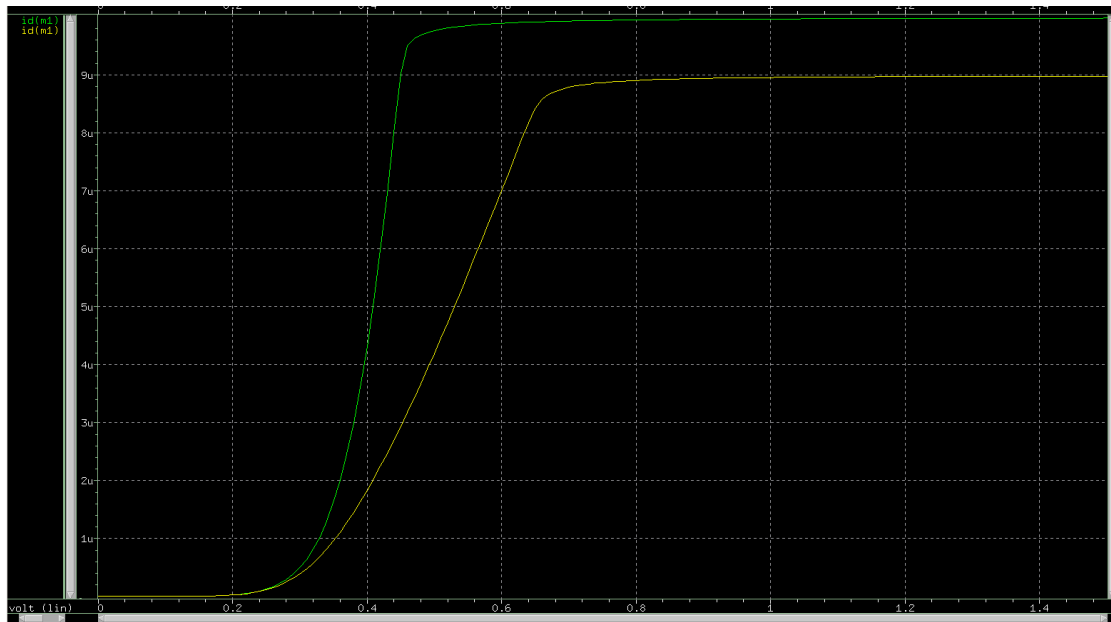
(iii)  $I_D$  of (b) is smaller than (a), because the voltage drop across  $R_S$  makes  $V_S$  higher, resulting in a smaller  $V_{GS}$ .



(green curve:(a), yellow curve:(b))

3.

Schematic:

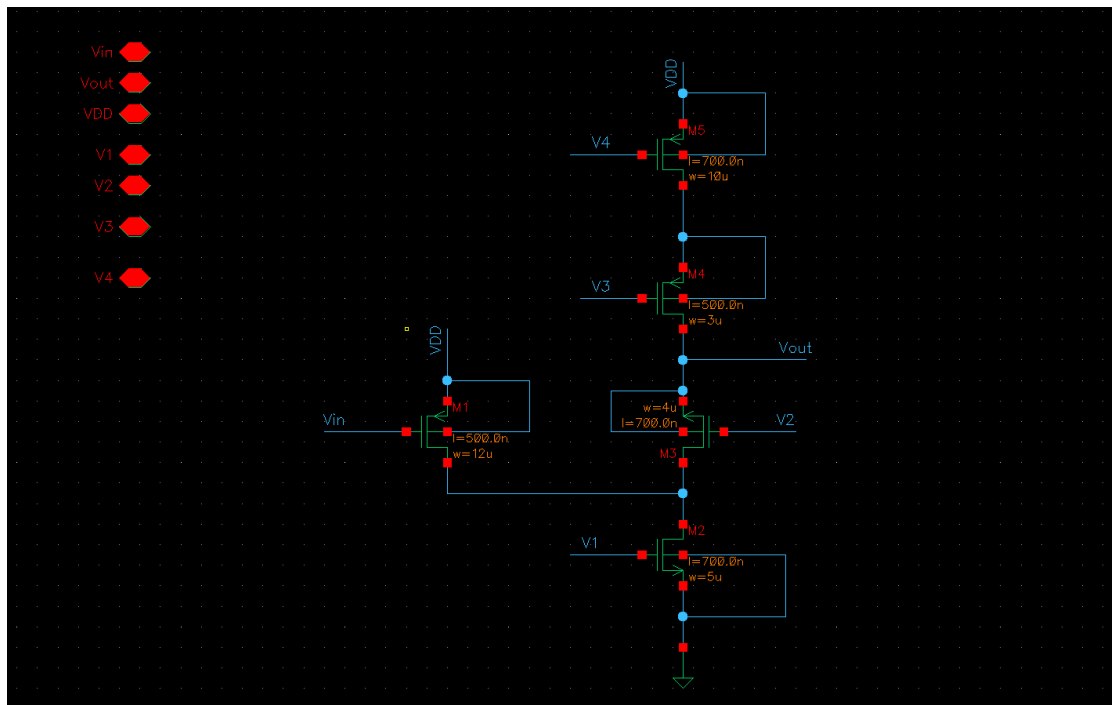

(a) My idea is: The ac gain is proportional to  $g_{m1}$ , so if we want a bigger gain, I design  $g_{m1}$  to be bigger. And design to make  $I_{d3} = I_{d4} = I_{d5} + I_{d1}$  as close as possible to 40uA, and meanwhile, keep all mos in saturation.

(W/L) M1:12u/0.5u, M2: 5u/0.7u, M3:4u/0.7u, M4:3u/0.5u, M5:10u/0.7u.  $I_{bias} = 41.2\mu A$ .

$$V_{out-swing} = V_{outmax} - V_{outmin} =$$

$$(V_{DD} - V_{dsat4} - V_{dsat5}) - (V_{dsat2} + V_{dsat3}) =$$

$$(1.8 - 117.87m - 94.295m) - (185.565m + 68.07m) = 1.3342V > 1V.$$




```

subckt
element 0:m1      0:m2      0:m3      0:m4      0:m5
model   0:p_18.1  0:n_18.1  0:n_18.1  0:p_18.1  0:p_18.1
region  Saturati  Saturati  Saturati  Saturati  Saturati
id      -38.8527u  41.2284u  2.3756u   -2.3756u   -2.3757u|
ibs     3.832e-21  -7.296e-21 -4.384e-22 2.885e-22 2.379e-22
ibd     863.5191a -120.1284a -305.3220a 105.3855a 26.7767a
vgs     -700.0000m 610.0000m 417.5937m -594.3872m -550.0000m
vds     -1.5176  282.4063m 860.3541m -601.6268m -55.6128m
vbs     0.        0.        0.        0.        0.
vth     -503.2950m 417.2219m 412.4830m -514.6767m -499.0154m
vdsat   -204.4876m 185.5654m 68.0703m  -117.8739m  -94.2951m from .lis file

```

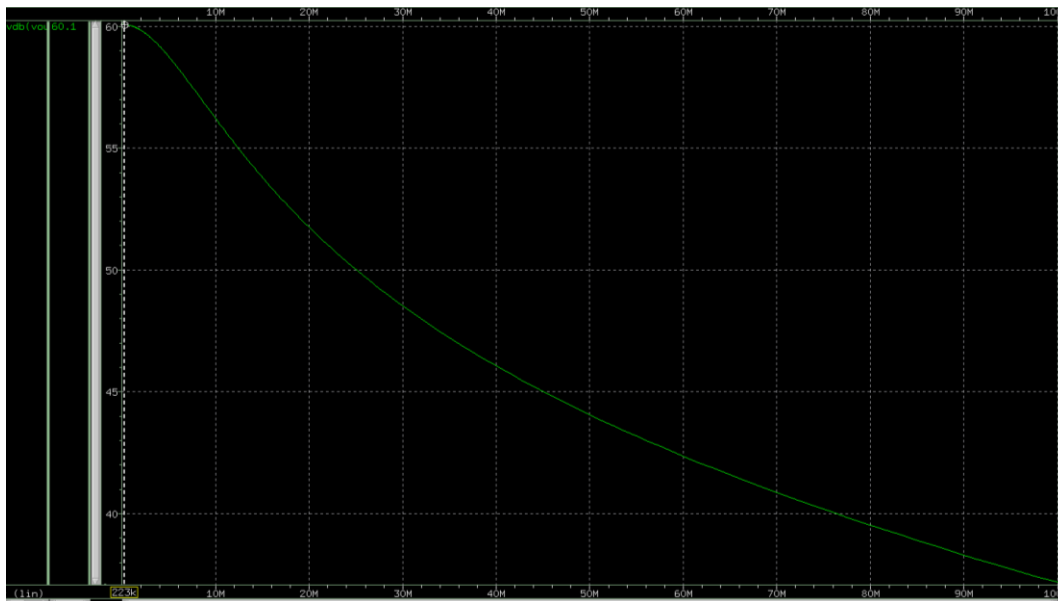The ac gain is **60.1dB** > 45dB at low frequency:




(b) Modify all the m(finger) in (a) to be double means to double the all the W in (a). And from the .lis file, we found it reasonable to have all the currents becomes two times of that of (a) since  $I_D$  is proportional to W, and all  $V_{dsat}$  remain the same, so  $V_{out-swing}$  is the same as (a).

```

subckt
element 0:m1      0:m2      0:m3      0:m4      0:m5
model   0:p_18.1  0:n_18.1  0:n_18.1  0:p_18.1  0:p_18.1
region  Saturati  Saturati  Saturati  Saturati  Saturati
id      -77.7054u  82.4567u  4.7513u   -4.7513u   -4.7513u
ibs     7.664e-21  -1.459e-20 -8.768e-22 5.770e-22 4.758e-22
ibd     1.7270f  -240.2567a -610.6440a 210.7709a 53.5533a
vgs     -700.0000m 610.0000m 417.5937m -594.3872m -550.0000m
vds     -1.5176  282.4063m 860.3541m -601.6268m -55.6128m
vbs     0.        0.        0.        0.        0.
vth     -503.2950m 417.2219m 412.4830m -514.6767m -499.0154m
vdsat   -204.4876m 185.5654m 68.0703m  -117.8739m  -94.2951m

```

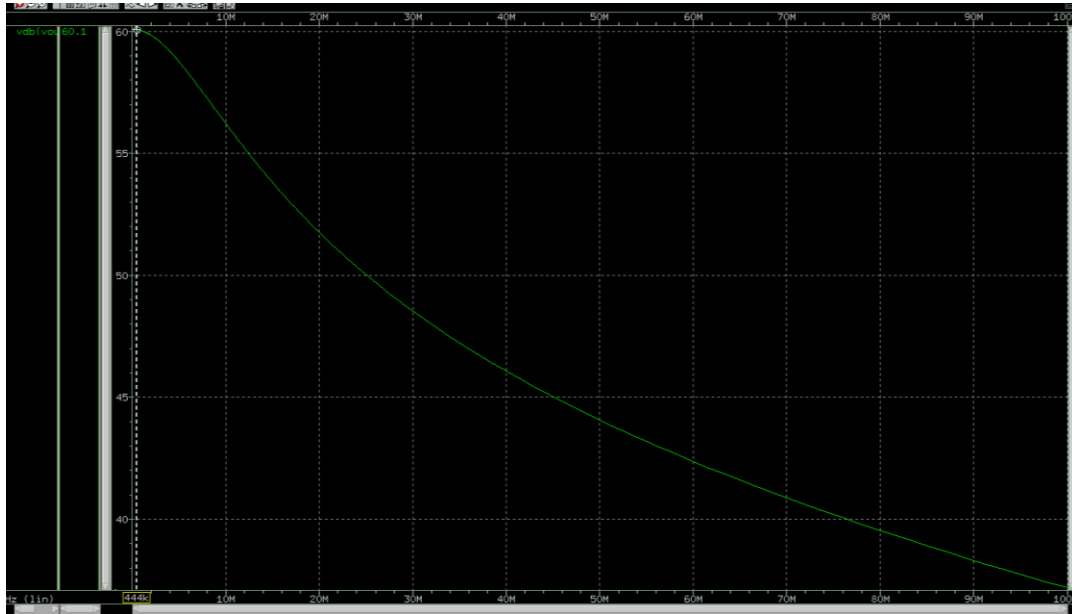As for ac gain, it's the same as that of (a):



Since  $g_m$  is proportional to  $W$ ,  $g_m$  becomes double, but on the other hand,  $r_o$  is proportional to  $1/I_D$ , so  $r_o$  becomes  $1/2$ .

$$A_v = -g_{m1}(g_{m4}(r_{o4} * r_{o5}) // g_{m3}(r_{o3}(r_{o2} // r_{o1})))$$


$$\Rightarrow 2((2 * 1/4) // 2(1/2(1/2))) \Rightarrow 2(1/2) = 1 \text{ (number represents times)}$$

remains the same.


4.

Schematic:


(a)

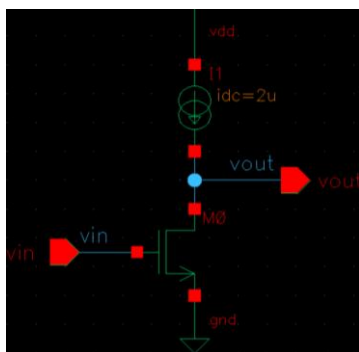

(c)

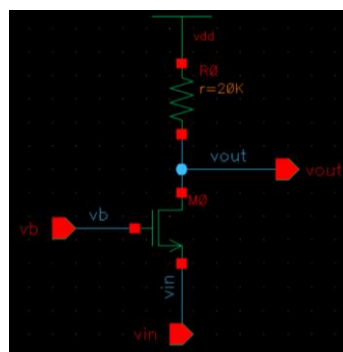


(e)

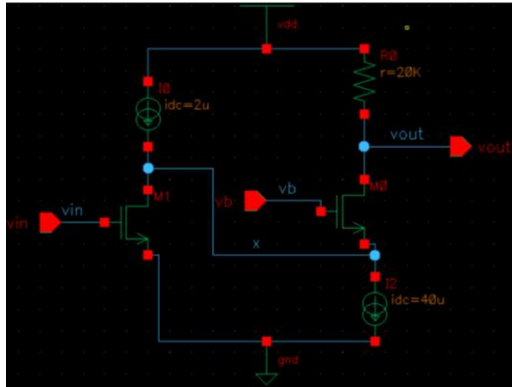


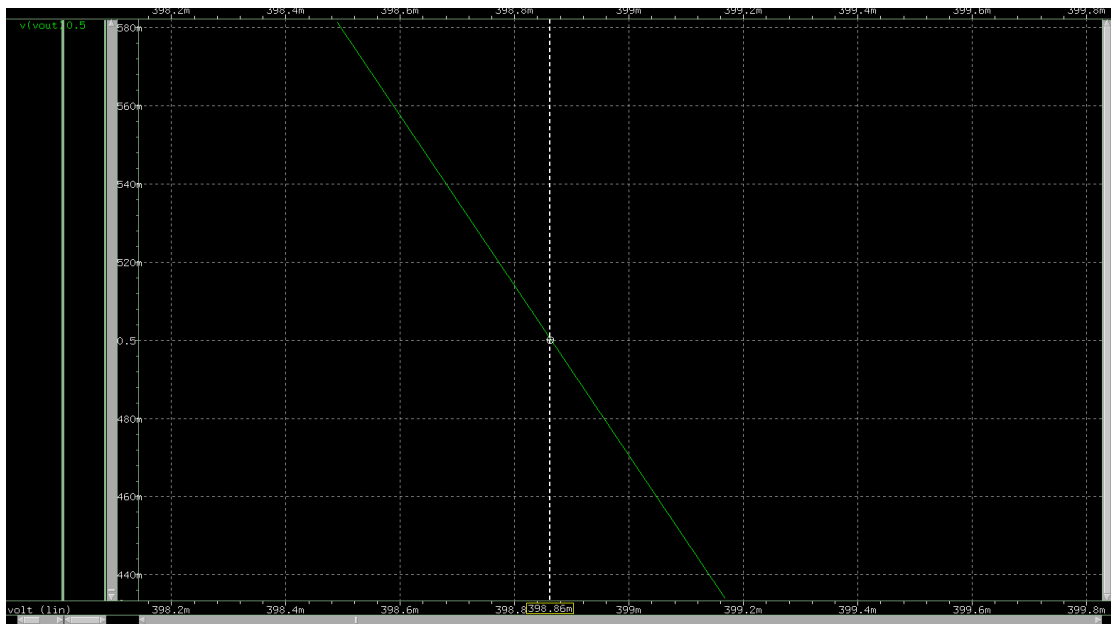(a) I design the size of nmos to be  $W/L = 10u/6u$ ,

and when  $V_{in} = 398.86mV$ ,  $V_{out} = 0.5V$ .



The ac gain  $A_1$  is **209** > 150:

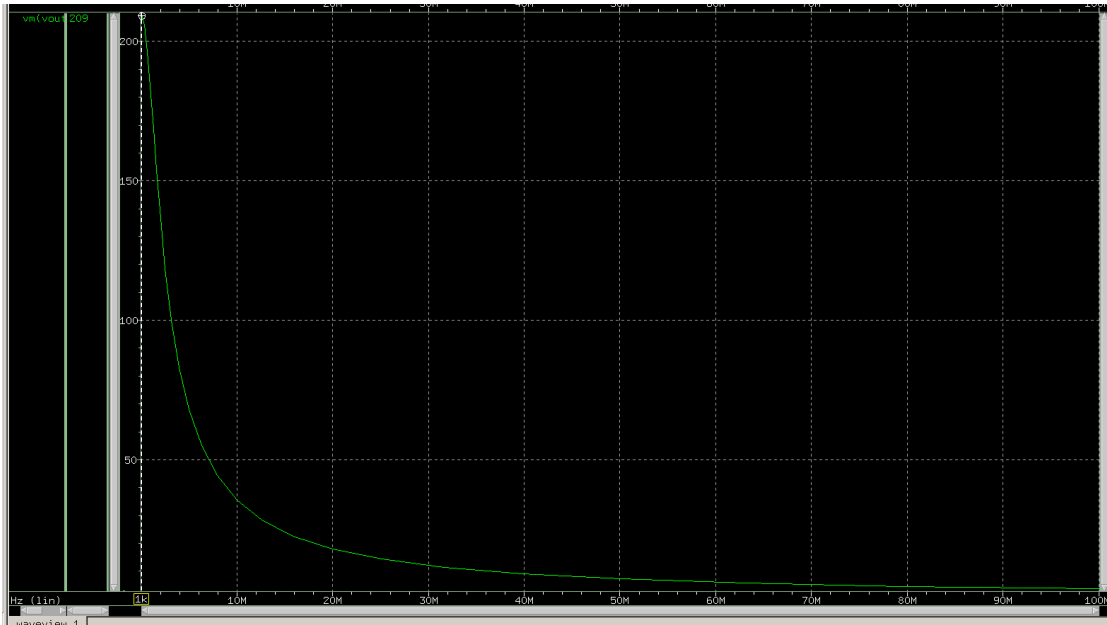

(b) Gain  $A_1 = -g_m * r_o = -g_m / g_{ds} = 32.2064\mu / 154.0038\text{n} = -209.127$ .


gm	32.2064u	
gds	154.0038n	from .lis file

Since  $g_m$  is proportional to  $1/L$  and  $r_o$  is proportional to  $L/I_D$  and thus  $L^2$ , Gain  $A_1 = -g_m * r_o$  is proportional to  $L$ , so to have a higher gain, we raise  $L$  bigger, but with constant  $I$ , we raise  $W$  bigger as well.

(c) I design the size of nmos to be  $W/L = 14\mu/1\mu$  and the bias voltage  $1.1005642\text{V}$  to have a static current  $40\mu\text{A}$ ,

region	Saturati	
id	40.0000u	from .lis file

and gain  $A_2 = 10.2 > 10$ .

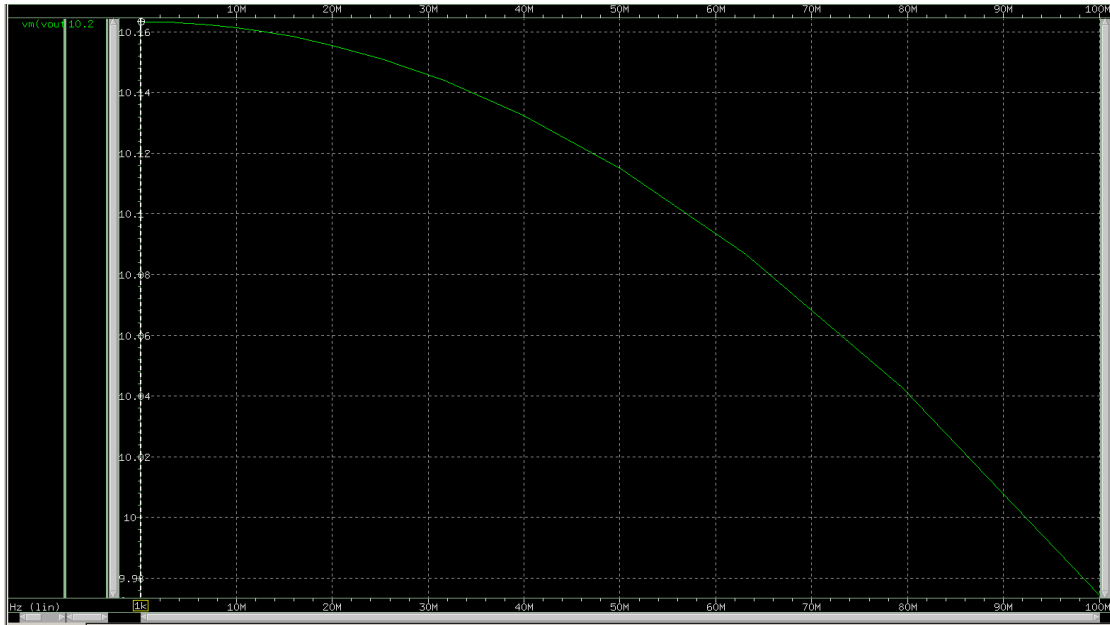

$$(d) \text{ Gain } A_2 = (g_m + g_{mb}) * (r_o // R_D) = (g_m + g_{mb}) * \left( \frac{1}{g_{ds}} // R_D \right) =$$

$$(497.6027\mu + 77.2249\mu) * (17461.20992) \doteq 10.03$$


gm	497.6027u	
gds	7.2698u	
gmb	77.2249u	from .lis file

(e)

(i) The DC bias stays the same.

(ii)  $A_1 * A_2$  is about  $-209 * 10 = -2090$ .

And the overall gain is **645m**.

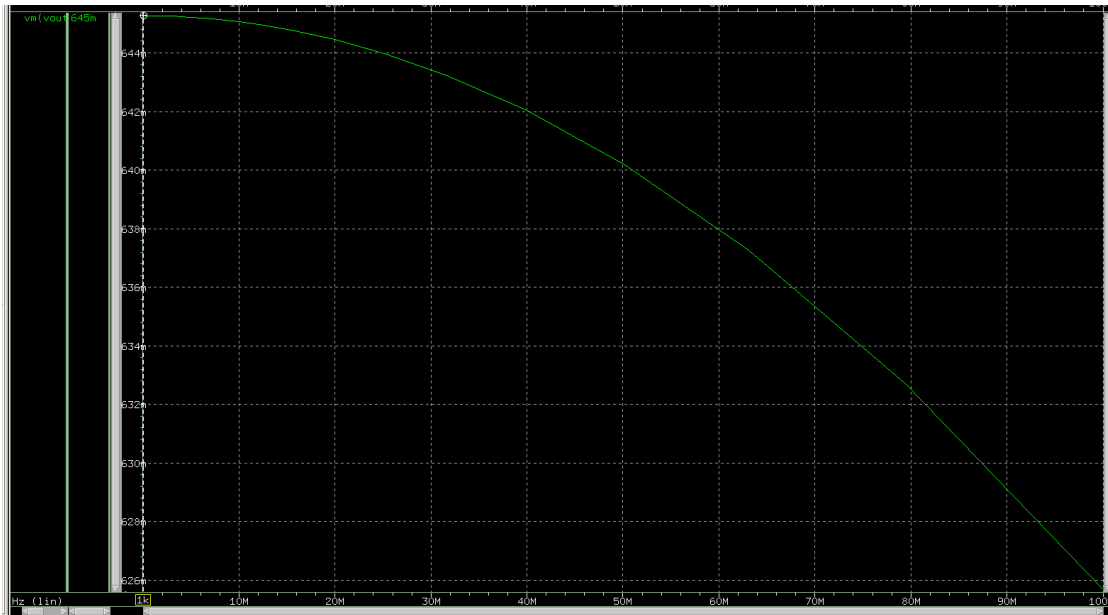

The overall gain is not equal to the originally  $A1 \cdot A2$ , because the  $R_{out}$  of the CS stage changes from  $r_{o1}$  to

$$r_{o1} // 1 / (g_{m2} + g_{mb2}) // r_{o2} =$$

$$6493346.268 // 1739.652 // 137555.366 = 1717.47$$

$$\text{So } A1 \text{ should adjust to } -g_{m1} * R_{out} = -32.2064u * 1717.47 =$$

$$0.0553. \text{ And the } R_{out} \text{ of the CG stage changes from } (r_{o2} // R_D)$$

$$\text{to } (r_{o2} * r_{o1} // R_D) \cong R_D, \text{ so } A2 \text{ should adjust to}$$

$$(g_{m2} + g_{mb2}) * R_D = 574.8276u * 20k \cong 11.49, \text{ which is only a}$$

small amount of change. So the major difference is from the CS

$$\text{stage. Here we get the overall gain } A1 * A2 = 0.053 * 11.49 \cong$$

635m.