

1. Design a PMOS source follower with  $V_{DD}=1.8V$  as shown in Fig. 1. (20%)
  - (a) Design the W/L sizes of  $M_1 \sim M_2$ , dc bias  $V_b$  and bias current. To get a voltage gain  $V_{out}/V_{in} > 0.95$  for  $V_{in}$  DC voltage from 0V to 1.2V. Plot the  $V_{in}-V_{out}$  transfer curve and comments the level shift and the relationship between bias current and sizes. (10%)
  - (b) In reality, the body effect exists. Please connect the body of  $M_1$  to  $V_{DD}$  and redesign the W/L sizes and  $V_b$  to get voltage gain  $V_{out}/V_{in} > 0.75$  for  $V_{in}$  DC voltage from 0V to 1.2V. Plot the  $V_{in}-V_{out}$  transfer curve. (5%)
  - (c) Comment on the differences between (a) and (b). (5%)

 


Fig. 1.

2. Design a common-source amplifier with a load  $R_D = 180K\Omega$  as shown in Fig. 2. (20%)
  - (a) With  $V_{DD} = 1.8V$ , design the W/L sizes of  $M_1$  and input dc bias  $V_{in}$  to get voltage ac gain  $A_V = V_{out}/V_{in} > 15$  and  $V_{out}$  dc voltage = 0.9V. (10%)
  - (b) Add a source degeneration resistor  $R_s = 20K\Omega$  as shown in Fig. 3. Redesign the dc bias  $V_{in}$  under the same output voltage and  $M_1$  W/L sizes. Check the voltage gain  $A_V = V_{out}/V_{in}$  and make a comment between (a) and (b). (10%)

 


Fig. 2.

 


Fig. 3.

3. Design a common-source amplifier with folded cascoded loading as shown in Fig. 4. (25%)
- (a) With  $V_{DD} = 1.8\text{ V}$  and  $I_{bias} = 40\mu\text{A}$  (bias current of  $M_2$ ), design the  $W/L$  sizes of  $M_1 \sim M_5$ , the dc bias  $V_1 \sim V_4$ , and input dc bias  $V_{in}$  to get voltage ac gain  $A_V = V_{out}/V_{in} > 45\text{ dB}$  and  $V_{out-swing} > 1\text{V}$ . Please explain your design methodology and results. (15%)
- (b) Keep  $W/L$  as the same but modify all the  $m(\text{finger})$  in (a) to be double, compare the differences of the bias current, voltage gain and output swing and comments. (10%)

 


Fig. 4.

4. Use HSPICE to simulate the circuits in Fig. 5 with  $V_{dd}=1.8\text{V}$  and do the calculation. (35%)
- (a) Design a common source stage with ac gain  $A_1 > 150$  and **output DC voltage=0.5 (static current=2uA)** as shown at Fig. 5. (a). (10%)
- (b) Base on the simulation parameter in .lis file, calculate the gain of common source and comment. (5%)
- (c) Design a common gate stage with gain  $A_2 > 10$  and **input DC voltage=0.5 (static current=40uA)** as shown at Fig. 5. (b). (10%)
- (d) Base on the simulation parameter in .lis file, calculate the gain of common gate and comment. (5%)
- (e) Connect two stage as shown at Fig. 5. (c). Whether the DC bias stays the same? The overall gain equals to  $A_1 \times A_2$  or not? If not, please explain. (5%)

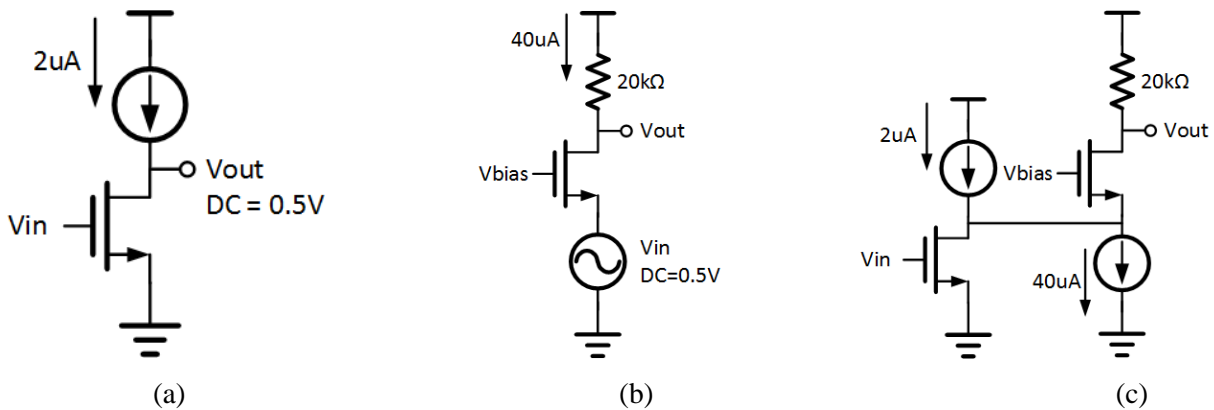


Fig. 5

✧ *The following should be included in your report (a) schematic (b) HSPICE netlist & simulation file (c) waveform with cursor values (d) comments.*