

Analog IC Design Homework 3



學號: 102061112

姓名: 謝博楊


(3) R_D to be larger, which $R_D = 100k$.

And my design is $(W/L)_{M1} = (W/L)_{M2} = 84u / 2.8u$.

from .lis file:

```
element  0:m3      0:m2      0:m1
model    0:n_18.1  0:n_18.1  0:n_18.1
region   Saturati Saturati  Saturati
id       20.0557u 10.0278u  10.0278u
```


The voltage gain= $25.3dB > 20dB$:

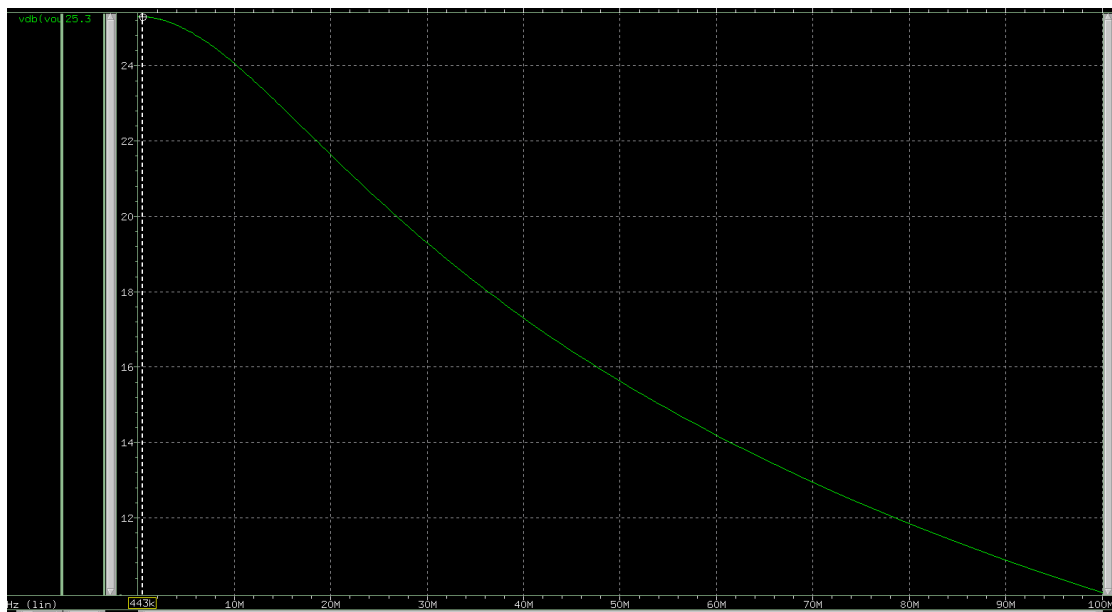


(b) $(W/L)_{M2}$ becomes $92.4u / 2u$.

(i) Without C_p :

$$|A_V| = 25.3dB, |A_{cm}| = 52.1dB$$

 


At low freq. $CMRR = |A_v / A_{cm}| = 25.3\text{dB} - (-52.1\text{dB}) = 77.4\text{dB}$

 


from the figure, **-3dB bandwidth without $C_p = 2.44\text{M}$.**

(ii) With C_p from P to ground:


$$|A_v| = 25.3\text{dB}, |A_{cm}| = 52.1\text{dB}$$

 

At low freq. $CMRR = |A_v / A_{cm}| = 25.3\text{dB} - (-52.1\text{dB}) = 77.4\text{dB}$
 is same as that without C_p .

 

 from the figure, **-3dB bandwidth with $C_p = 1.73\text{M}$.**



Red curve: CMRR with C_p ; **Blue** curve: CMRR without C_p

(iii) Comment:

The common-mode to differential conversion becomes significant at high frequencies, since r_{o3} is shunted by C_p .

$$A_{CM-DM} = -\frac{\Delta g_m R_D}{(g_{m1} + g_{m2})(r_{o3} // C_p) + 1} \text{ and at high frequencies,}$$

$Z(C_p) = 1/j\omega C_p$ becomes smaller, so $r_{o3} // C_p$ becomes smaller, and A_{CM-DM} becomes larger, resulting in smaller CMRR.

I compare the -3dB bandwidth, and the one without C_p is bigger than the one with C_p . It's reasonable since CMRR with C_p decrease faster, resulting in smaller bandwidth.

(c)

To calculate $V_{in,CM}$ for all MOS saturation:


```
element 0:m3      0:m2      0:m1
model   0:n_18.1  0:n_18.1  0:n_18.1
region  Saturati Saturati Saturati
id      20.0557u  10.0278u  10.0278u
ibs     -3.245e-21 -2.8168f -2.8168f
ibd     -365.4617a -4.7805f -4.7805f
vgs     490.0000m  430.2507m  430.2507m
vds     469.7493m  327.4665m  327.4665m
vbs     0.         -469.7493m -469.7493m
vth     443.4527m  426.6507m  426.6507m from .lis file
```


$$V_{GS1} + (V_{GS3} - V_{TH3}) \leq V_{in,CM} \leq \min[V_{DD} - R_D \frac{I_{SS}}{2} + V_{TH}, V_{DD}]$$

$$\rightarrow 0.43025 + (0.49 - 0.44345) \leq V_{in,CM} \leq 1.8 - 100k * \frac{20u}{2} + 0.42665$$

$$\rightarrow 0.4768 \leq V_{in,CM} \leq 1.22665$$

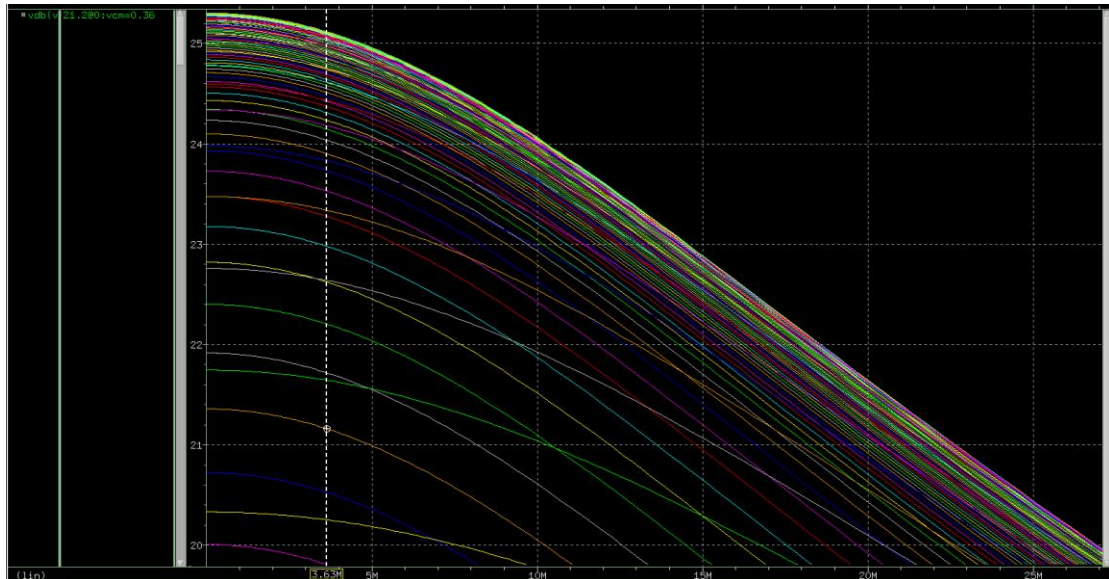And from simulation, $0.36 \leq V_{in,CM} \leq 0.91$



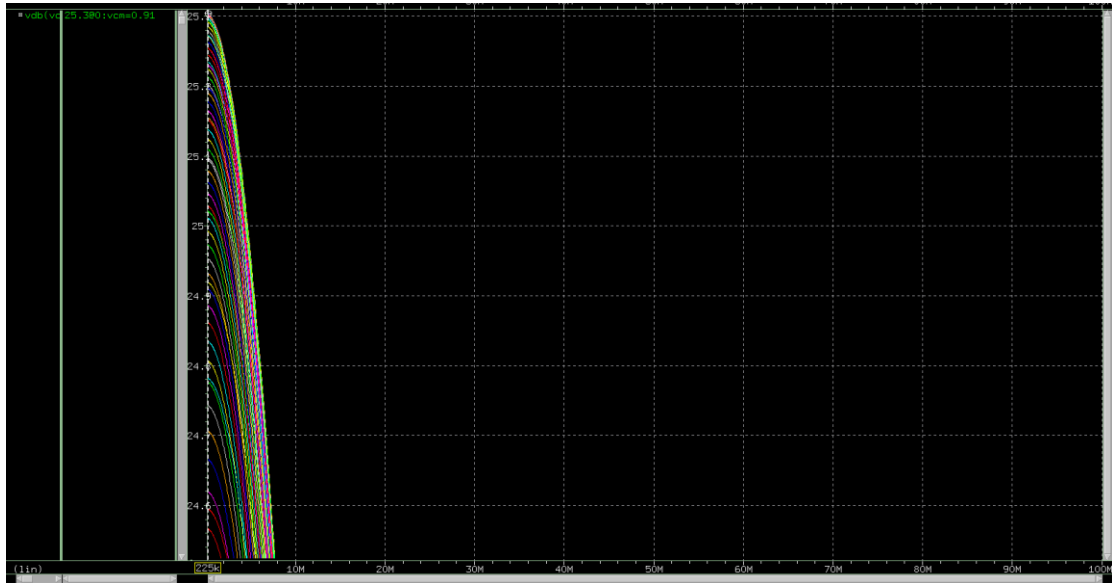

So combine above results, our desire IMCR is $0.4768 \leq V_{in,CM} \leq$


0.91

(d)

The maximum differential input that the circuit can handle:

$$\Delta V_{in} = \sqrt{\frac{2I_{d3}}{\mu_n C_{ox} W/L}} = \sqrt{2} (V_{GS1} - V_{TH}) = \sqrt{2} (0.43 - 0.426)$$

$$= 0.00565V$$

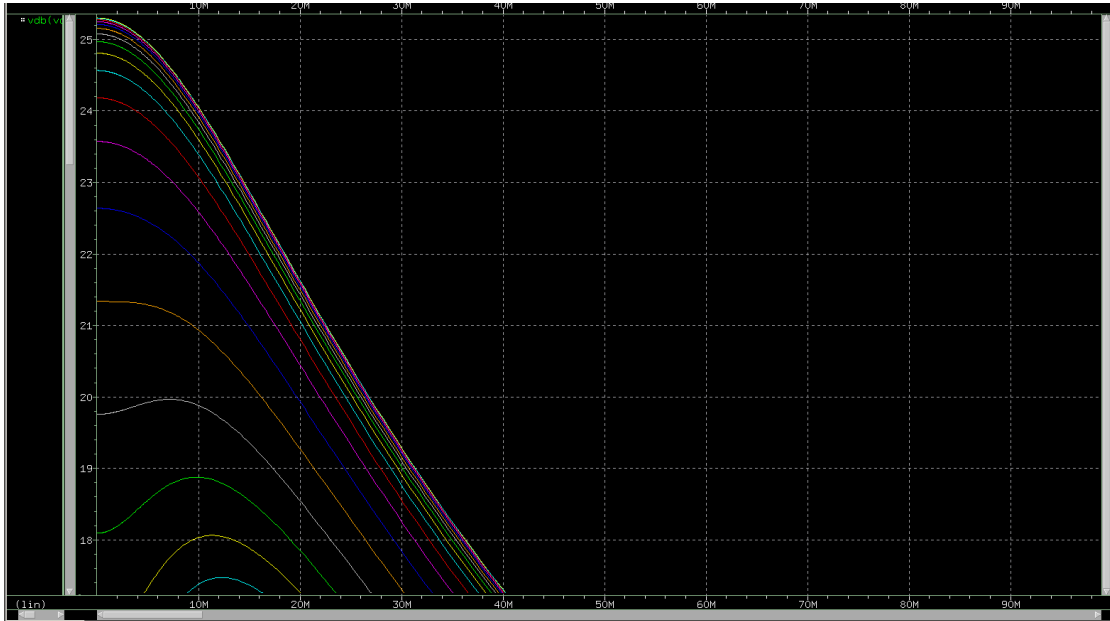

Above figure is the simulation, and find the one with all MOS in saturation from .lis file (shown below),

```
*** parameter d = 8.965E-01 ***
```

```
subckt
element 0:m3 0:m2 0:m1
model 0:n_18.1 0:n_18.1 0:n_18.1
region Saturati Saturati Saturati
id 20.0560u 9.3848u 10.6712u
```

```
*** parameter d = 9.035E-01 ***
```

```
subckt
element 0:m3 0:m2 0:m1
model 0:n_18.1 0:n_18.1 0:n_18.1
region Saturati Saturati Saturati
id 20.0560u 10.6712u 9.3848u
```


So the input differential maximum is $0.9035 - 0.8965 = 0.007V$

and the input differential range ΔV_{in} is **from 0 to 0.0035**.


It's reasonable that it's smaller than calculation, since we want all MOS to be saturation.

(e)

Schematic:

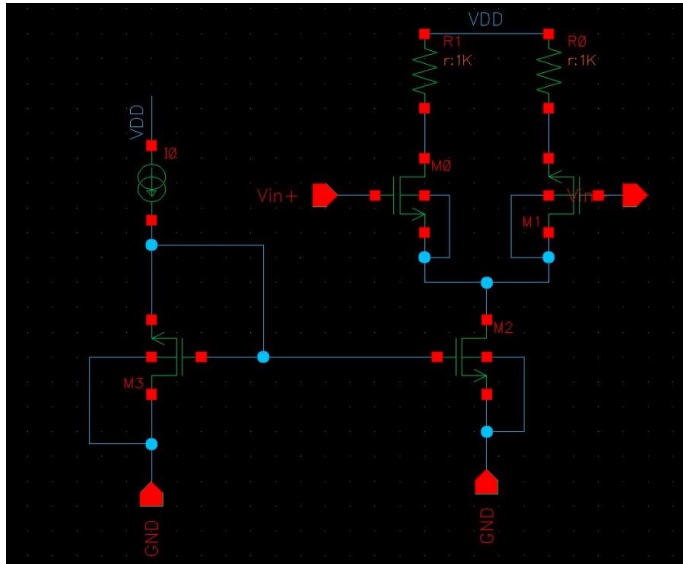


 The gain of using ideal voltage source to generate V_b :



Green curve: TT Yellow curve: FF Blue curve: SS

 The gain of using current mirror to generate V_b :



Green curve: TT Yellow curve: FF Red curve: SS

Comment:

(i) For TT corner, both methods generating bias voltage will have all MOS in saturation, and reach a voltage gain of 25.3.

(ii) For FF corner, when using current mirror, we can still get a voltage gain of 25.2 and all MOS in saturation at the same time.

But when using ideal voltage source, the gain $|A_v|$ can reach 37.5, but not all MOS in saturation.

```

element  0:m3      0:m2      0:m1
model    0:n_18.1  0:n_18.1  0:n_18.1
region   Saturati  Linear    Linear
id       32.1835u  16.0918u  16.0918u  from .lis file

```

(iii) For SS corner, when using current mirror, we can still get a voltage gain of 25.2 and all MOS in saturation at the same time.

But when using ideal voltage source, the gain will drop to 20.5


and not all MOS in saturation.

element	0:m3	0:m2	0:m1	
model	0:n_18.1	0:n_18.1	0:n_18.1	
region	Saturati	Cutoff	Cutoff	
id	9.8075u	4.9037u	4.9037u	from .lis file

(iv) We can observe that using current mirror to generate bias voltage is better in all three TT, FF, SS corners, since when operating in different corners, the parameters changed, so if we use the same ideal voltage source, it might not operate in saturation.

2.

Schematic:

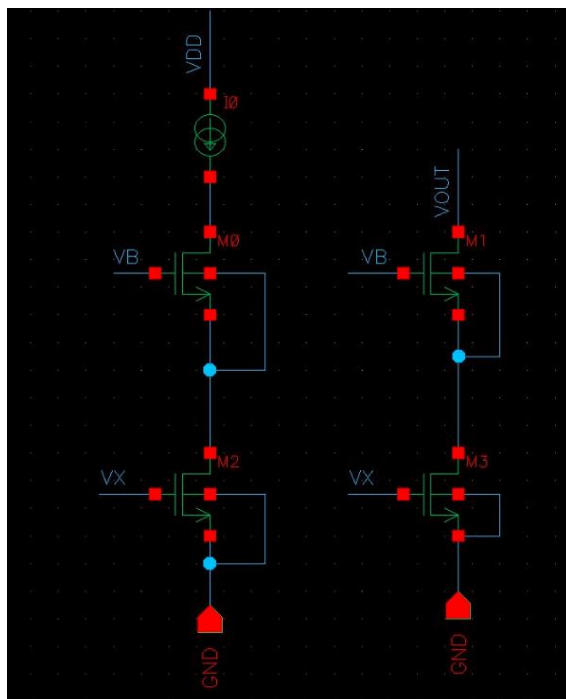


(a)

We want I_{out} to be 16uA and I_{ref} is 4uA, so we want

$4(W/L)_{1,2} = (W/L)_{3,4}$. I use the same length for all of the transistors so as to minimize errors due to the side diffusion of the source and drain areas, and make the multiple finger of 4.

For M1, M2 in saturation, $V_{GS2} + (V_{GS1} - V_{TH1}) \leq V_b \leq$

$V_{GS1} + V_{TH2}$

 

(b)

M6 is guaranteed to be in saturation, since it's gate and drain are connected. But with all transistors in saturation region, M5

can only be in linear region, because $V_{in1} = V_{GS5} = V_{DS5} +$

V_{GS6} , $V_{GS6} > V_{th}$ and thus $V_{GS5} - V_{DS5} > V_{th}$.

element	0:m4	0:m3	0:m2	0:m1	0:m5	0:m6
model	0:n_18.1	0:n_18.1	0:n_18.1	0:n_18.1	0:n_18.1	0:n_18.1
region	Saturati	Saturati	Saturati	Saturati	Linear	Saturati
id	15.9293u	15.9293u	4.0000u	4.0000u	5.1174u	5.1174u


So we can calculate the current:

$$\text{For M6: } I_D = \frac{1}{2} \mu_n C_{ox} (W/L)_6 V_{ov}^2$$

$$\text{For M5: } I_D = \frac{1}{2} \mu_n C_{ox} (W/L)_5 (2(V_{gs} - V_{th}) V_{ov} - V_{ov}^2)$$


After calculation, we found that $(W/L)_6$ is equal to $(W/L)_5$ times 3, so I design $(W/L)_5 = 2\mu/4.5\mu$ and $(W/L)_6 = 2\mu/1.5\mu$.

 And I_{D4} can reach 16μ , same as the result of giving bias voltage. And there is about 40mV difference from the original one, but I reckon that a roughly 5% difference is acceptable.




(c)

Figure of output current when using bias generation circuit:

 

Green curve: TT Yellow curve: FF Blue curve: SS

Figure of output current when using ideal voltage source:

 

Green curve: TT Yellow curve: FF Blue curve: SS

Comment:

(i) Using bias generation circuit, we have I_{out} close to 16uA, and from .lis file, we found only M5 in linear region as expected.

(ii) Using ideal voltage source, we have I_{out} close to 16uA as well, we concern that there might be transistor other than M5 not being in saturation. But in this case, from .lis file (shown below), we found it alright.

TT:

element	0:m4	0:m3	0:m2	0:m1	0:m5	0:m6
model	0:n_18.1	0:n_18.1	0:n_18.1	0:n_18.1	0:n_18.1	0:n_18.1
region	Saturati	Saturati	Saturati	Saturati	Linear	Saturati
id	15.9195u	15.9195u	4.0000u	4.0000u	4.0000u	4.0000u

FF:

element	0:m4	0:m3	0:m2	0:m1	0:m5	0:m6
model	0:n_18.1	0:n_18.1	0:n_18.1	0:n_18.1	0:n_18.1	0:n_18.1
region	Saturati	Saturati	Saturati	Saturati	Linear	Saturati
id	15.8676u	15.8676u	4.0000u	4.0000u	4.0000u	4.0000u

SS:

element	0:m4	0:m3	0:m2	0:m1	0:m5	0:m6
model	0:n_18.1	0:n_18.1	0:n_18.1	0:n_18.1	0:n_18.1	0:n_18.1
region	Saturati	Saturati	Saturati	Saturati	Linear	Saturati
id	15.9063u	15.9063u	4.0000u	4.0000u	4.0000u	4.0000u

(d) M6 is guaranteed to be in saturation, since its gate and drain are connected. But with all transistors in saturation region, M5 can only be in linear region, because $V_{in1} = V_{GS5} = V_{DS5} + V_{GS6}$, $V_{GS6} > V_{th}$ and thus $V_{GS5} - V_{DS5} > V_{th}$.

