

1. Use composer and hspice to simulate the circuits in Fig. 1 with $V_{dd}=1.8V$ and do the calculation. (40%)
 - (a) Design a common source stage with gain $A_1 > 100$ and **output DC voltage=0.5 (static current=2uA)** as shown at Fig. 1. (a). (5%)
 - (b) Base on the simulation parameter of .lis file to calculate gain of common source and comment. (5%)
 - (c) Design a common gate stage with gain $A_2 > 10$ and **input DC voltage=0.5 (static current=40uA)** as shown at Fig. 1. (b). (5%)
 - (d) Base on the simulation parameter of .lis file to calculate gain of common gate and comment. (5%)
 - (e) Connect two stage as shown at Fig. 1. (c). Whether the DC bias stays the same? The overall gain equals to $A_1 \times A_2$ or not? If not, why not? (20%)

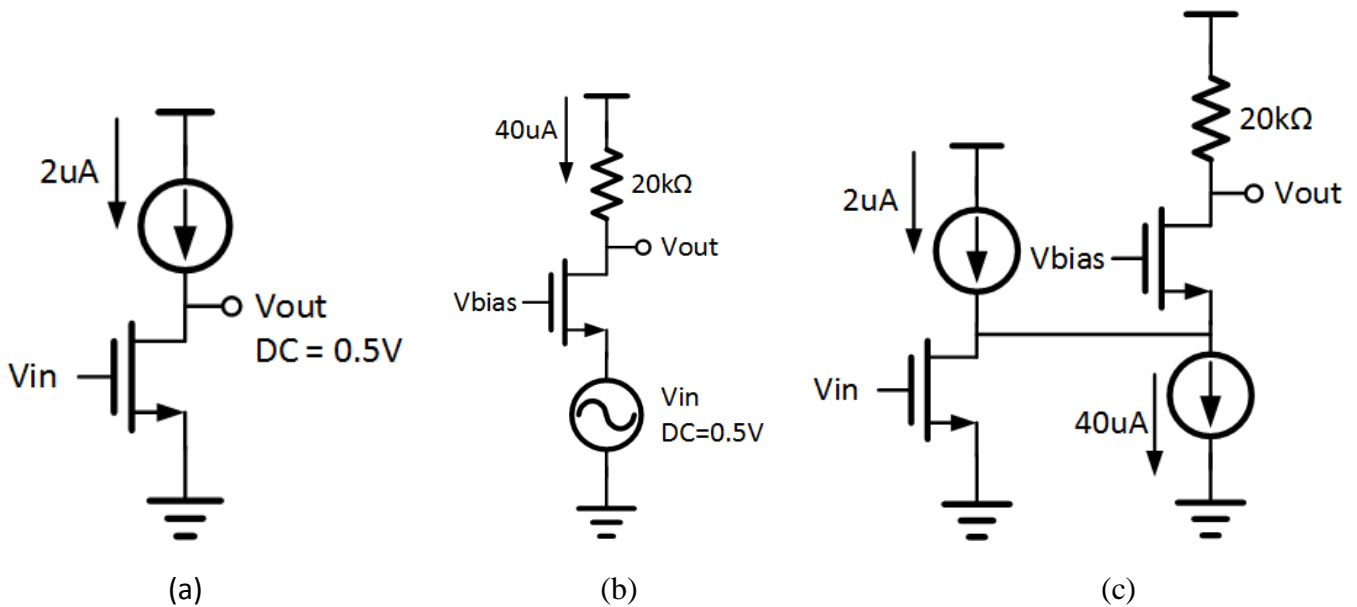


Fig. 1.

2. Design a common-source amplifier with cascaded loading as shown in Fig. 2. (30%)
 - (a) With $V_{dd}=1.8V$ and $I_{bias}=15uA$, design the W/L sizes of M1~M4, the dc bias to get voltage gain $A_v = V_{out}/V_{in} > 50dB$ and $V_{out-swing} > 1V$. (20%)
 - (b) Keep W/L as the same and double all of m(finger) in (a), check the differences of the bias current, voltage gain and output swing and make a comment. (10%)

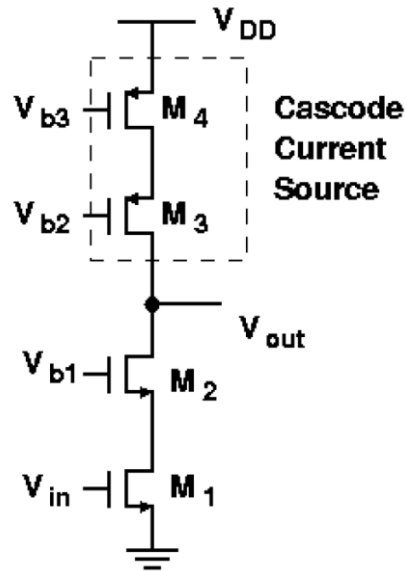


Fig. 2.

3. Design a source-follower amplifier with $V_{DD}=1.8V$ as shown in Fig. 3. (20%)

- Design the W/L sizes and V_b to get voltage gain $A_v=V_{out}/V_{in}>0.8$ for V_{in} DC voltage from 0.5V to 1.8V. (5%)
- Assume the deep-nwell is available. Design the W/L sizes and V_b to get voltage gain $A_v=V_{out}/V_{in}>0.96$ for V_{in} DC voltage from 0.5V to 1.8V. (5%)
- Comment on the differences between (a) and (b). (10%)

 


Fig. 3.

4. Assume the fabrication process is suffered from process variation, the length of input devices of Fig. 2. (M1) (Problem 2. (a)) and Fig. 3. (M1)(Problem 3. (a)) become 97% smaller. What happens to the gain of these amplifiers? Which one is more sensitive to the misalignment of MOS dimension? Why? (10%)

✧ *The following should be included in your report (a) schematic (b) HSPICE netlist & simulation file (c) waveform with cursor values (d) comments.*