

A close-up, dark green and black image of a printed circuit board (PCB) with intricate white and gold traces and components.



CHAPTER 11

Bandgap References

Outline

- 1. General Consideration**
2. Supply-Independent Biasing
3. Temperature-Independent Reference
4. PTAT Current Generation / Constant-Gm Biasing
5. Speed and Noise Issue / Case Study

Reference Generator

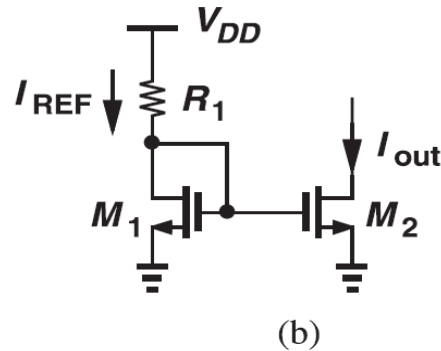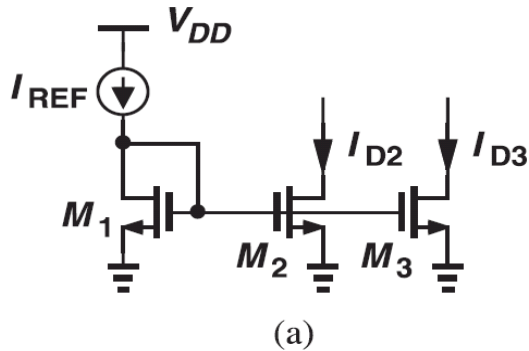

$$\Delta I_{out} = \frac{\Delta V_{DD}}{R_1 + 1/g_{m1}} \cdot \frac{(W/L)_2}{(W/L)_1}$$


- To establish a DC voltage or current that is ***independent of the supply and process*** and has a well-defined behavior with ***temperature***.
- The required temperature dependence assumes one of three forms
 - Proportional to absolute temperature (PTAT)
 - Constant - G_m behavior
 - Temperature Independent.
- The output current of the circuit is quite sensitive to V_{DD} .

Outline


 
1. General Consideration
- 2. Supply-Independent Biasing**
3. Temperature-Independent Reference
4. PTAT Current Generation / Constant-Gm Biasing
5. Speed and Noise Issue / Case Study

Self-biased Circuit

- **Self-biased circuit** : Supply Independent Biasing
- If M_1 - M_4 operate in saturation and $\lambda = 0$, then $I_{out} = K I_{REF}$
- The current levels in the left and right branches become indefinitely.



Supply Independent Current Generator

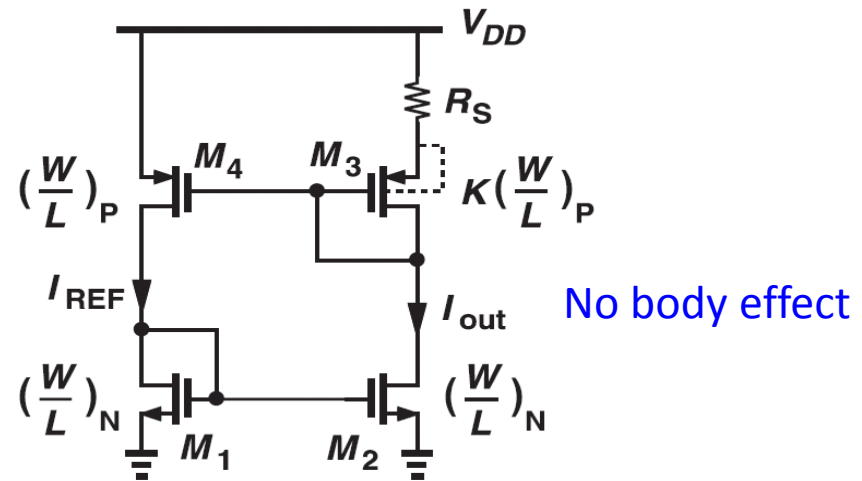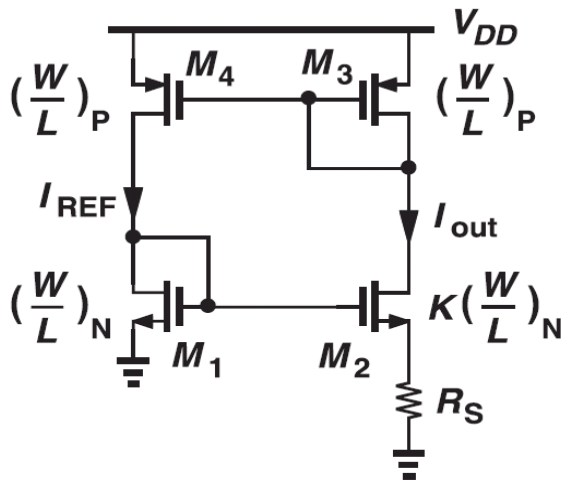

$$I_{out} = I_{REF}, \quad V_{GS1} = V_{GS2} + I_{D2}R_S, \quad \sqrt{\frac{2I_{out}}{\mu_n C_{ox} (W/L)_N}} + V_{TH1} = \sqrt{\frac{2I_{out}}{\mu_n C_{ox} K (W/L)_N}} + V_{TH2} + I_{out}R_S$$

$$\sqrt{\frac{2I_{out}}{\mu_n C_{ox} (W/L)_N}} \left(1 - \frac{1}{\sqrt{K}}\right) = I_{out}R_S, \quad I_{out} = \frac{2}{\mu_n C_{ox} K (W/L)_N} \cdot \frac{1}{R_S^2} \left(1 - \frac{1}{\sqrt{K}}\right)^2 \implies \text{independent of } V_{DD}$$

- Use R_S to determine the output current.
- The current is independent of the supply voltage, but still a function of process and temperature.
- The corresponding G_m is a constant (depending on R_S and K).
- Long channels are used for all of the transistors in the circuit.


$$g_m = \sqrt{2\mu_n C_{ox} \left(\frac{W}{L}\right)_N} I_D = \frac{2}{R_S} \left(1 - \frac{1}{\sqrt{K}}\right)$$

Start-Up Circuit

- If all of the transistors carry zero current when the supply is turned on, they may remain off indefinitely.
 - The circuit can settle in one of two different operation conditions.
- A start-up circuit is required.
 - A mechanism that drives the circuit out of the degenerate bias point when the supply is turned on.
 - M_3 and M_1 , and hence M_2 and M_4 cannot remain off.
 - M_5 remains off after start up.
 - This technique is practical only if

$$V_{TH1} + V_{TH5} + V_{TH3} < V_{DD} \implies M_5 \text{ "ON" at start up}$$

$$V_{GS1} + V_{TH5} + |V_{GS3}| > V_{DD} \implies M_5 \text{ "OFF" after start up}$$

 

di_{out}/dV_{DD} with $\lambda \neq 0$

- Assume, $\lambda \neq 0$, estimate the change in I_{out} for a small change ΔV_{DD} in the supply voltage
- Let $R_1=r_{O1} || (1/g_{m1})$, $R_3=r_{O3} || (1/g_{m3})$, we have

$$\frac{V_{DD} - V_X}{r_{O4}} + I_{out} R_3 g_{m4} = \frac{V_X}{R_1}, \quad G_{m2} = \frac{I_{out}}{V_X}$$

$$\frac{I_{out}}{V_{DD}} = \frac{1}{r_{O4}} \left[\frac{1}{G_{m2}(r_{O4} || R_1)} - g_{m4} R_3 \right]^{-1}$$

- Where $G_{m2} = \frac{g_{m2} r_{O2}}{R_S + r_{O2} + (g_{m2} + g_{mb2}) R_S r_{O2}}$

- If $r_{O4} = \infty$ $\frac{\Delta I_{out}}{\Delta V_{DD}} \approx 0$

 


圖 11.4

Outline

1. General Consideration
2. Supply-Independent Biasing
- 3. Temperature-Independent Reference**
4. PTAT Current Generation / Constant-Gm Biasing
5. Speed and Noise Issue / Case Study

Temperature Independent References

- If a reference is temperature independent, then it is usually process-independent as well.
- If two quantities having opposite temperature coefficients (TCs) are added with proper weighting, the result displays a zero TC.
- To obtain a reference voltage V_{REF} with zero TC: $V_{REF} = \alpha_1 V_1 + \alpha_2 V_2 \Rightarrow \alpha_1 \frac{\partial V_1}{\partial T} + \alpha_2 \frac{\partial V_2}{\partial T} = 0$
- Negative TC voltage
 - The forward voltage of a PN-junction diode exhibits a negative TC.

$$I_C = I_S \exp \frac{V_{BE}}{V_T}, \quad V_T = \frac{kT}{q}, \quad \mu \propto \mu_0 T^m, \quad m \approx -3/2, \quad n_i^2 \propto T^3 \exp[-E_g / (kT)]$$


$$E_g \approx 1.12eV \quad \text{Bandgap energy, } I_S \propto \mu k T n_i^2 = b T^{4+m} \exp \frac{-E_g}{kT}, \quad \frac{\partial V_{BE}}{\partial T} = \frac{\partial V_T}{\partial T} \ln \frac{I_C}{I_S} - \frac{V_T}{I_S} \frac{\partial I_S}{\partial T}$$

$$\frac{\partial I_S}{\partial T} = b(4+m)T^{3+m} \exp \frac{-E_g}{kT} + bT^{4+m} \left(\exp \frac{-E_g}{kT} \right) \left(\frac{E_g}{kT^2} \right), \quad \frac{V_T}{I_S} \frac{\partial I_S}{\partial T} = (4+m) \frac{V_T}{T} + \frac{E_g}{kT^2} V_T$$

$$\frac{\partial V_{BE}}{\partial T} = \frac{V_T}{T} \ln \frac{I_C}{I_S} - (4+m) \frac{V_T}{T} - \frac{E_g}{kT^2} V_T = \frac{V_{BE} - (4+m)V_T - E_g / q}{T}$$

– For $V_{BE} \approx 750mV, \frac{\partial V_{BE}}{\partial T} \approx -1.5mV / ^\circ K$

Generation of Positive-TC Voltage

 


- If two identical transistors ($I_{S1} = I_{S2}$) are biased at collector currents of $nI_0 = I_0$, and their base current are negligible

$$\Delta V_{BE} = V_{BE1} - V_{BE2} = V_T \ln \frac{nI_0}{I_{S1}} - V_T \ln \frac{I_0}{I_{S2}} = V_T \ln n$$

- Thus, V_{BE} difference exhibits a positive temperature coefficient (Proportional To Absolute Temperature : PTAT)

$$\frac{\partial \Delta V_{BE}}{\partial T} = \frac{k}{q} \ln n$$

Bandgap Reference

 

$$V_{REF} = \alpha_1 V_{BE} + \alpha_2 (V_T \ln n)$$

$$\frac{\partial \Delta V_{BE}}{\partial T} \approx -1.5 \text{ mV} / ^\circ \text{K}, \quad \frac{\partial V_T}{\partial T} \approx 0.087 \text{ mV} / ^\circ \text{K}$$

$$\alpha_1 = 1, \quad \alpha_2 \ln n (0.087 \text{ mV} / ^\circ \text{K}) = 1.5 \text{ mV} / ^\circ \text{K}$$

- We have

$$\alpha_2 \ln n \approx 17.2, \quad V_{REF} \approx V_{BE} + 17.2 V_T \approx 1.25 \text{ V}$$

- Force V_{O1} and V_{O2} to be equal


$$V_{BE1} = RI + V_{BE2}, \quad RI = V_{BE1} - V_{BE2} = V_T \ln n$$

$$RI = V_{BE1} - V_{BE2} = V_T \ln n, \quad V_{O2} = V_{BE2} + V_T \ln n$$

$$V_{out} = V_{BE2} + \frac{V_T \ln n}{R_3} (R_3 + R_2) = V_{BE2} + (V_T \ln n) \left(1 + \frac{R_2}{R_3} \right)$$

- For a zero TC, we must have
 
$$\left(1 + \frac{R_2}{R_3} \right) \ln n \approx 17.2, \quad \text{e.g., we may choose } n = 31 \text{ and } \frac{R_2}{R_3} = 4$$



Collector Current Variation

$$\frac{\partial V_{BE}}{\partial T} \approx -1.5mV / ^\circ K \quad \text{for a constant current}$$

But, the collector currents of Q_1 and Q_2 are proportional to V_T

$$I_{C1} = I_{C2} \approx (V_T \ln n) / R_3, \quad \frac{\partial V_{BE}}{\partial T} = \frac{\partial V_T}{\partial T} \ln \frac{I_C}{I_S} + V_T \left(\frac{1}{I_C} \frac{\partial I_C}{\partial T} - \frac{1}{I_S} \frac{\partial I_S}{\partial T} \right)$$


Since $\partial I_C / \partial T \approx (V_T \ln n) / (R_3 T) = I_C / T$, we have

$$\frac{\partial V_{BE}}{\partial T} = \frac{\partial V_T}{\partial T} \ln \frac{I_C}{I_S} + V_T \left(\frac{1}{I_C} \frac{\partial I_C}{\partial T} - \frac{1}{I_S} \frac{\partial I_S}{\partial T} \right) \Rightarrow \frac{\partial V_{BE}}{\partial T} = \frac{\partial V_T}{\partial T} \ln \frac{I_C}{I_S} + \frac{V_T}{T} - \frac{V_T}{I_S} \frac{\partial I_S}{\partial T}$$


$$\frac{\partial V_{BE}}{\partial T} = \frac{V_{BE} - (3 + m)V_T - E_g / q}{T} \quad \text{compared to} \quad \frac{V_{BE} - (4 + m)V_T - E_g / q}{T}$$

Thus the TC is slightly less negative than $-1.5mV/^\circ K$


Compatibility with CMOS Technology

 

 A *pnp* transistor can be formed as p⁺/n-well/p-sub



Op Amp Offset and Output Impedance

 

$$V_{BE1} - V_{OS} \approx V_{BE2} + R_3 I_{C2}$$


$$V_{out} = V_{BE2} + (R_3 + R_2) I_{C2}$$

$$V_{out} = V_{BE2} + (R_3 + R_2) \frac{V_{BE1} - V_{BE2} - V_{OS}}{R_3}$$

$$= V_{BE2} + \left(1 + \frac{R_2}{R_3}\right) (V_T \ln n - V_{OS})$$

- V_{OS} is amplified by $1 + R_2/R_3$
- V_{OS} itself varies with temperature, raising the temperature coefficient of the output voltage.

Reduce Effect of OP AMP Offset

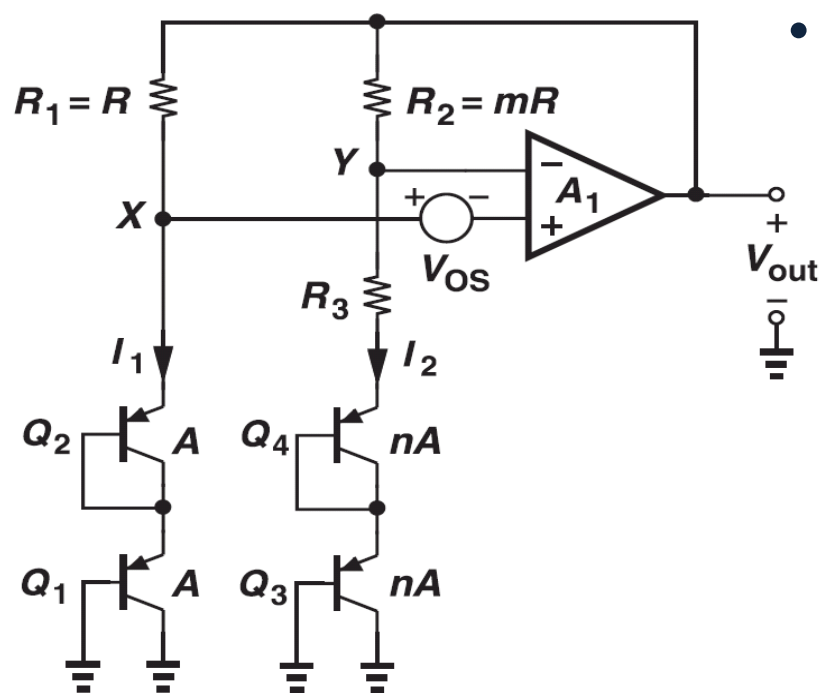

- To lower the effect of V_{OS}
 - Large devices in a carefully chosen topology so as to minimize the offset.
 - The collector currents of Q1 and Q2 can be ratioed by a factor of m such that (by R_1 and R_2)

$$\Delta V_{BE} = V_T \ln(mn)$$

- Use two pn junction in series to double ΔV_{BE}


$$V_{BE1} + V_{BE2} - V_{OS} = V_{BE3} + V_{BE4} + R_3 I_2$$

$$V_{out} = V_{BE3} + V_{BE4} + (R_3 + R_2) I_2$$

$$V_{out} = V_{BE3} + V_{BE4} + (R_3 + R_2) \frac{2V_T \ln(mn) - V_{OS}}{R_3} = 2V_{BE} + \left(1 + \frac{R_2}{R_3}\right) [2V_T \ln(mn) - V_{OS}] \approx 2 \times 1.25V = 2.5V$$

- Difficult to generate by the op amp at low supply voltage.
- Not feasible in a standard CMOS technology because the collectors of Q2 and Q4 are not grounded.

Topologies with Grounded Collectors

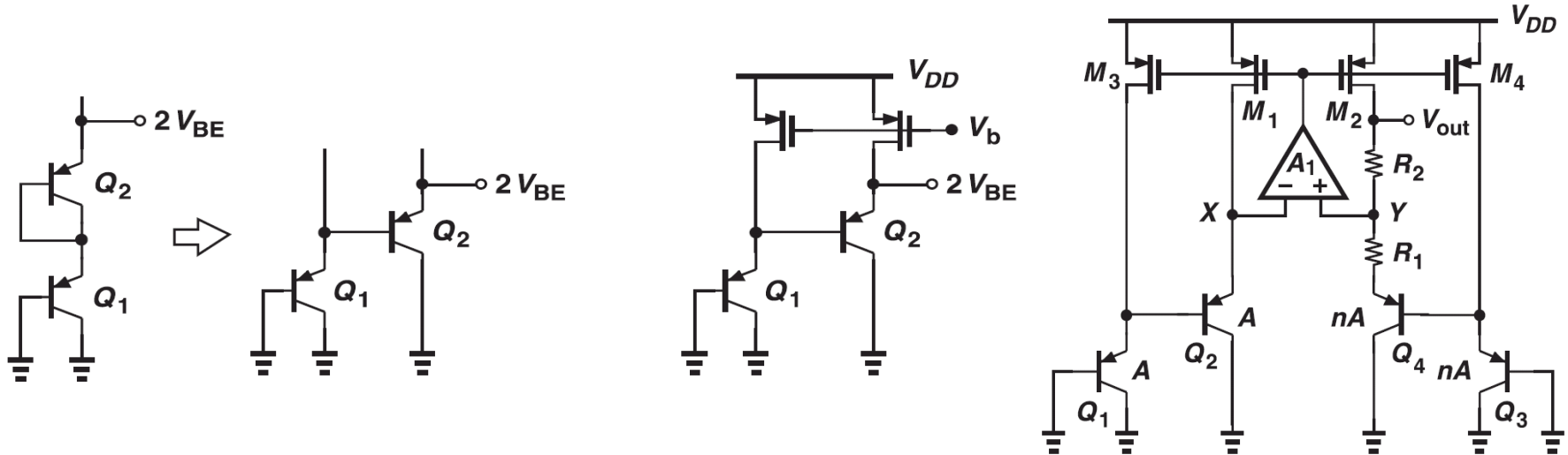

- Must ensure that the bias currents of both transistors have the same behavior with temperature.
 - Bias each transistor with current source.
- The OP amp experiences no resistive loading, but the mismatch and channel length modulation of the PMOS devices induce error at the output.
- The current gain of native *pnp* transistors are low.
 - Generate an error in the emitter current of Q1 and Q3.
 - A means of base current cancellation may be necessary.

Feedback Polarity

- The feedback signal produced by the OP amp returns to both of its input.
- The negative feedback factor is given by

$$\beta_N = \frac{1/g_{m2} + R_3}{1/g_{m2} + R_3 + R_2}$$


- The positive feedback factor is given by

$$\beta_P = \frac{1/g_{m1}}{1/g_{m1} + R_1}$$

- To ensure an overall negative feedback, we must have

$$2\beta_P < \beta_N$$

 - So that the circuits transient response remains well-behaved with large capacitive load



Bandgap Reference

- Since

$$V_{REF} = V_{BE} + V_T \ln n, \quad \frac{\partial V_{REF}}{\partial T} = \frac{\partial V_{BE}}{\partial T} + \frac{V_T}{T} \ln n = 0$$

- We have

$$\frac{V_{BE} - (4+m)V_T - E_g/q}{T} = -\frac{V_T}{T} \ln n, \quad V_{REF} = \frac{E_g}{q} + (4+m)V_T$$

- The reference voltage exhibiting a nominally-zero TC is given by a few fundamental numbers


- The bandgap voltage of silicon, E_g/q
 - The temperature exponent of mobility, m
 - The thermal voltage, V_T
- } $T \rightarrow 0 \Rightarrow V_{REF} \rightarrow E_g/q$

- Supply Dependence and Start-up


- The output voltage is independent of the supply voltage so long as the open-loop gain of the op amp is sufficiently high.
- Start-up techniques can be added to ensure the op amp turns on when the supply is applied.
- The supply rejection of the circuit typically degrades at high frequencies.

Curvature Correction

 - Bandgap voltages exhibit a finite curvature
 - Their TC is typically zero at one temperature and positive or negative at other temperature.
 - The curvature arises from temperature variation of base emitter voltages, collector currents, and offset voltages.



 
- Due to large offsets and process variations, samples of a bandgap reference display substantially different zero-TC temperatures.



Outline

1. General Consideration
2. Supply-Independent Biasing
3. Temperature-Independent Reference
- 4. PTAT Current Generation / Constant-Gm Biasing**
5. Speed and Noise Issue / Case Study

PTAT Current Generation

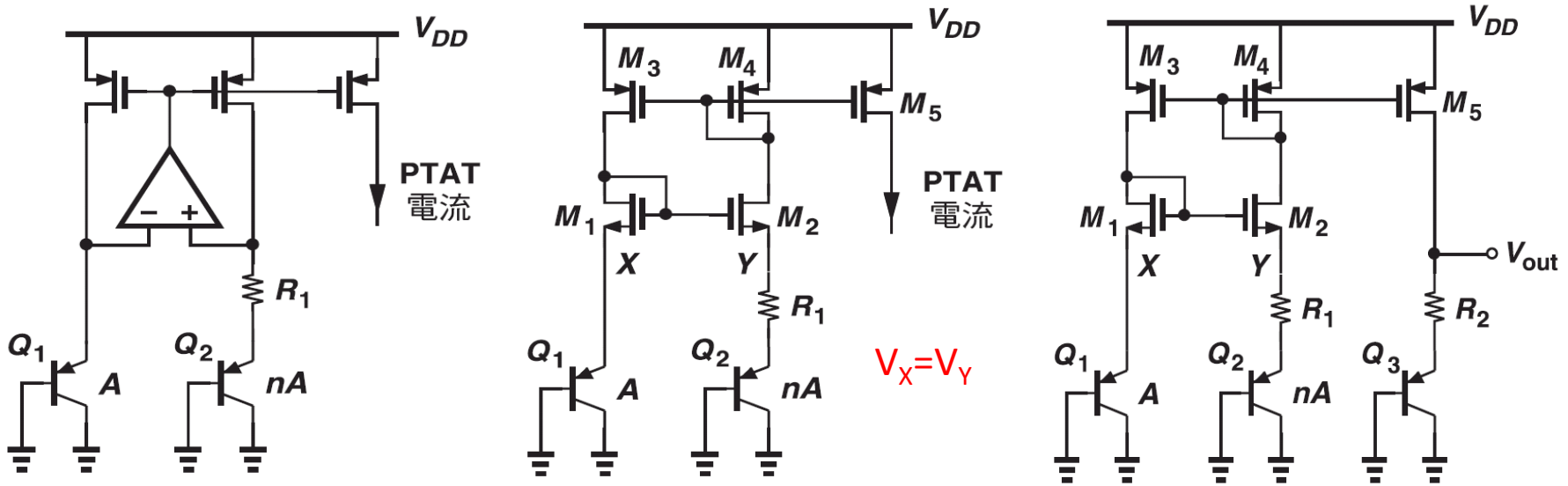

- Assume that M1-M2 and M3-M4 are identical pairs



$$\text{For } I_{D1} = I_{D2} \Rightarrow V_X = V_Y \Rightarrow I_{D1} = I_{D2} = (V_T \ln n) / R_1$$

- Due to mismatch between the transistors and the temperature coefficient of R_1 , the variation of I_{D5} deviates from the ideal equation.
- Can be readily modified to provide a bandgap reference voltage.

$$V_{REF} = V_{BE3} + \frac{R_2}{R_1} V_T \ln n$$

- Mismatches of the PMOS devices introduce error in V_{out} .

Constant Gm Biasing

 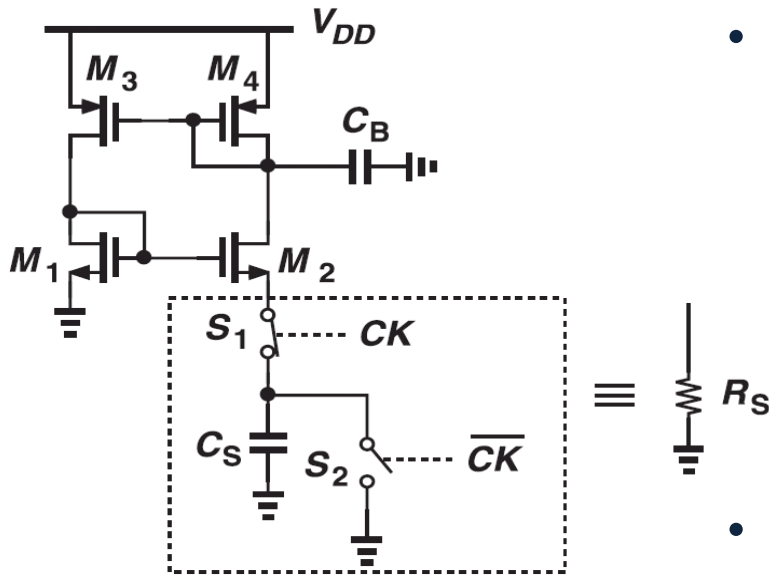

- The transconductance of MOSFETs determine
 - Noise
 - Small signal gain
 - Speed

$$I_{out} = \frac{2}{\mu_n C_{ox} (W/L)_N} \frac{1}{R_S^2} \left(1 - \frac{1}{\sqrt{K}}\right)^2$$

$$g_{m1} = \sqrt{2\mu_n C_{ox} \left(\frac{W}{L}\right)_N I_{D1}} = \frac{2}{R_S} \left(1 - \frac{1}{\sqrt{K}}\right)$$

- The value of R_S does vary with temperature and process
 - Replace R_S by switched capacitor equivalent


$$R_S = \frac{1}{C_S f_{CK}}$$

- The absolute value of capacitor is typically more tightly controlled and the TC of capacitors is much smaller than that of resistors.
 - V-to-I conversion with high accuracy



Outline

1. General Consideration
2. Supply-Independent Biasing
3. Temperature-Independent Reference
4. PTAT Current Generation / Constant-Gm Biasing
- 5. Speed and Noise Issue / Case Study**

Speed and Noise Issues

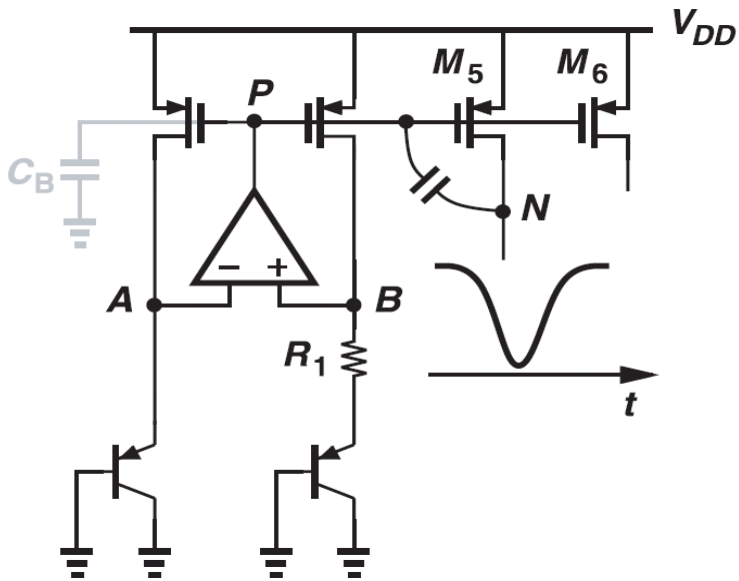


- Assuming the voltage at node N is heavily disturbed by the circuit fed by M_5
 - The OP amp can not maintain V_p , I_{bias} of M_5 & M_6 experience large transient changes.
 - Transient duration of P may be quite long.
 - May require a high-speed OP amp.
- Node P can be bypass to ground by C_B .
 - Requiring the op amp to be of one stage nature
 - Applying a disturbance at the output and observing the settling behavior.

 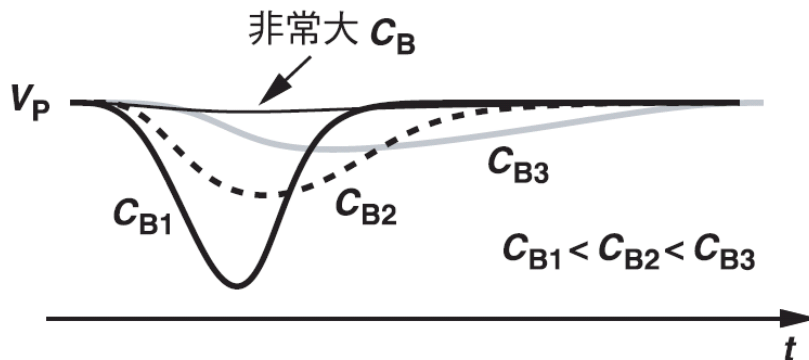

R_{out} of the Bandgap Reference

 - Output Impedance of the Bandgap Reference




$$V_{AB} = -g_{mP} V_X \frac{1}{g_{mN}} + g_{mP} V_X \left(\frac{1}{g_{mN}} + R_1 \right) = g_{mP} V_X R_1$$

$$I_X = \frac{V_X + g_{mP} V_X R_1 A(s)}{R_{out}}$$


$$\frac{V_X}{I_X} = \frac{R_{out}}{1 + g_{mP} R_1 A(s)} = \frac{R_{out}}{1 + g_{mP} R_1 \frac{A_0}{1 + s/\omega_0}}$$
 
$$= \frac{R_{out}}{1 + g_{mP} R_1 A_0} \frac{1 + \frac{s}{\omega_0}}{1 + \frac{s}{(1 + g_{mP} R_1 A_0)\omega_0}}$$



$$|Z_{out}| = \frac{R_{out}}{1 + g_{mP} R_1 A_0} \left| \frac{1 + j(1 + g_{mP} R_1 A_0)}{1 + j} \right| = \frac{R_{out}}{\sqrt{2}}$$

Noise in Reference Generator

 

- Taking into account the input referred noise voltage of the op amp, the small signal drain currents of M1 and M2 are equal to

$$\frac{V_{n,out}}{R_1 + g_{mN}^{-1}}$$

- We have

$$V_p = -\frac{V_{n,out}}{R_1 + g_{mN}^{-1}} \cdot \frac{1}{g_{mP}}$$

- The differential voltage at the input of the op amp as




$$-\frac{V_{n,out}}{R_1 + g_{mN}^{-1}} \cdot \frac{1}{g_{mP}} \cdot \frac{1}{A_0}$$

$$\frac{V_{n,out}}{R_1 + g_{mN}^{-1}} \cdot \frac{1}{g_{mN}} - \frac{V_{n,out}}{g_{mP} A_0 (R_1 + g_{mN}^{-1})} = V_{n,op} + V_{n,out}, \quad V_{n,out} \left[\frac{1}{R_1 + g_{mN}^{-1}} \left(\frac{1}{g_{mN}} - \frac{V_{n,out}}{g_{mP} A_0} \right) - 1 \right] = V_{n,op}$$

$$\text{Typically } g_{mP} A_0 \gg g_{mN} \gg R_1^{-1}$$

$$|V_{n,out}| \approx V_{n,op}$$

Case Study-I

   

- 2 series B-E voltages in each branch to reduce the effect of MOSFET mismatches.
- PMOS current mirror arrangement ensures equal collector currents for Q_1 - Q_4 .
- Use cascode current mirror to resolve channel length modulation.
- Use self-biased cascode to obviate the need for V_{b1} and V_{b2} .
 - R_2 and R_3 sustain proper voltages to allow all MOSFETS to remain in saturation

Generation of a Floating Ref. Voltage

- M_{11} sets the gate voltage of M_9 at $V_{BE4} + V_{GS11}$

$$I_{D9} = \frac{V_{BE4}}{R_6} \Rightarrow V_{R4} = V_{BE4} \frac{R_4}{R_6}$$


- If M_{10} is identical to M_2

$$|I_{D10}| = 2 \frac{V_T \ln n}{R_1} \Rightarrow V_{R5} = 2(V_T \ln n) \frac{R_5}{R_1}$$


- The OP amp ensures that

$$V_E \approx V_F \Rightarrow V_{out} = \frac{R_4}{R_6} V_{BE4} + 2 \frac{R_5}{R_1} V_T \ln n$$

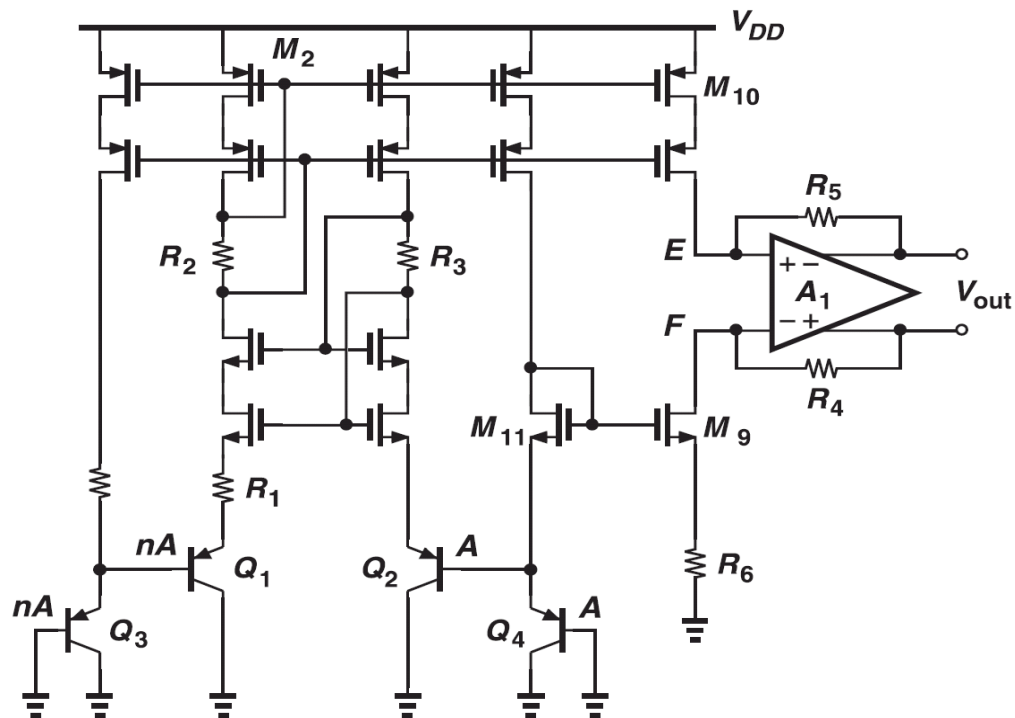- This design regulates the supply voltage of the core and the OP amp to enhance the PSRR




To Improve PSRR

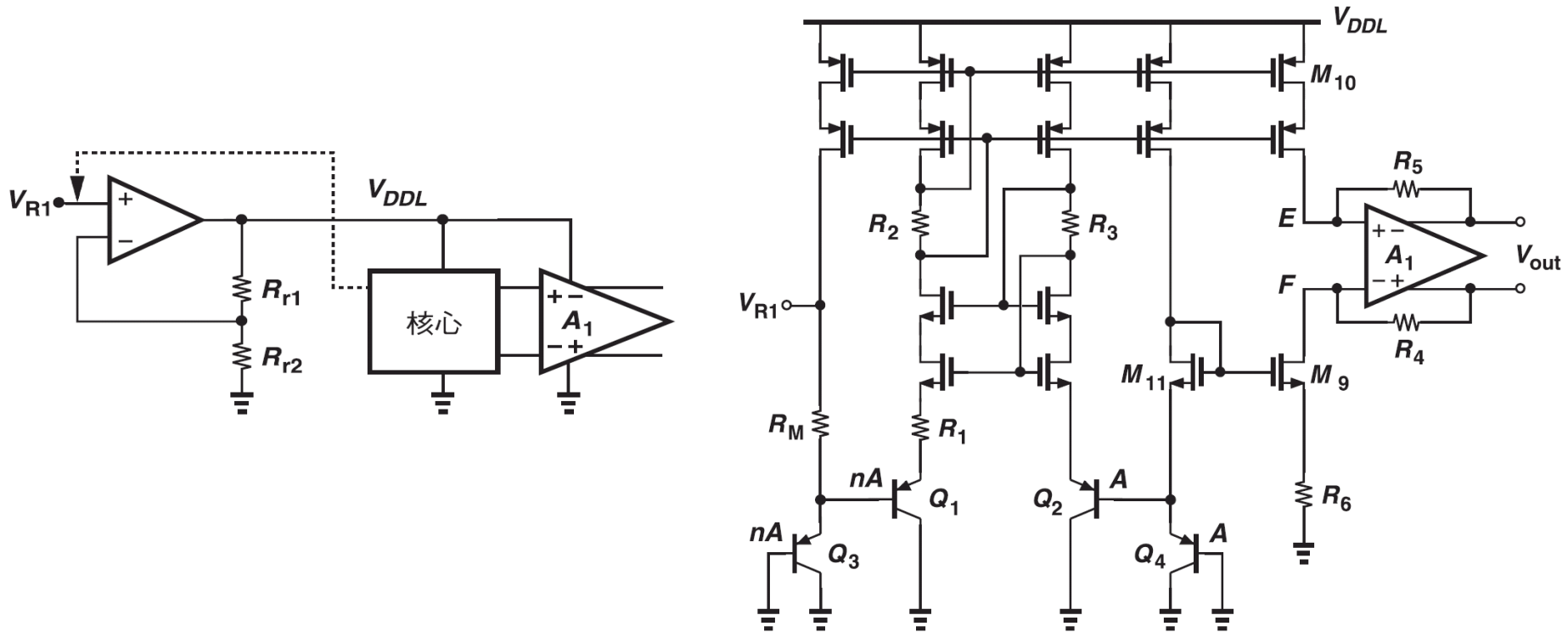

- A local supply V_{DDL} is defined by a reference V_{R1} and the ratio of R_{r1} and R_{r2} .
- To minimize the dependence of V_{R1} upon the supply, this voltage is established inside the core.

Overall Circuit of the Bandgap Gen.

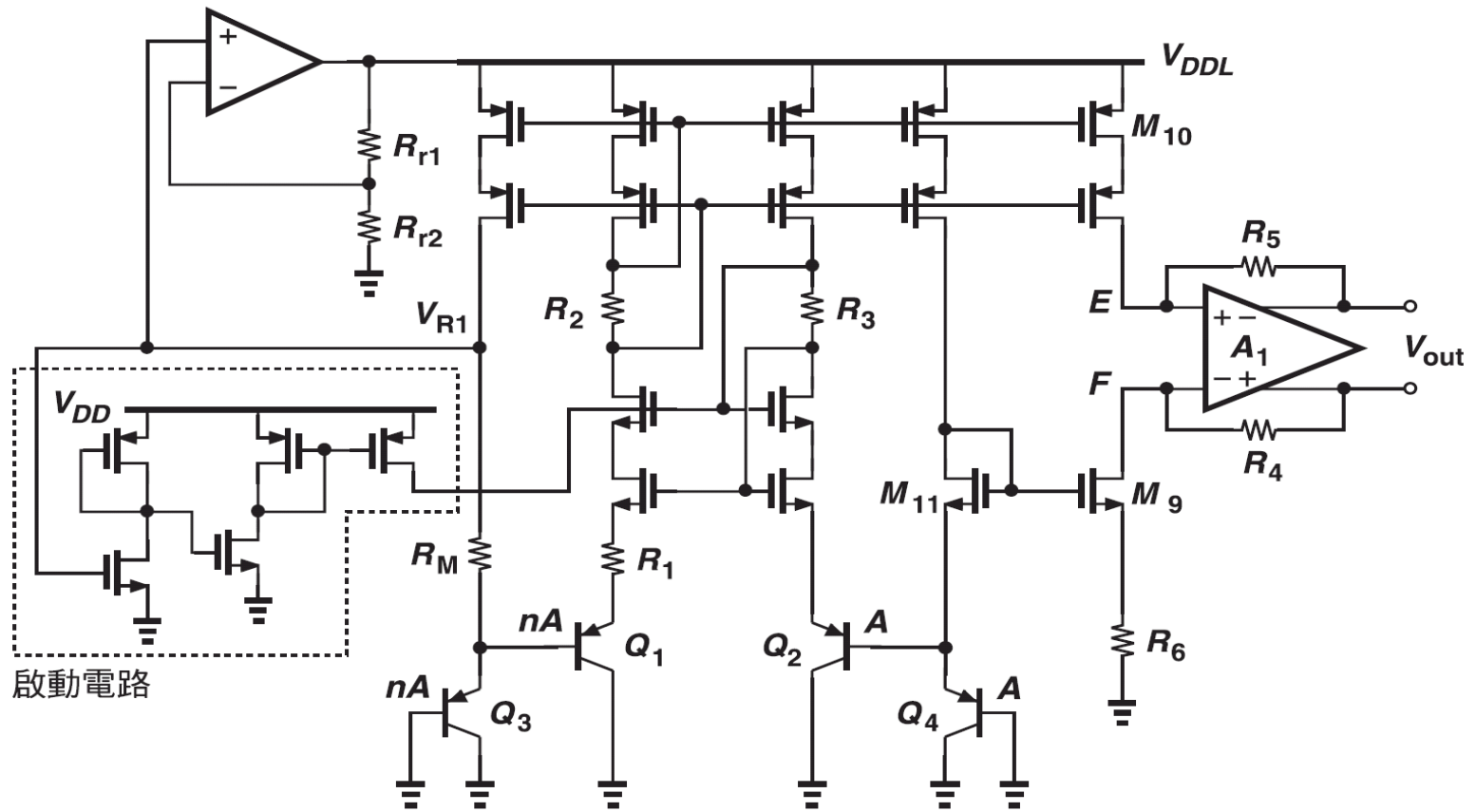

- A start-up circuit is also used.
- Operating from a 5V supply. $V_{out} = 2V$.
- Supply rejection is 94dB at low frequencies, dropping to 58 dB at 100 kHz.

Bonus Sharing

- 每位企業家都該看的10段YouTube影片
 - <http://www.bnext.com.tw/article/view/cid/103/id/18714>
- **Steve Jobs Stanford Commencement Speech 2005**
 - http://www.youtube.com/watch?v=D1R-jKKp3NA&feature=player_embedded&hd=1
 - <http://stanley5.blogspot.com/2007/01/steve-jobs-stanford-commencement.html>
- 求知若飢，虛心若愚（Stay Hungry, Stay Foolish）
- 謝謝大家這學期的投入.... It's a great experience for me..
 - 記得去按 “ **讚!** ”