



# CHAPTER 5

# Current Mirror

# Outline



---

- 1. Basic Current Mirrors**
2. Cascode Current Mirrors
3. Active Current Mirrors
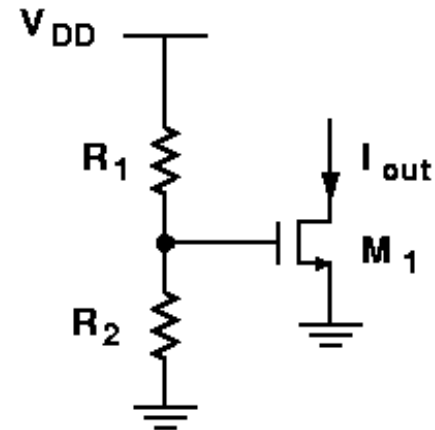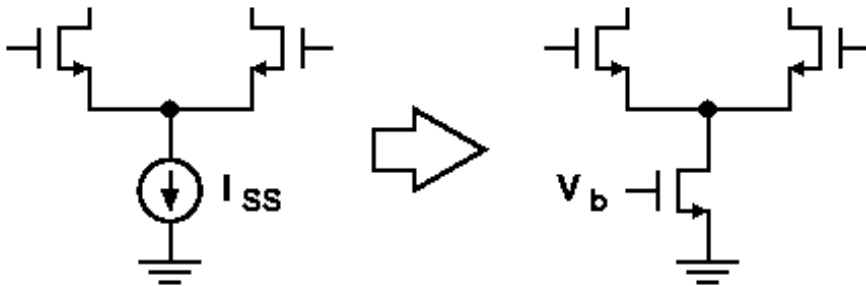
# Current Source Issues

- Design issues



- Voltage headroom.
- Output impedance.
- Supply, process, and temperature dependence.
- Matching.



$$I_{out} \approx \frac{1}{2} \mu_n C_{ox} \frac{W}{L} \left( \frac{R_2}{R_1 + R_2} V_{DD} - V_{TH} \right)^2$$


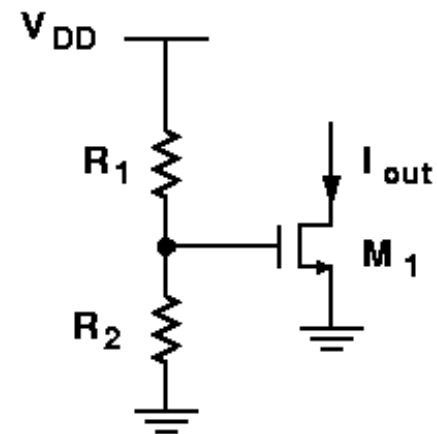
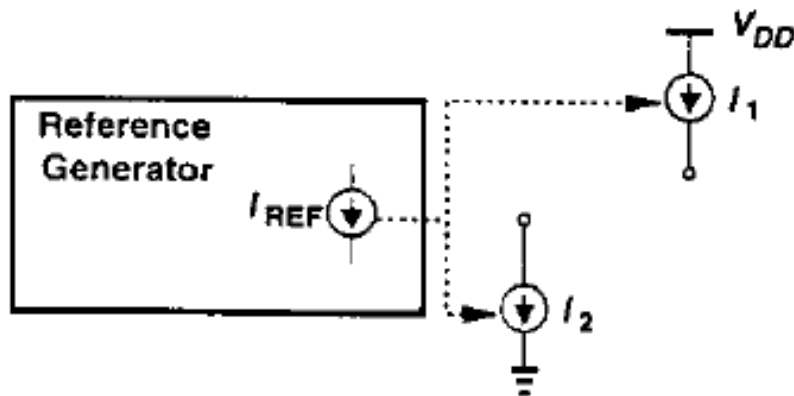
# Current Source with Constant $V_b$

- Depending on supply, process, and temperature.
- The threshold voltage may vary by 100 mV from wafer to wafer.
- Both  $\mu_n$  and  $V_{TH}$  exhibit temperature dependence.
- The issue becomes more severe as the device is biased with a smaller overdrive voltage. (200mV  $V_{ov}$ , 50mV  $\Delta V_{TH}$  cause 44% error)
- If the gate-source voltage of a MOSFET is precisely defined, then its drain current is not.
  - Copying currents from a reference.



# Basic Current Mirror

- For  $I_{out} = I_{REF}$

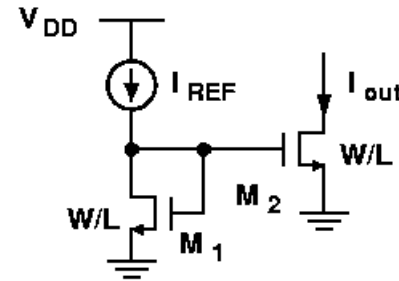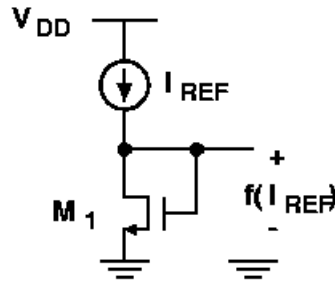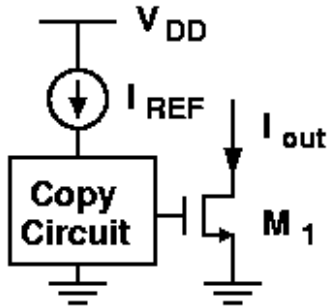

$$V_{GS} = f^{-1}(I_{REF})$$

$$ff^{-1}(I_{REF}) = I_{REF}$$

$$I_{REF} = \frac{1}{2} \mu_n C_{ox} \left( \frac{W}{L} \right)_1 (V_{GS} - V_{TH})^2$$

$$I_{out} = \frac{1}{2} \mu_n C_{ox} \left( \frac{W}{L} \right)_2 (V_{GS} - V_{TH})^2$$


$$\frac{I_{out}}{I_{REF}} = \frac{(W/L)_2}{(W/L)_1}$$

- It allows precise copying of the current with no dependence on process and temperature.


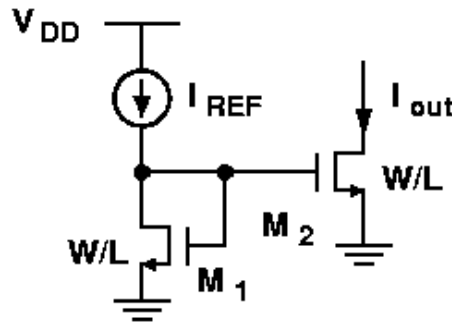
# Current Mirror with $r_o$

- Channel length modulation effect results in significant error in copying currents.



$$I_{D1} = \frac{1}{2} \mu_n C_{ox} \left( \frac{W}{L} \right)_1 (V_{GS} - V_{TH})^2 (1 + \lambda V_{DS1}), \quad I_{D2} = \frac{1}{2} \mu_n C_{ox} \left( \frac{W}{L} \right)_2 (V_{GS} - V_{TH})^2 (1 + \lambda V_{DS2})$$

- As  $\frac{I_{D2}}{I_{D1}} = \frac{(W/L)_2}{(W/L)_1} \frac{1 + \lambda V_{DS2}}{1 + \lambda V_{DS1}}$ , for  $I_{D1} = I_{D2}$ ,  $V_{DS1}$  must be equal to  $V_{DS2}$ .
- Use cascode structure to improve the ratio accuracy of current mirror.


# Outline

---

1. Basic Current Mirrors
- 2. Cascode Current Mirrors**
3. Active Current Mirrors



# Cascode Current Mirror

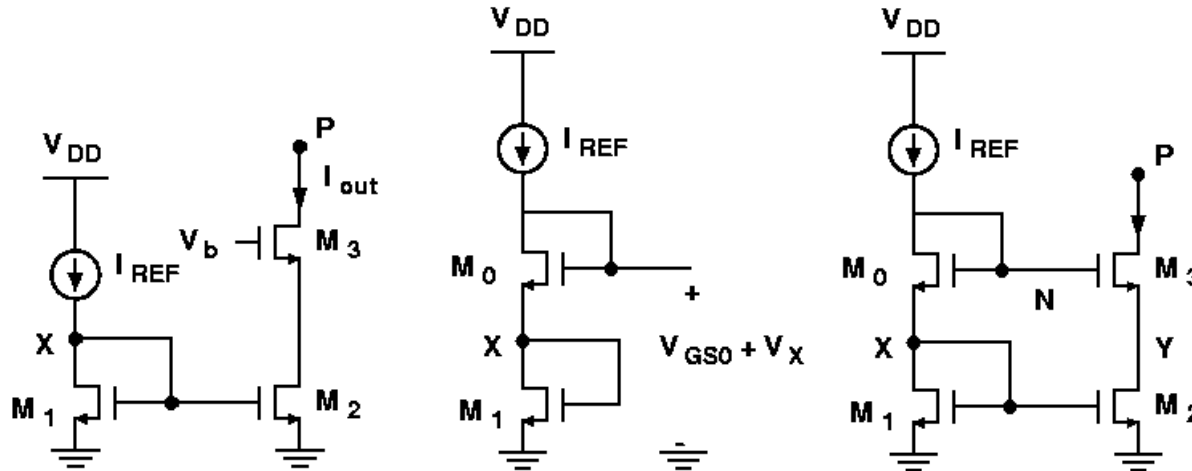

- $V_b$  is chosen such that  $V_Y = V_X$ .

$$V_b - V_{GS3} = V_X, \quad V_b = V_{GS3} + V_X, \quad V_N = V_{GS0} + V_X$$

$$\text{if } \frac{(W/L)_3}{(W/L)_0} = \frac{(W/L)_2}{(W/L)_1}, \text{ then } V_{GS0} = V_{GS3} \text{ and } V_X = V_Y$$

- Such accuracy is obtained at the cost of the voltage headroom consumed by  $M_3$ .

# Cascode Current Mirror



- The minimum allowable voltage at node P is equal to

$$\begin{aligned} V_N - V_{TH} &= V_{GS1} + V_{GS0} - V_{TH} \\ &= (V_{GS1} - V_{TH}) + (V_{GS0} - V_{TH}) + V_{TH} \end{aligned}$$

- The voltage of  $V_N = V_{GS1} + V_{GS0}$
- For  $M_2$  to be in saturation region,  $V_b$  can be chosen as low as


$$V_b = V_{GS3} + V_{DS2}$$

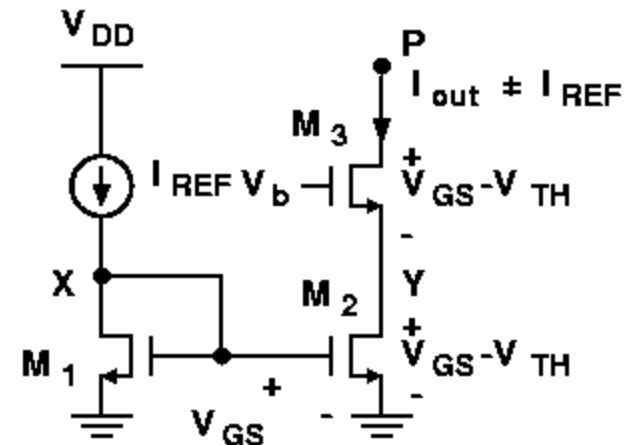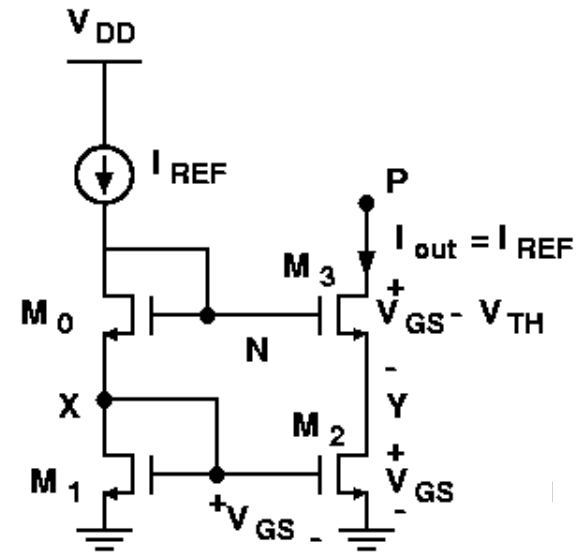- But the output current does not accurately track  $I_{REF}$ .



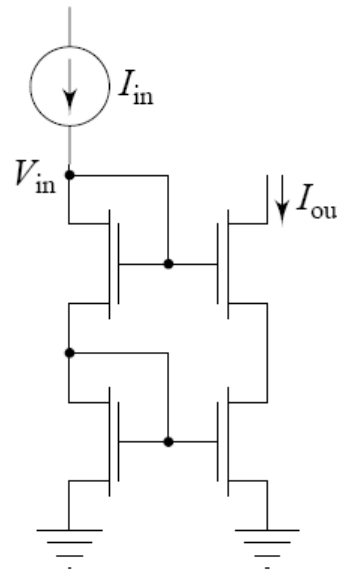
# Cascode Current Mirror

- Each of these mirrors is self biasing, has a high output impedance, and provides a low systematic transfer error.
- Each requires an input voltage of two diode drops.
- Each has an output compliance voltage of a diode drop plus a saturation voltage.
- Neither is suitable for use with a low power supply voltage.



Stacked

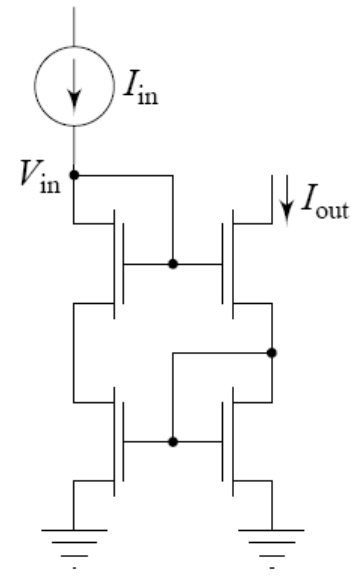

Super Wilson

# Wide-Swing Cascode Current Mirror

- To eliminate the accuracy-headroom trade-off.

- For M2 to be saturated

$$V_b - V_{TH2} \leq V_X (= V_{GS1})$$

- For M1 to be saturated

$$V_{GS1} - V_{TH1} \leq V_A (= V_b - V_{GS2})$$

- Thus


$$V_{GS2} + (V_{GS1} - V_{TH1}) \leq V_b \leq V_{GS1} + V_{TH2}$$

- A solution exist if

$$V_{GS2} + (V_{GS1} - V_{TH1}) \leq V_{GS1} + V_{TH2} \Rightarrow V_{GS2} - V_{TH2} \leq V_{TH1}$$

- Let
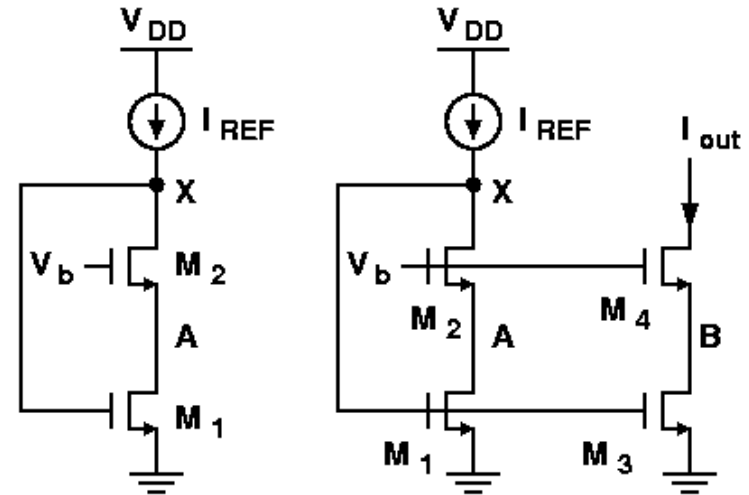
$$V_{GS2} = V_{GS4} \Rightarrow V_b = V_{GS2} + (V_{GS1} - V_{TH1}) = V_{GS4} + (V_{GS3} - V_{TH3})$$



# Wide-Swing Cascode Current Mirror

- Generation of biased voltage  $V_b$

- Let  $V_{GS5} \approx V_{GS2}$
- $V_{DS6} = V_{GS6} - I_1 R_b = V_{DS1}$
- $\Rightarrow$  If  $V_{GS6} = V_{GS1}$
- $\Rightarrow I_1 R_b = V_{TH6} = V_{TH1}$

- Some inaccuracy arises because  $M_5$  does not suffer from body effect whereas  $M_2$  does.
- $I_1 R_b$  is not well controlled.



- The diode connected  $M_7$  has a large W/L such that

$$V_{GS7} \approx V_{TH7}$$

$$V_{DS6} \approx V_{GS6} - V_{TH7}$$


$$V_b = V_{GS5} + V_{GS6} - V_{TH7}$$

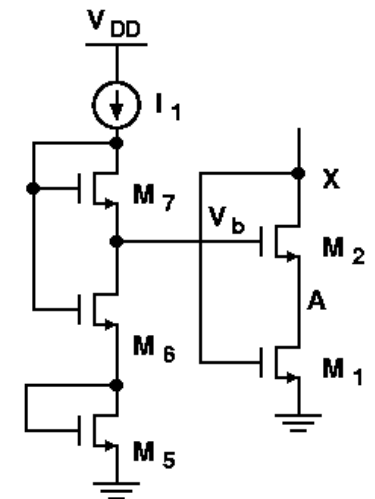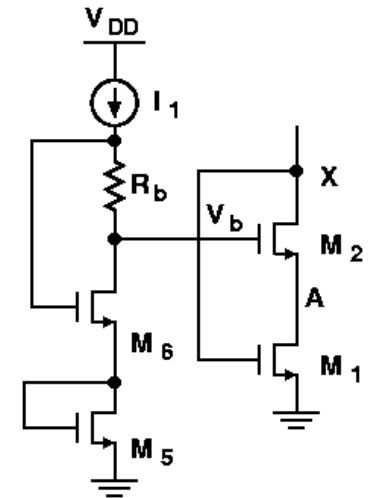- This circuit suffers from similar errors due to body effect.



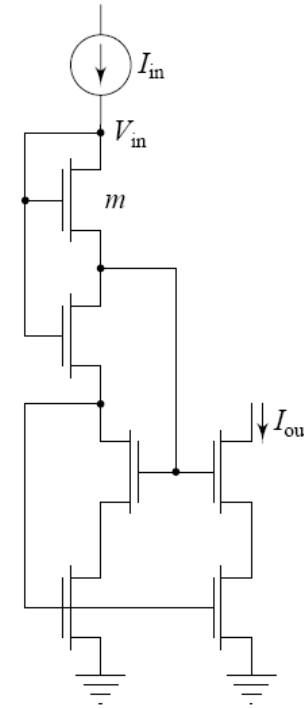
# Wide-Swing Cascode Current Mirror

- All Self biasing, has a high output impedance, and provides a low systematic transfer error.
- Each has an output compliance voltage of two saturation voltages.
- The Ssoch mirror requires an input voltage of two diode drops, which makes it unsuitable for low-voltage applications.
- The Brooks-Rybicki mirror requires an input voltage of a diode drop plus a saturation voltage, but requires a different value of  $R$  for every  $I_{in}$ .



Ssoch

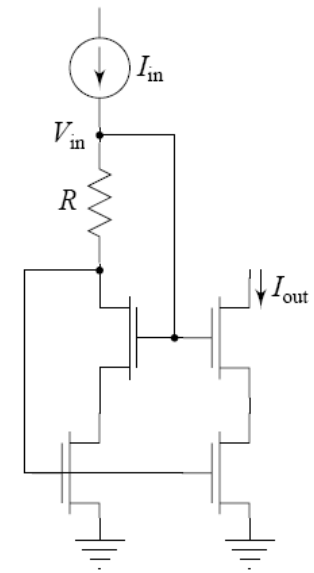

Brooks & Rybicki

# Wide-Swing Cascode + SF Level Shifter

- Shift the gate voltage of  $M_3$  down with respect to  $V_N$  by interposing a source follower.
- Let  $M_S$ 's  $V_{GSs} = V_{TH3}$ ,

$$V_{N'} \approx V_N - V_{TH3}$$

$$V_B = V_{GS1} + V_{GS0} - V_{TH3} - V_{GS3} = V_{GS1} - V_{TH3}$$


- $M_S$  is biased at a very low current density,

$$V_{GSs} - V_{THs} \approx \sqrt{\frac{2I}{\mu_n C_{ox} W / L}}$$

- $M_2$  is at the edge of the saturation region.
- Substantial current mismatch is introduced for


$$V_{DS2} \neq V_{DS1}$$

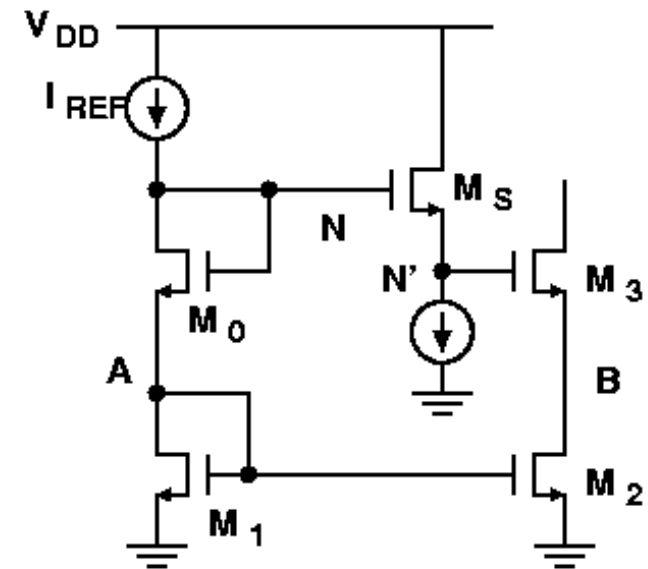- If the body effect of  $M_0$ ,  $M_S$ , and  $M_3$  is considered, it is difficult to guarantee that  $M_2$  operates in saturation.


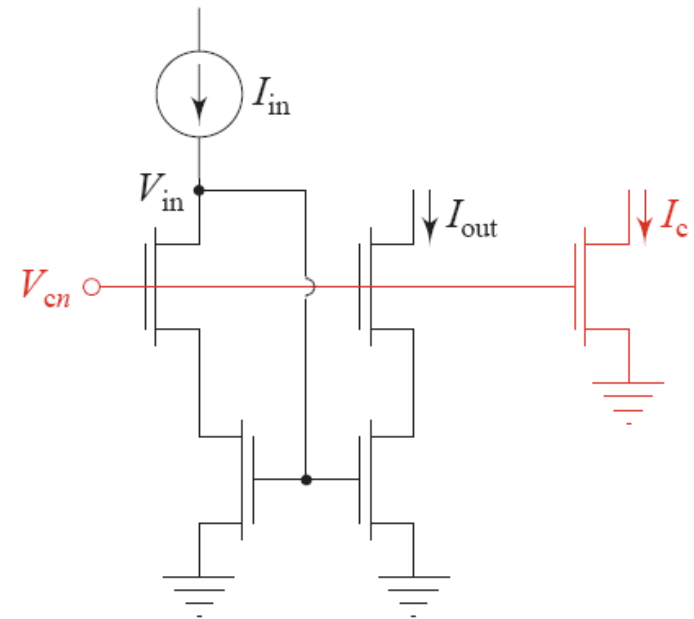
# Wide-Swing Cascode Current Mirror

- To facilitate low-voltage operation, we can remove the cascode bias-voltage generation from the input branch.
- The output compliance voltage remains two saturation voltages.
- The input voltage becomes a diode drop, comparable to that of a simple mirror.
- *The optimal value of  $V_{cn}$  depends on  $I_{in}$ , which sometimes requires us to generate  $V_{cn}$  adaptively.*





Babanezhad & Gregorian


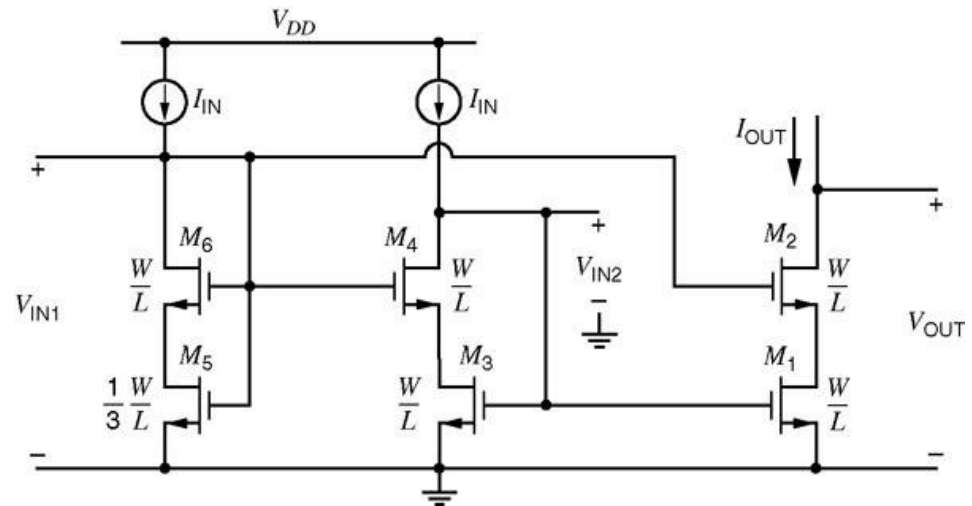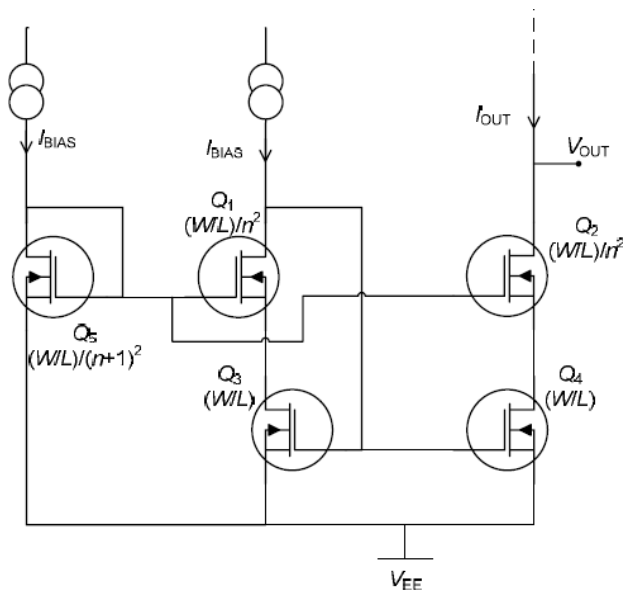
# Wide-Swing Cascode Current Mirror

- $V_{OUT} = V_{DS2} + V_{DS4} = V_{OD2} + V_{OD4}$  and  $V_{OD4} = nV_{OD2}$
- $V_{OUT\ min} = V_{OD2} + nV_{OD2} = (n+1)V_{OD}$ , Often  $n = 1$ ;  $V_{OUT\ min} = 2(V_{GS2} - V_t)$




$$V_{IN1} = V_{DS5} + V_{DS6} = V_t + 2V_{OV}$$

$$V_{IN2} = V_{GS3} = V_t + V_{OV}$$
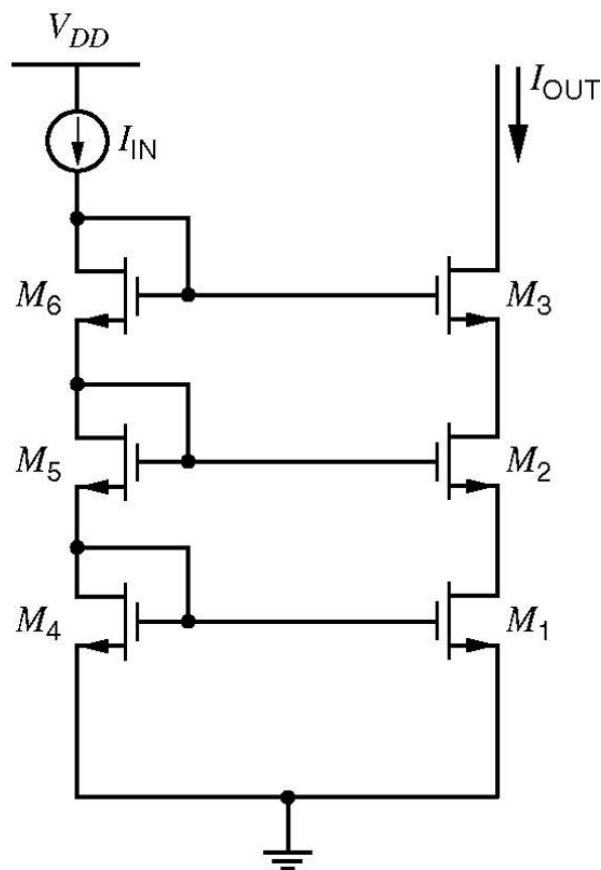
# Double-Cascode Current Mirror

- Higher output impedance, more current ratio accuracy
- Smaller output swing






# Outline

---

1. Basic Current Mirrors
2. Cascode Current Mirrors
- 3. Active Current Mirrors**
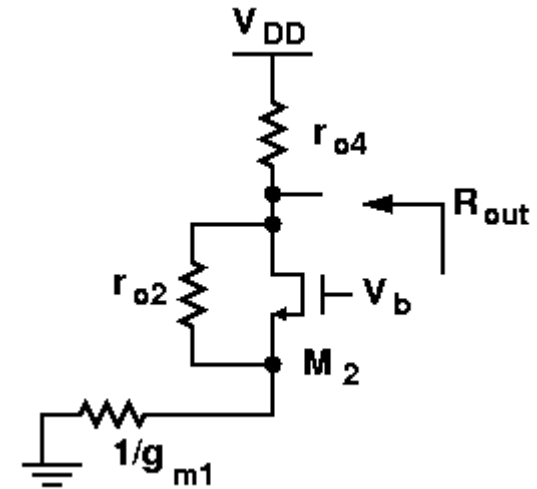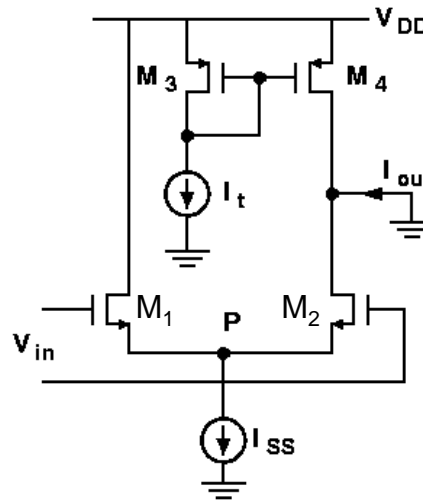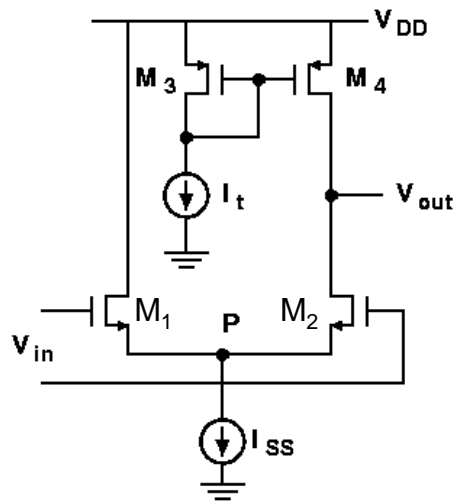
# Active Current Mirror

- Current mirror can also process signals



$$|A_v| = G_m R_{out} \quad G_m = \frac{I_{out}}{V_{in}} = \frac{g_{m1} V_{in} / 2}{V_{in}} = \frac{g_{m1}}{2}$$

- The output impedance looking into the drain of  $M_2$  is



$$(1 + g_{m2} r_{o2}) (1 / g_{m1,2}) + r_{o2} = 2r_{o2} + 1 / g_{m1} \approx 2r_{o2}$$

- Thus,

$$R_{out} \approx (2r_{o2}) \parallel r_{o4} \Rightarrow |A_v| \approx \frac{g_{m1}}{2} [(2r_{o2}) \parallel r_{o4}] \quad \text{If } r_{o4} \rightarrow \infty \Rightarrow |A_v| \approx g_{m1} r_{o2}$$

# Active Current Mirror

- An Alternative Solution

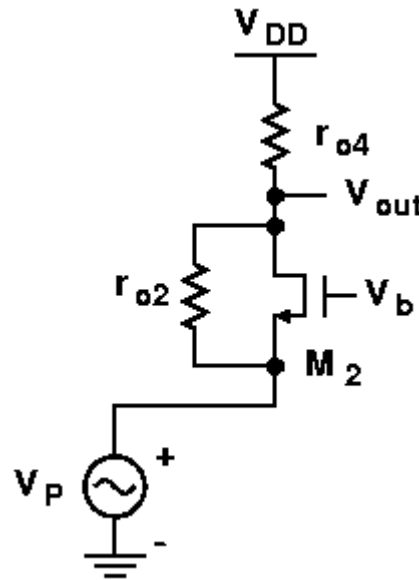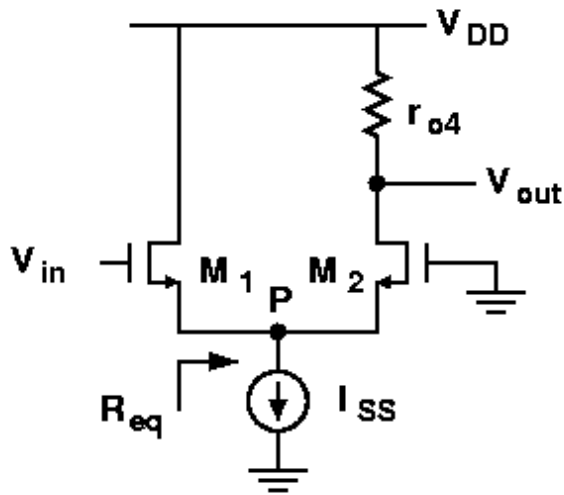

$$\frac{V_{out}}{V_{in}} = \frac{V_{out}}{V_p} \frac{V_p}{V_{in}} \quad \frac{V_p}{V_{in}} = \frac{R_{eq}}{R_{eq} + \frac{1}{g_{m1}}}$$




$$R_{eq} \approx \frac{1}{g_{m2}} + \frac{r_{O4}}{g_{m2}r_{O2}} = \frac{1}{g_{m2}} \left( 1 + \frac{r_{O4}}{r_{O2}} \right)$$

$$\frac{V_p}{V_{in}} = \frac{\frac{1}{g_{m2}} \left( 1 + \frac{r_{O4}}{r_{O2}} \right)}{\frac{1}{g_{m1}} + \frac{1}{g_{m2}} \left( 1 + \frac{r_{O4}}{r_{O2}} \right)} = \frac{1 + \frac{r_{O4}}{r_{O2}}}{2 + \frac{r_{O4}}{r_{O2}}}$$


$$\frac{V_{out}}{V_{in}} = \frac{1 + \frac{r_{O4}}{r_{O2}}}{2 + \frac{r_{O4}}{r_{O2}}} \cdot \frac{g_{m2}r_{O2}}{1 + \frac{r_{O2}}{r_{O4}}} = \frac{g_{m2}r_{O2}r_{O4}}{2r_{O2} + r_{O4}} = \frac{g_{m2}}{2} [(2r_{O2}) \parallel r_{O4}]$$
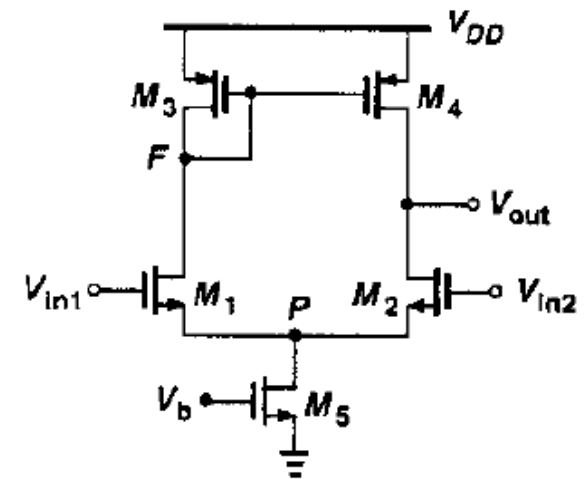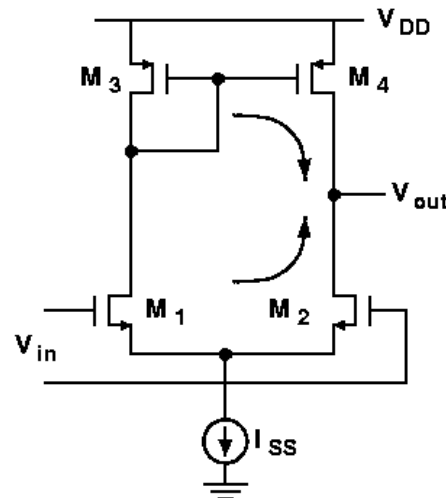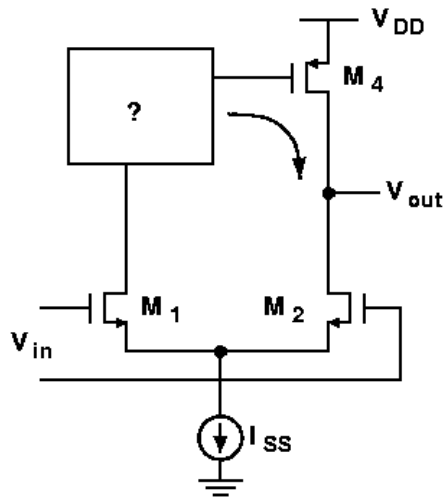
# Differential to Single-Ended Amplifier

- Current combination utilizing current mirror.





- If  $V_{in1}$  is much more negative than  $V_{in2}$ ,  $M_1$  is off and so are  $M_3$  and  $M_4$ . Both  $M_2$  and  $M_5$  operate in deep triode region.
- For a small  $|V_{in1} - V_{in2}|$ ,  $M_1 - M_4$  are saturated  $\Rightarrow$  high gain
- The minimum input voltage level of  $V_{in2} = V_{GS1,2} + V_{DS5,min}$
- With perfect symmetry,  $V_{out} = V_F = V_{DD} - |V_{GS3}|$ .
- But  $V_{out}$  can vary a lot if device mismatches occur.

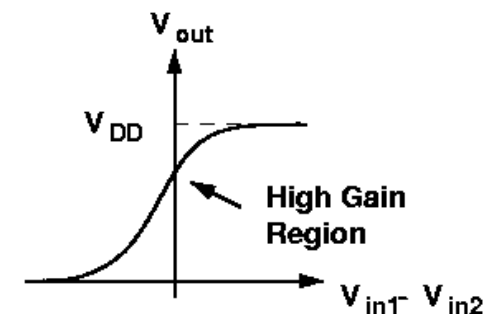


# Small-Signal Analysis

- Node "P" is not a virtual ground since amplitude of  $V_X \neq V_Y$
- Find  $G_m$  and  $R_{out}$ ,  $|A_v| = G_m R_{out}$

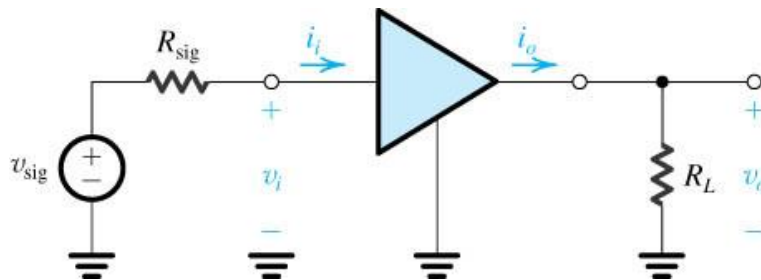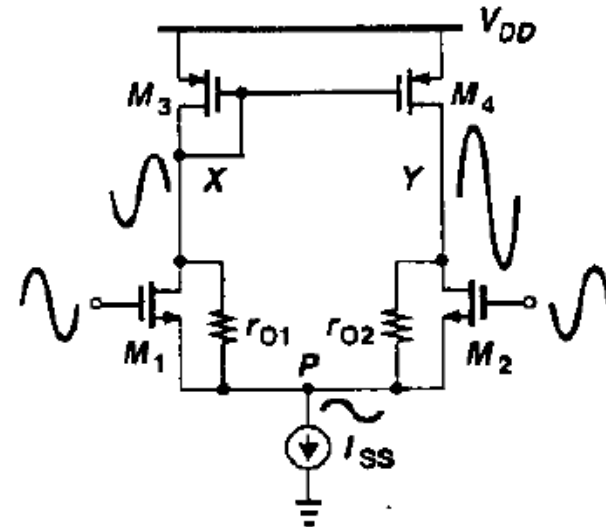

Short-circuit  
Transconductance

$$G_m \equiv \left. \frac{i_o}{v_i} \right|_{R_L=0}$$

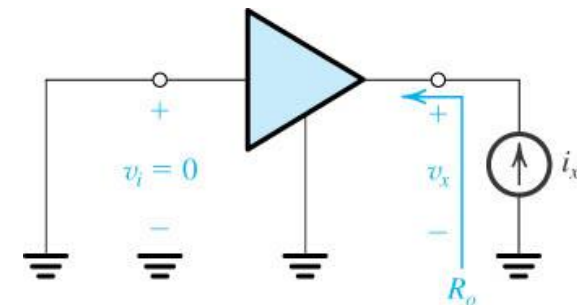


Output resistance  
of amplifier proper

$$R_o \equiv \left. \frac{v_x}{i_x} \right|_{v_i=0}$$

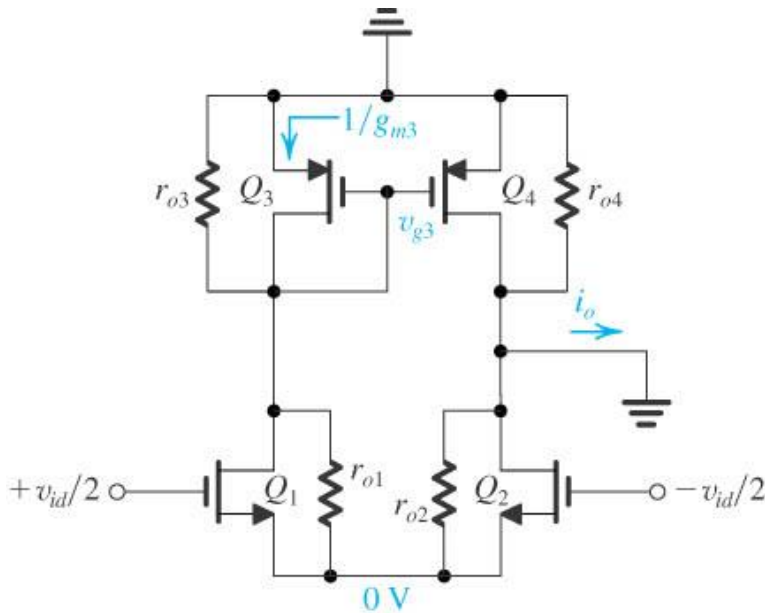
# Transconductance $G_m$

- The impedance from Q1 drain to ground is small, it makes source node as virtual ground.



$$R_{Q_1\text{-Drain}} = \frac{1}{g_{m3}} \parallel r_{o3} \parallel r_{o1}$$
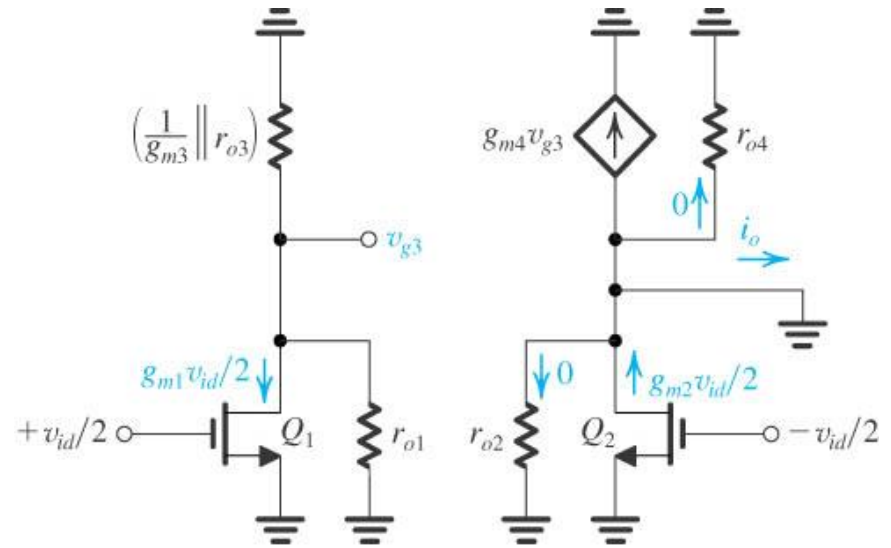
$$v_{g3} = -g_{m1} \left( \frac{v_{id}}{2} \right) \left( \frac{1}{g_{m3}} \parallel r_{o3} \parallel r_{o1} \right) \approx - \left( \frac{g_{m1}}{g_{m3}} \right) \left( \frac{v_{id}}{2} \right)$$




$$i_o = -g_{m4}v_{g3} + g_{m2}(v_{id}/2)$$

$$i_o = g_{m1} \left( \frac{g_{m4}}{g_{m3}} \right) \left( \frac{v_{id}}{2} \right) + g_{m2} \left( \frac{v_{id}}{2} \right)$$

$$g_{m3} = g_{m4}, g_{m1} = g_{m2} = g_m, i_o = g_m v_{id}, G_m = g_m$$


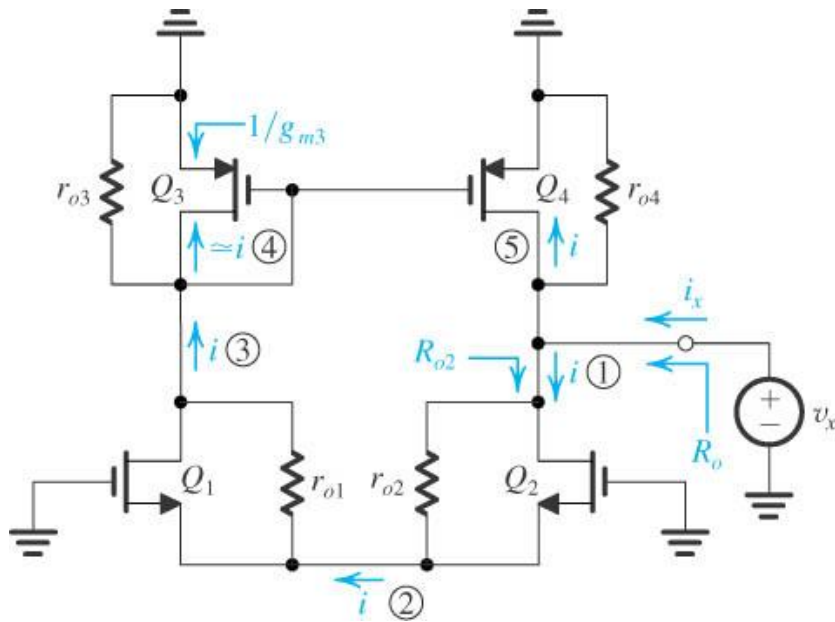
# Determining the Output Resistance $R_o$



$$R_{o2} = r_{o2} + (1 + g_{m2}r_{o2})(1/g_{m1}) \approx 2r_{o2}$$

For  $g_{m1} = g_{m2} = g_m$ ,  $g_{m2}r_{o2} \gg 1$   
 $\Rightarrow R_{o2} \cong 2r_{o2}$

$$i_x = \frac{v_x}{R_{o2}} + \frac{v_x}{r_{o4}}$$

$$R_o = R_{o2} \parallel r_{o4} \cong \frac{1}{2}r_o$$


- $G_m = g_{m1,2} \cong g_m, R_{out} = R_o \cong \frac{1}{2}r_o$
- $|A_v| = G_m R_{out} = g_m [(2r_{o2}) \parallel r_{o4}] \cong \frac{1}{2}g_m r_o$

compared to p.21

$$A_v = \frac{g_{m2}}{2} [(2r_{o2}) \parallel r_{o4}],$$

6dB improved

# Common-Mode Gain and CMRR

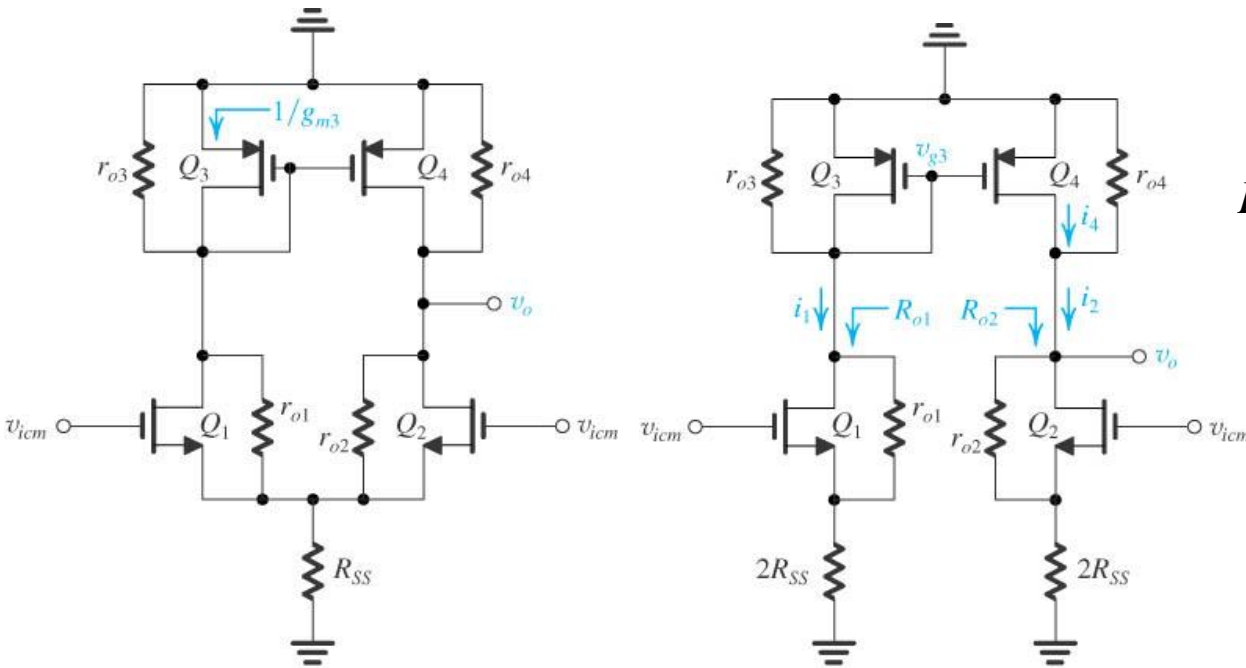

$$i_1 = i_2 \cong \frac{v_{icm}}{2R_{SS}}$$

Let  $r_{o1} = r_{o2} = r_o$     $g_{m1} = g_{m2} = g_m$

$$R_{o1} = R_{o2} = r_o + 2R_{SS} + 2g_m r_o R_{SS}$$

$$v_{g3} = -i_1 \left( \frac{1}{g_{m3}} \parallel r_{o3} \right)$$

$$i_4 = -g_{m4} v_{g3} = i_1 g_{m4} \left( \frac{1}{g_{m3}} \parallel r_{o3} \right)$$

$$v_o = (i_4 - i_2) r_{o4} = \left[ i_1 g_{m4} \left( \frac{1}{g_{m3}} \parallel r_{o3} \right) - i_2 \right] r_{o4}$$

$$A_{cm} \equiv \frac{v_o}{v_{icm}} = -\frac{1}{2R_{SS}} \frac{r_{o4}}{1 + g_{m3} r_{o3}} \approx -\frac{1}{2g_{m3} R_{SS}}$$



$$CMRR \equiv \frac{|A_d|}{|A_{cm}|} = [g_m (r_{o2} \parallel r_{o4})] [2g_{m3} R_{SS}]$$

$$CMRR = (g_m r_o) (g_m R_{SS})$$

- The active-loaded MOS differential amplifier has a low  $A_{cm}$  and a high CMRR.
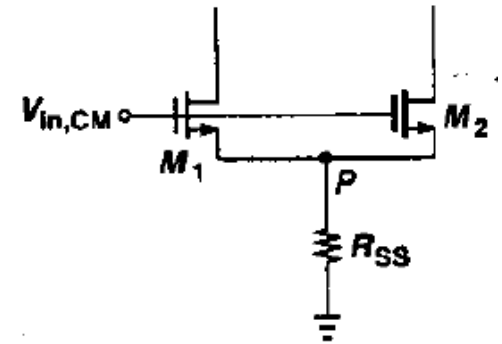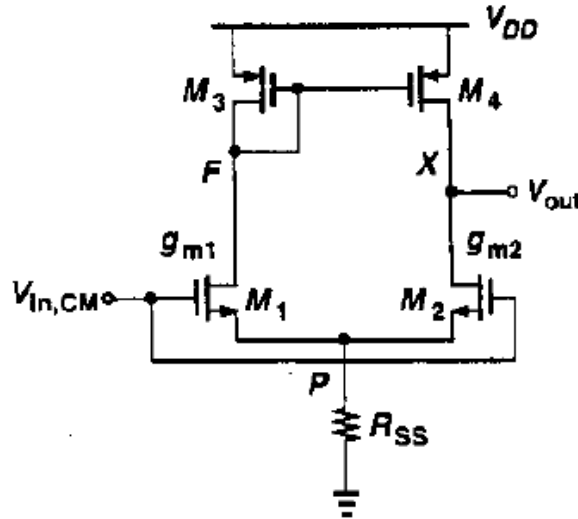
# Differential Pair with $g_m$ Mismatch

- Voltage change at  $P$  can be obtained by considering  $M_1$  and  $M_2$  as a single transistor in a SF configuration.



$$\Delta V_P = \Delta V_{in,CM} \frac{R_{SS}}{R_{SS} + \frac{1}{g_{m1} + g_{m2}}}$$

$$\Delta I_{D1} = g_{m1} (\Delta V_{in,CM} - \Delta V_P) = \frac{\Delta V_{in,CM}}{R_{SS} + \frac{1}{g_{m1} + g_{m2}}} \frac{g_{m1}}{g_{m1} + g_{m2}}, \quad \Delta I_{D2} = g_{m2} (\Delta V_{in,CM} - \Delta V_P) = \frac{\Delta V_{in,CM}}{R_{SS} + \frac{1}{g_{m1} + g_{m2}}} \frac{g_{m2}}{g_{m1} + g_{m2}}$$

$$\Delta I_{D4} = \Delta I_{D1} \left( \frac{1}{g_{m3}} \parallel r_{O3} \right) g_{m4}, \quad \Delta V_{out} = [\Delta I_{D4} - \Delta I_{D2}] r_{O4} = \left[ \frac{g_{m1} \Delta V_{in,CM}}{1 + (g_{m1} + g_{m2}) R_{SS}} \frac{r_{O3}}{r_{O3} + \frac{1}{g_{m3}}} - \frac{g_{m2} \Delta V_{in,CM}}{1 + (g_{m1} + g_{m2}) R_{SS}} \right] r_{O4}$$

$$\Delta V_{out} = \frac{\Delta V_{in,CM}}{1 + (g_{m1} + g_{m2}) R_{SS}} \frac{(g_{m1} - g_{m2}) r_{O3} - g_{m2} / g_{m3}}{r_{O3} + \frac{1}{g_{m3}}} r_{O4}, \quad \frac{\Delta V_{out}}{\Delta V_{in,CM}} \approx \frac{(g_{m1} - g_{m2}) r_{O3} - g_{m2} / g_{m3}}{1 + (g_{m1} + g_{m2}) R_{SS}}$$