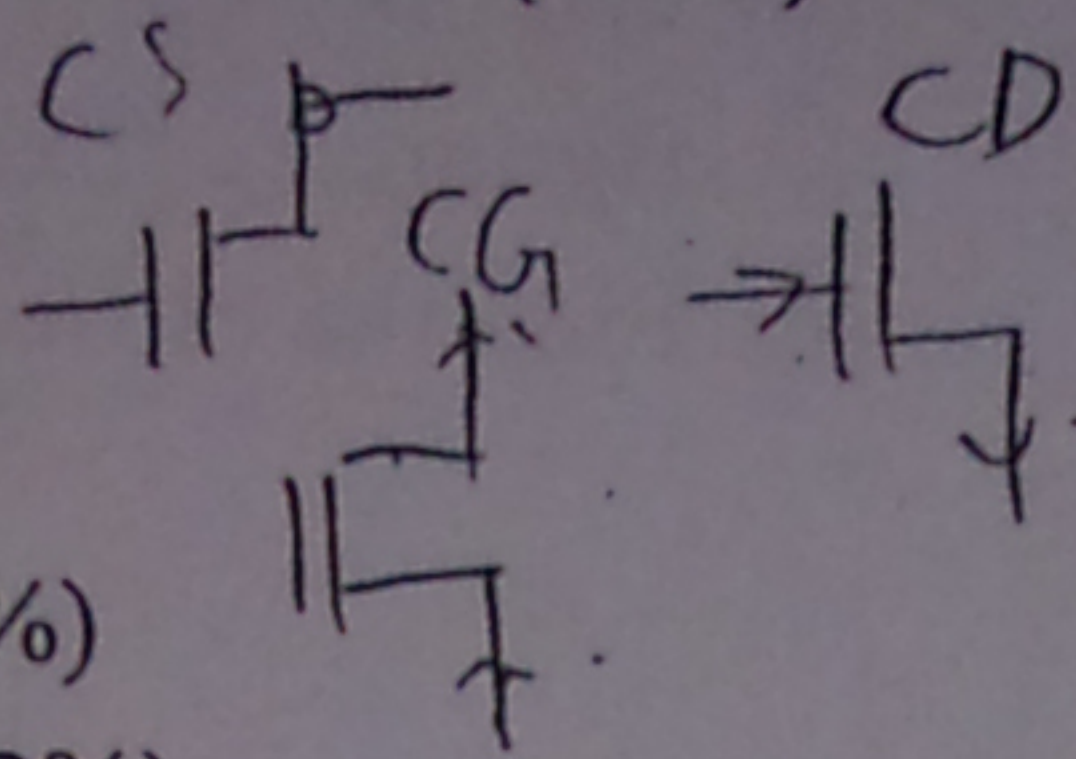


1. Assume the 4 types of single stage amplifiers (CS, CG, and CD) use same MOS, bias at same current, having same R_{load} , C_{load} , and are driven by same source resistance R_s . Please make the ranking based on following parameters (10%)

- (a) DC voltage gain. (2%)
- (b) Input capacitance. (2%)
- (c) Output resistance. (2%)
- (d) Input pole frequency. (2%)
- (e) Output pole frequency. (2%)



2. A common source amplifier is shown in Fig. 2 with the MOSFET bias of g_m and $r_o = \infty$. (4%)

- (a) Use Miller effect to find the equivalent C_{in} at node X and C_{out} at node V_{out} . (2%)
- (b) Find the correlated input pole ω_{in} and output pole ω_{out} . (2%)

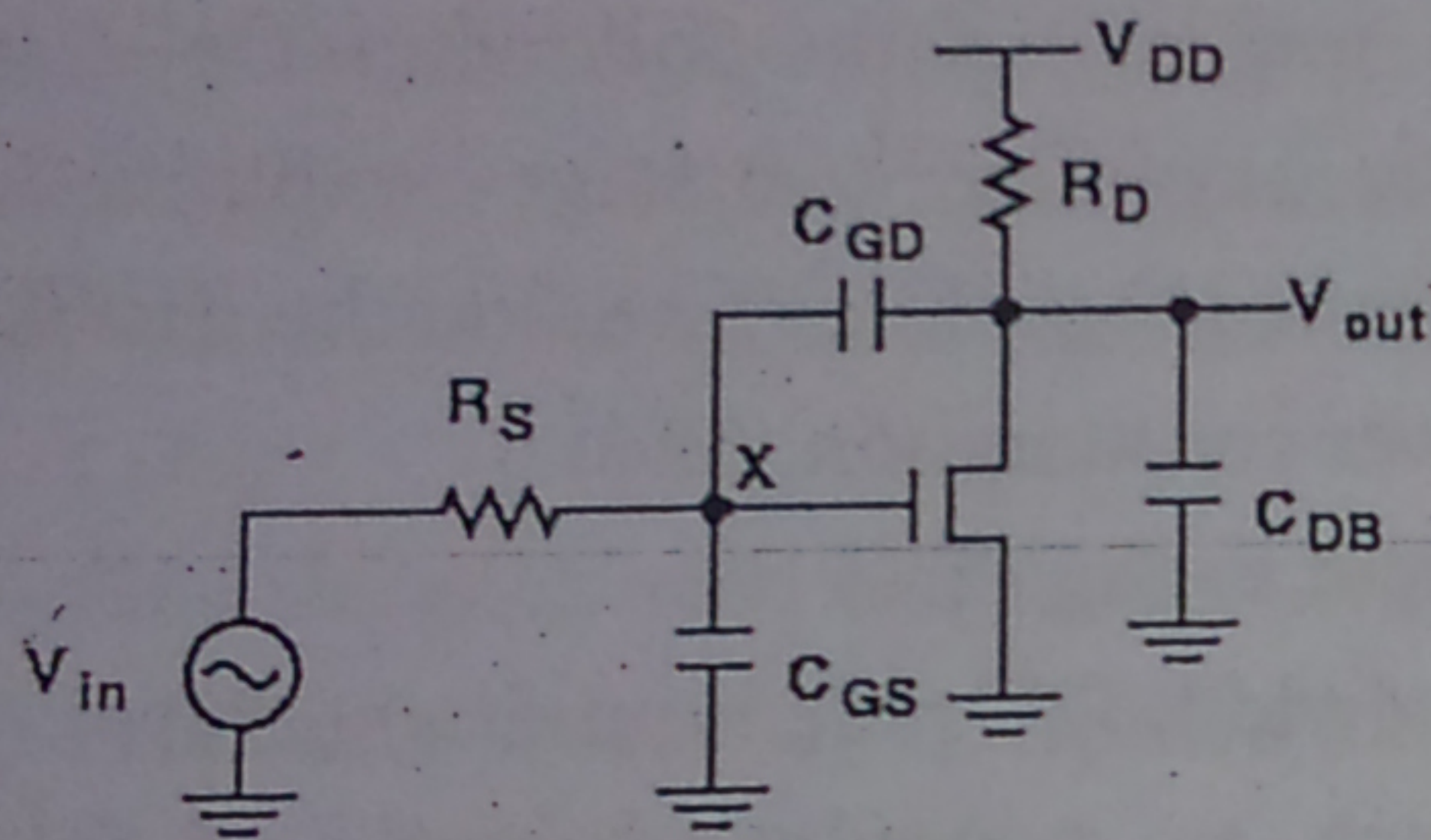


Fig. 2

3. A differential pair with capacitance loading is shown in Fig. 3 (6%)

- (a) Find the node of dominant pole and express it in terms of r_{ox} and C_x . (2%)
- (b) Find the node of second pole and express it in terms of g_{mx} and C_x . (2%)
- (c) Find the zero and express it in terms of g_{mx} and C_x . (2%)

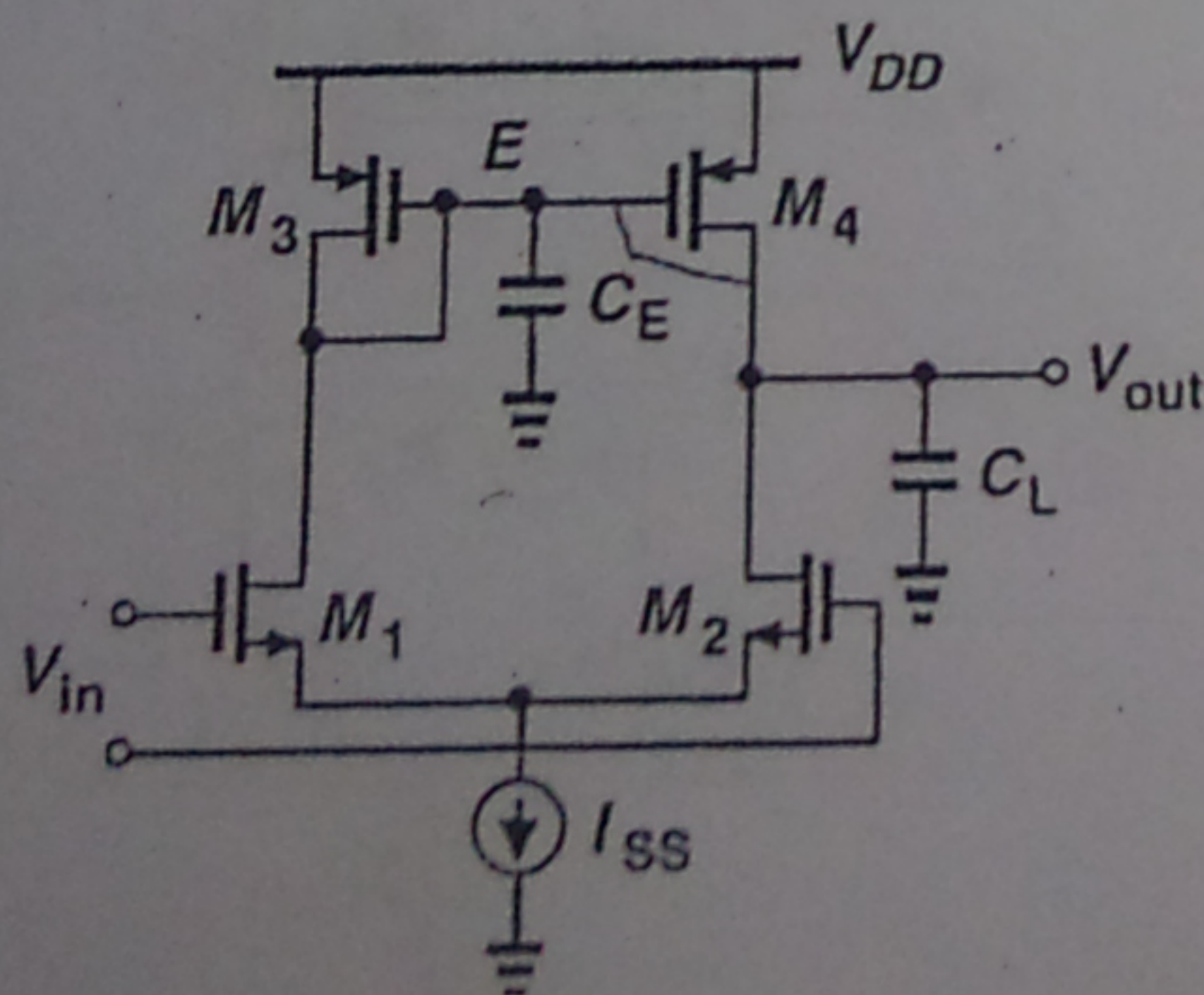


Fig. 3

- 4. Explain the following terminologies (10%)
 - (a) Power Spectrum (Spectral) Density. (2%)
 - (b) White Noise. (2%)
 - (c) Corner Frequency. (2%)
 - (d) 1/f Noise. (2%)
 - (e) Input-referred noise. (2%)

5. A common source amplifier is shown in Fig. 5. The thermal noise of $R_D = 4kTR_D$. The thermal noise and flicker noise of M_1 are $\overline{I_n^2} = 4kTg_m(\frac{2}{3})$ and $\overline{V_n^2} = \frac{K}{C_{ox}WL} \cdot \frac{1}{f}$. (10%)

- (a) Derive the input referred noise $\overline{V_{n,in}^2}$ due to thermal noise. (5%)
- (b) Derive the input referred noise $\overline{V_{n,in}^2}$ due to flicker noise. (5%)

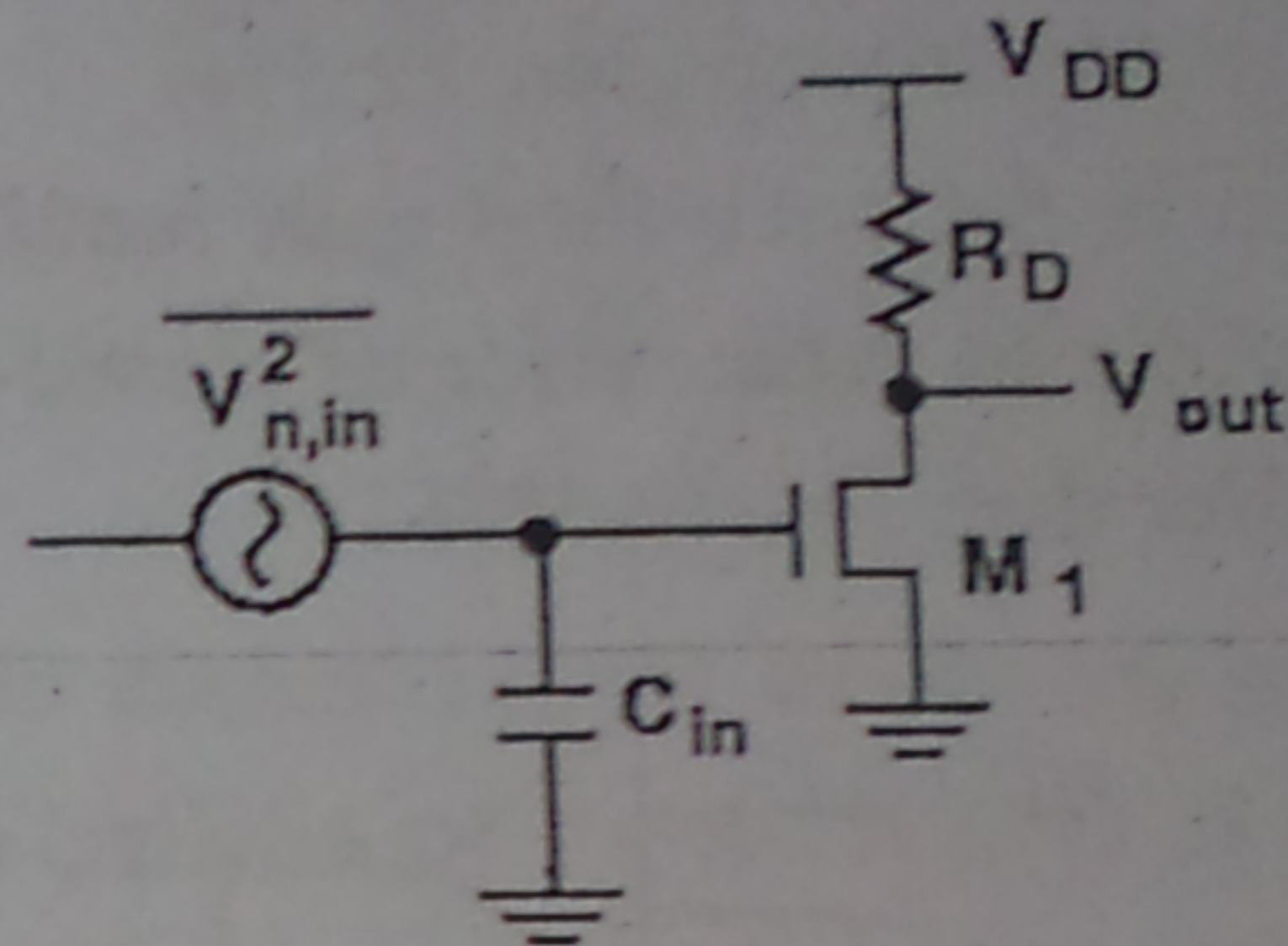


Fig. 5

6. Explain the definitions and purposes of the following terminologies. (10%)

- (a) Common mode feedback. (2%)
- (b) Frequency compensation. (2%)
- (c) Barkhausen's Criteria. (2%)
- (d) Slewing in an Op Amp. (2%)
- (e) Phase margin. (2%)

7. A general block diagram of feedback system is shown in Fig. 7. Assume the input and output resistances of feed-forward amplifier are R_{in} and R_{out} . (10%)

- (a) Find the loop gain. (2%)
- (b) Find the closed loop gain. (2%)
- (c) Find the input impedance of closed-loop amplifier. (2%)

- (d) Find the output impedance of closed-loop amplifier. (2%)
- (e) Explain *gain degeneration* of closed-loop system compared to open-loop. (2%)

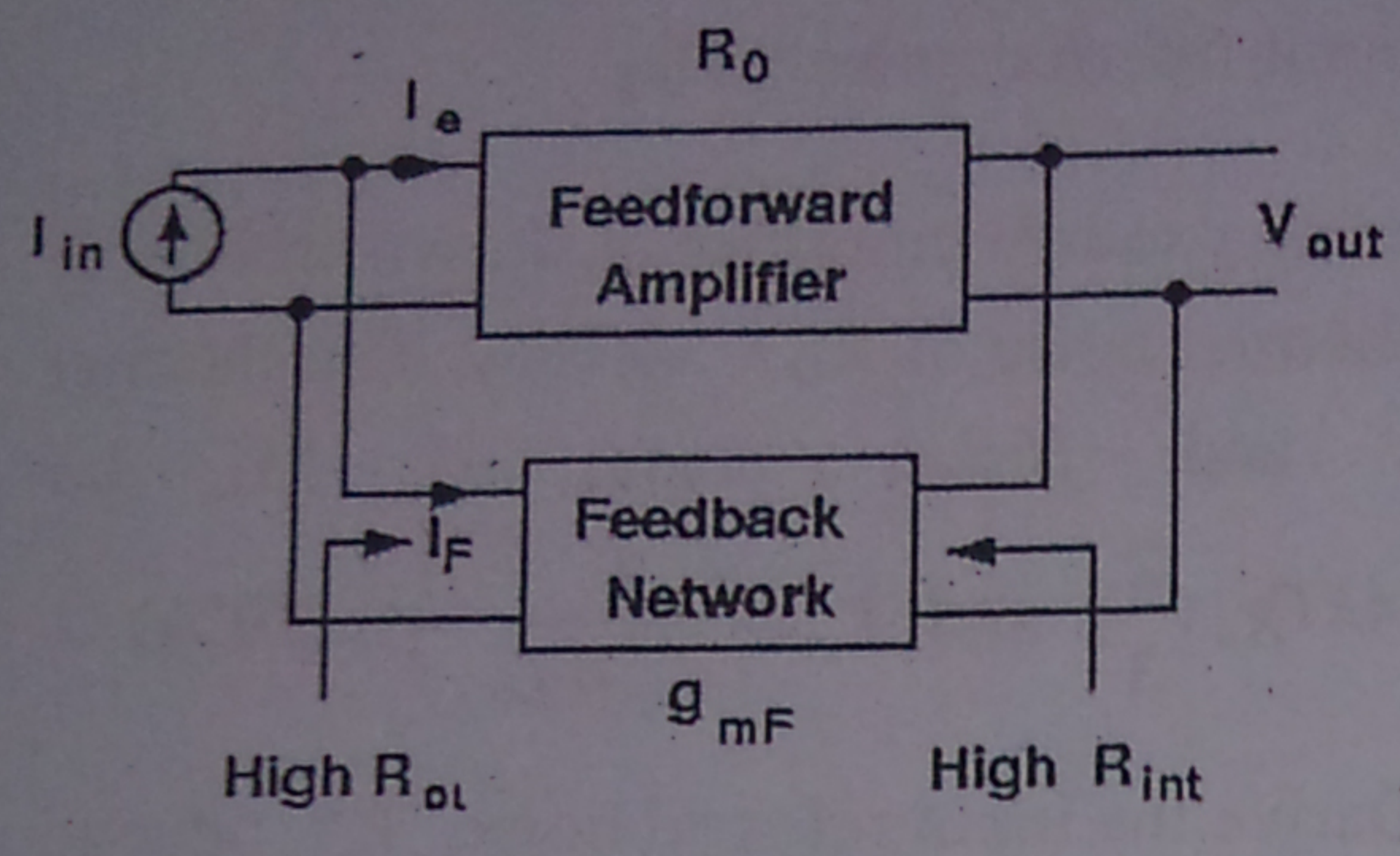


Fig. 7

8. A closed-loop amplifier is shown in Fig. 9 with $R_1 = 900\text{K}\Omega$ and $R_2 = 100\text{K}\Omega$. (5%)

- (a) With the gain of Op Amp = ∞ , find the ideal closed-loop gain. (2.5%)
- (b) What is the open-loop gain requirement of Op Amp to get an error of closed-loop gain smaller than 1%. (2.5%)

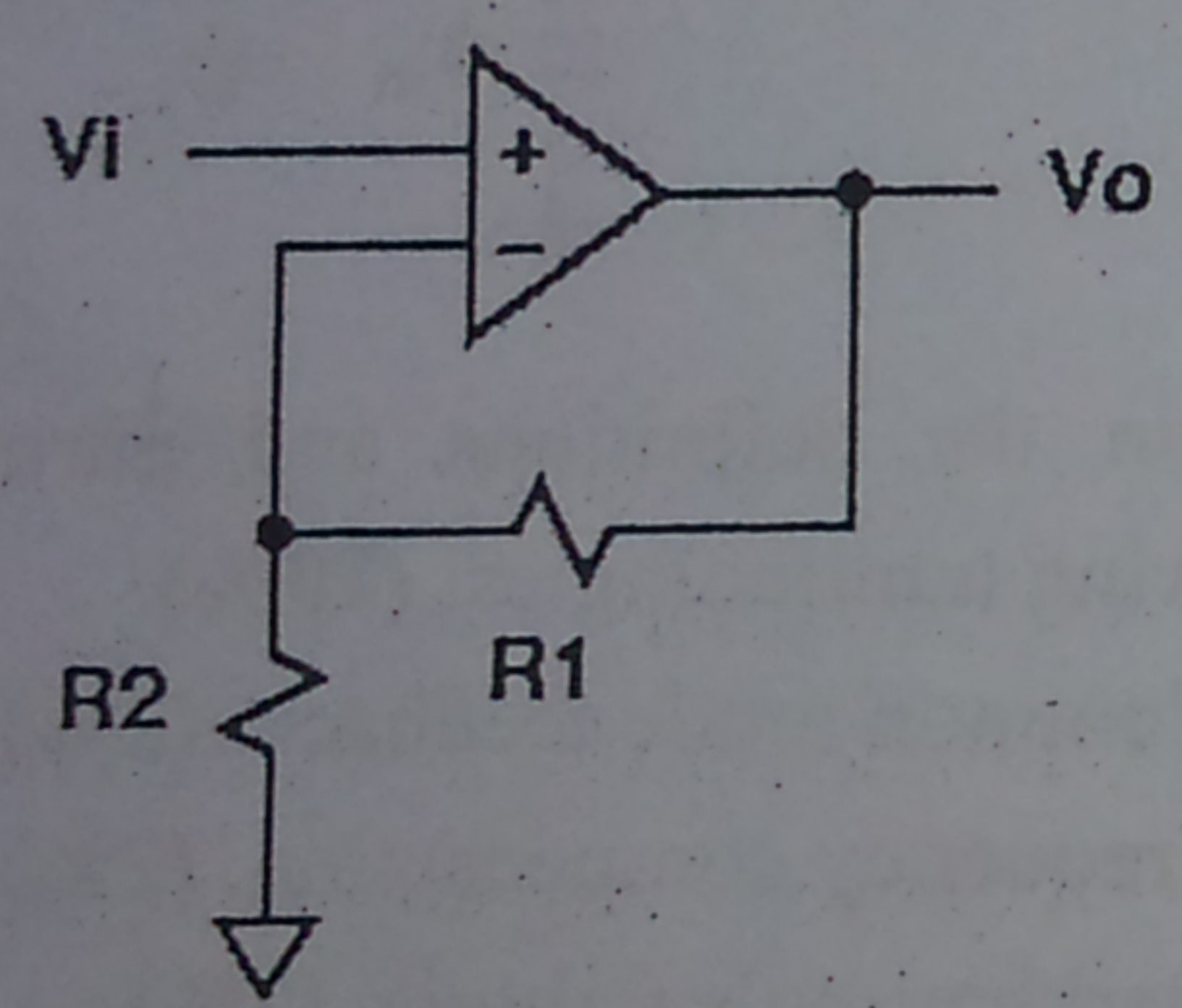


Fig. 8

An impedance boosting circuit is as shown in Fig. 10. Find the R_{out} in term of r_{ox} and g_{mx} . (5%)

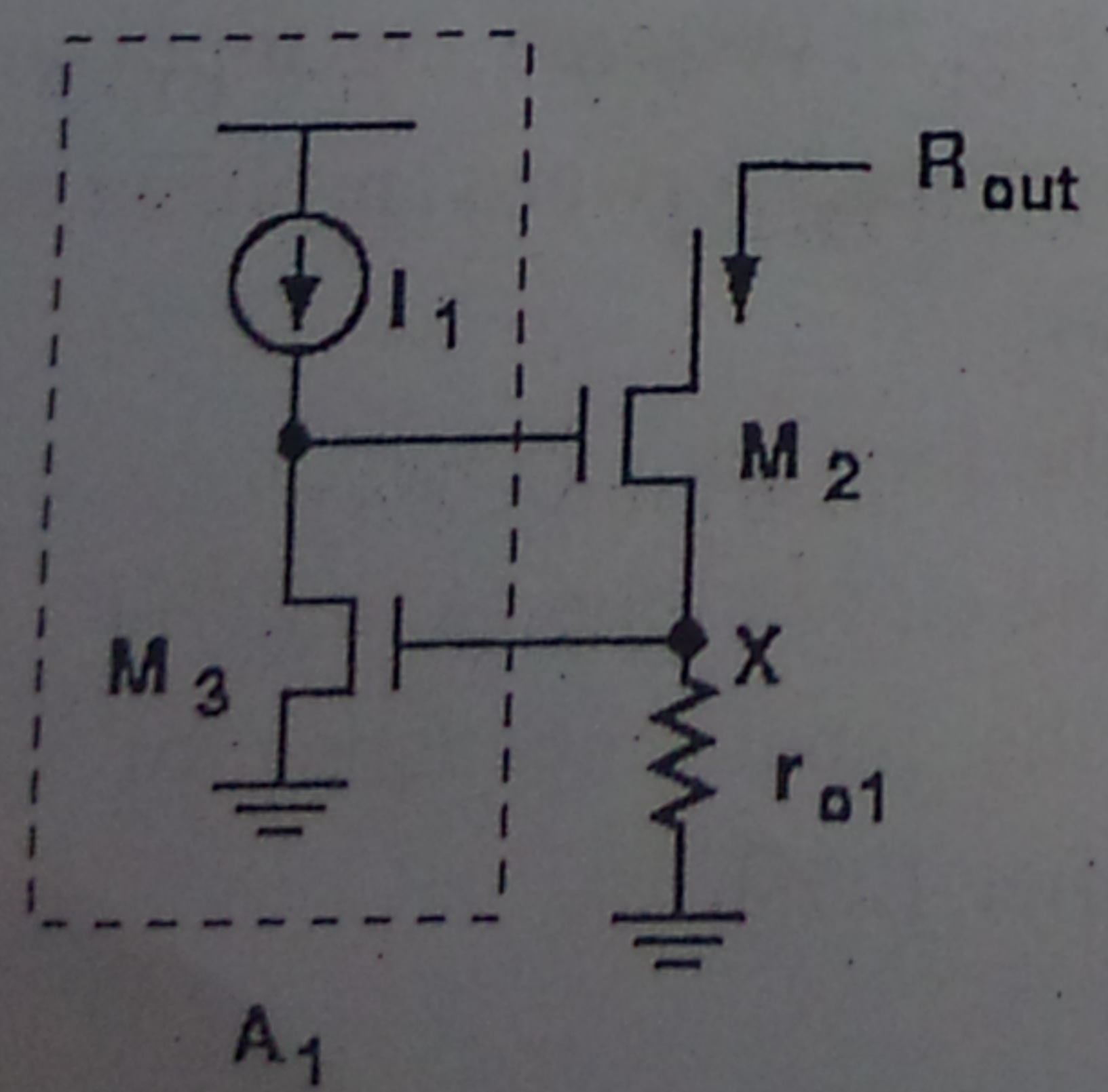


Fig. 9

- 10. A voltage-voltage feedback amplifier as shown in Fig. 11 is biased with g_{m1} of M_1 and g_{m2} of M_2 . (10%)
 - a) Find the feedback factor. (2%)
 - b) Find the open-loop gain with loading effect. (ignore r_o effect) (4%)
 - c) Find the closed-loop gain V_{out}/V_{in} . (4%)

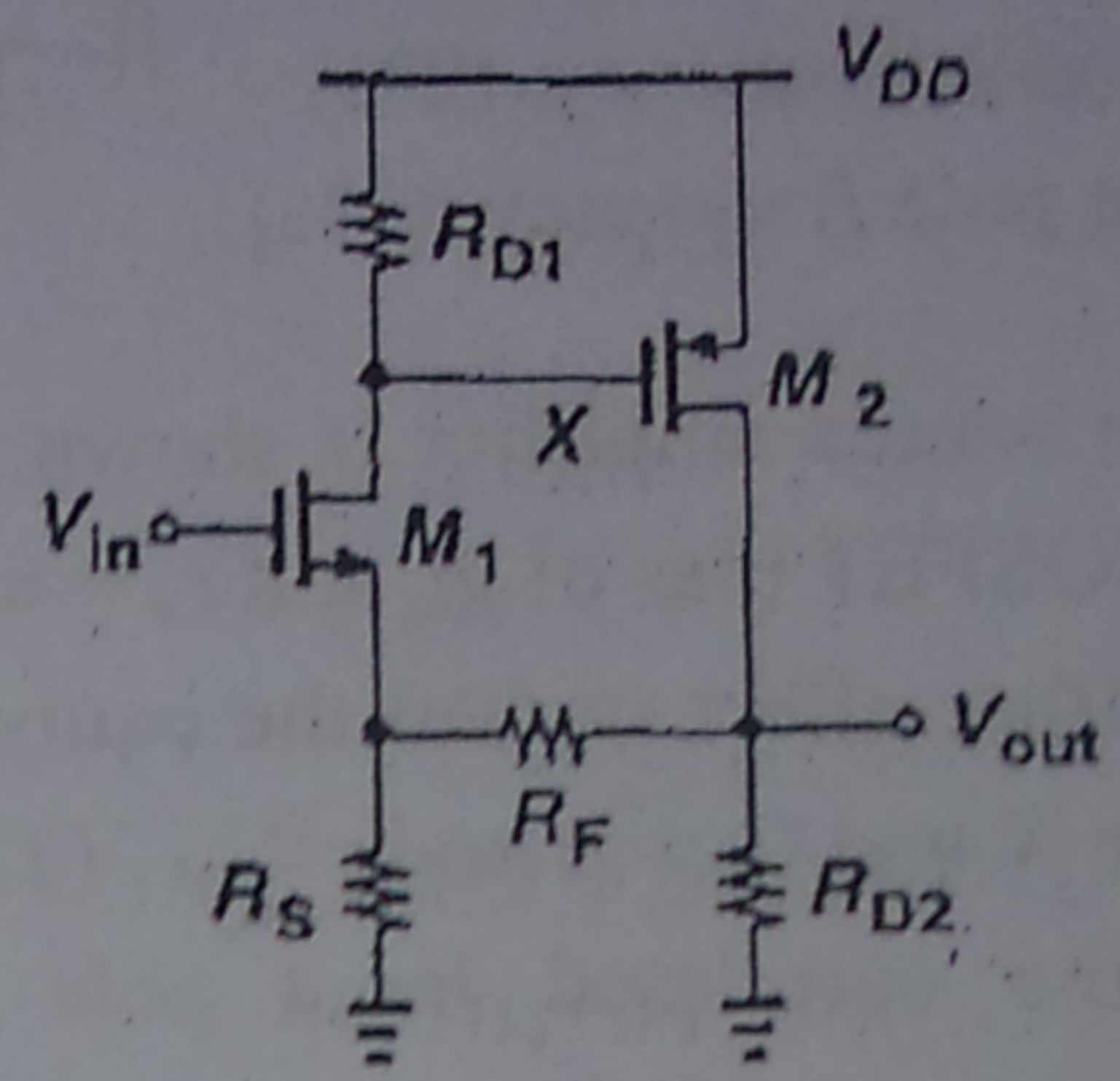


Fig. 10

- 11. Make a ranking of the following Op Amps: telescopic amplifier, two-stage amplifier, and folded-cascode amplifier based on the. (10%)
 - (a) Power consumption. (2%)
 - (b) Output swing (2%)
 - (c) Bandwidth (2nd pole locations) (2%)
 - (d) Sketch an example schematic of folded-cascode amp. (2%)
 - (e) Sketch an example schematic of gain-booster telescopic amp. (2%)

12. Sketch a common-mode feedback circuit for the telescopic Op Amp is shown in Fig. 12. (5%)

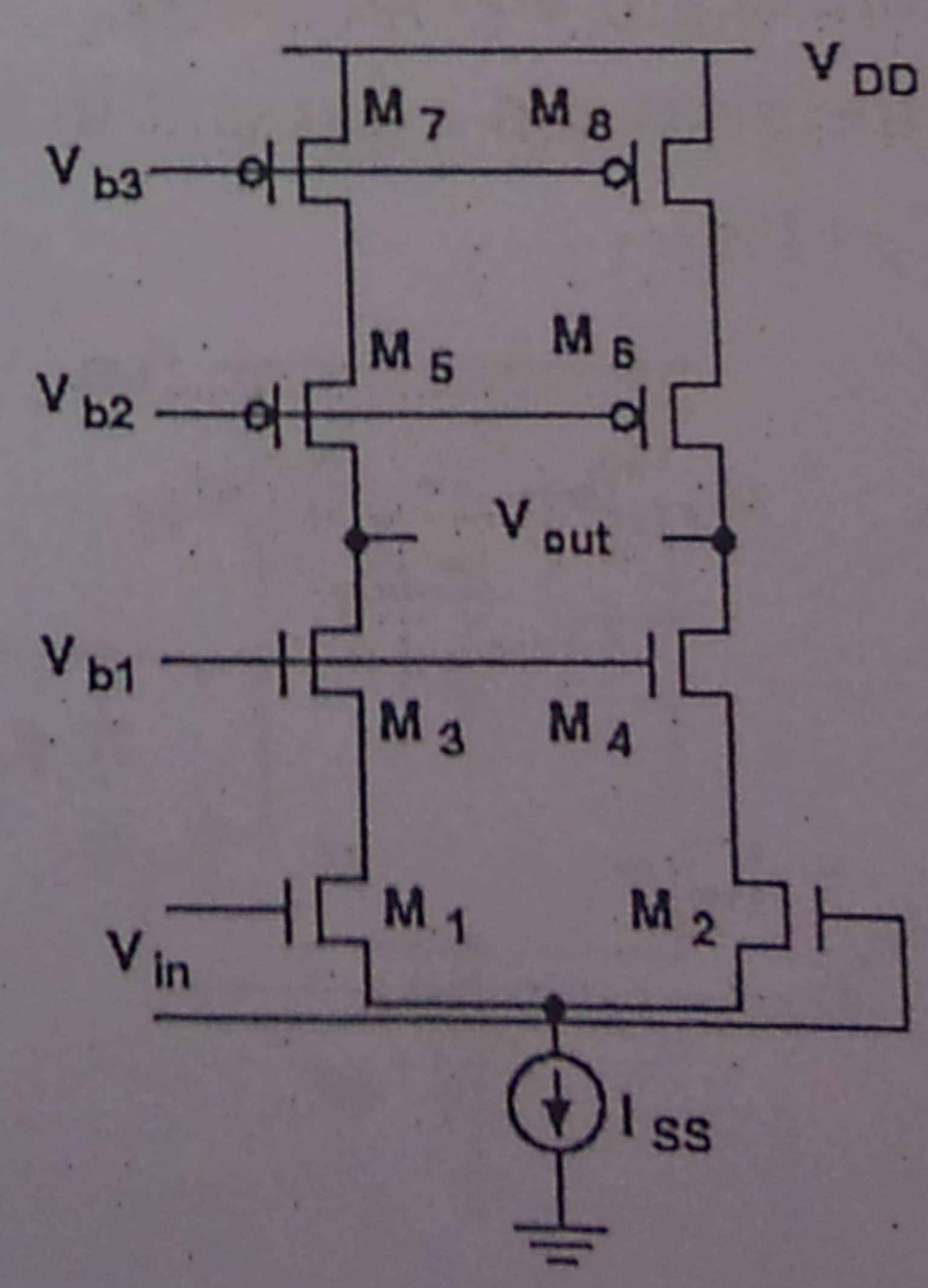


Fig. 12

13. A unity-gain voltage buffer implemented by telescopic Op Amp with $V_{TH} = 0.5V$, $V_{GSx} = 0.7V$, and $V_{ISS} = 0.3V$ is shown in Fig. 13. (4%)

- (a) Find the minimum output voltage. (2%)
- (b) Find the maximum output voltage. (2%)

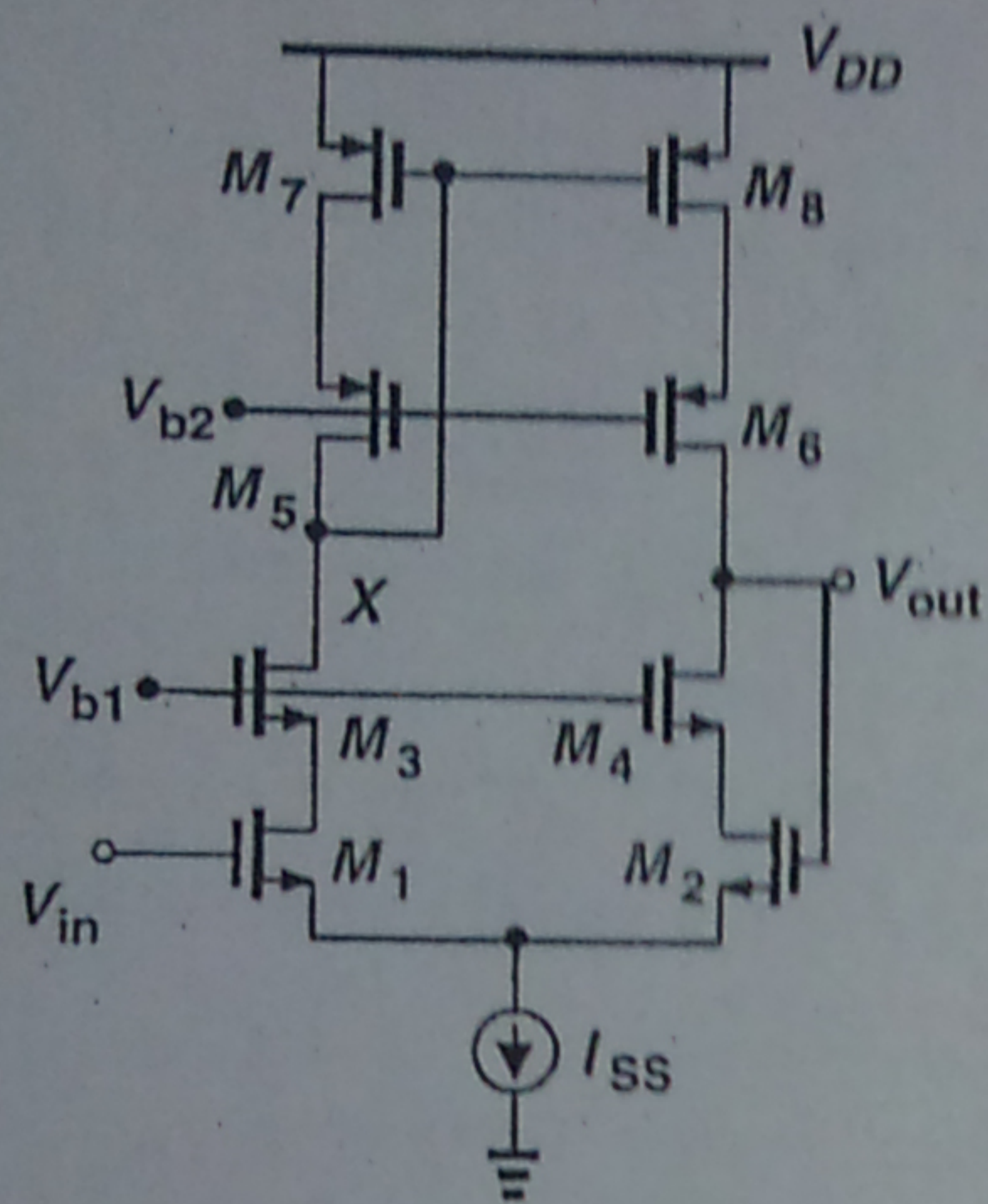


Fig. 13

14. Assume an Op Amp with DC-gain = 80dB, pole1 = 10Mhz, and pole2 = 1000Mhz. (6%)

- (a) Sketch the Bode-Plot (amplitude & phase). (2%)
- (b) Find the unity-gain frequency. (2%)
- (c) Propose a frequency compensation method to get a PM=45°. (2%)

15. Find slew rates of the following Op Amps with $I_{SS} = 1\mu A$ and $I_1 = 2\mu A$. (4%)

- (a) Telescopic amplifier with $C_L = 1pF$. (2%)
- (b) 2-stage OP Amp with capacitor $C_C = 0.1pF$. (2%)

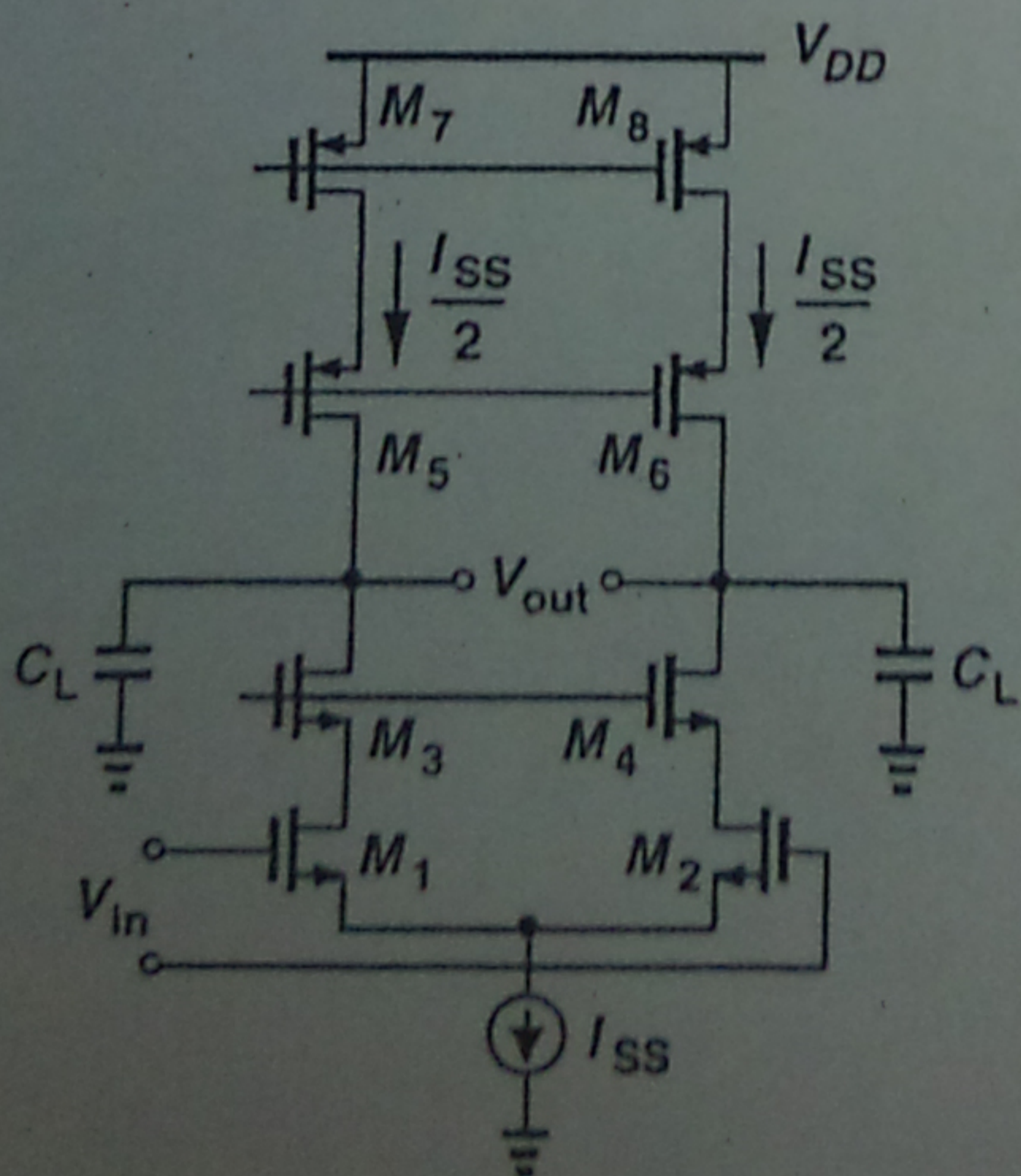


Fig. 15(a)

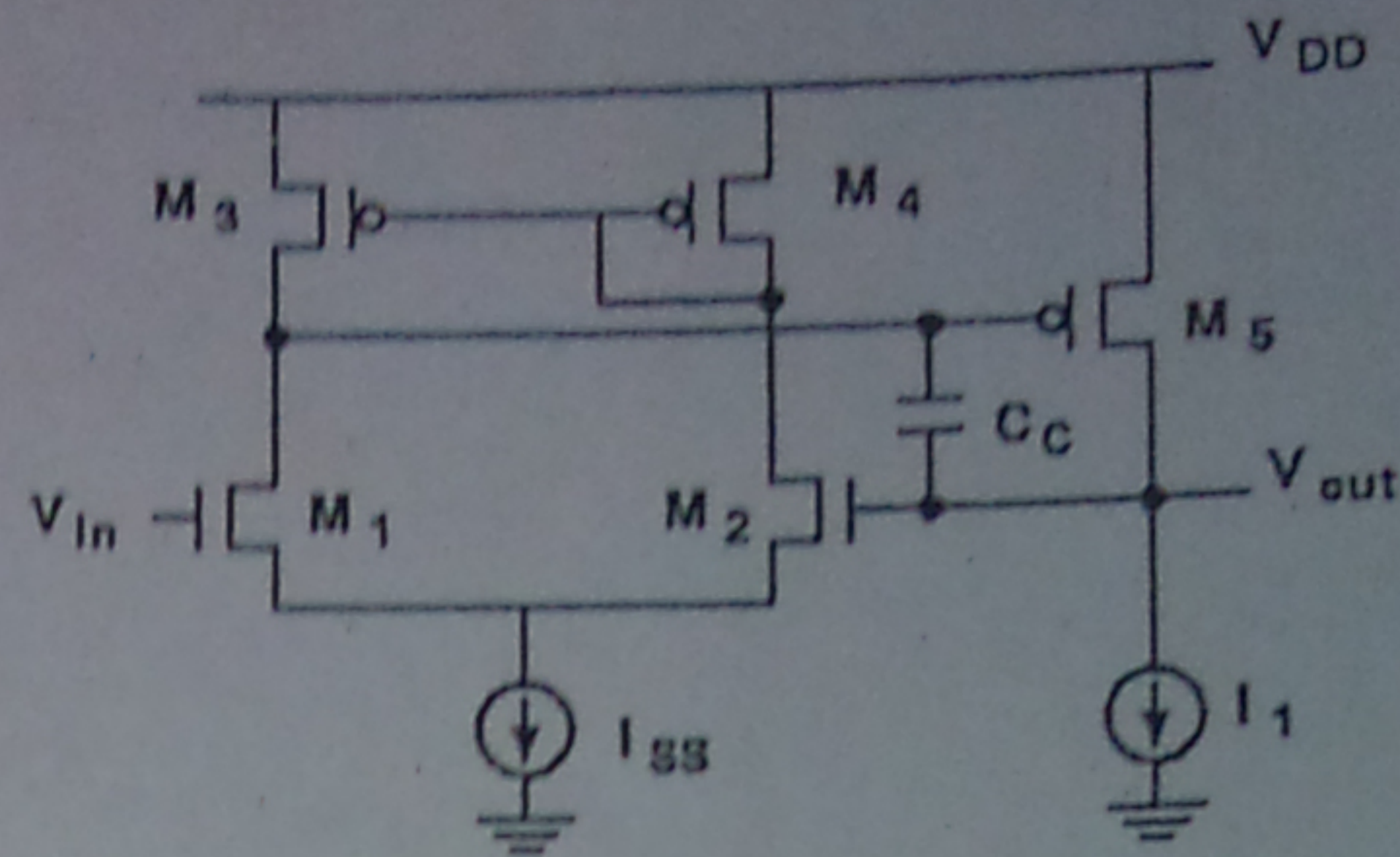


Fig. 15(b)

16. A two-stage Op Amp is shown in Fig. 16 with two low-frequency pole and 0° PM. (4%)

- (a) How to do the frequency compensation by adding C_C . (2%)
- (b) How to solve the right-half-plan zero issue introduced by compensation. (2%)

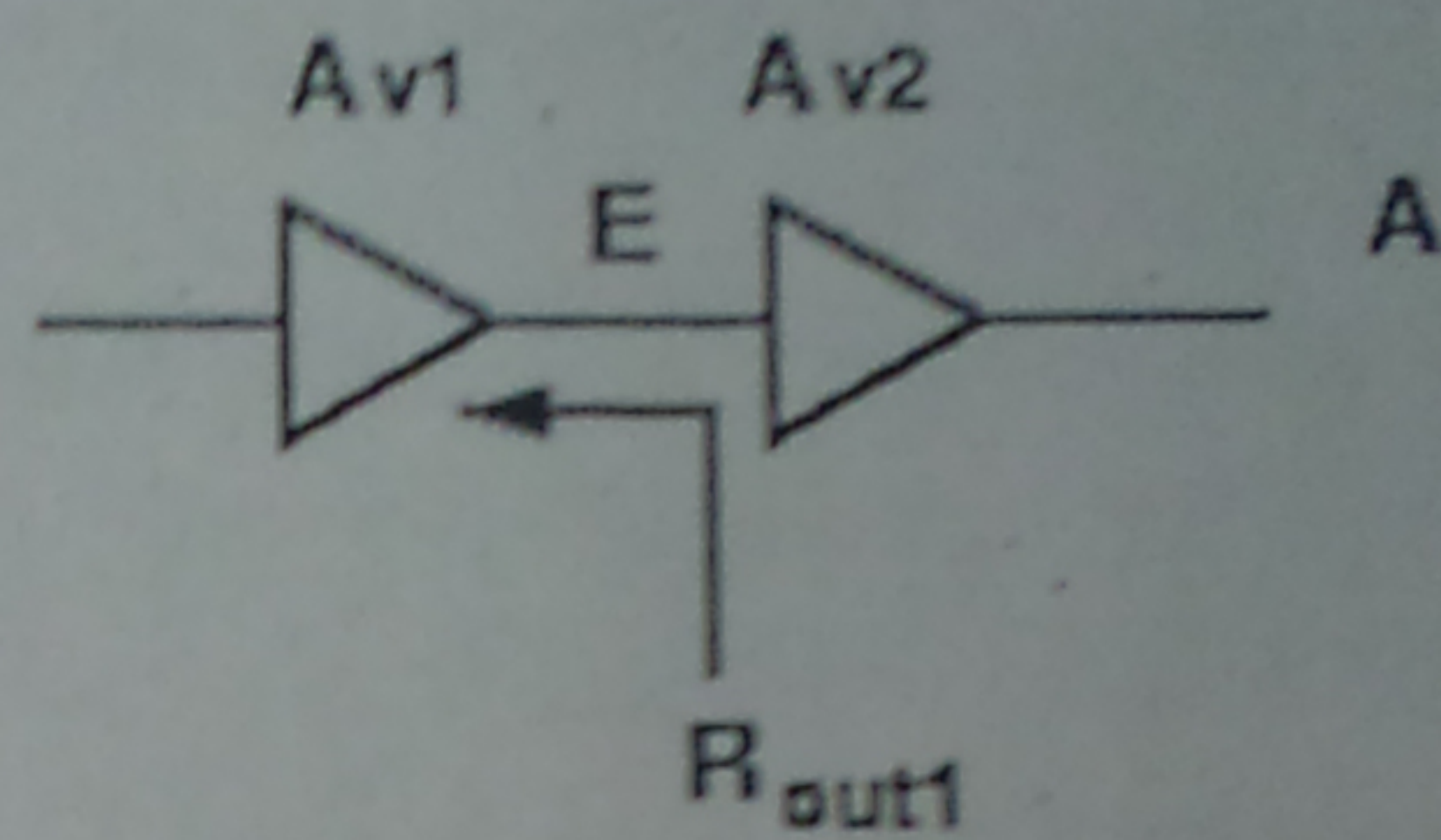


Fig. 16

17. A cascode current mirror as shown in Fig. 12, assume all MOSs are biased with $|V_{ov}| = 200mV$, $|V_{th}| = 0.5V$, $I_{REF} = 10\mu A$, $g_m = 2mA/V$, $r_o = 100k\Omega$, $(W/L)_3/(W/L)_1 = (W/L)_4/(W/L)_2 = 4$, and $V_{DD} = 1.8V$. (4%)

- (a) Find the minimum V_b and related output voltage V_{out} for correct current mirror operation. (2%)
- (b) Find the output resistance R_{out} . (2%)

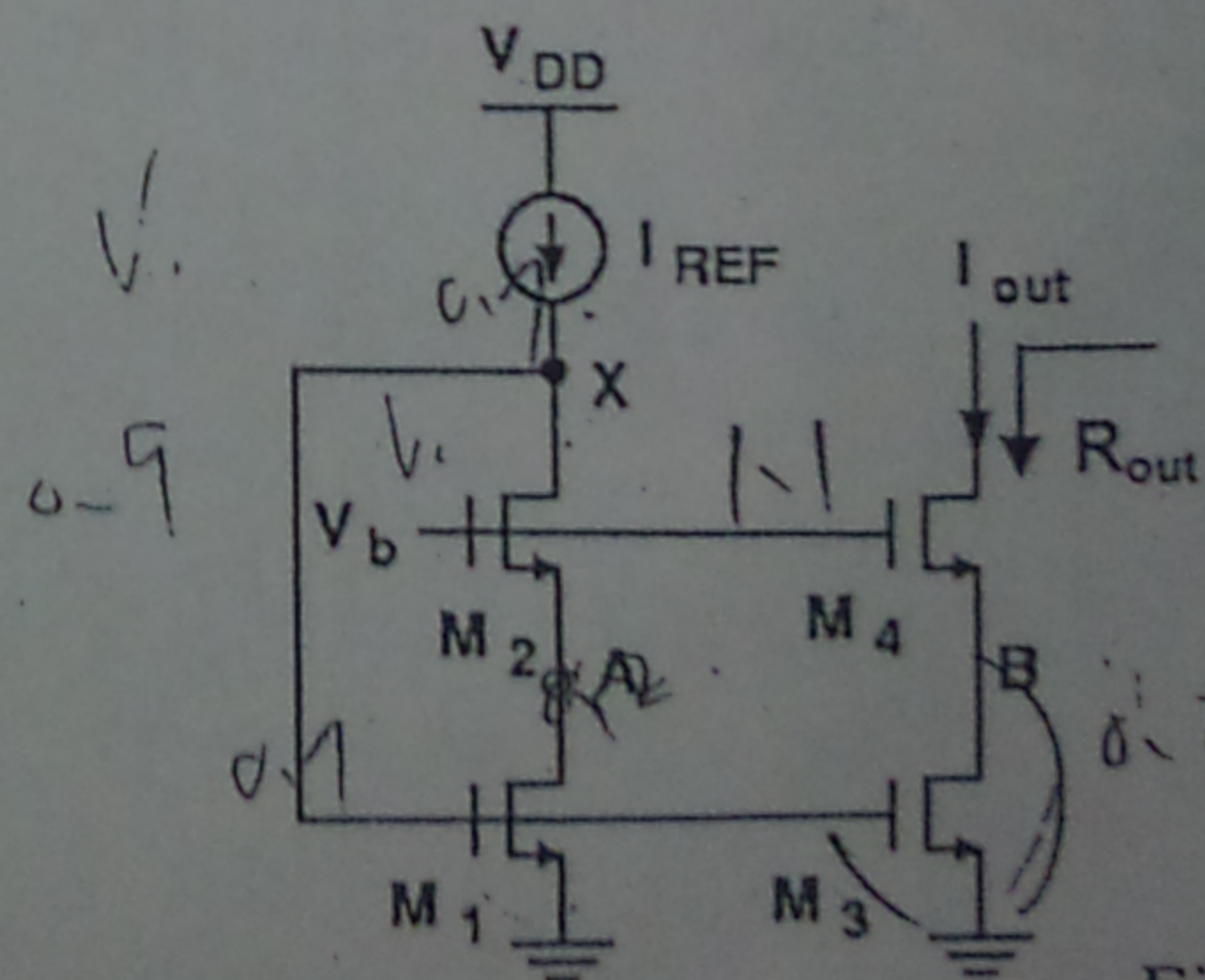


Fig. 12

18. Assume $r_o = \infty$, $g_{mb} \neq 0$ in the circuit of Fig.

19. (4%)

(a) Sketch the small-signal equivalent circuit. (2%)

(2%)

(b) Find the voltage gain V_{out}/V_{in} . (2%)

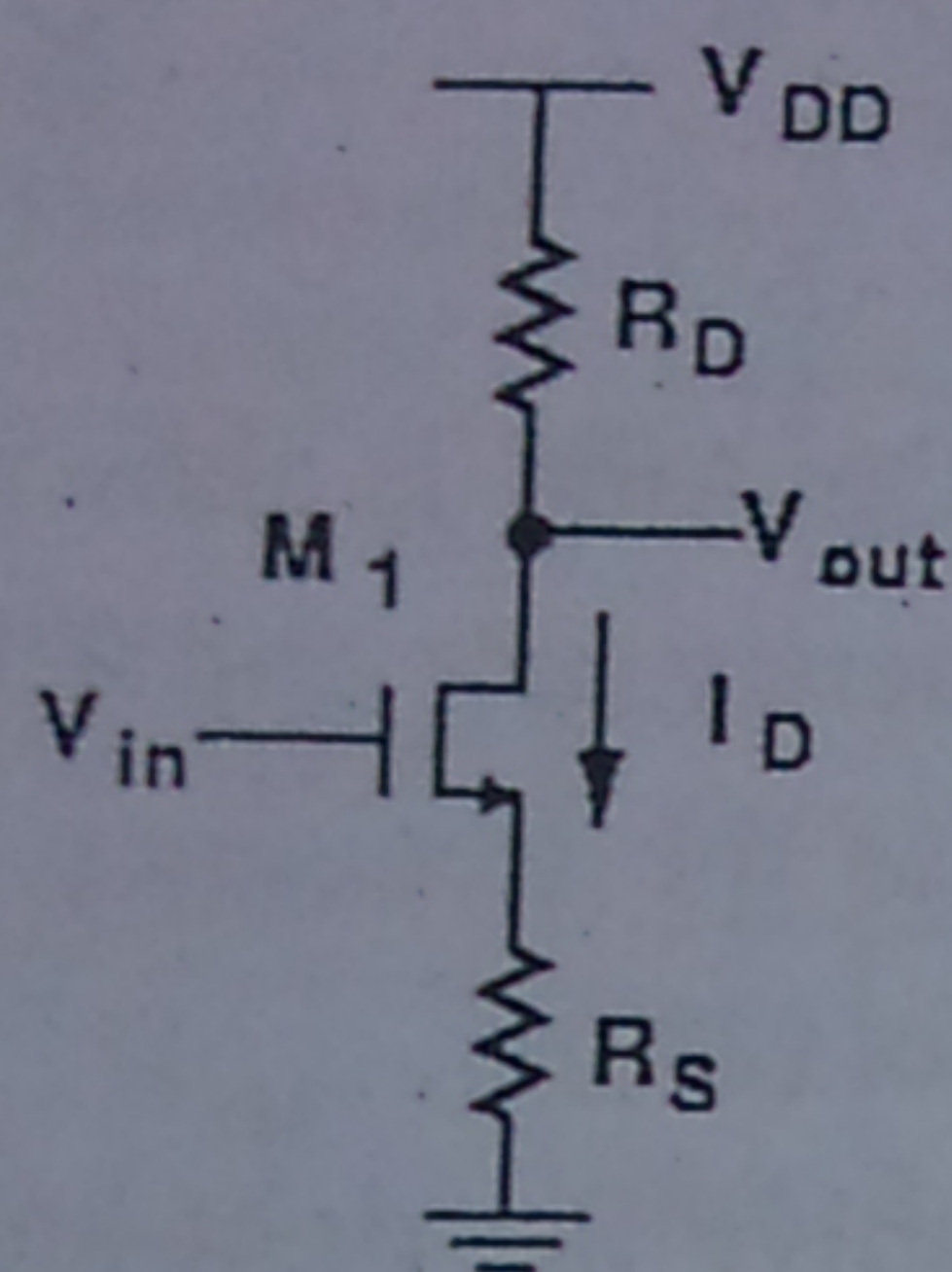


Fig. 19

19. Answer the following questions with TRUE or FALSE: (9%)

(a) The voltage gain of source follower is independent of body effect. (1%)

(b) Common gate amplifier is commonly used as current buffer due to its low input impedance. (1%)

(c) Junction capacitance is proportional to area and reverse-bias. (1%)

(d) The depletion width of p/n ratio (W_p/W_n) in diode is correlated to doping concentration (N_A/N_D) as $W_p/W_n = N_D/N_A$. (1%)

(e) Hot carrier effect is due to the high vertical electrical field of channel. (1%)

(f) The main free carrier in pMOS is hole and from source/drain. (1%)


(g) The channel charge of MOSFET is proportional to $W \cdot L$ and overdrive voltage V_{ov} as well. (1%)

(h) The drain current of nMOS at subthreshold region is exponential proportional to applied V_{gs} . (1%)

(i) For nMOS at saturation region, $C_{GS} > C_{GD}$. (1%)

Reference Material


➤ For current-voltage feedback (Z)

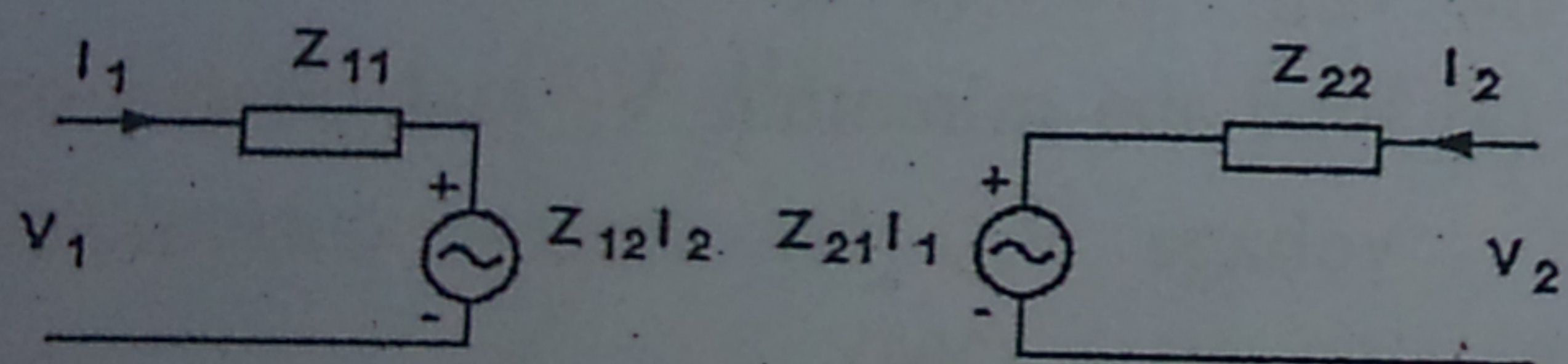

$$V_1 = Z_{11}I_1 + Z_{12}I_2$$

$$V_2 = Z_{21}I_1 + Z_{22}I_2$$


➤ For voltage-current feedback (Y)

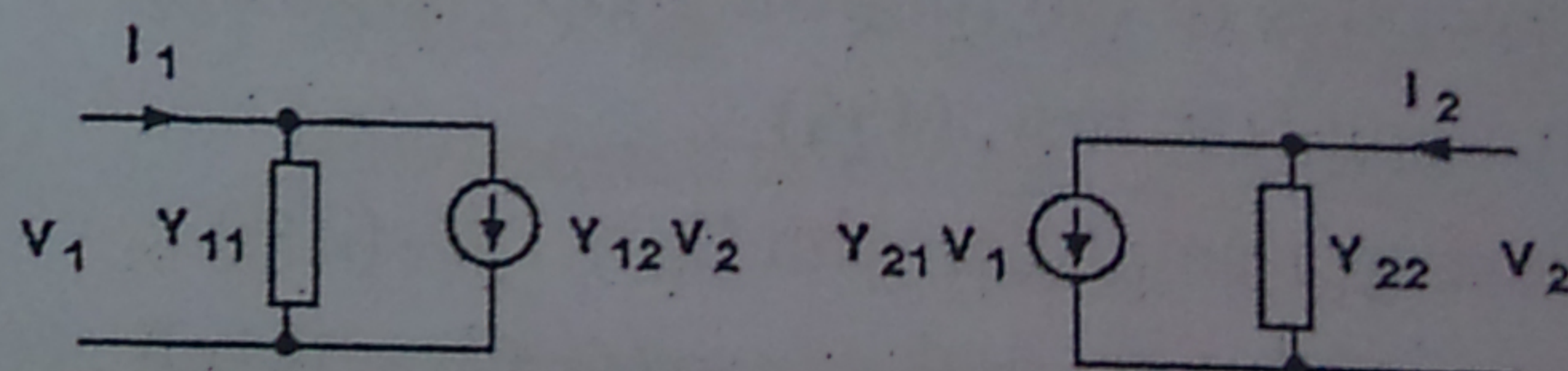

$$I_1 = Y_{11}V_1 + Y_{12}V_2$$

$$I_2 = Y_{21}V_1 + Y_{22}V_2$$


➤ For current-current feedback (H)

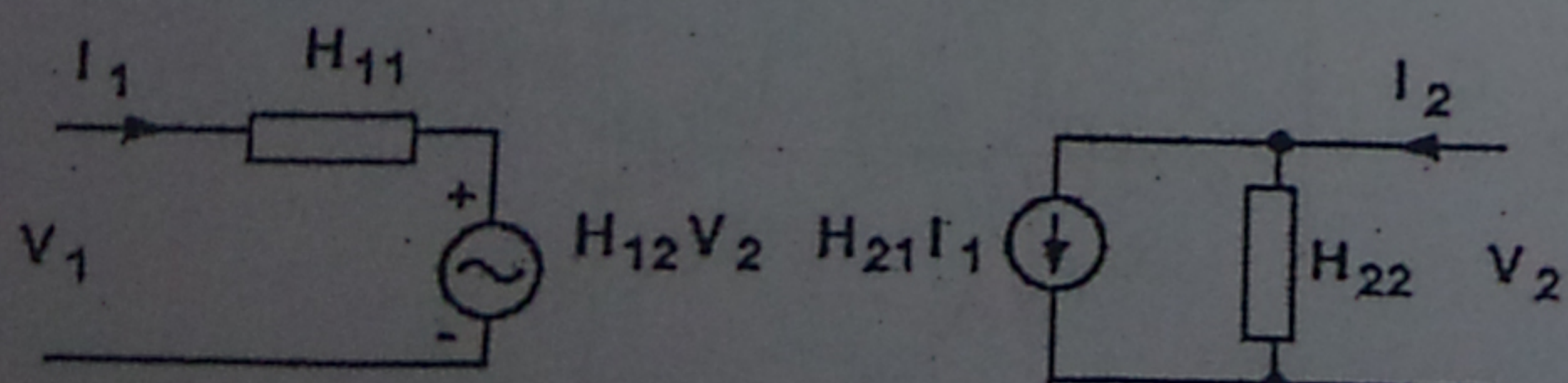

$$V_1 = H_{11}I_1 + H_{12}V_2$$

$$I_2 = H_{21}I_1 + H_{22}V_2$$

➤ For voltage-voltage feedback (G)

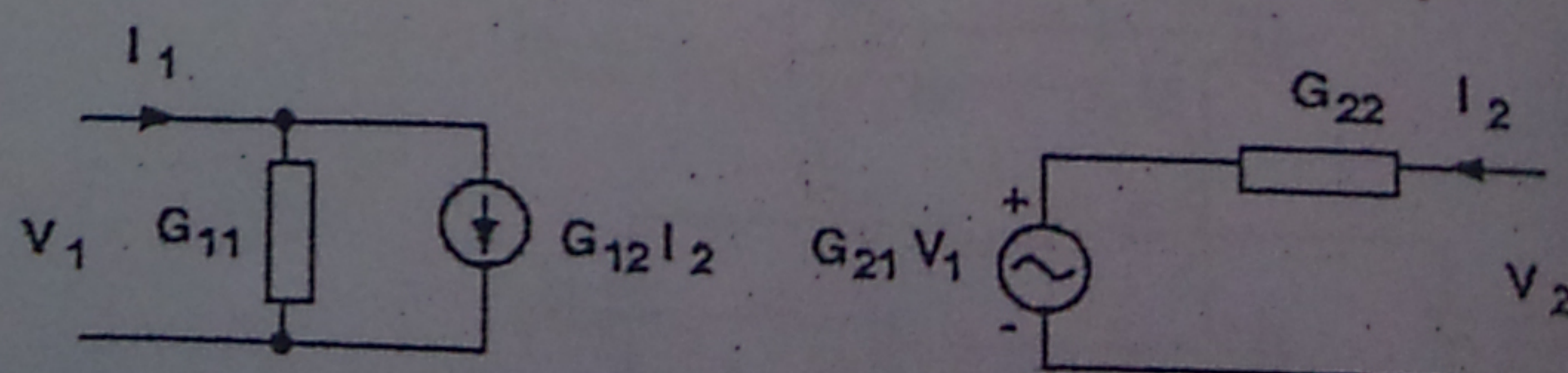

$$I_1 = G_{11}V_1 + G_{12}I_2$$

$$V_2 = G_{21}V_1 + G_{22}I_2$$