 


2013 Analog IC: Final Examination (130%)

1. Derive the equations of Miller effect to express Z_1 and Z_2 in terms of A and Z . (5%)



2. A common source amplifier is shown in Fig. 2 with $g_m = 2\text{mA/V}$, $R_D = R_S = 100\text{k}\Omega$, $C_{GS} = 5\text{fF} = C_{GD} = C_{DB} = 5\text{fF}$, and $r_o = \infty$. (10%)

- (a) Use Miller effect to find the equivalent C_{in} at node X and C_{out} at node V_{out} . (2.5%)
- (b) Find the correlated input pole ω_{in} and output pole ω_{out} . (2.5%)
- (c) Derive and find the zero ω_z . (2.5%)
- (d) Find Z_{in} at high frequency with $Z(C_{GD})=0$. (2.5%)

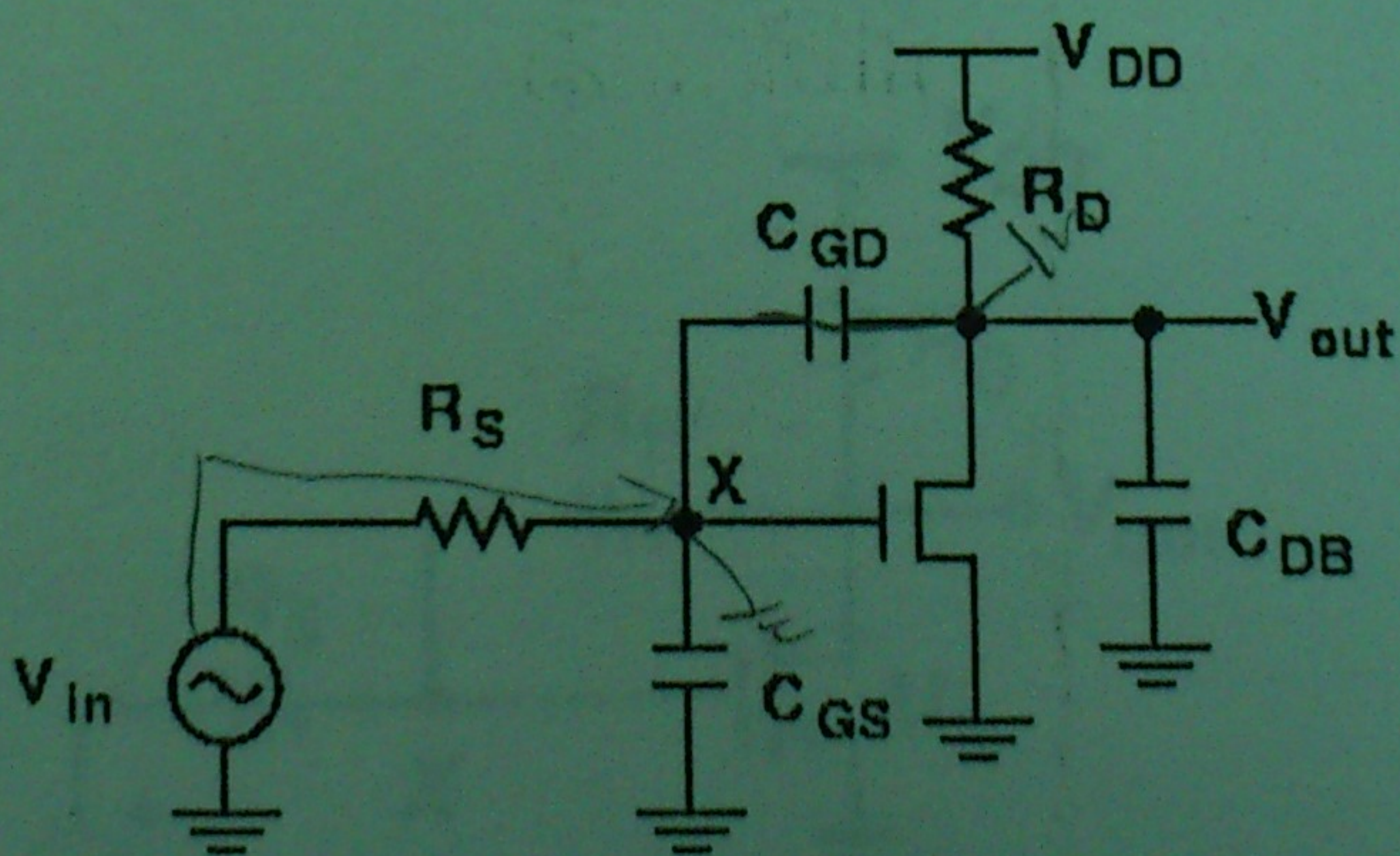


Fig. 2

3. A differential pair with capacitance loading is shown in Fig. 3 with all $g_m = 2\text{mA/V}$, $R_{out} = 50\text{k}\Omega$, $C_E = 20\text{fF}$, $C_L = 100\text{fF}$ and $r_o = \infty$. (10%)

- (a) Find the value of dominant pole ω_{-1} . (2.5%)

- (d) Find Z_{in} at high frequency with $Z(C_{GD})=0$.
(2.5%)

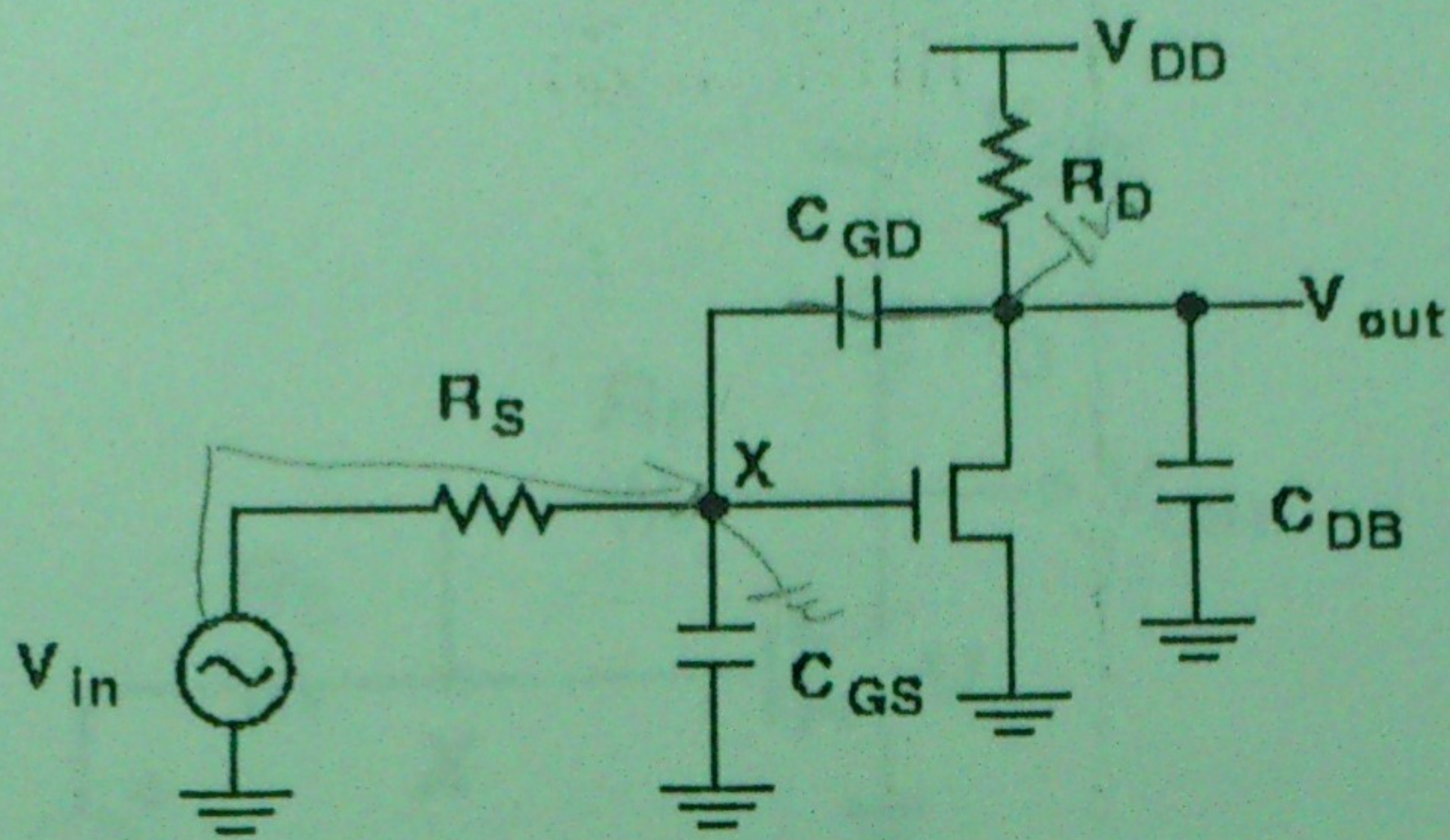


Fig. 2

3. A differential pair with capacitance loading is shown in Fig. 3 with all $g_m = 2\text{mA/V}$, $R_{out} = 50\text{k}\Omega$, $C_E = 20\text{fF}$, $C_L = 100\text{fF}$ and $r_o = \infty$. (10%)
- Find the value of dominant pole ω_{p1} . (2.5%)
 - Find the value of second pole ω_{p2} . (2.5%)
 - Find the value of zero ω_z . (2.5%)
 - Explain the relation of ω_z and ω_{p2} . (2.5%)

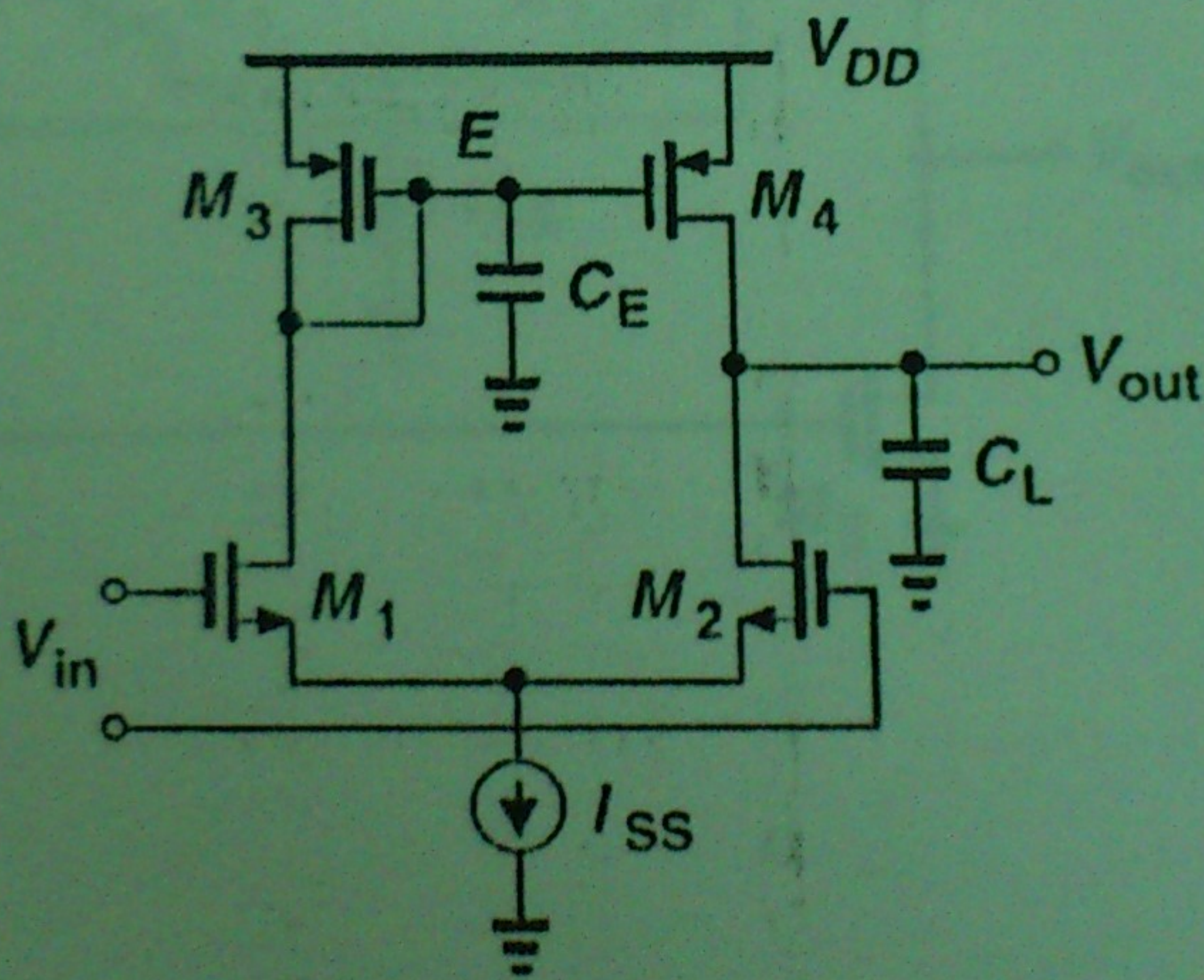


Fig. 3

$$\frac{1}{sC(1+A)}$$

$$Z = \frac{1}{sC}$$

$$Z_{eff} = \frac{1}{sC(1+A)}^{1/4}$$

4. In Fig. 4, M_1 and M_2 are biased with $g_m = 1\text{mA/V}$ and $r_o = 100\text{k}\Omega$. The thermal noise of M_1 (M_2) is $\overline{i_n^2} = 4kTg_m(2/3)$, $4kT = 1.5 \times 10^{-20} \text{V}^2/(\text{Hz} \cdot \Omega)$. (10%)

(a) Find the output referred noise $\overline{v_{n,out}^2}$. (4%)

(b) Find the input referred noise $\overline{v_{n,in}^2}$. (4%)

(c) How to modify g_{m1} and g_{m2} to improve the noise performance? (2%)

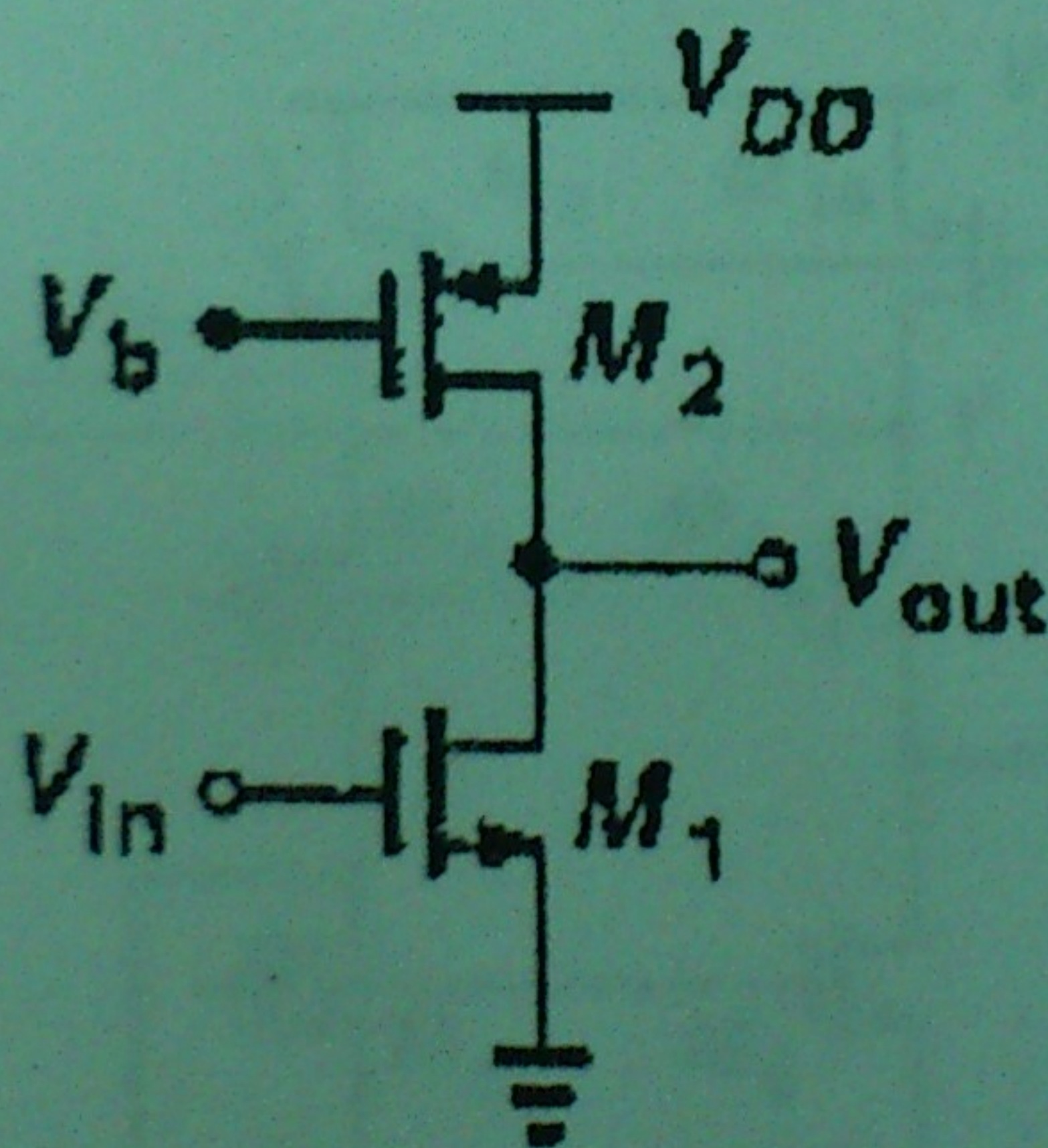


Fig. 4

5. In Fig. 5, the input and output impedance of feed-forward amplifier are R_{in} and R_{out} . (10%)

(a) Find the loop gain. (2%)

(b) Find the closed loop gain. (2%)

(c) Find the input impedance of closed-loop amplifier. (2%)

(d) Find the output impedance of closed loop

5. In Fig. 5, the input and output impedance of feed-forward amplifier are R_{in} and R_{out} . (10%)
- Find the loop gain. (2%)
 - Find the closed loop gain. (2%)
 - Find the input impedance of closed-loop amplifier. (2%)
 - Find the output impedance of closed-loop amplifier. (2%)
 - Explain *bandwidth modification* of closed loop system compared to open loop. (2%)

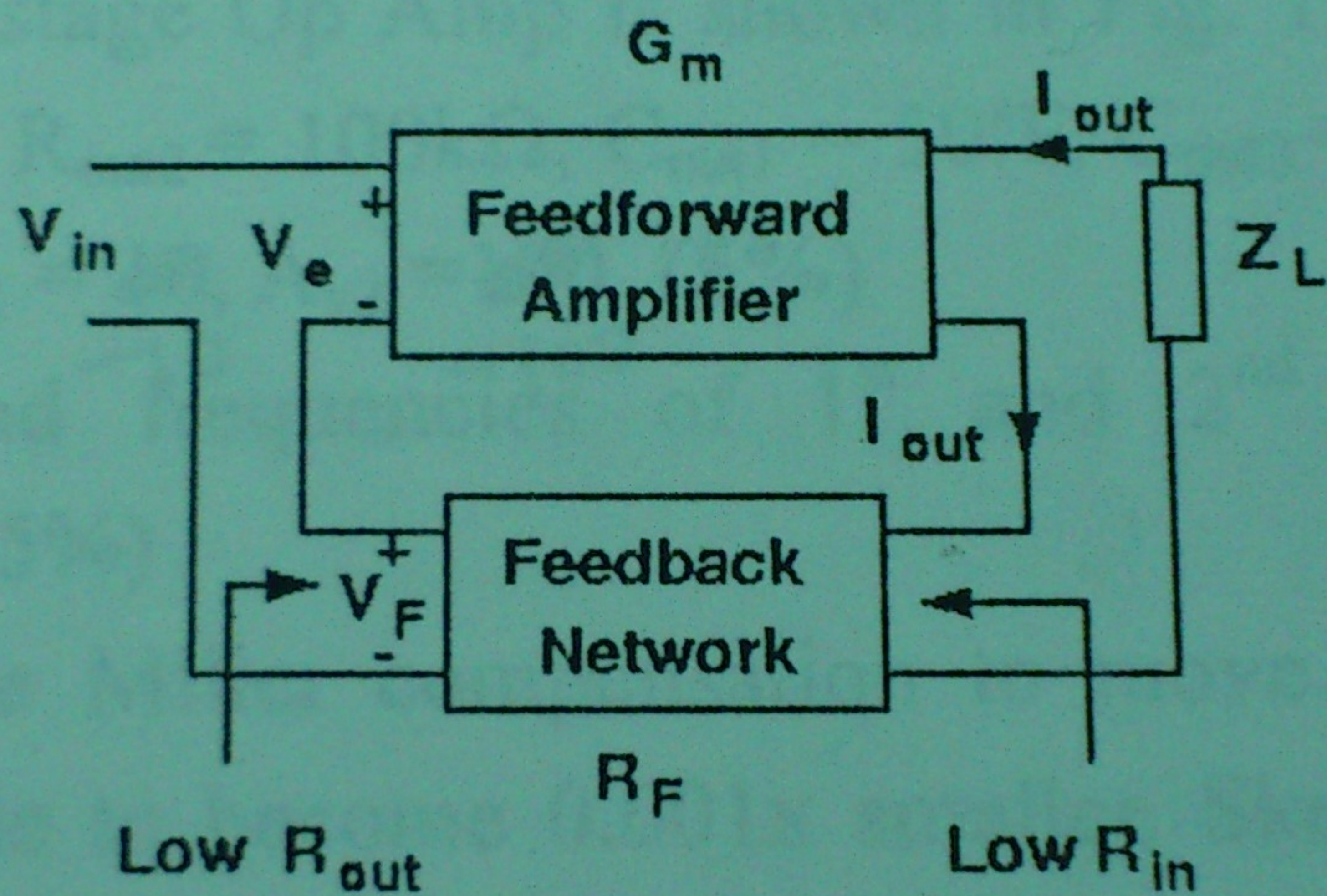


Fig. 5

6. Explain the following terminologies (10%)
- Power Spectrum (Spectral) Density. (2%)
 - Flicker noise. (2%)
 - Corner Frequency. (2%)
 - Phase margin. (2%)
 - Noise bandwidth. (2%)

2013 Analog IC: Final Examination (130%)

7. Fig 7 shows an impedance boosting circuit with $R_S = 50k\Omega$. M_2 and M_3 are biased with $g_m = 2mA/V$ and $r_o = 100k\Omega$. Find the R_{out} . (5%)

 


Fig. 7

8. A shunt-series feedback amplifier as shown in Fig. 8 is biased with $g_m = 2mA/V$, $R_D = R_S = 100k\Omega$, $R_F = 50k\Omega$ and $r_o = \infty$. (10%)

- (a) Find the feedback factor. (2%)
 (b) Find the open-loop gain with loading effect. (4%)
 (c) Find the closed-loop gain V_{out}/V_{in} . (4%)

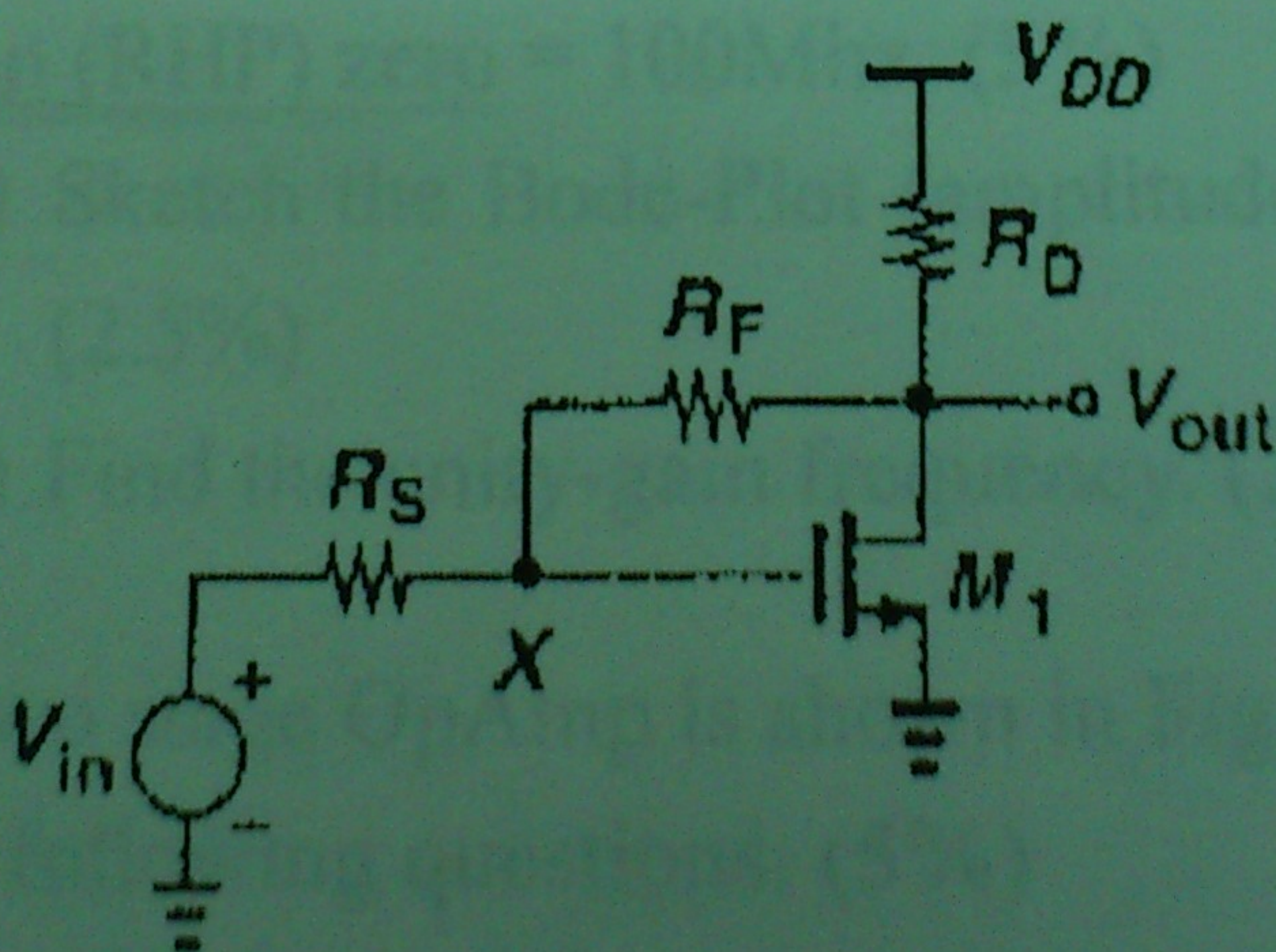



Fig. 10

9. Sketch a common-mode feedback circuit for the 2-stage Op Amp as shown in Fig. 9. (5%)



10. Find sle
10 with

- (a) Fol
(b) 2-s
0.4
(c) W
no
(d) SL
(2

 

11. A
R
at

(b) Find the open-loop gain with loading effect.

(4%)

(c) Find the closed-loop gain V_{out}/V_{in} . (4%)

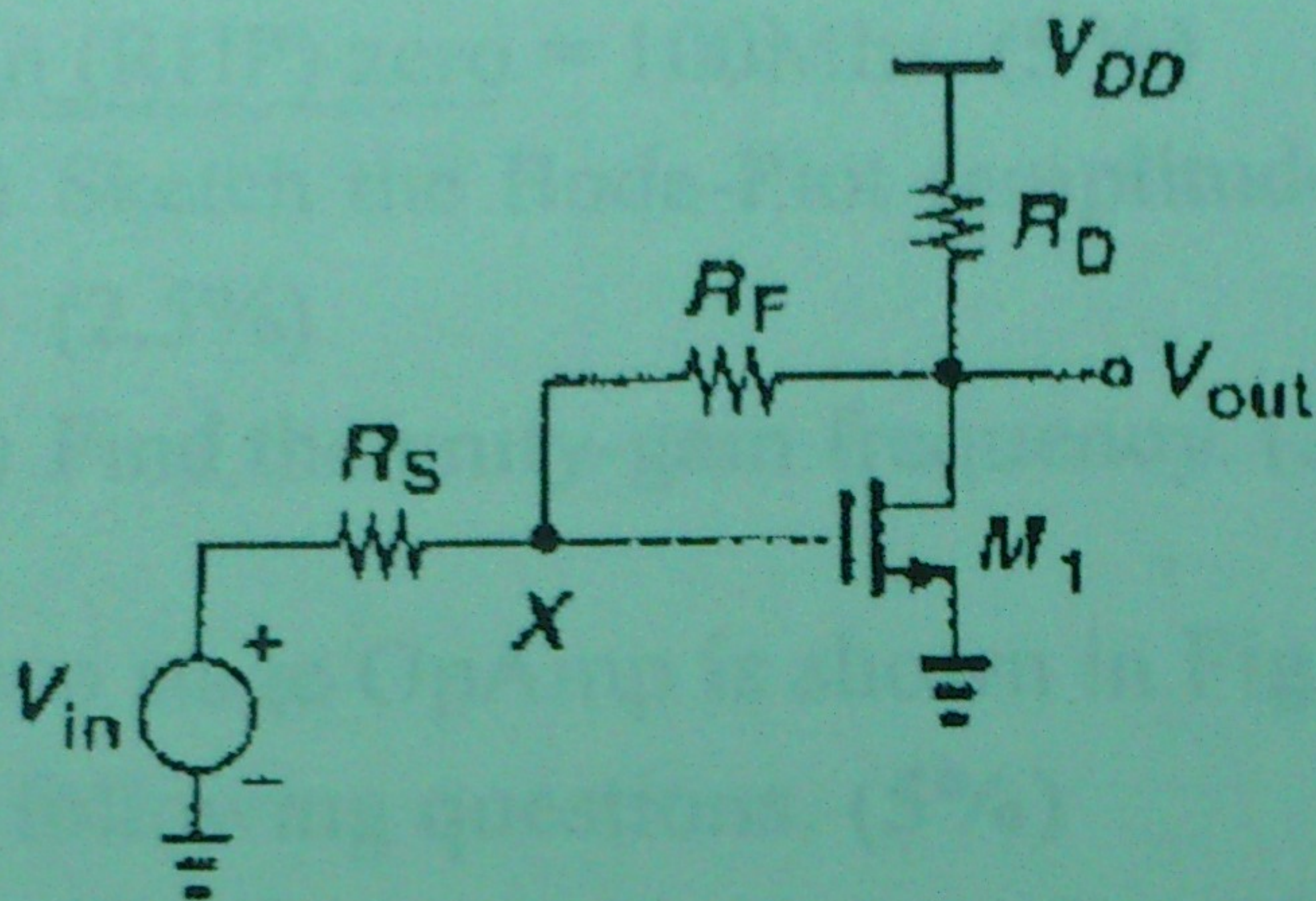


Fig. 10

11.

9. Sketch a common-mode feedback circuit for the 2-stage Op Amp as shown in Fig. 9. (5%)

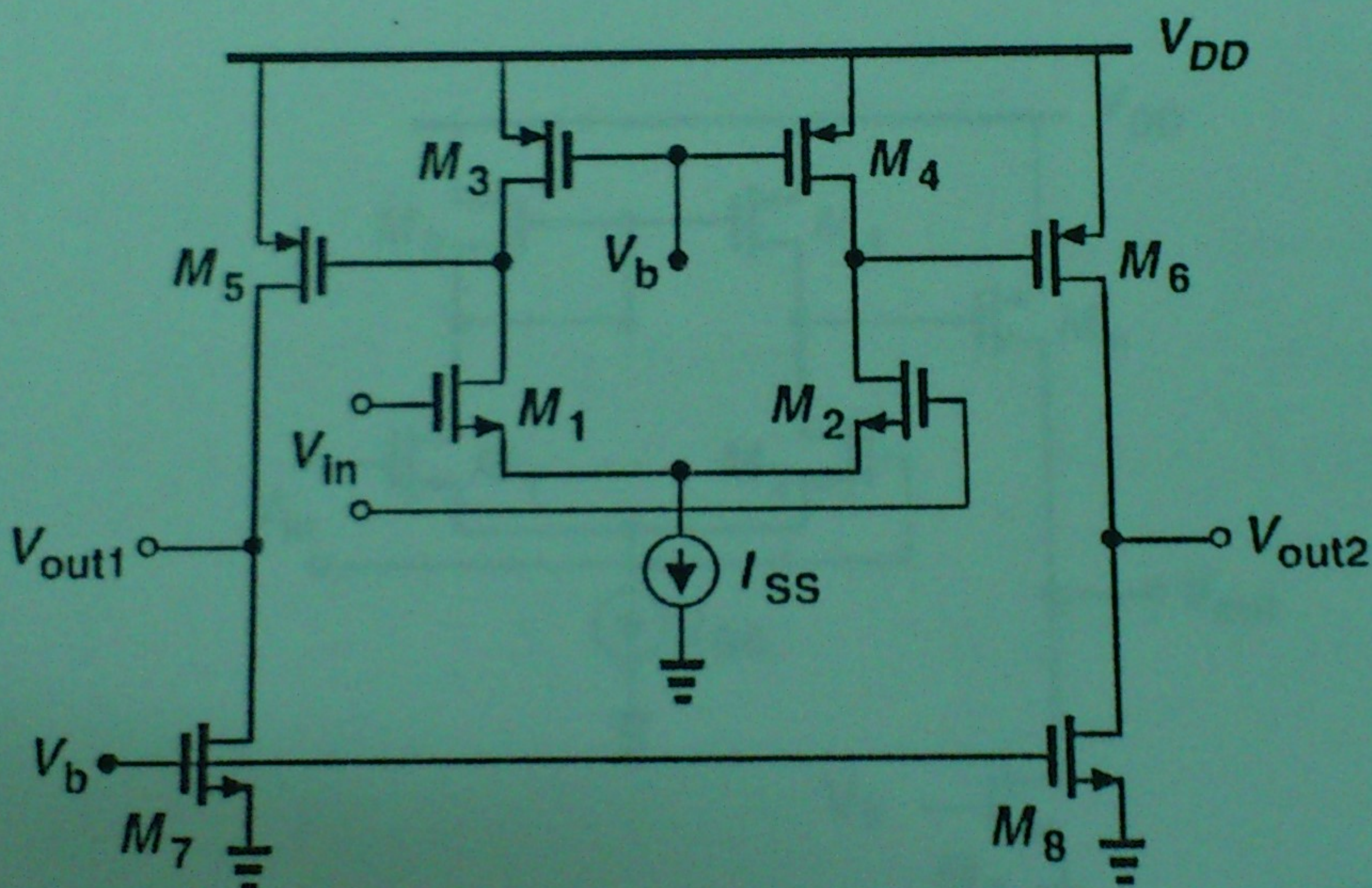


Fig. 9

th = 10. Find slew rates of the following Op Amps in Fig. 10 with $I_{SS} = 10\mu A$. (10%)

- 單位?
- (a) Folded cascode Amp with $C_L = 2pF$. (2.5%)
 - (b) 2-stage OP Amp with $C_1 = 0.2pF$ and $C_2 = 0.4pF$. (2.5%)
 - (c) With $I_d(M_9) = 8\mu A$, explain the behavior of node voltage X when slewing. (2.5%)
 - (d) Sketch a possible solution of condition (c). (2.5%)

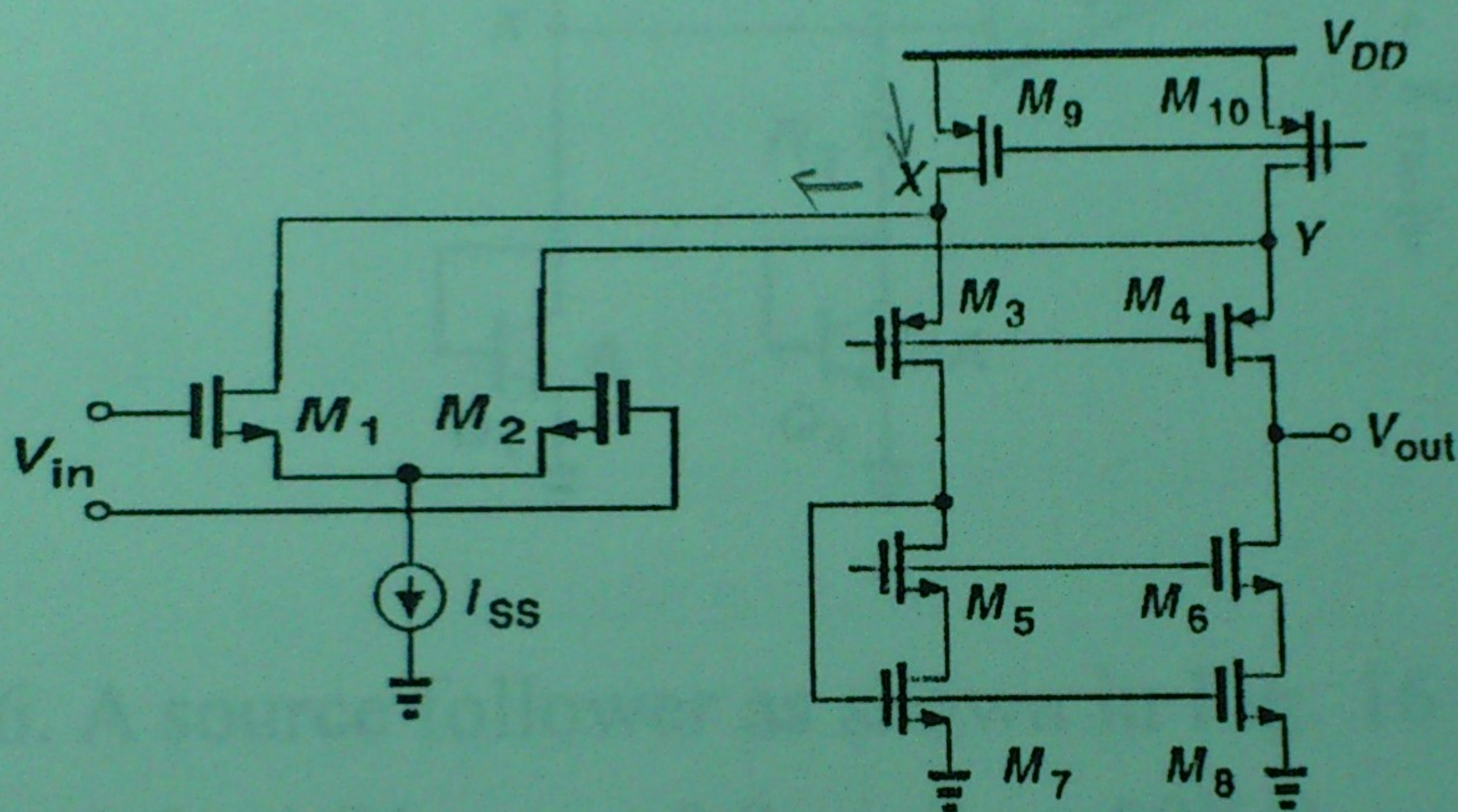


Fig. 10(a)

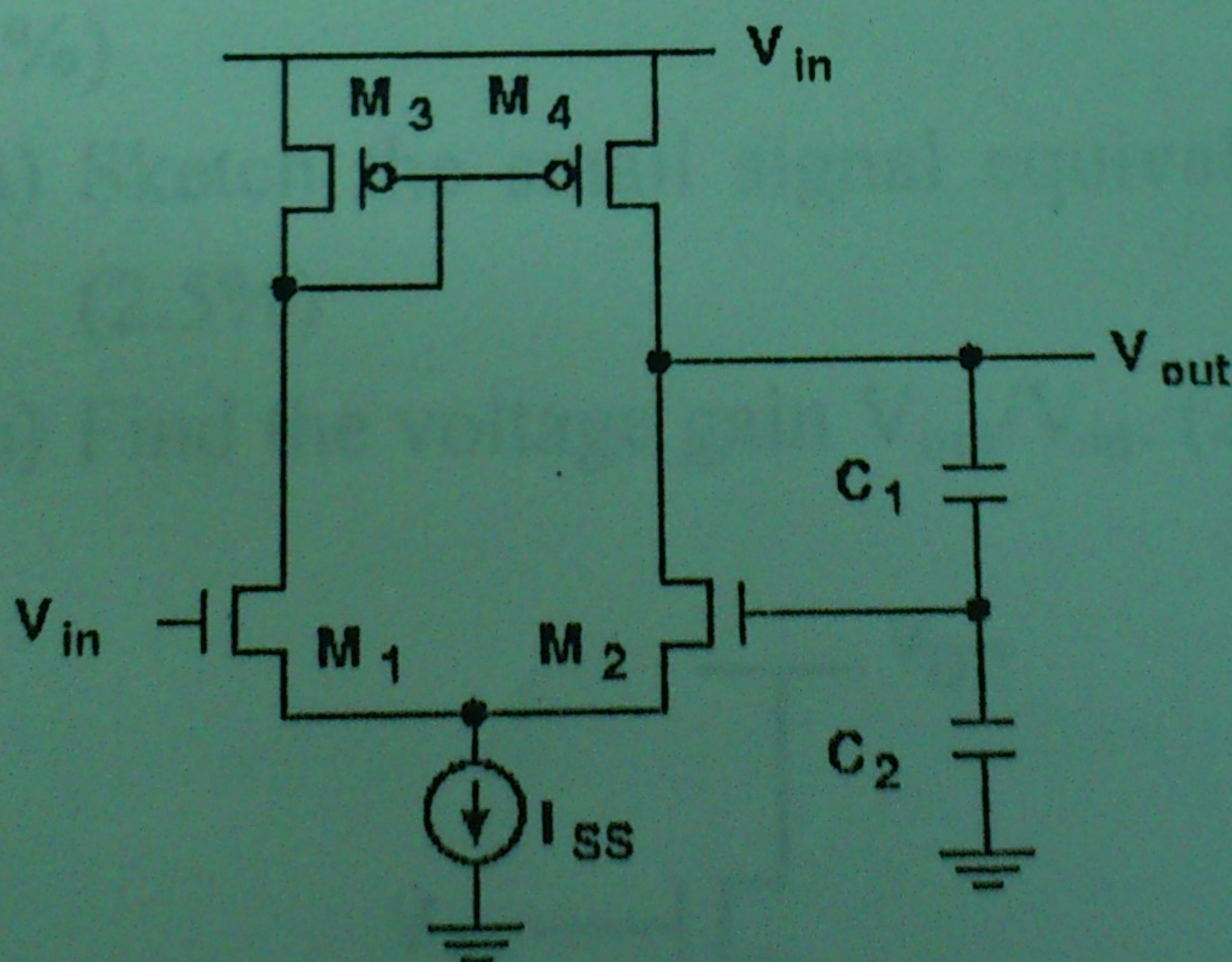


Fig. 10(b)

11. A two-stage Op Amp is shown in Fig. 11 with $R_{out1} = R_{out2} = 100k\Omega$, $C_{out1} = 50fF$, $C_{out2} = 10fF$, and $A_{v1} = 40$, $A_{v2} = 100$. (5%)

- (a) Find frequencies of 1st and 2nd poles.
 (Handwritten: -10, -100)

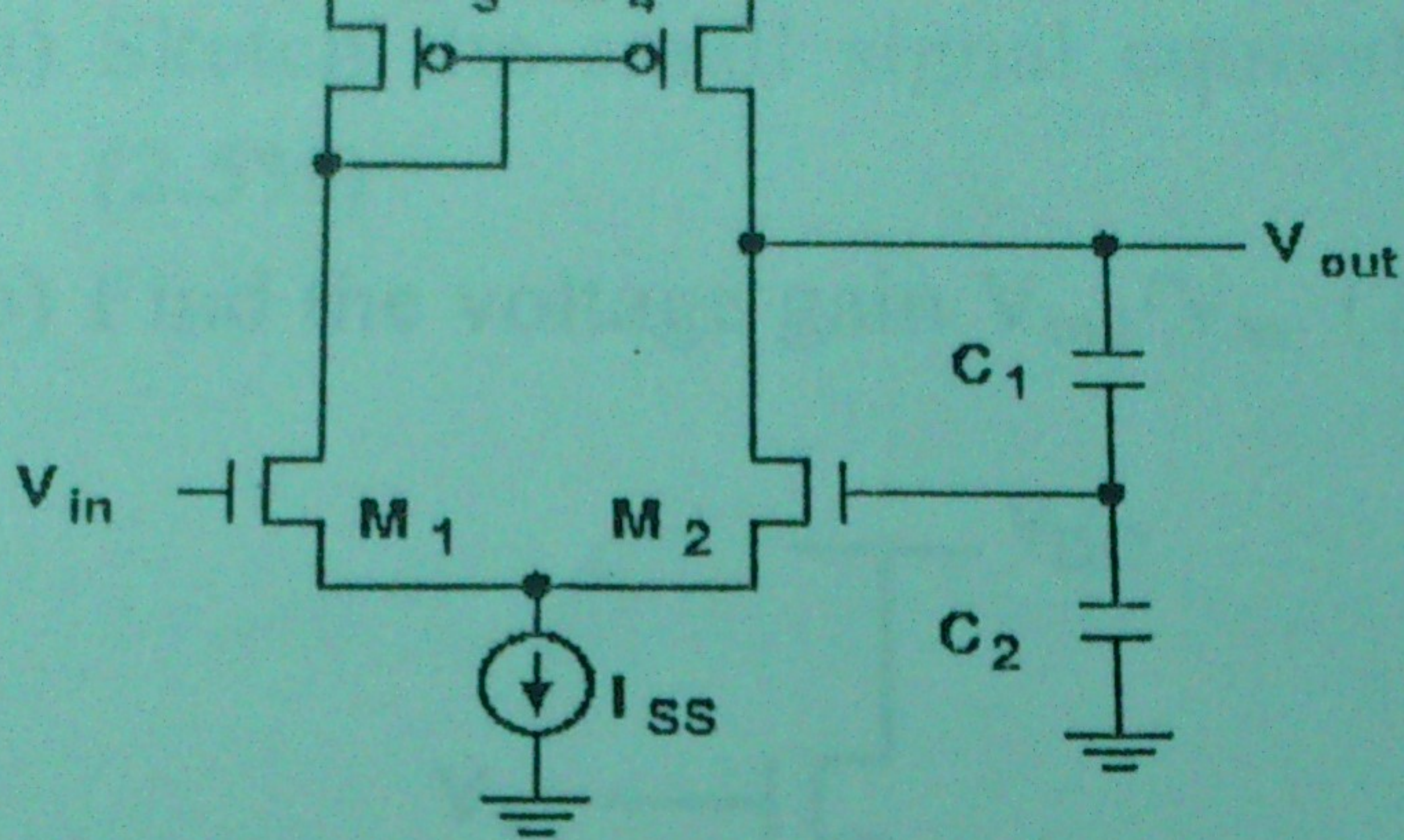


Fig. 10(b)

11. A two-stage Op Amp is shown in Fig. 11 with $R_{out1} = R_{out2} = 100k\Omega$, $C_{out1} = 50fF$, $C_{out2} = 10fF$, and $A_{v1} = 10$, $A_{v2} = 100$. (5%)

(a) Find frequencies of 1st and 2nd poles. (2.5%)

(b) Use Miller compensation to move the 1st pole to become 0.001x smaller. Sketch the compensated circuit and find the value of C_c . (2.5%)

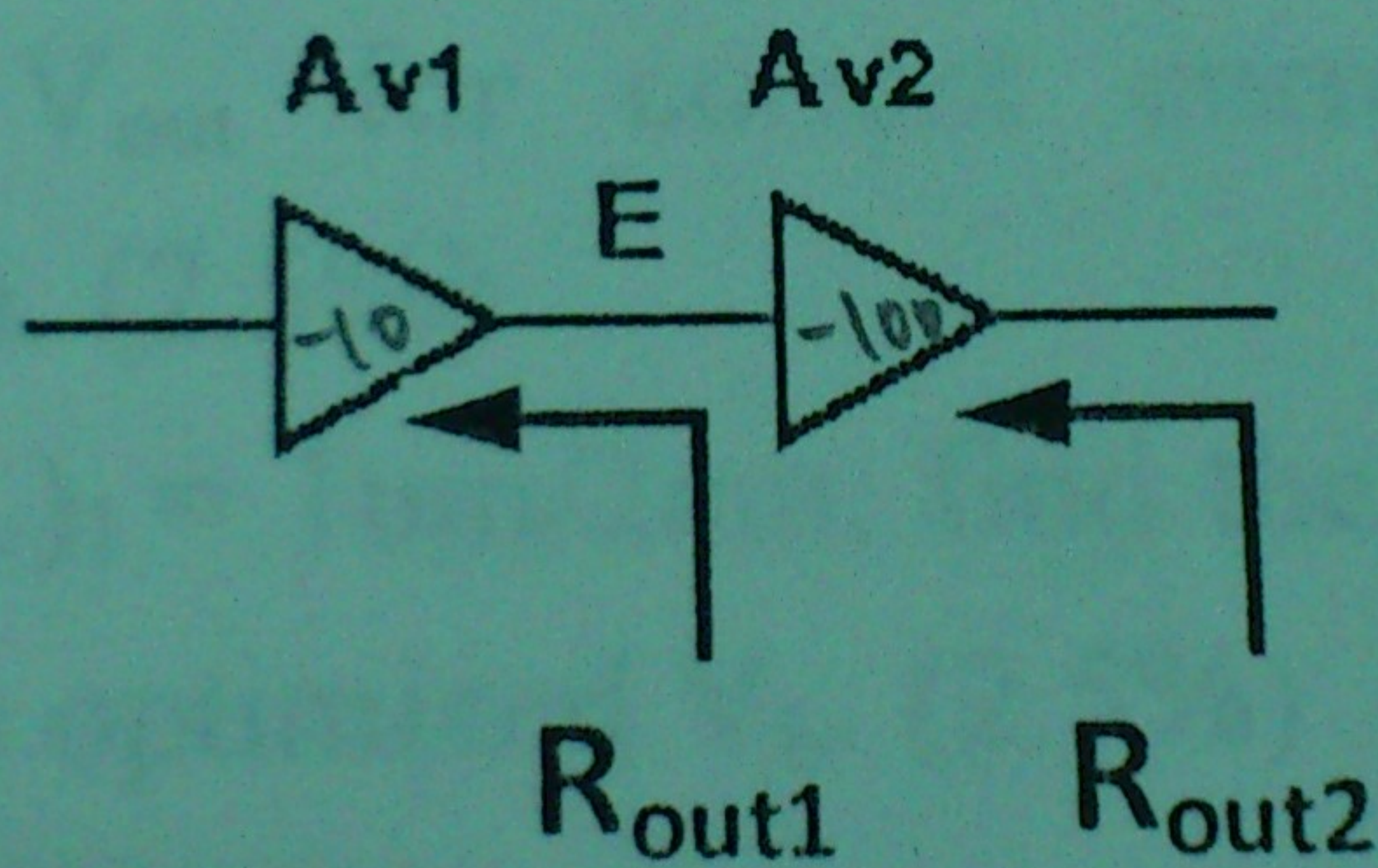


Fig. 11

CCHsieh 2013.06.18

2013 Analog IC: Final Examination (130%)

12. A telescopic amplifier is shown in Fig. 12 with $V_{TH} = 0.6V$ and $V_{ov} = 200mV$ for each MOS, and $V_{b1} = 1.2V$. (5%)

$\sqrt{65} = 0.8$

- (a) Find the maximum and minimum output voltage. (2.5%)
- (b) Find the maximum output swing. (2.5%)

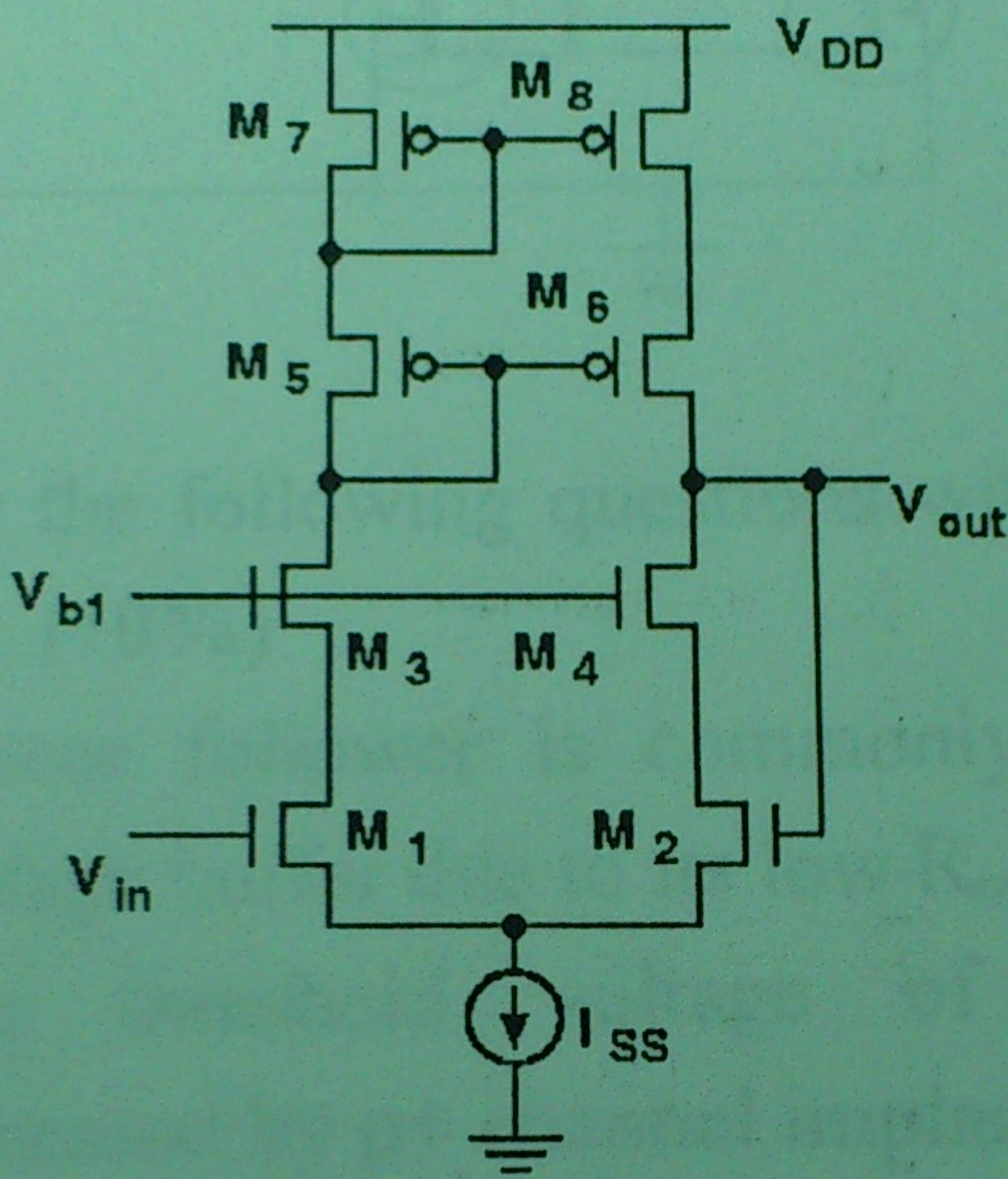


Fig. 12

13. Assume an OpAmp with DC-gain = 60dB, pole1 = 1Mhz, pole2 = 1000Mhz, and right half plan (RHP) zero = 100Mhz. (5%)

- (a) Sketch the Bode-Plot (amplitude & phase). (2.5%)
- (b) Find the unity-gain frequency. (2.5%)

14. A two stage OpAmp is shown in Fig. 14, answer the following questions. (5%)

- (a) Sketch a compensation C_c and explain the pole-splitting effect. (2.5%)
- (b) Explain the right half plane zero effect and provide one solution. (2.5%)

15. A Ban

15. As

ΔV_{BE3}

dV_{BE3}

(a) D

(b) F

16. A s

1.5

(5

(a

(

17.

 


Fig. 12

16. A s
1.5
(5
(a

13. Assume an OpAmp with DC-gain = 60dB, pole1 = 1Mhz, pole2 = 1000Mhz, and right half plane (RHP) zero = 100Mhz. (5%)
- (a) Sketch the Bode-Plot (amplitude & phase). (2.5%)
 - (b) Find the unity-gain frequency. (2.5%)

14. A two stage OpAmp is shown in Fig. 14, answer the following questions. (5%)

- (a) Sketch a compensation C_c and explain the pole-splitting effect. (2.5%)
- (b) Explain the right half plane zero effect and provide one solution. (2.5%)

17

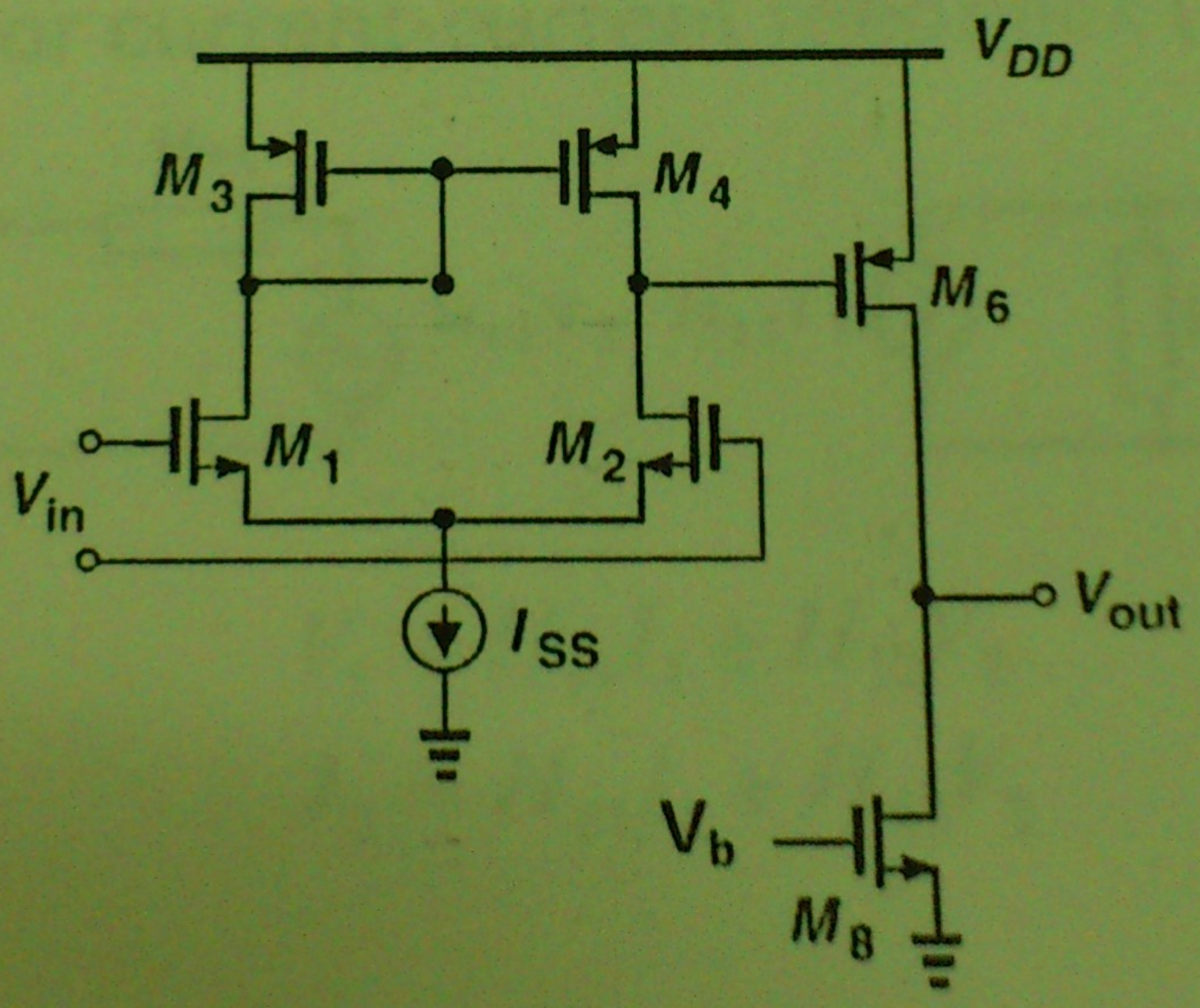


Fig. 14

15. A Bandgap voltage reference is shown in Fig. 15. Assume $n = 8$, $I_{C1} = I_{C2} = I_{B3}$, $V_{BE1} = 0.7V$, $\Delta V_{BE}(Q_1 - Q_2) = V_T \ln(n)$, $dV_T/dT = 0.08mV/K$, $dV_{BE3}/dT = -1.5mV/K$. (5%)

(a) Design R_2/R_3 to get $dV_{out}/dT = 0$. (2.5%)

(b) Find the $V_{out} = ?$ volts in (a). (2.5%)

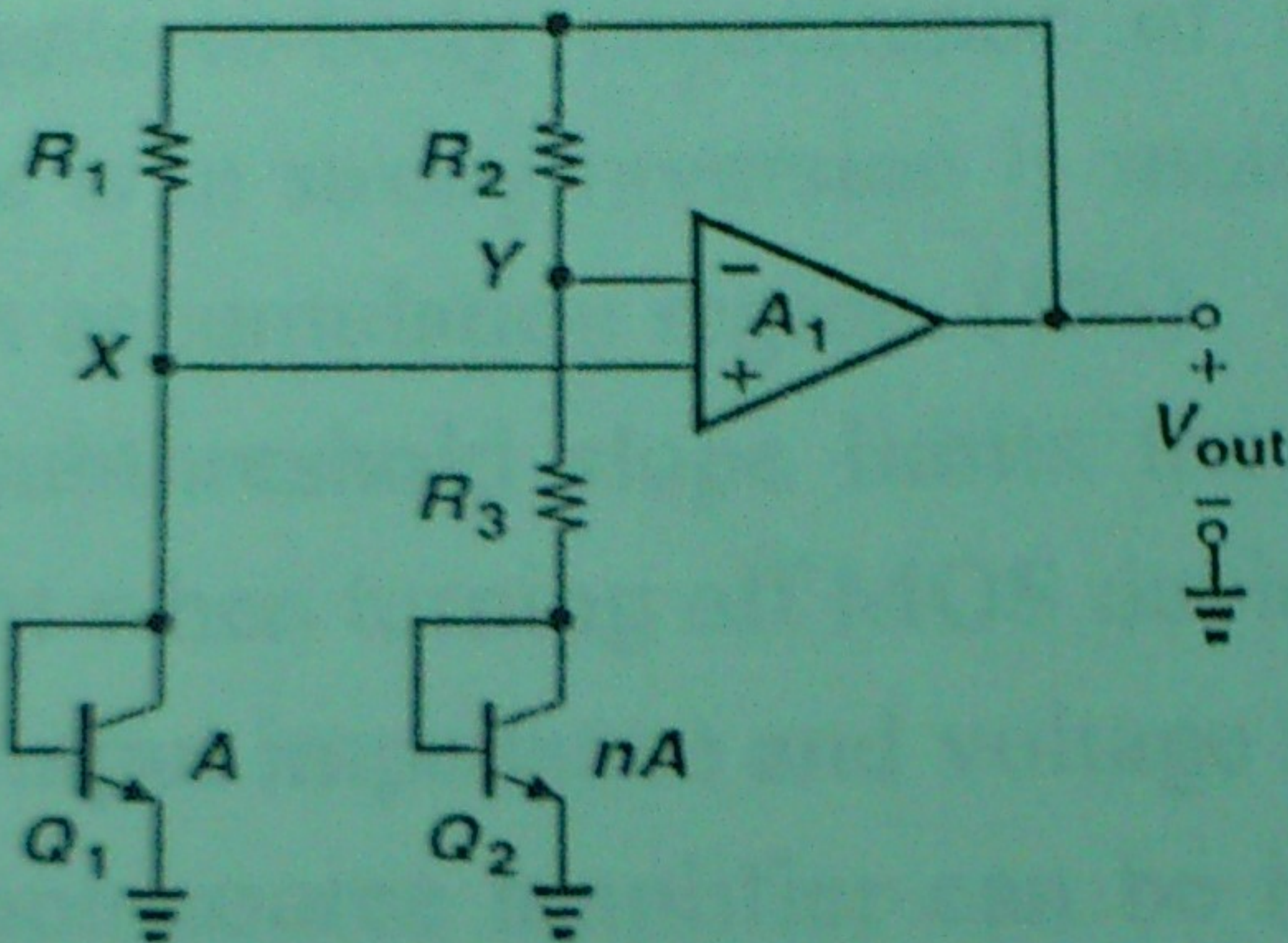


Fig. 15

16. A source follower as shown in Fig. 16 with $g_m = 1.5mA/V$, $g_{mb} = 0.2g_m$, $R_S = 50K\Omega$, and $r_o = \infty$. (5%)

(a) Sketch the small signal equivalent circuit. (2.5%)

(b) Find the voltage gain V_{out}/V_{in} . (2.5%)

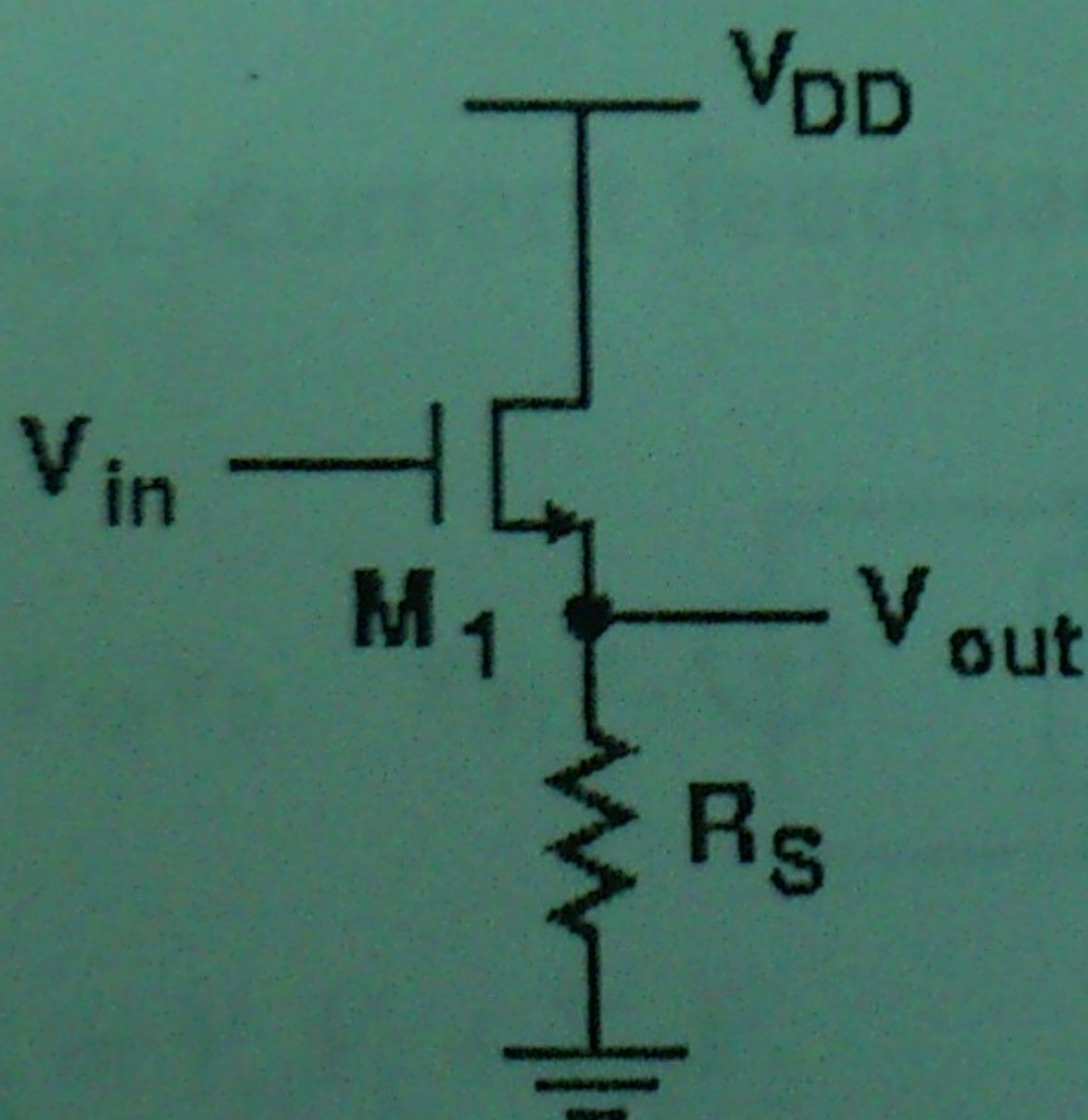


Fig. 16

17. A cascode current mirror as shown in Fig. 17, assume $Q_1 \sim Q_4$ are biased with $|V_{ov}| = 200mV$, $|V_h| = 0.6V$, $I_{BIAS} = 5\mu A$, $g_m = 2mA/V$, $r_o =$

16. A source follower as shown in Fig. 16 with $g_m = 1.5\text{mA/V}$, $g_{mb} = 0.2g_m$, $R_S = 50\text{k}\Omega$, and $r_o = \infty$. (5%)

(a) Sketch the small signal equivalent circuit. (2.5%)

(b) Find the voltage gain V_{out}/V_{in} . (2.5%)

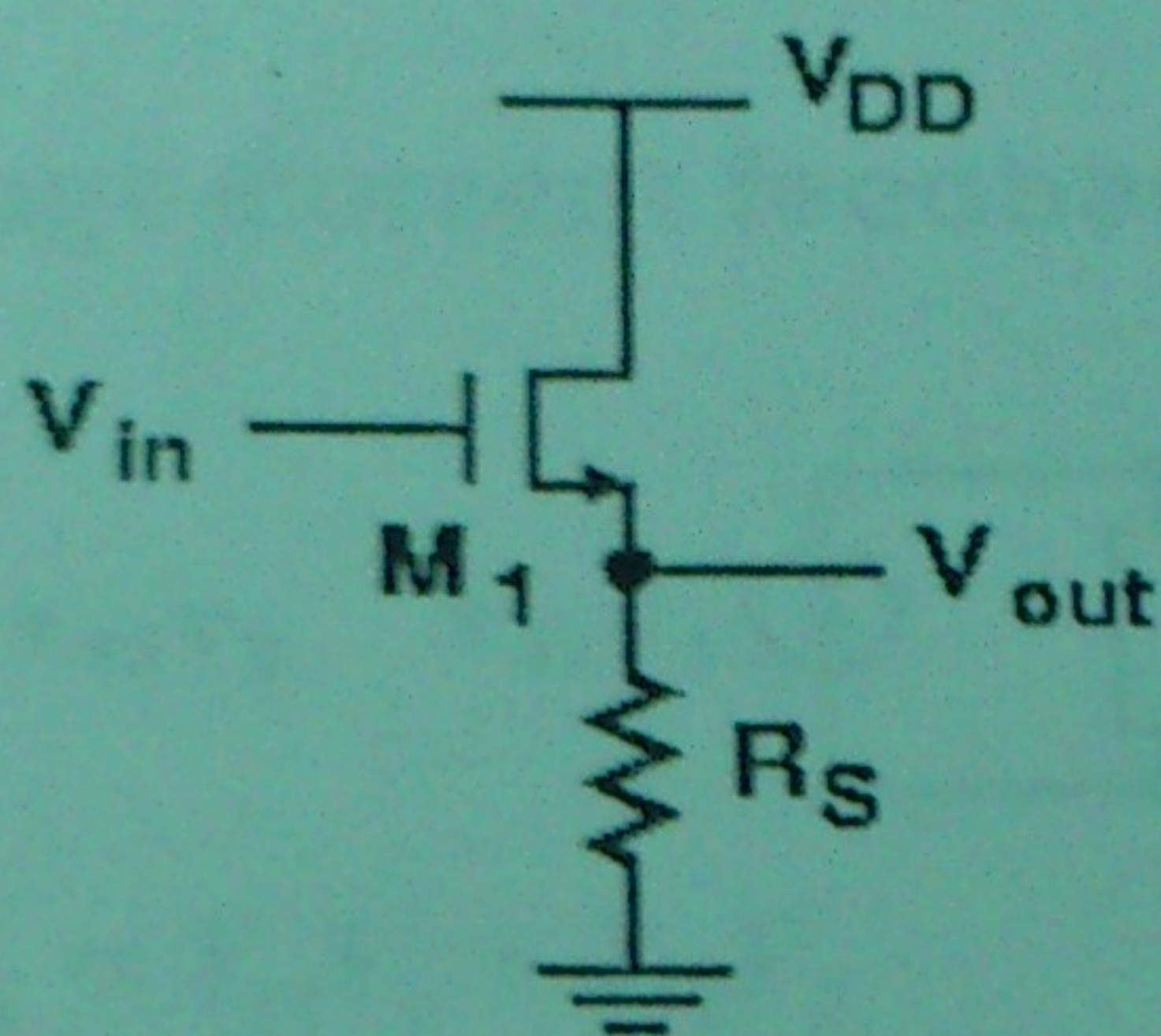



Fig. 16

17. A cascode current mirror as shown in Fig. 17, assume $Q_1 \sim Q_4$ are biased with $|V_{ov}| = 200\text{mV}$, $|V_{th}| = 0.6\text{V}$, $I_{BIAS} = 5\mu\text{A}$, $g_m = 2\text{mA/V}$, $r_o = 100\text{k}\Omega$, $(W/L)_1 = (W/L)_3$, $(W/L)_2/(W/L)_1 = (W/L)_4/(W/L)_3 = 4$, and $V_{DD} = 1.8\text{V}$. (5%)

(a) Find the optimized V_b and related output voltage V_{out} for correct current mirror operation. (2.5%)

(b) For $(W/L)_1 = 1\mu\text{m}/2\mu\text{m}$, find the size of Q_5 to get the optimized V_b . (2.5%)

2013 Analog IC: Final Examination (130%)

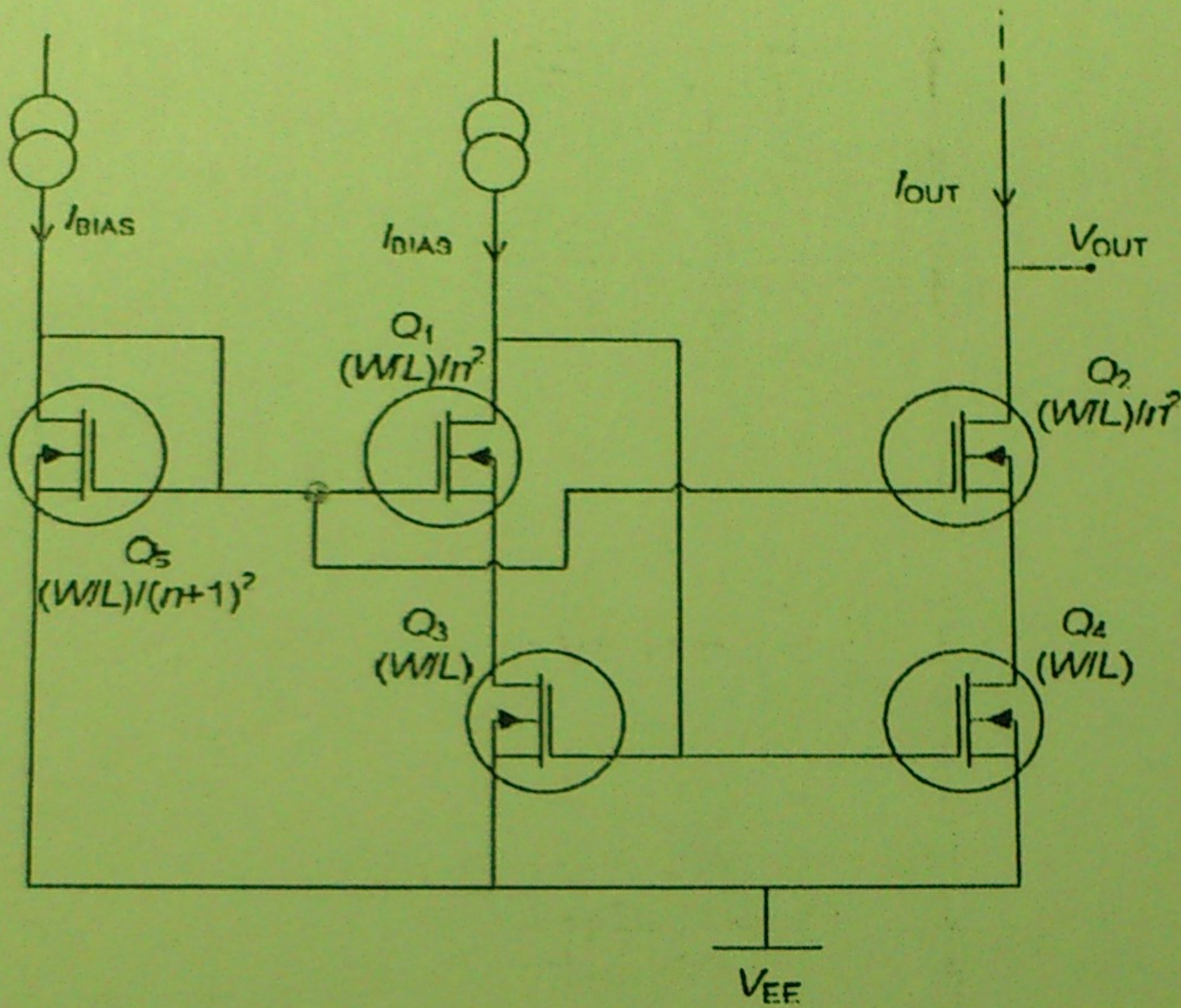

$g_m = \sqrt{2\mu C_{ox}}$

Fig. 17

18. Answer the following questions with TRUE or FALSE: (10%)

- (a) Source follower is commonly used as a voltage buffer due to its low R_{out} . (1%)
- (b) The threshold voltage of nMOS is increased by p+ channel implantation. (1%)
- (c) Differential amplifier has smaller common noise and low power performance. (1%)

Reference Material

➤ For current-voltage feedback (Z)



g_m

4/4

- (d) Junction capacitance is proportional to device length. (1%)
- (e) The transconductance g_m of MOSFET is proportional to V_{ov} at a known constant biasing current. (1%)
- (f) The g_m of pMOS is larger than nMOS at same bias current and device size. (1%)
- (g) The gate-to-body capacitance of a MOS device is in strong inversion is smaller than that in accumulation region. (1%)
- (h) The subthreshold slope limits the leakage current when turning off MOS device. (1%)
- (i) The output impedance and voltage swing of common-source amplifier can be increased by a cascode structure. (1%)
- (j) The r_o of MOSFET will be decreased at high V_{DS} bias due to the channel length modulation effect. (1%)

➤ For voltage-current feedback (Y)




Differential amplifier has smaller common noise and low power performance. (1%)

high V_{DS} bias due to the channel length modulation effect. (1%)

$\frac{A_{mid}}{A_{mid}} = \frac{P_{mid}}{P_{mid}}$

Reference Material


➤ For current-voltage feedback (Z)

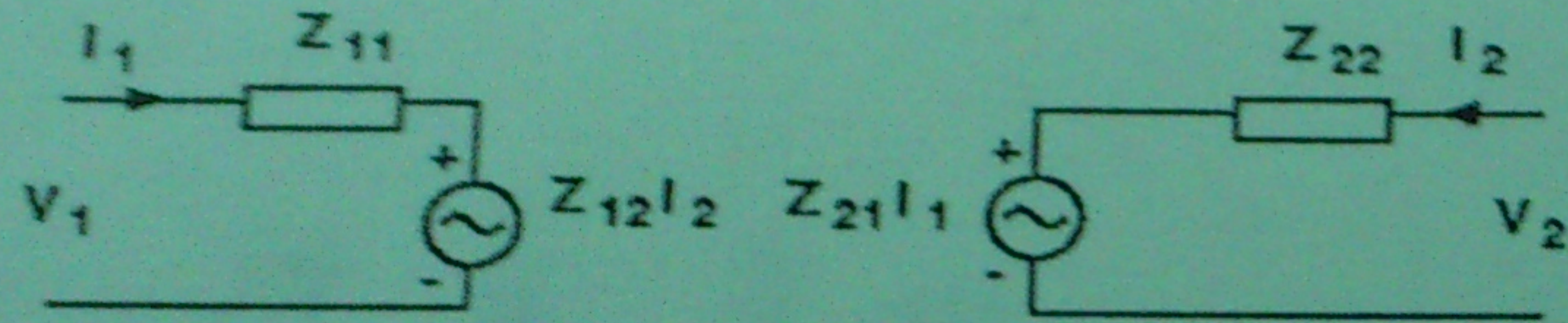

$$V_1 = Z_{11}I_1 + Z_{12}I_2$$

$$V_2 = Z_{21}I_1 + Z_{22}I_2$$


➤ For voltage-current feedback (Y)

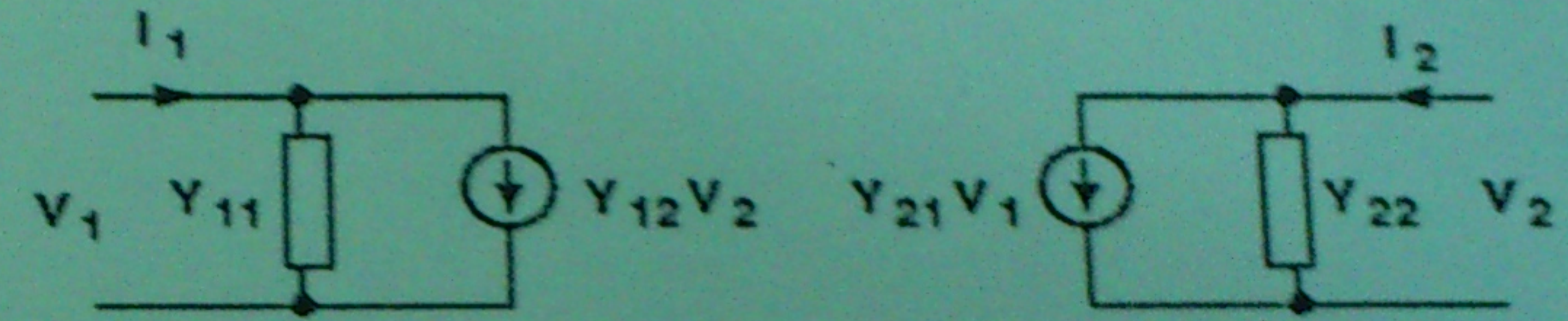

$$I_1 = Y_{11}V_1 + Y_{12}V_2$$

$$I_2 = Y_{21}V_1 + Y_{22}V_2$$


➤ For current-current feedback (H)

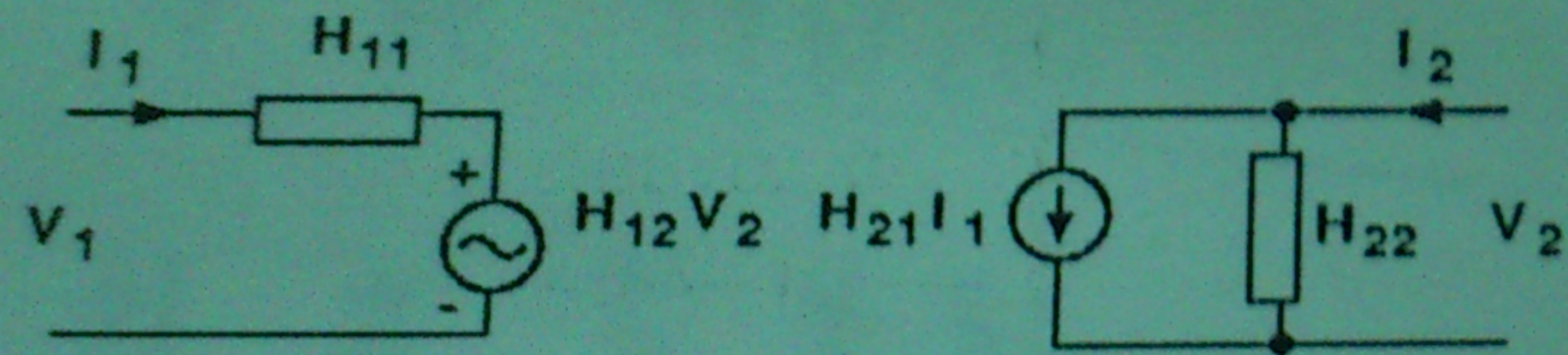

$$V_1 = H_{11}I_1 + H_{12}V_2$$

$$I_2 = H_{21}I_1 + H_{22}V_2$$

➤ For voltage-voltage feedback (G)

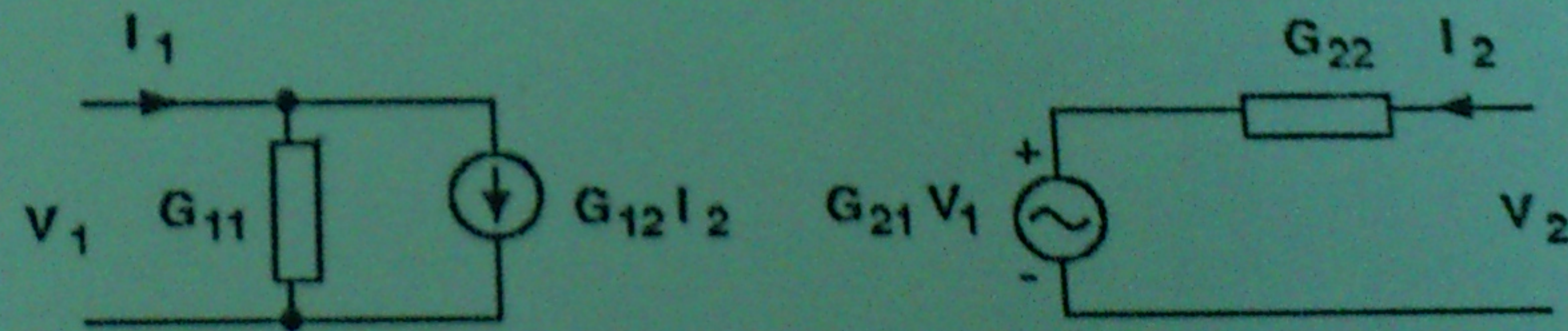

$$I_1 = G_{11}V_1 + G_{12}I_2$$

$$V_2 = G_{21}V_1 + G_{22}I_2$$