

2012 Analog IC: Midterm Examination (110%)

1. Answer definitions of the following effects and explain the physical mechanisms. (10%)

- (a) Hot carrier effect. (2%)
- (b) Mobility Degradation. (2%)
- (c) Punch Through. (2%)
- (d) Body effect. (2%)
- (e) Velocity Saturation. (2%)

2. A NMOS is biased with a gate voltage V_G and a drain voltage V_D as shown in Fig. 2. (10%)

- (a) Sketch the I_D - V_D transfer curves with different V_G . (2.5%)
- (b) Illustrate the boundary line of linear / saturation regions on the curves. (2.5%)
- (c) Illustrate the early voltage and r_o . (2.5%)
- (d) Illustrate the threshold voltage V_{TH} . (2.5%)

 


Fig. 2

3. Figure 3 shows a NMOS with parameters of

 


Fig. 2

3. Figure 3 shows a NMOS with parameters of $V_{TH} = 0.7V$, $W = 10\mu m$, $L = 1\mu m$, $C_{ox} = 1fF/\mu m^2$ and $C_{ov} = 0.1fF/\mu m$. (10%)

- (a) Find and sketch the capacitances of C_{EN} and C_{EF} as V_X varies from 0 to 3V, identify V_X value of the transition point also. (5%)
- (b) Sketch the capacitances of C_{FB} and C_{NB} as V_X varies from 0 to 3V, identify V_X value of the cross point also. (5%)

 


Fig. 3

1.3



4. Fig. 4 is a layout of CMOS inverter. (5%)
 (a) Draw the cross section from A-A'. (2.5%)
 (b) Identify and make the orders of masks in semiconductor process flow. (2.5%)

 


Fig. 4

5. Fig. 5 is a common-source amplifier. (5%)
 (a) Sketch the small signal equivalent circuit. (2.5%)
 (b) Derive the equation of voltage gain V_{out}/V_{in} in terms of $g_{m<n>}$, $g_{mb<n>}$ and $r_{o<n>}$. (2.5%)


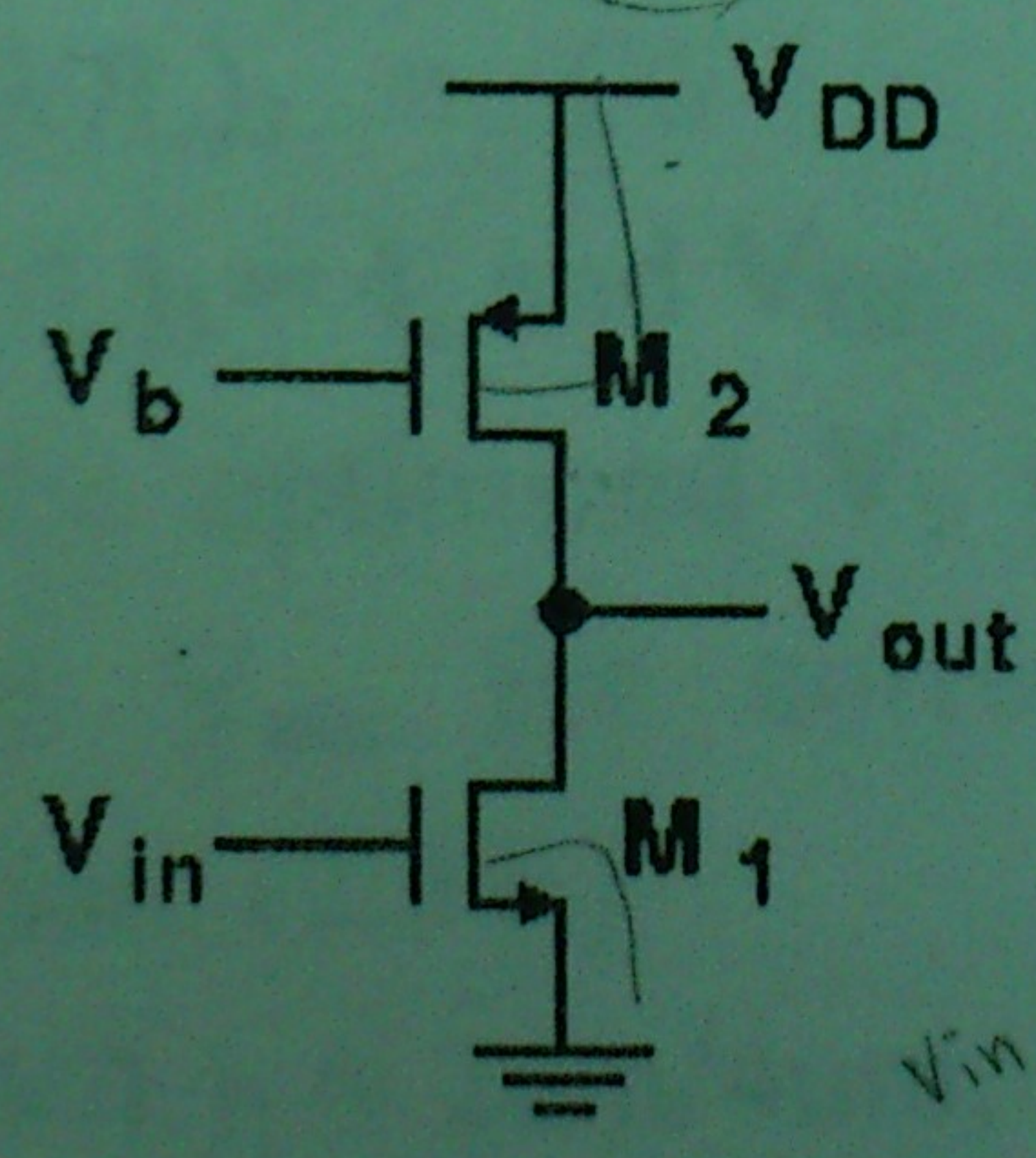


Fig. 5

6. Assume $r_o = 100k$, $I_D = 10\mu A$, $|V_{ov}| = 200mV$, $g_{mb} = 0$, and $R_S = 100K\Omega$ in Fig. 6. (5%)
 (a) Sketch the small signal equivalent circuit.

 

in terms of $g_{m\langle n \rangle}$, $g_{mb\langle n \rangle}$ and $r_{o\langle n \rangle}$. (2.5%)


 
 


Fig. 5

6. Assume $r_o = 100k$, $I_D = 10\mu A$, $|V_{ov}| = 200mV$, $g_{mb} = 0$, and $R_S = 100K\Omega$ in Fig. 6. (5%)

(a) Sketch the small signal equivalent circuit. (2.5%)

 
(b) Find the output resistance R_{out} . (2.5%)



$$g_{m1} = \frac{2I_D}{V_{ov}}$$

$$\frac{1 + g_{m1} R_S}{r_o + R_S}$$

Fig. 6

 

$$I_D = \mu_n C_{ox} \frac{W}{L} ((V_{GS} - V_{TH})V_{DS} - \frac{1}{2}V_{DS}^2)$$

$$I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH})^2 (1 + \lambda V_{DS})$$

2012 Analog IC: Midterm Examination (110%)

7. Write down the drain current equations of MOSFET in triode and saturation region with channel length modulation effect. (5%)

8. A source follower as shown in Fig. 8 with $g_m = 2\text{mA/V}$, $g_{mb} = 0.2g_m$, $R_S = 100\text{k}\Omega$, and $r_o = \infty$. (5%)

(a) Sketch the small signal equivalent circuit. (2.5%)

(b) Find the voltage gain V_{out}/V_{in} . (2.5%)


 


Fig. 8

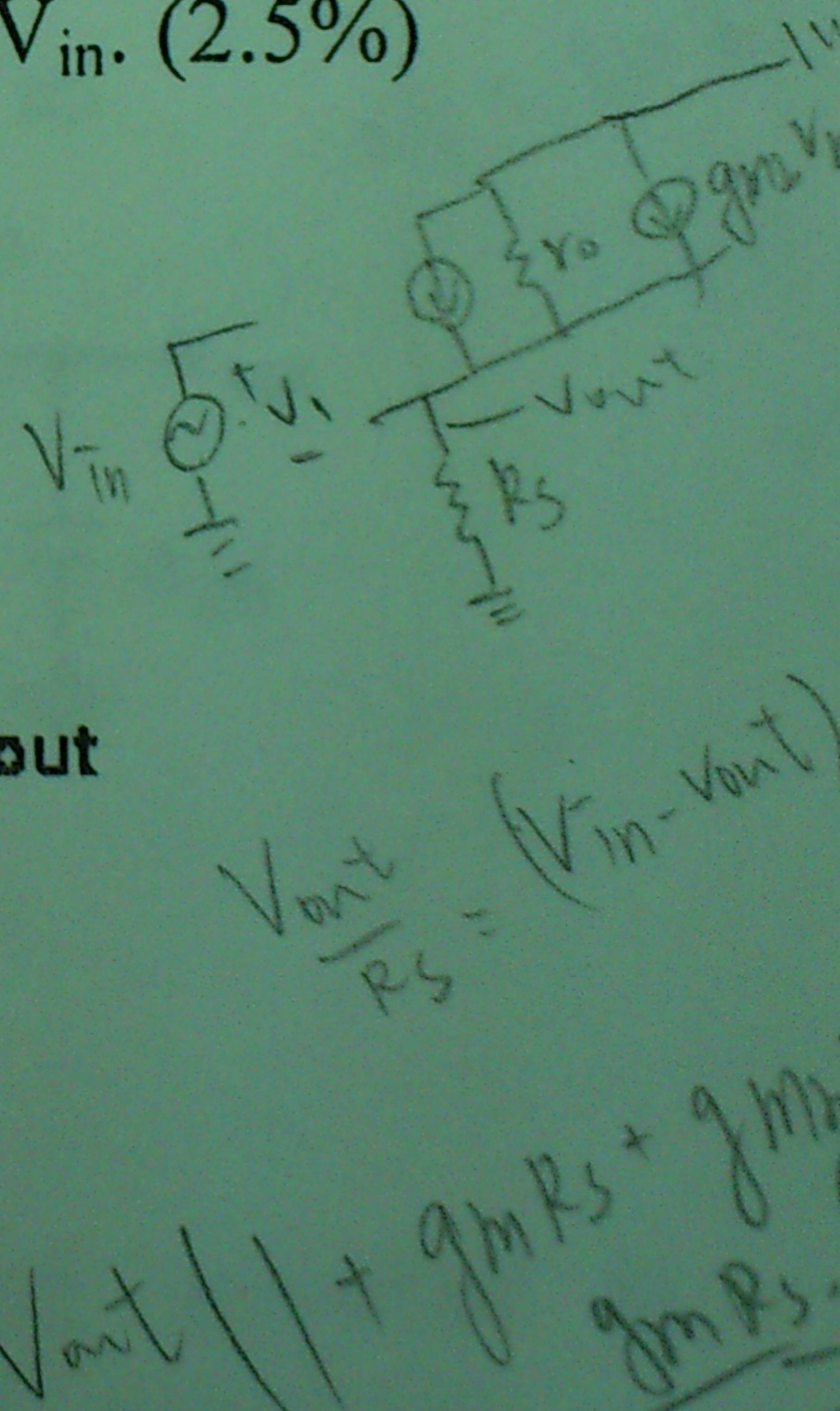

$$\frac{V_{out}}{R_S} = (V_{in} - V_{out})$$

$$V_{out} \parallel + g_m R_S + g_m$$

$$A_v = \frac{g_m R_S}{1 + g_m R_S}$$

9. A differential pair is shown in Fig. 9. Assume all the MOSFETs are biased with $|V_{ov}| = 200\text{mV}$ and $|V_{TH}| = 0.6\text{V}$. The $I_D(M_3) = 20\mu\text{A}$, $g_{m1} = g_{m2} = 2\text{mA/V}$, $R_{D1} = R_{D2} = 100\text{k}\Omega$, $r_o(M_1) = r_o(M_2)$

 


Fig. 8

Handwritten notes for Fig. 8:

$$V_{out} / R_s = (V_{in} - V_{out})$$

$$A_v = \frac{g_m R_s}{1 + (g_m + g_{m3}) R_s}$$

9. A differential pair is shown in Fig. 9. Assume all the MOSFETs are biased with $|V_{ov}| = 200\text{mV}$ and $|V_{TH}| = 0.6\text{V}$. The $I_D(M_3) = 20\mu\text{A}$, $g_{m1} = g_{m2} = 2\text{mA/V}$, $R_{D1} = R_{D2} = 100\text{k}\Omega$, $r_o(M_1) = r_o(M_2) = r_o(M_3) = 200\text{k}\Omega$, and $V_{DD} = 1.8\text{V}$. (10%)

(a) Find the differential gain $A_{v,DM}$. (2.5%)

(b) Find the common-mode gain $A_{v,CM}$. (2.5%)

(c) Find the maximum differential input signal range. (2.5%)

(d) Find the input common mode range. (2.5%)

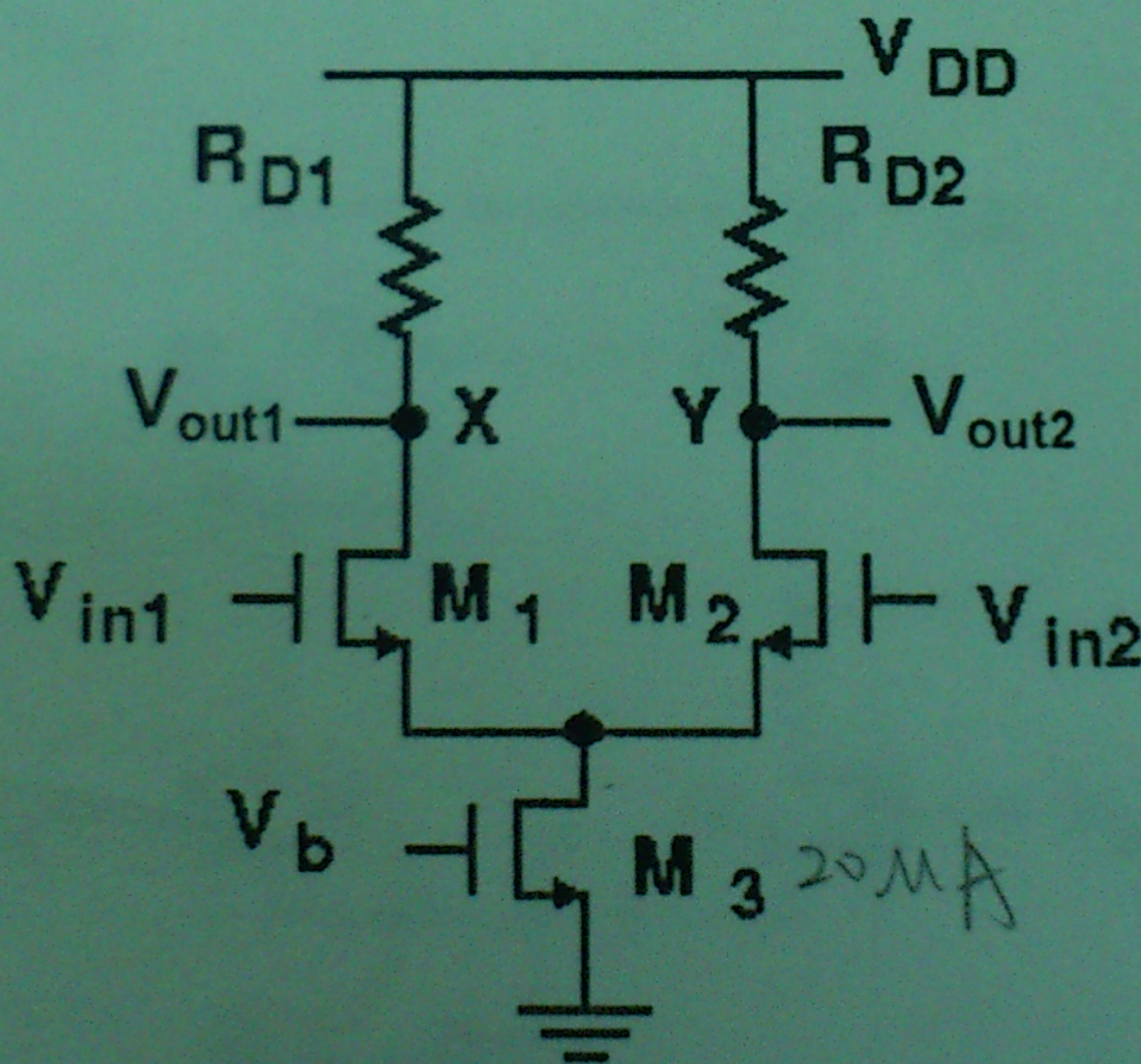


Fig. 9

Handwritten notes for Fig. 9:

$10\text{M} \times 100\text{k} = 10^{-5} \times 10^5 = 10^0 = 1$

$A_{v,DM} = \frac{2I_{DSS}}{\mu C_{ox} \frac{W}{L}}$

$A_{v,CM} = \frac{R_D g_m}{1 + 2g_m R_{SS}}$

$A_{v,DM} = \mu C_{ox} \frac{W}{L} (V_{as} - V_{TH})$

1.4
5
12

$$\frac{I_{out}}{I_{REF}} = \frac{4 \left(1 + \frac{1}{50} \times 0.5\right)}{\left(1 + \frac{1}{50} \times 0.7\right)}$$

2/3

10. A current mirror as shown in Fig. 10, assume all MOSs are biased with $|V_{ov}| = 200\text{mV}$, $|V_{TH}| = 0.5\text{V}$, $I_{REF} = 10\mu\text{A}$, $(W/L)_2/(W/L)_1 = 4$, and $V_{DD} = 1.8\text{V}$. (5%)

(a) Assume early voltage $V_A = 50\text{V}$, find I_{out} at $V_{out} = 0.5\text{V}$. (2.5%)

(b) Find the minimum output voltage V_{out} for current source I_{out} . (2.5%) *电流源按比例*

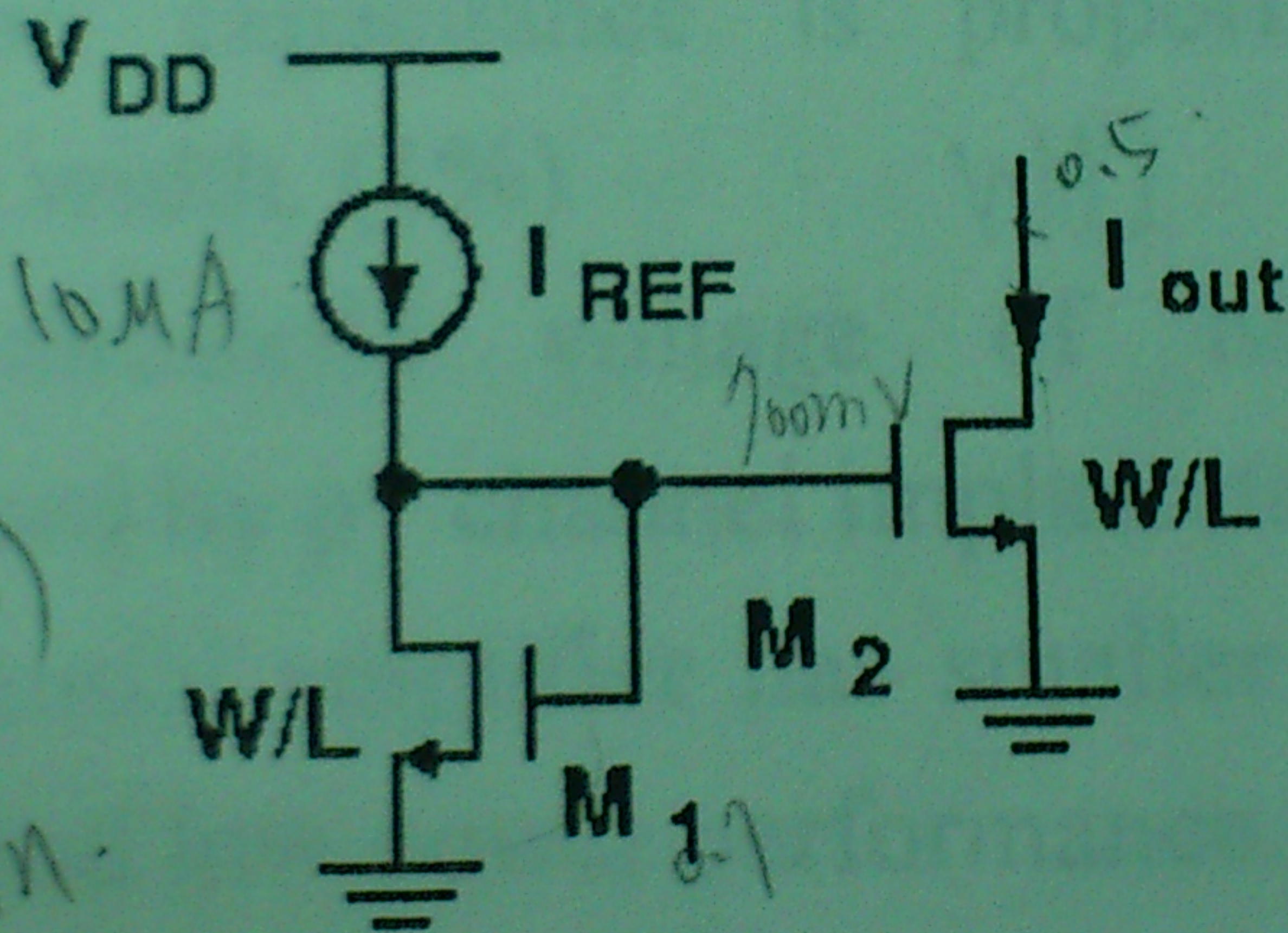


Fig. 10

11. A cascode current mirror as shown in Fig. 11, assume all MOSs are biased with $|V_{ov}| = 200\text{mV}$, $|V_{th}| = 0.5\text{V}$, $I_{BIAS} = 10\mu\text{A}$, $g_m = 2\text{mA/V}$, $r_o = 100\text{k}\Omega$, $(W/L)_1 = (W/L)_3$, $(W/L)_2/(W/L)_1 = (W/L)_4/(W/L)_3 = 4$, and $V_{DD} = 1.8\text{V}$. (5%)

(a) Find the optimized V_b and related output

 


Fig. 10

11. A cascode current mirror as shown in Fig. 11, assume all MOSs are biased with $|V_{ov}| = 200\text{mV}$, $|V_{th}| = 0.5\text{V}$, $I_{BIAS} = 10\mu\text{A}$, $g_m = 2\text{mA/V}$, $r_o = 100\text{k}\Omega$, $(W/L)_1 = (W/L)_3$, $(W/L)_2/(W/L)_1 = (W/L)_4/(W/L)_3 = 4$, and $V_{DD} = 1.8\text{V}$. (5%)

(a) Find the optimized V_b and related output voltage V_{out} for correct current mirror operation. (2.5%)

(b) For $(W/L)_1 = 2\mu\text{m}/4\mu\text{m}$, find the size of Q_5 to get the optimized V_b . (2.5%)

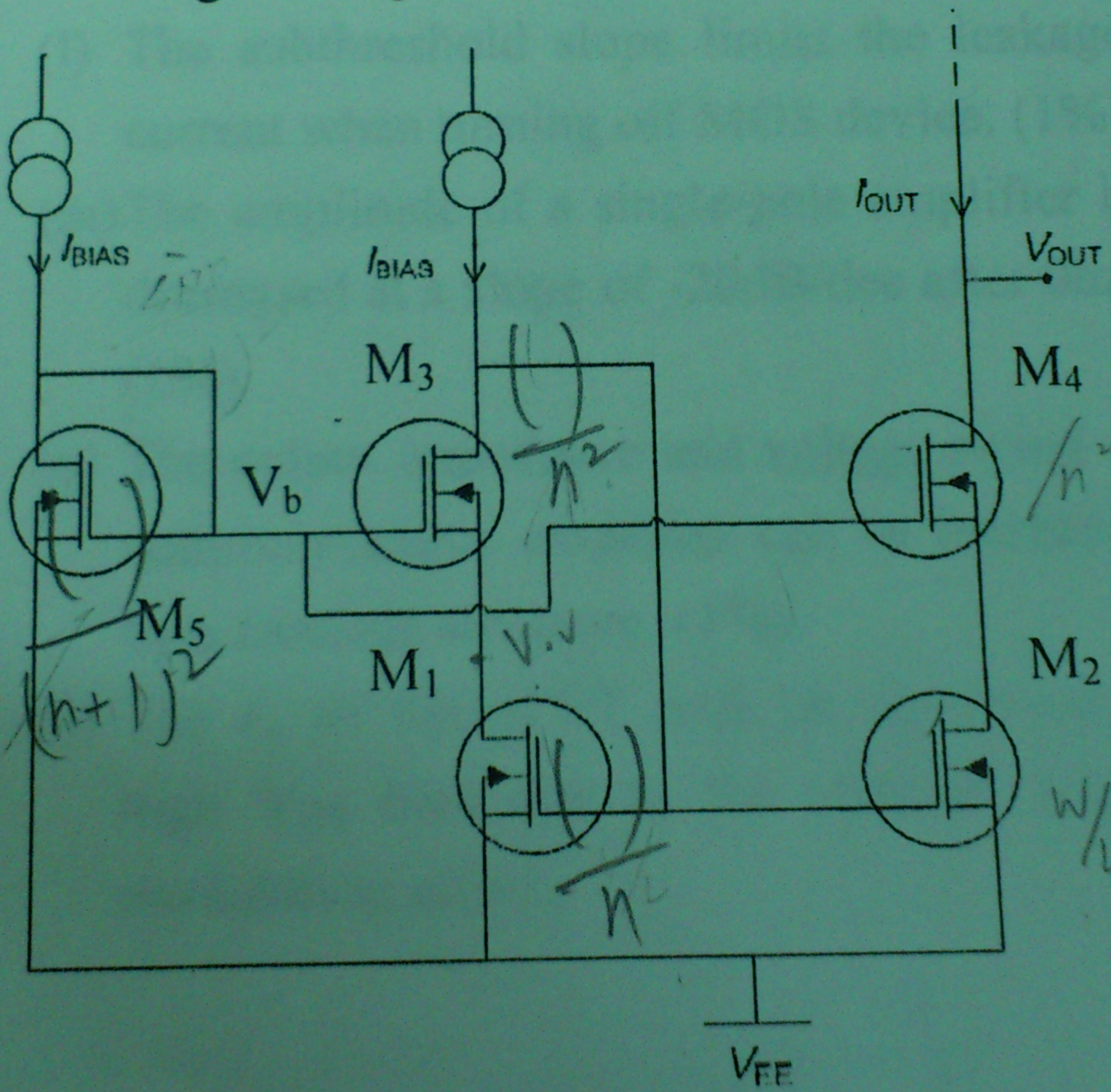


Fig. 11

2012 Analog IC: Midterm Examination (110%)

12. A common source amplifier is shown in Fig. 12 with the MOSFET bias of $g_m = 2\text{mA/V}$, $r_o = 100\text{k}\Omega$, $R_S = 10\text{k}\Omega$ and $R_D = 100\text{k}\Omega$. Assume $C_{GD} = C_{GS} = 5\text{fF}$ and $C_{DB} = C_{SB} = 2\text{fF}$. (10%)

- (a) Use Miller effect to find the equivalent C_{in} at node X and C_{out} at node V_{out} . (5%)
- (b) Find the correlated input pole ω_{in} and output pole ω_{out} . (5%)

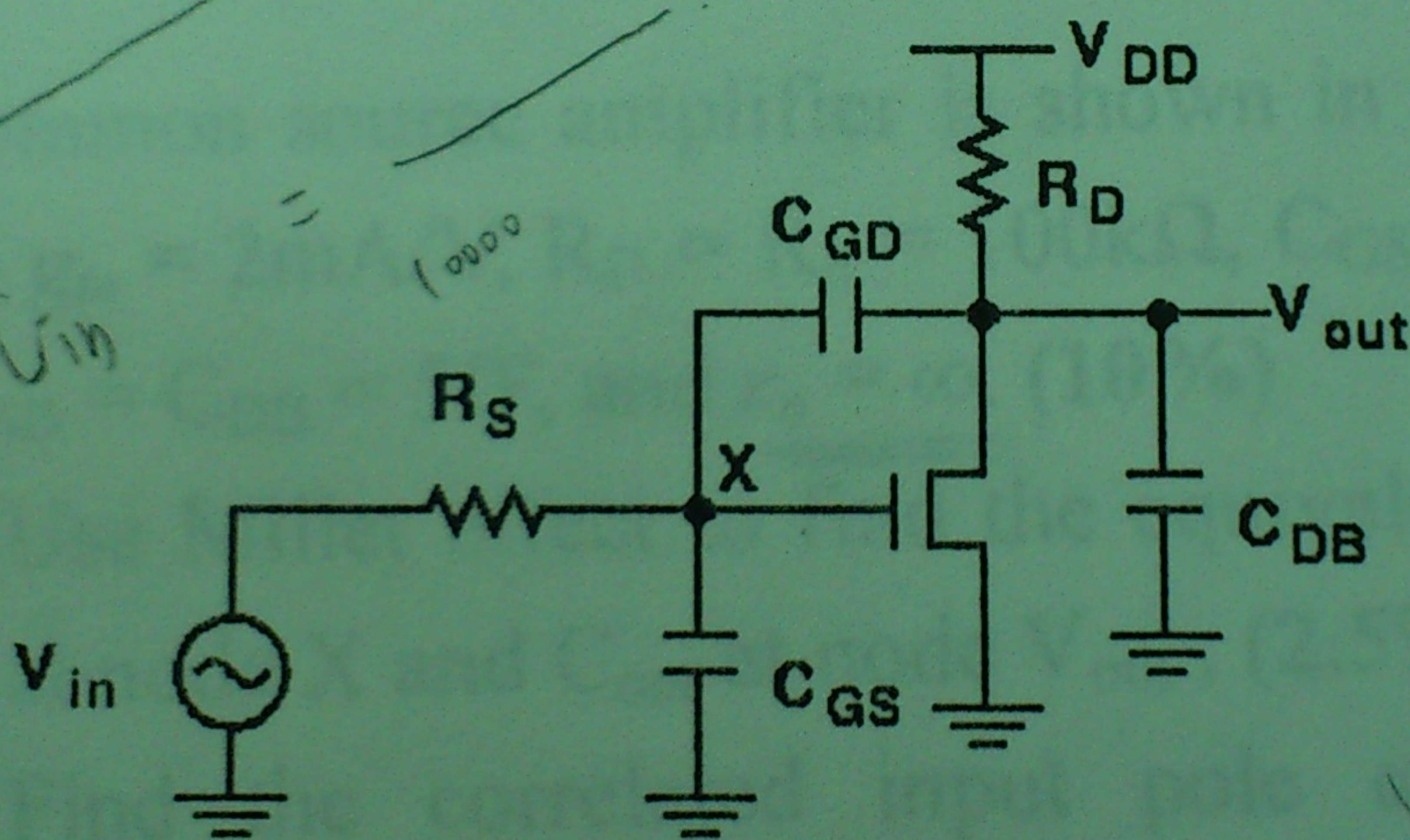


Fig. 12

13. A differential to single-ended amplifier is shown in Fig. 13. Assume all the MOSFETs are biased with $|V_{ov}| = 200\text{mV}$, $|V_{th}| = 0.6\text{V}$, $r_o = 100\text{k}\Omega$, and $g_m = 1\text{mA/V}$. The $I_D(M_5) = 10\mu\text{A}$ and $V_{DD} = 1.8\text{V}$. (10%)

- (a) Find the minimum input DC bias voltage.

 


Fig. 12

13. A differential to single-ended amplifier is shown in Fig. 13. Assume all the MOSFETs are biased with $|V_{ov}| = 200\text{mV}$, $|V_{th}| = 0.6\text{V}$, $r_o = 100\text{k}\Omega$, and $g_m = 1\text{mA/V}$. The $I_D(M_5) = 10\mu\text{A}$ and $V_{DD} = 1.8\text{V}$. (10%)

- (a) Find the minimum input DC bias voltage. (2.5%)
- (b) Find the maximum output swing V_{out} . (2.5%)
- (c) Find the differential gain $V_{out}/(V_{in1} - V_{in2})$. (2.5%)
- (d) Assume $A_{v,CM} = 1/(2g_m r_o)$, find the CMRR. (2.5%)

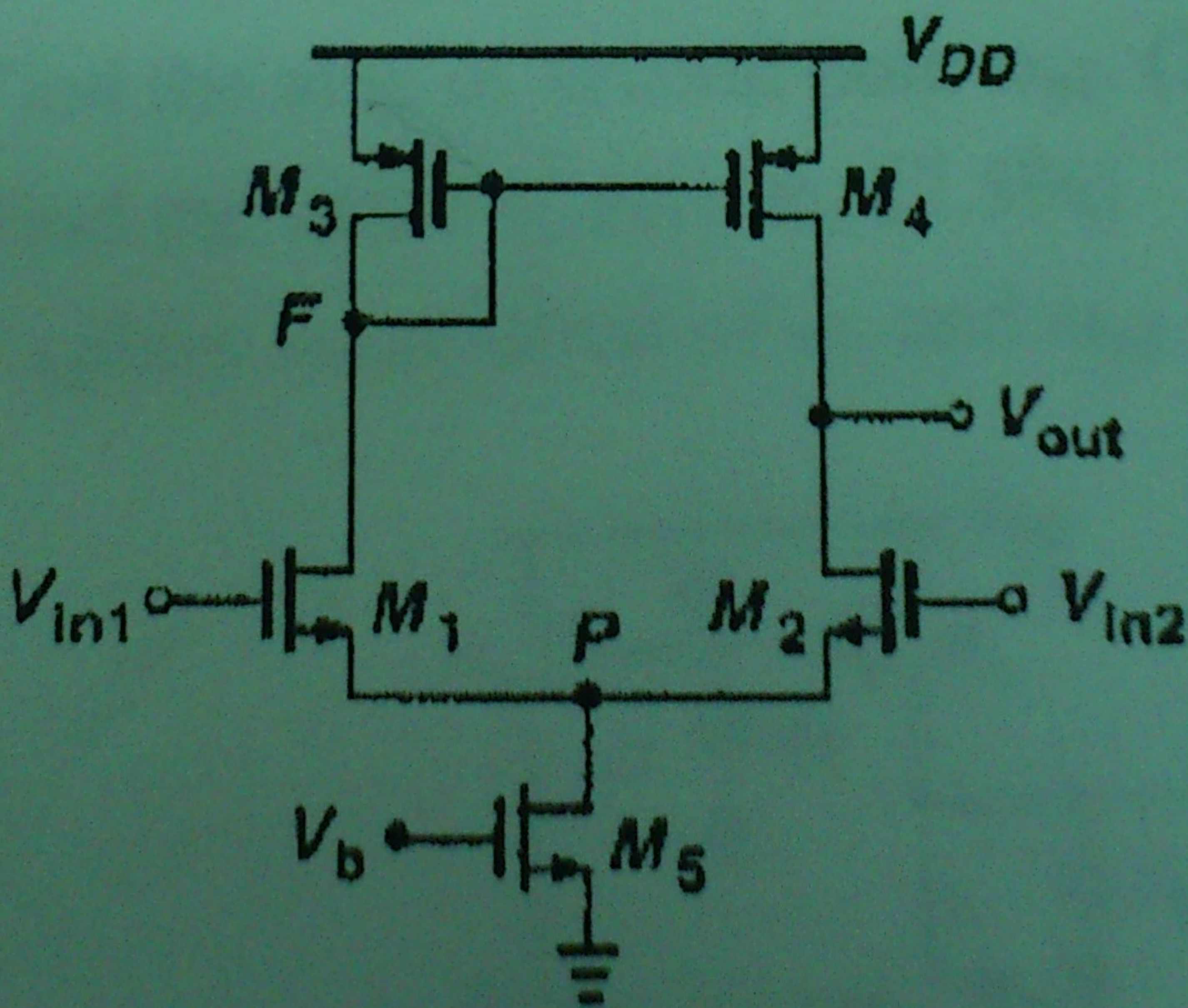


Fig. 13

Handwritten notes at the bottom of the page include circled 'E', 'T', and 'GB', and the expression g_m .

14. Answer the following questions with TRUE or FALSE: (15%)

- (a) Source/drain is implanted before gate formation. (1%) F
- (b) Source follower is commonly used as a voltage buffer due to its low R_{out} . (1%) T
- (c) Common gate amplifier is commonly used as current buffer due to its low R_{in} . (1%) T
- (d) Junction capacitance is proportional to device width. (1%) T
- (e) The threshold voltage of nMOS is increased by p+ channel implantation. (1%) T
- (f) Differential amplifier has smaller common noise and low power performance. (1%) F
- (g) Available voltage swing can be increased by using a larger bias current. (1%) F
- (h) Chemical vapor deposition is used to form the source/drain region. (1%) F
- (i) The transconductance g_m of MOSFET is proportional to *width* at a known constant biasing current. (1%) F
- (j) The g_m of pMOS is larger than nMOS at same bias current and device size. (1%) F
- (k) The gate-to-body capacitance of a MOS device is almost the same in strong inversion and accumulation region. (1%) T
- (l) The subthreshold slope limits the leakage current when turning off MOS device. (1%) T

noise and low power performance. (1%)

- (g) Available voltage swing can be increased by using a larger bias current. (1%) F
- (h) Chemical vapor deposition is used to form the source/drain region. (1%) F
- (i) The transconductance g_m of MOSFET is proportional to *width* at a known constant biasing current. (1%) F
- (j) The g_m of pMOS is larger than nMOS at same bias current and device size. (1%) F
- (k) The gate-to-body capacitance of a MOS device is almost the same in strong inversion and accumulation region. (1%) T
- (l) The subthreshold slope limits the leakage current when turning off MOS device. (1%) T
- (m) The amplitude of a single-pole amplifier is decreased at a slope of -20dB/dec after 0hz. (1%) F
- (n) The output impedance and voltage swing of common-source amplifier can be increased by a cascode structure. (1%) F
- (o) The r_o of MOSFET will be decreased at high V_{DS} bias due to the channel length modulation effect. F

$g_m = \sqrt{2\mu C_{ox} W I_D}$ g_m